

8-by-8 Bit Shift/Add Multiplier

**Giovanni D'Aliesio
ID: 4860519**

**Digital Design & Synthesis
COEN 6501
Department of
Electrical & Computer Engineering
Concordia University
December 2003**

Table of Contents

| | | |
|---|--|-----------|
| 1 | INTRODUCTION | 4 |
| 1.1 | DESIGN FLOW | 4 |
| 2 | GENERAL REQUIREMENTS..... | 6 |
| 3 | DESIGN SPECIFICATIONS | 7 |
| 3.1 | CONTROLLER DESIGN | 7 |
| 3.1.1 | <i>Design</i> | 7 |
| 3.1.2 | <i>Simulation & Timing</i> | 8 |
| 3.2 | MULTPLICAND BLOCK DESIGN | 9 |
| 3.2.1 | <i>Design</i> | 9 |
| 3.2.2 | <i>Simulation & Timing</i> | 10 |
| 3.3 | MULTIPLIER/RESULT BLOCK DESIGN | 10 |
| 3.3.1 | <i>Design</i> | 10 |
| 3.3.2 | <i>Simulation & Timing</i> | 12 |
| 3.4 | ADDER DESIGN | 12 |
| 3.4.1 | <i>Design</i> | 12 |
| 3.4.2 | <i>Simulation & Timing</i> | 14 |
| 3.5 | MULTIPLIER DESIGN | 15 |
| 3.5.1 | <i>Design</i> | 15 |
| 3.5.2 | <i>Test Bench</i> | 15 |
| 3.5.3 | <i>Simulation & Timing</i> | 16 |
| 4 | DESIGN ENHANCEMENTS..... | 17 |
| 4.1 | TIMING..... | 17 |
| 4.2 | SYNTHESIS | 18 |
| 4.3 | PLACE & ROUTE | 18 |
| 4.4 | TARGET..... | 19 |
| 4.5 | DESIGN IMPROVEMENTS | 20 |
| 4.6 | ADDER SELECTION..... | 20 |
| 4.7 | 32-BIT EXPANSION..... | 21 |
| 5 | CONCLUSION | 22 |
| APPENDIX A: VHDL SOURCE CODE..... | | 23 |
| | VHDL: CONTROLLER..... | 23 |
| | VHDL: MULTIPLICAND..... | 25 |
| | VHDL: MULTIPPLIER_RESULT | 28 |
| | VHDL: ADDER..... | 30 |
| | VHDL: MULTIPLIER..... | 34 |
| | VHDL: TESTBENCH..... | 36 |
| | VHDL: 32-BIT MULTIPLIER | 38 |
| | VHDL: 32-BIT MULTIPLIER TESTBENCH..... | 46 |
| APPENDIX B: SIMULATION RESULT FILES..... | | 48 |
| APPENDIX C: SYNTHESIS REPORT FILES..... | | 51 |
| APPENDIX D: PLACE & ROUTE REPORT FILES | | 56 |

List of Figures

| | |
|--|----|
| FIGURE 1-1: FPGA DESIGN FLOW | 4 |
| FIGURE 2-1: ADD/SHIFT MULTIPLIER BLOCK DIAGRAM | 6 |
| FIGURE 3-1: MULTIPLIER DESIGN BLOCK DIAGRAM | 7 |
| FIGURE 3-2: CONTROLLER FSM DIAGRAM | 8 |
| FIGURE 3-3: CONTROLLER SIMULATION TIMING DIAGRAM | 8 |
| FIGURE 3-4: STRUCTURAL D FLIP-FLOP | 9 |
| FIGURE 3-5: MULTIPLICAND DIAGRAM | 9 |
| FIGURE 3-6: MULTIPLICAND SIMULATION TIMING DIAGRAM | 10 |
| FIGURE 3-7: MULTIPLIER_RESULT BLOCK DIAGRAM | 11 |
| FIGURE 3-8: MULTIPLIER_RESULT REGISTER DIAGRAM | 11 |
| FIGURE 3-9: MULTIPLIER_RESULT SIMULATION TIMING DIAGRAM | 12 |
| FIGURE 3-10: RIPPLE CARRY ADDER BLOCK DIAGRAM | 13 |
| FIGURE 3-11: CARRY SELECT ADDER BLOCK DIAGRAM | 13 |
| FIGURE 3-12: RIPPLE CARRY ADDER SIMULATION TIMING DIAGRAM | 14 |
| FIGURE 3-13: CARRY SAVE ADDER SIMULATION TIMING DIAGRAM | 14 |
| FIGURE 3-14: TESTBENCH SIMULATION BLOCK DIAGRAM | 15 |
| FIGURE 3-15: COMPLETE MULTIPLIER SIMULATION TIMING DIAGRAM | 16 |
| FIGURE 4-1: MINIMUM LATENCY TIMING DIAGRAM | 17 |
| FIGURE 4-2: MAXIMUM LATENCY TIMING DIAGRAM | 18 |
| FIGURE 4-3: DETAILED VIEW OF VIRTEX SLICE | 19 |
| FIGURE 4-4: COMPLETE 32-BIT MULTIPLIER SIMULATION TIMING DIAGRAM | 21 |

List of Tables

| | |
|---|----|
| TABLE 4-1: XILINX VIRTEX XCV50 DEVICE DETAILS | 19 |
| TABLE 4-2: AREA & SPEED FOR VARIOUS ADDER DESIGNS | 20 |

1 INTRODUCTION

The objective of this project is to go through a design cycle from initial conception to simulation. In this case, it has been taken several steps further and synthesis as well as place & route was also achieved. The goal is to design and simulate an 8-by-8 bit shift/add multiplier. The result is a completely synthesized 8-by-8 bit and 32-by-32 bit shift/add multiplier with various design options for speed and area.

1.1 Design Flow

The VHDL entry, simulation, synthesis and place & route was performed using a variety of high performance, UNIX based CAD tools. The complete design flow is shown in Figure 1-1.

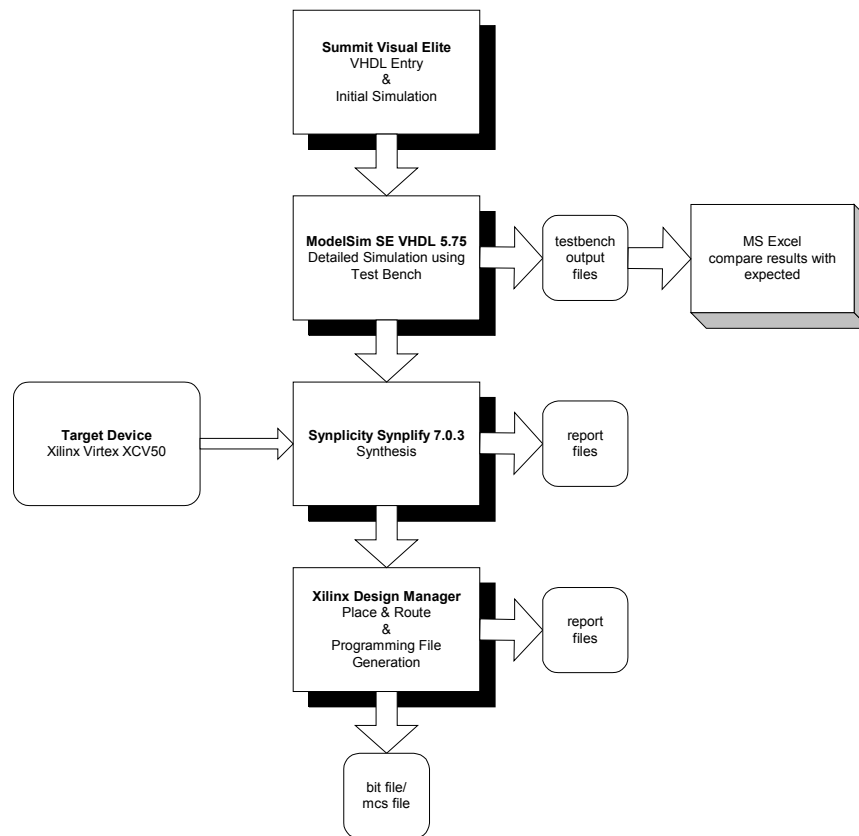


Figure 1-1: FPGA Design Flow

Initial VHDL entry was done in Summit Visual Elite. This tool provided the functionality to compile the code and to perform initial simulation. The simulation performed at this level was mainly to verify block level functionality and timing correctness. Once the blocks were coded and verified, a more advanced simulation tool was used, namely ModelSim. In this case, a complete test bench was developed which performed many multiplications and saved the result in a file. This file was then compared to the expected results in order to confirm proper functionality. Upon successful testing, the design was then synthesized using Synplicity's Synplify and the technology library for the Xilinx Virtex XCV50. Finally, Xilinx Design Manager was used to place and route the design, and generate the appropriate programming files.

2 GENERAL REQUIREMENTS

The requirement is to design an 8-by-8 bit multiplier based on the shift and add method. The overall architecture is shown in Figure 2-1. The multiplier shall accept as inputs an 8-bit multiplier and 8-bit multiplicand as well as a Start signal. The multiplier shall then calculate the result using the shift and add method and provide the 16-bit result along with a Stop signal. The design shall be coded in VHDL and simulated for proper functionality and timing.

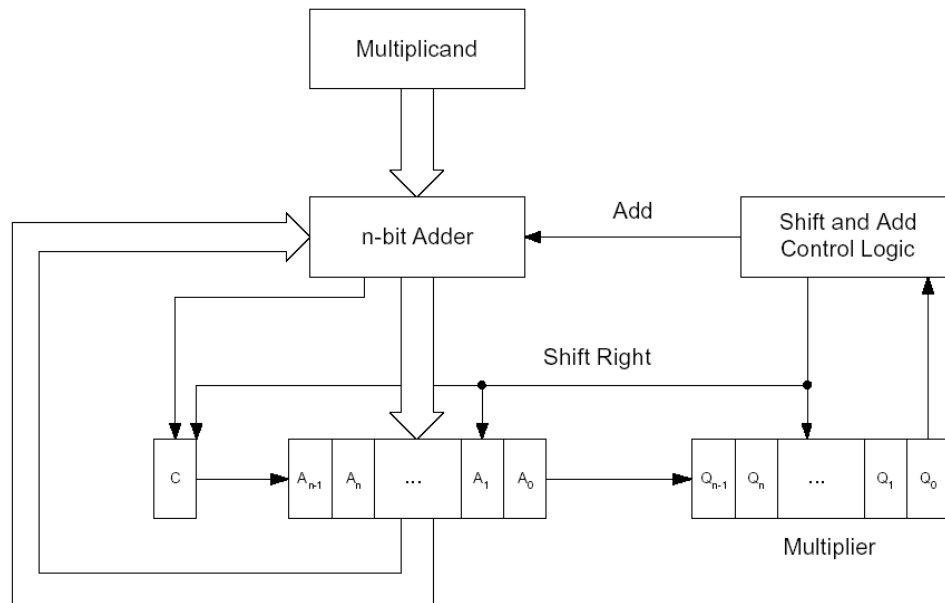


Figure 2-1: Add/Shift Multiplier Block Diagram

3 DESIGN SPECIFICATIONS

The design was implemented using a mixture of both structural design and rtl level design. In each case the choice of style is described. The block diagram shown in Figure 3-1 details the breakdown of VHDL modules. In the following sections each of the modules are described in greater detail and associated diagrams, simulation outputs and timing are provided.

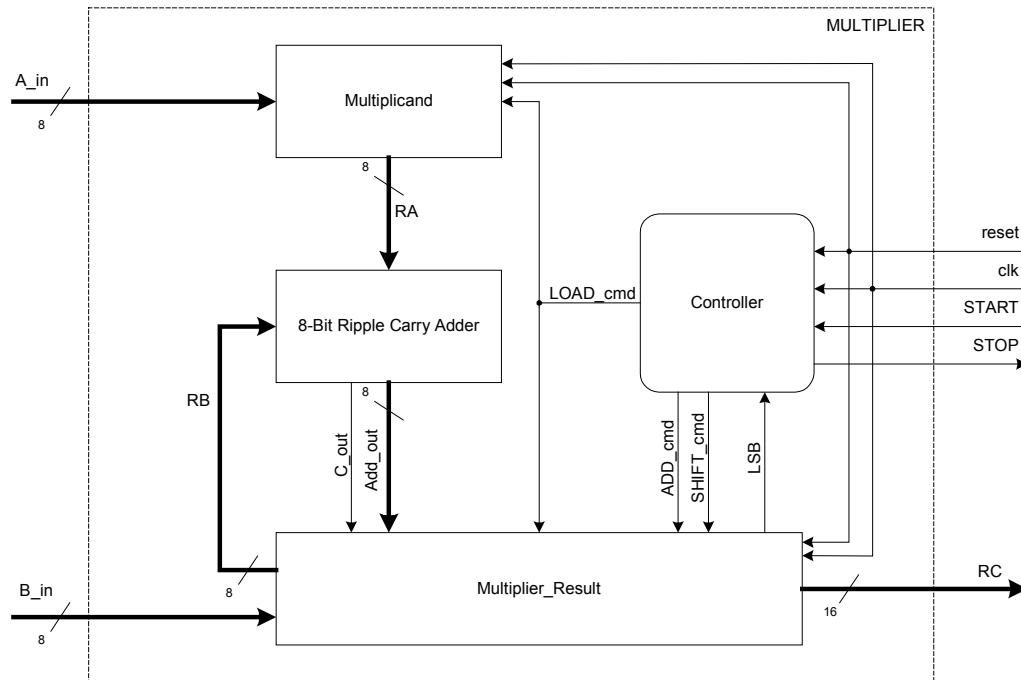


Figure 3-1: Multiplier Design Block Diagram

3.1 Controller Design

The Controller is the control unit of the multiplier. It receives a START signal and consequently commands all other modules until the result is obtained and it outputs a STOP signal.

3.1.1 Design

The design was implemented as a finite state machine with states and transition logic as shown in Figure 3-2. The Start signal transitions the state machine out of the idle state and into the initialize state whereby it commands the multiplicand and multiplier to be loaded into registers. Once loaded, the state machine goes through a series of test and shift, or test, add and shift operations depending on the status of the LSB bit. Upon reaching the maximum count for the multiplication cycle, the state machine goes back to the idle state and outputs a Stop signal.

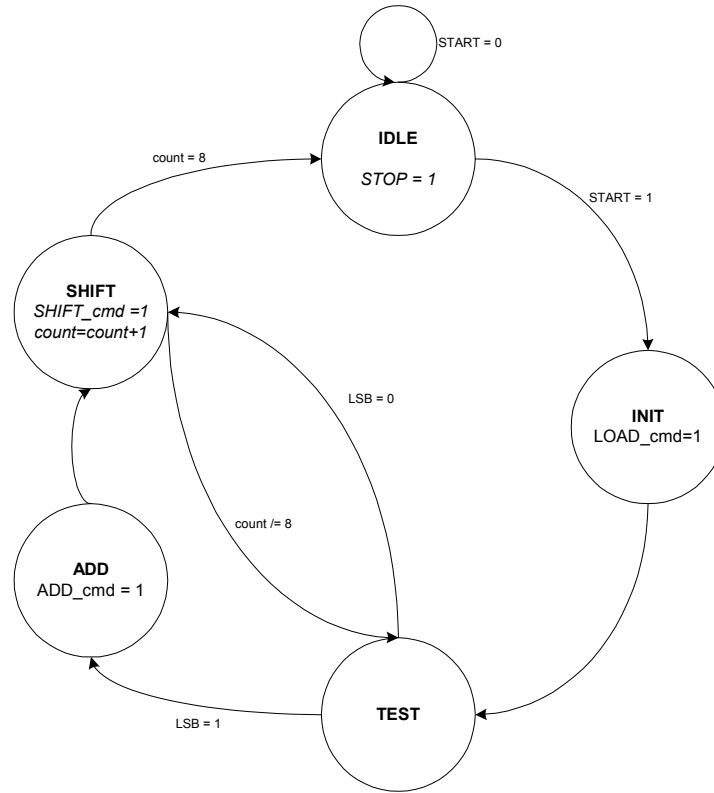


Figure 3-2: Controller FSM Diagram

The associated VHDL source code is included in Appendix A: VHDL Source Code.

3.1.2 Simulation & Timing

The controller is synchronous to the clock and transitions through the various states occur on the rising clock edge. As can be seen from the timing diagram in Figure 3-3, the Start signal transitions the state machine out of the idle state only when sampled by the rising clock edge. Upon entering the initialize state, the LOAD_cmd is generated. During each test state, the LSB is sampled. If the LSB was high, the add state is entered and the controller generates the ADD_cmd. If the LSB was low, or once the add state is exited, the shift state is entered and the controller generates the SHIFT_cmd. Upon reaching the maximum count for the multiplication cycle, the state machine goes back to the idle state and outputs a stop signal.

 


Figure 3-3: Controller Simulation Timing Diagram

3.2 Multiplicand Block Design

The Multiplicand block is composed of 8 D Flip-Flop blocks, which store the “A” byte for processing during the complete multiplication cycle. The register is loaded with the LOAD_cmd signal from the Controller.

3.2.1 Design

The basic design for the Multiplicand block is that of an 8-bit register. The top-level multiplicand module generates an 8-bit register from individual 1-bit D Flip-Flops. The individual D flip-flops have been designed both structurally and behaviorally and the synthesized results are compared in section 4.6. The structural design follows the diagram in Figure 3-4. The detailed diagram of the Multiplicand module is shown in Figure 3-5. The byte is loaded into the register only when the LOAD_cmd is received from the Controller and the register is cleared when a global reset is applied.

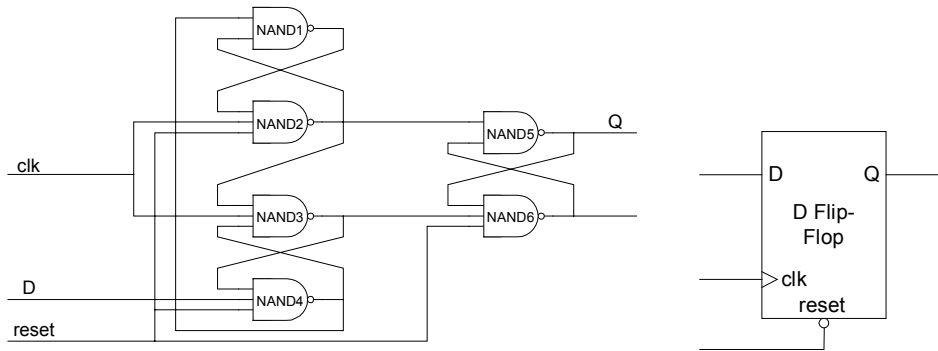


Figure 3-4: Structural D Flip-Flop

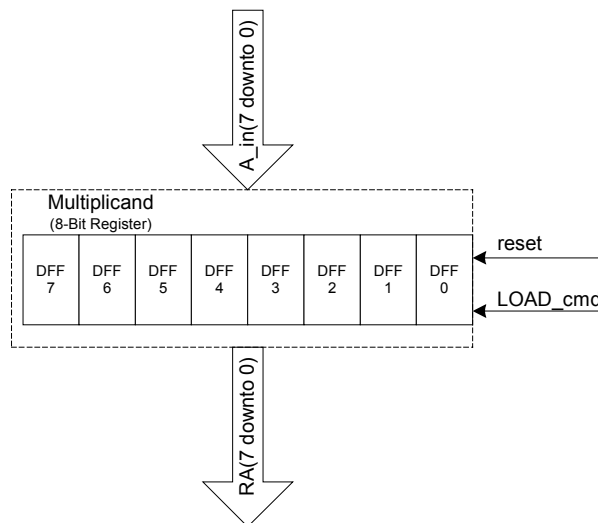


Figure 3-5: Multiplicand Diagram

The associated VHDL source code is included in Appendix A: VHDL Source Code.

3.2.2 Simulation & Timing

The timing and simulation results are identical regardless of the flip-flop design (structural or behavioral). The timing diagram in Figure 3-6 displays the functionality of the 8-bit register. The input, A_in, is only loaded into the register on the rising edge of the LOAD_cmd signal and remains in the register until the next time the LOAD_cmd signal is asserted.

 


Figure 3-6: Multiplicand Simulation Timing Diagram

3.3 Multiplier/Result Block Design

The Multiplier/Result block stores the multiplier (“B” byte) as well as the accumulated output of the adder. It allows the register to be logically shifted right and provides one of the Adder’s inputs. The Multiplier/Result block consists of a 17-bit shift register and a multiplexer in order to provide this functionality.

3.3.1 Design

The design of the Multiplier/Result module was performed at the RTL level. A block diagram of this module is shown in Figure 3-7 and the register assignment details are shown in Figure 3-8. The input to the module is the multiplier, B_in, which is loaded into bits 0 to 7 of the register when the LOAD_cmd is asserted. The adder block outputs (Cout and adder_out) are also inputs to the module. The outputs of the module are, LSB, bit 0 of the register, RB, bits 8 to 15 of the register, and RC, bits 0 to 15 of the register. LSB is fed back to the controller to determine the next state, while RB is fed into the adder in order to be summed with the multiplicand. RC is the final multiplication result and is considered valid only when the controller asserts the STOP signal. If the Multiplier_Result receives a SHIFT_cmd without a prior ADD_cmd, the register will be shifted logically to the right. If the ADD_cmd precedes the SHIFT_cmd, bits 1 to 7 of the register will be placed into positions 0 to 6 while the 9 inputs bits from the adder will be placed into positions 7 to 15 of the register. This is essentially equivalent to storing the adder results and then shifting the entire register.

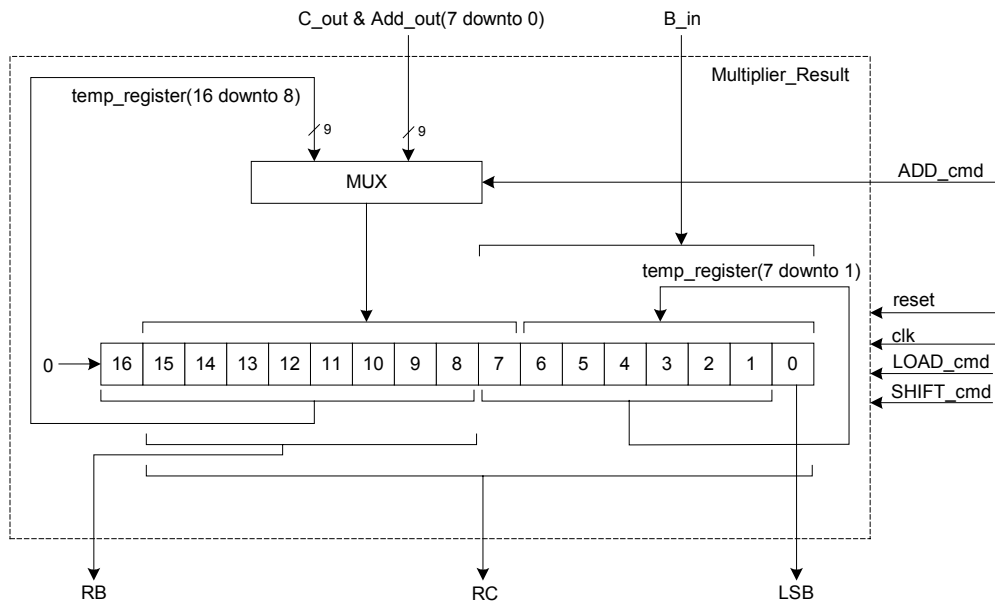


Figure 3-7: Multiplier_Result Block Diagram

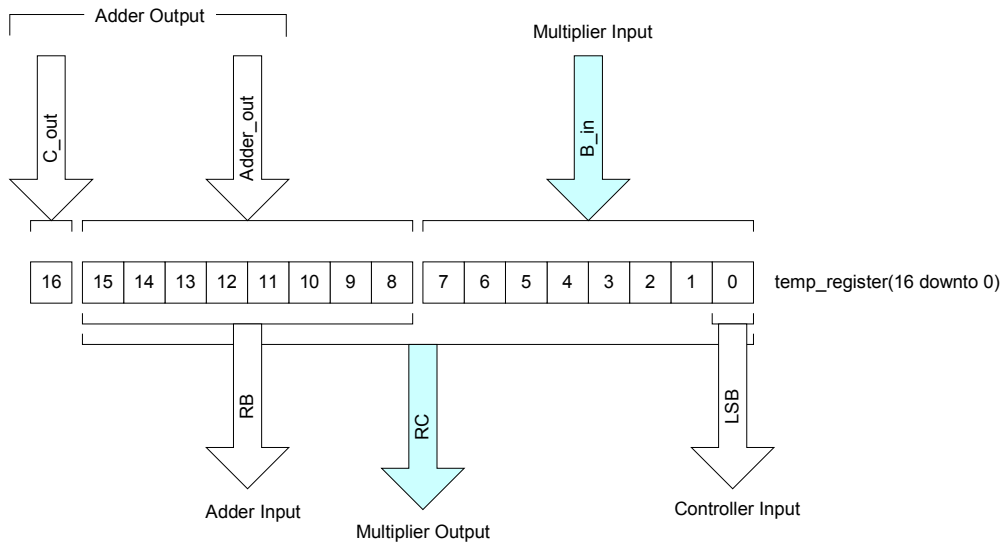


Figure 3-8: Multiplier_Result Register Diagram

The associated VHDL source code is included in Appendix A: VHDL Source Code.

3.3.2 Simulation & Timing

The timing diagram for the Multiplier_Result simulation is shown in Figure 3-9. The 17-bit register as shown in Figure 3-8, contains all the data that will be used as outputs of the module. From the timing diagram, it can be seen that once the LOAD_cmd is received, temp_register is loaded with the input byte “b_in”, in this case 0x96. If the SHIFT_cmd is received without a prior ADD_cmd, the contents of temp_register will be logically shifted right. This can be seen on the next clock edge when 0x96 is shifted to become 0x4B. If the ADD_cmd is received prior to the SHIFT_cmd, the 8 to 16 bits of temp_register will be loaded with the “add_out” input byte and the register will be logically shifted right. This can be seen on the next clock edge when 0xA is loaded into temp_register which contains 0x4B. This changes temp_register to equal 0xA4B which gets shifted right to become 0x525 as shown in the timing diagram.

 


Figure 3-9: Multiplier_Result Simulation Timing Diagram

3.4 Adder Design

The adder design is the most influential part of the multiplier in terms of the area and speed achievable. This is due to the large iterations of additions performed in the multiplication cycle. In this project, two types of adders were designed and compared. In this section, only a description of the design will be presented, while the comparison details will be left to section 4.6.

3.4.1 Design

The main function of the adder block is to sum two bytes together. The main building block of the adders described in the following paragraph is the Full Adder. This block is designed structurally and accepts 2 inputs while generating 1 sum output and 1 carry output.

The 8-bit ripple carry adder is composed of 8 individual full adders connected in a chain as shown in Figure 3-10. In this case, the carry out of each full adder is the carry in of the following full adder. The limiting speed factor in this approach is the delay from the first full adder to the outputs of the final full adder. In order to try and improve the speed of the adder, consequently enhancing the overall speed, the carry-select adder shown in Figure 3-11 was also implemented and compared to the original ripple carry adder. The carry-select adder is composed of three 4-bit

ripple carry adder blocks whereby the carry out of the first ripple carry adder selects which of the other two ripple carry adders to send to the output. In this case the limiting factor is the delay from the input of the first 4-bit ripple-carry-adder to its carry out which controls the multiplexer.

 


Figure 3-10: Ripple Carry Adder Block Diagram

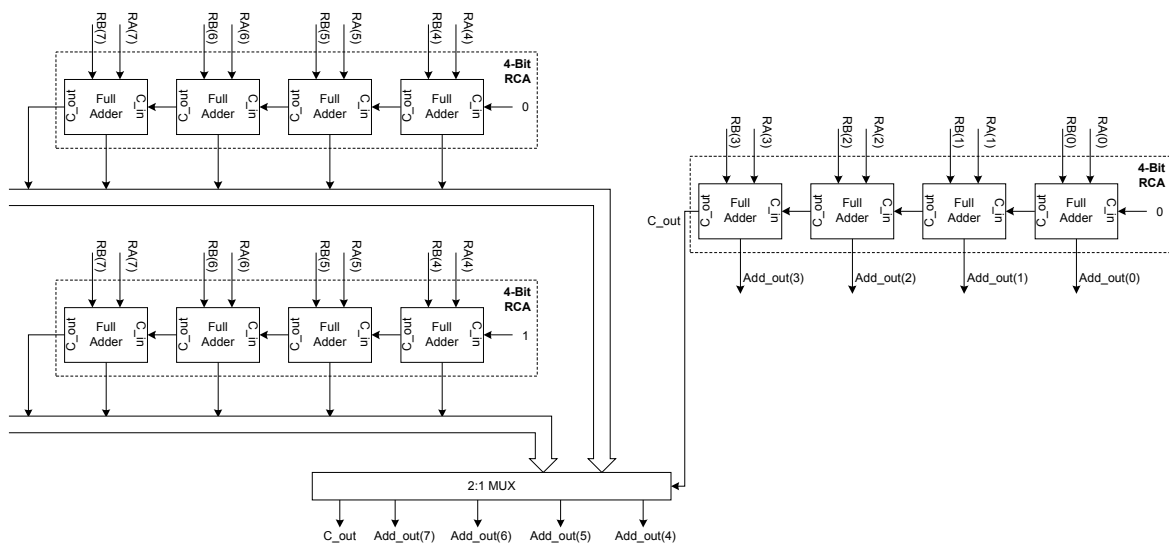


Figure 3-11: Carry Select Adder Block Diagram

The associated VHDL source code is included in Appendix A: VHDL Source Code.

3.4.2 Simulation & Timing

The simulation of both the ripple-carry-adder and the carry-select-adder are shown in Figure 3-12 and Figure 3-13 respectively. As can be seen from the simulation output of the ripple-carry-adder, the addition of 0xA and 0x5 gives the result 0xF, which is correct. In this particular addition, no carry-out signals were generated by the full adders and as such the internal vector representing the carry-out's, c_temp, remained 0. In the subsequent addition of 0x7 and 0xA, the result is observed to be 0x11, which is also correct. In this addition, carry-out's occur for full adder blocks 2, 3, and 4, hence the carry-out vector should be 0x1C (11100) which is observed in the timing diagram.

 


Figure 3-12: Ripple Carry Adder Simulation Timing Diagram

The simulation output of the Carry Select Adder shown in Figure 3-13, displays both scenarios when selecting the higher order nibble. In the case of adding 0b11101110 and 0b00000000, the carry out of the first four bit addition is 0 and thus the result is 0b11101110 and not 0b11111110. In the case of adding 0b11101110 and 0b01110111, the carry out of the first four bit addition is 1 and thus the result is 0b01100101 and not 0b01010101.

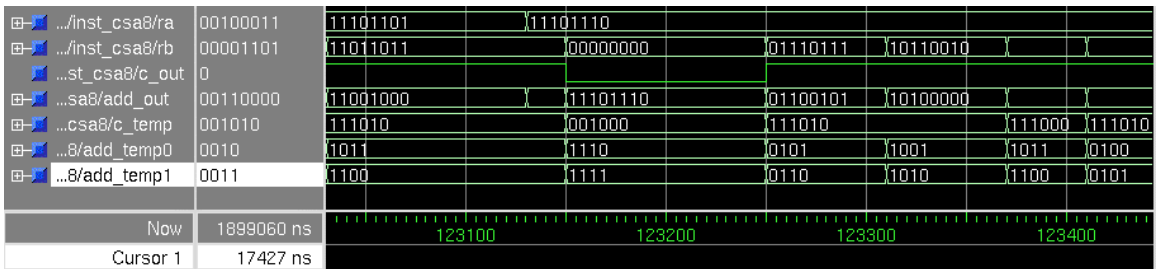


Figure 3-13: Carry Save Adder Simulation Timing Diagram

3.5 Multiplier Design

3.5.1 Design

The complete multiplier is simply a top-level module which instantiates all the lower level functional modules described in the previous sections.

The associated VHDL source code is included in Appendix A: VHDL Source Code.

3.5.2 Test Bench

The Test Bench is designed such that it can provide a series of stimuli to the Multiplier and log the results obtained. The log file, included in Appendix B: Simulation Result Files contains the multiplicand and multiplier sent to the Multiplier as well as the result received. In order to quickly validate the results, the log file is imported into an Excel spreadsheet (included on the CD) whereby an automatic comparison is performed between the theoretical results and the experimental results. A block diagram of the Test Bench architecture is shown in Figure 3-14 below.

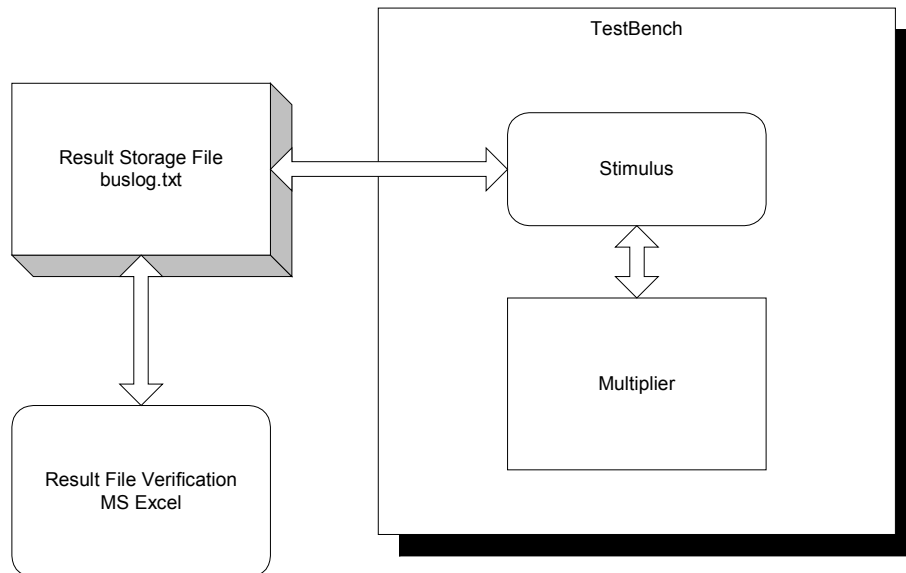


Figure 3-14: TestBench Simulation Block Diagram

The associated VHDL source code is included in Appendix A: VHDL Source Code.

3.5.3 Simulation & Timing

The timing diagram displayed in Figure 3-15 shows one complete multiplication cycle from the Start signal to the Stop signal. In the test case shown, the “A” byte is 0xA (10) and the “B” byte is 0x96 (150). The expected result is 0x5DC (1500) which is obtained once the Stop signal is asserted at the end of the multiplication cycle. While the timing diagram in Figure 3-15 only displays one multiplication cycle, Appendix B: Simulation Result Files contains the results of many multiplication cycles.

 


Figure 3-15: Complete Multiplier Simulation Timing Diagram

4 DESIGN ENHANCEMENTS

4.1 Timing

Timing is of great concern in any digital system. In this case there are two ways of looking at the timing issues. The first is the timing requirements of generating the fastest clock while respecting each individual timing requirement such that the functionality is not compromised. The second is the overall latency of the operation. This is the time, or amount of clock cycles that it takes from the Start signal to the Stop signal.

Frequency of operation is determined by analyzing the critical path of the system. That is, the path with the longest delay. From observation, one can guess that the longest path will likely be due to the long string of adders, each of which requires an input from the previous one. This observation is confirmed by analyzing the synthesis report found in Appendix C: Synthesis Report Files. In the case of the design using the ripple-carry-adder, the longest delay would be from the input of the first adder to the output of the last (eighth) adder. As confirmed by the report, the critical path is from temp_register[8] to temp_register[15]. This corresponds to the eight adder string as shown in Figure 3-8. Upon locating the critical path, a new adder design was used to reduce the delay. The timing report shown in Appendix C: Synthesis Report Files, for the case of the carry-select-adder, indicates the critical path to be from temp_register[8] to temp_register[12]. This corresponds to the input of the 4-bit ripple-carry-adder module to the carry-out which selects the appropriate result of the next stage 4-bit ripple-carry-adder. As expected, this delay is shorter than the previous adder design and thus a faster clock frequency is realized.

In the case of latency, depending on the input values, various cycle times are observed. Minimum latency occurs when the multiplier is 0x00 therefore the LSB is always 0 and the add state is never entered. The minimum latency is 17 clock cycles (1 init state + 8 bits X 2 states, test and shift). This scenario is shown in Figure 4-1 below.

 


Figure 4-1: Minimum Latency Timing Diagram

Maximum latency occurs when the multiplier is 0xFF therefore the LSB is always one and the add state is always entered. The maximum latency is 25 clock cycles (1 init state + 8 bits X 3 states, test, add and shift). This scenario is shown in Figure 4-2 below.

 


Figure 4-2: Maximum Latency Timing Diagram

4.2 Synthesis

For the purposes of this project, very little constraints were imposed on the design to be synthesized. Neither pin-out, stringent timing, synthesis effort level nor was area optimization specified. Synthesis was performed using Synplicity's Synplify CAD tool. The target device was selected along with the source VHDL file and constraints file. In turn the tool synthesized the design using the target library and generated the netlist as well as several reports. The complete output files are available on the CD-ROM, however an excerpt of the relevant timing and area details are included in Appendix C: Synthesis Report Files herein.

4.3 Place & Route

Place & Route was performed using Xilinx's Design Manager. The netlist file created during the synthesis phase was imported into the tool which routed the design in the appropriate target and generated a bit file which is used to physically program the device. Several reports were also generated which detail post layout timing and area. The complete output files are available on the CD-ROM. A view of the mapped out design using the tool's floorplanner is included as Appendix D: Place & Route Report Files herein.

4.4 Target

The target selected for the synthesis and place & route is the Xilinx Virtex XCV50. The XCV50 is the smallest device in the Virtex family and was chosen simply to outline the place and route process. The device details are outlined in Table 4-1 below. A detailed view of the Virtex slice is shown in Figure 4-3.

Table 4-1: Xilinx Virtex XCV50 Device Details

| Device | System Gates | CLB Array | Logic Cells | Maximum Available I/O | Block RAM Bits | Maximum SelectRAM+™ Bits |
|--------|--------------|-----------|-------------|-----------------------|----------------|--------------------------|
| XCV50 | 57,906 | 16x24 | 1,728 | 180 | 32,768 | 24,576 |

 


Figure 4-3: Detailed View of Virtex Slice

In order to gain an insight into the variations between devices and the effect on speed and area, one multiplier design was also synthesized using an Actel ACT3 A1415A-3 device. As this comparison can itself be a topic for a large project, the synthesis results are only included here as topic of interest. No detailed analysis was performed on the Actel device.

4.5 Design Improvements

Throughout the project, several improvements were realized in order to enhance the experience of implementing the multiplier. Several adders were implemented in order to investigate the effect on speed and area. In some cases both structural and behavioral VHDL was created for the same module in order to get an insight into its effects on timing and area. A 32-bit version of the multiplier was also implemented. Many further enhancements can be seen coming out of this project. Optimal designs for adders can achieve greater speed, while using several target-specific VHDL modules can reduce the total area.

4.6 Adder Selection

The following table summarizes the area and speed reported by the synthesis and place & route tools for each of the designs. As expected, the design using the carry-select-adder is faster than the ripple-carry-adder version however takes up more area. It is also expected that the 32-bit version of the multiplier is slower and takes nearly four times as much area as its 8-bit counterpart. The interesting observation is that the same 8-bit multiplier using the ripple-carry-adder takes up more area when the D flip-flops of the Multiplicand block are designed structurally as compared to behaviorally. This can be credited to the design of the slice as shown in Figure 4-3. In specifying the structure of the D flip-flop, the CAD tool will generate register as specified instead of using a structure native to the target. Even more interesting is the fact that once this design undergoes place & route, the speed also drops considerably. This is probably due to the fact that the delay in creating the flip-flop structurally is now greater than the adder delay. This is supported by the mapping diagram included as Appendix D: Place & Route Report Files. Included in the table is also the timing result obtained when synthesizing the same ripple-carry-adder version of the multiplier using an Actel ACT 3 device as the target. This demonstrates the effect the device has on actual timing regardless of design being implemented, since in this case it is the same design.

Table 4-2: Area & Speed for Various Adder Designs

| Adder Type | Synthesis | | | Place & Route | | |
|---|-----------|---------------------|------------|---------------|---------------|-----------------------|
| | Max Freq. | Critical Path Delay | Area (Lut) | Max Freq. | Area (SLICES) | Area (Eq. Gate Count) |
| Ripple Carry Adder (DFF structural) | 92.9 MHz | 10.762 ns | 77 | 47.0 MHz | 40 | 662 |
| Ripple Carry Adder (DFF behavioral) | 92.9 MHz | 10.762 ns | 45 | 81.2 MHz | 24 | 534 |
| Ripple Carry Adder (DFF behavioral) Synthesized Actel | 42.9MHz | 23.29 ns | * | ** | ** | ** |
| Carry Select Adder (DFF behavioral) | 116.2 MHz | 8.602 ns | 50 | 105.2 MHz | 27 | 564 |
| 32-Bit RCA (DFF behavioral) | 38.1 MHz | 26.242 ns | 142 | 22.6 MHz | 73 | 1705 |

*Area for Actel is in terms of cells: 44 combinational cells & 33 sequential cells

** Place & Route was not performed for Actel Target

4.7 32-Bit Expansion

The standard 8-by-8 bit multiplier design using the ripple-carry-adder and behavioral D flip-flops was expanded to accept 32-bit multipliers and multiplicands. The design can be further optimized, particularly with regards to the 32-bit ripple-carry-adder since the delay introduced in this long string of adders degrades the speed considerably. As shown in Appendix C: Synthesis Report Files, the critical path for the 32-bit design is from temp_reg[32] to temp_reg[63] which corresponds to the inputs of the first full adder in the ripple-carry-adder chain to the output of the last full adder in the chain.

The associated VHDL source code for both the 32-by-32 bit multiplier and its associated test bench is included in Appendix A: VHDL Source Code.

The timing diagram displayed in Figure 4-4 shows one complete multiplication cycle for the 32-by-32 bit version of the multiplier. In the test case shown, the “A” byte is 0xF4240 (1000000) and the “B” byte is 0x1E8480 (2000000). The expected result is 0x1D1A94A2000 (2000000000000) which is obtained once the Stop signal is asserted at the end of the multiplication cycle. While the timing diagram in Figure 4-4 only displays one multiplication cycle, Appendix B: Simulation Result Files contains the results of many multiplication cycles.

 


Figure 4-4: Complete 32-Bit Multiplier Simulation Timing Diagram

5 CONCLUSION

The goal of the project, to design an 8-by-8 bit multiplier using the add and shift method, was achieved. The multiplier was designed, coded in VHDL and simulated using the appropriate CAD tools. As an added value to the project, several designs were implemented in order to compare speed and area. Designs were also synthesized using various targets and place & route was also performed for a particular Xilinx device. The design was also expanded to a 32-bit version and similar synthesis and place & route analysis was achieved.

The added work performed for this project, can themselves become a complete topic for another project. For example, the effect of adder design on speed and area can itself be a large research project while optimizing constraints for efficient synthesis is often a critical step when implementing designs in industry. Everyone wants the highest density and fastest speed achievable from their designs.

APPENDIX A: VHDL SOURCE CODE

VHDL: Controller

```
-----  
--  
-- Library Name : DSD  
-- Unit Name : Controller  
--  
-----  
-----  
-- Date : Mon Oct 27 12:36:47 2003  
--  
-- Author : Giovanni D'Aliesio  
--  
-- Description : Controller is a finite state machine  
-- that performs the following in each  
-- state:  
-- IDLE > samples the START signal  
-- INIT > commands the registers to be  
-- loaded  
-- TEST > samples the LSB  
-- ADD > indicates the Add result to be stored  
-- SHIFT > commands the register to be shifted  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
  
entity Controller is  
port (reset : in std_logic ;  
clk : in std_logic ;  
START : in std_logic ;  
LSB : in std_logic ;  
ADD_cmd : out std_logic ;  
SHIFT_cmd : out std_logic ;  
LOAD_cmd : out std_logic ;  
STOP : out std_logic);  
end;  
  
-----  
architecture rtl of Controller is  
  
signal temp_count : std_logic_vector(2 downto 0);  
  
-- declare states  
type state_typ is (IDLE, INIT, TEST, ADD, SHIFT);  
signal state : state_typ;  
  
begin  
  
process (clk, reset)  
begin  
if reset='0' then  
state <= IDLE;  
temp_count <= "000";  
  
elsif (clk'event and clk='1') then
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
case state is

  when IDLE =>
    if START = '1' then
      state <= INIT;
    else
      state <= IDLE;
    end if;

  when INIT =>
    state <= TEST;

  when TEST =>
    if LSB = '0' then
      state <= SHIFT;
    else
      state <= ADD;
    end if;

  when ADD =>
    state <= SHIFT;

  when SHIFT =>
    if temp_count = "111" then -- verify if finished
      temp_count <= "000";    -- re-initialize counter
      state <= IDLE;          -- ready for next multiply
    else
      temp_count <= temp_count + 1; -- increment counter
      state <= TEST;
    end if;

end case;

end if;

end process;

STOP <= '1' when state = IDLE else '0';
ADD_cmd <= '1' when state = ADD else '0';
SHIFT_cmd <= '1' when state = SHIFT else '0';
LOAD_cmd <= '1' when state = INIT else '0';

end rtl;
```


VHDL: Multiplicand

Behavioral D Flip-Flop:

```
-----  
--  
-- Library Name : DSD  
-- Unit Name : DFF  
--  
-----  
-----  
-- Date : Mon Oct 27 13:32:59 2003  
--  
-- Author : Giovanni D'Aliesio  
--  
-- Description : DFF is an active high D flip flop  
-- with asynchronous clear.  
--  
-----  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity DFF is  
port (reset : in std_logic ;  
      clk : in std_logic ;  
      D : in std_logic ;  
      Q : out std_logic);  
end;  
  
-----  
architecture behav of DFF is  
begin  
  
    process (clk, reset)  
    begin  
        if reset='0' then  
            Q <= '0'; -- clear register  
  
            elsif (clk'event and clk='1') then  
                Q <= D; -- load register  
            end if;  
        end process;  
    end behav;
```

Structural D Flip-Flop:

```
-----  
-----  
-- Date : Mon Oct 27 13:32:59 2003  
--  
-- Author : Giovanni D'Aliesio  
--  
-- Description : DFF is an active high D flip flop  
-- with asynchronous clear.  
--  
-----  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity DFF is
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
port (reset      : in  std_logic ;
      clk        : in  std_logic ;
      D          : in  std_logic ;
      Q          : out std_logic);
end;

-----
architecture struc of DFF is

signal NAND_temp : std_logic_vector(6 downto 1);

component NAND_2
  port (
    IN1  : in  std_logic;
    IN2  : in  std_logic;
    OUT1 : out std_logic
  );
end component;

component NAND_3
  port (
    IN1  : in  std_logic;
    IN2  : in  std_logic;
    IN3  : in  std_logic;
    OUT1 : out std_logic
  );
end component;

begin

NAND1: NAND_2 port map (NAND_temp(4), NAND_temp(2), NAND_temp(1));
NAND2: NAND_3 port map (NAND_temp(1), clk, reset, NAND_temp(2));
NAND3: NAND_3 port map (NAND_temp(2), clk, NAND_temp(4), NAND_temp(3));
NAND4: NAND_3 port map (NAND_temp(3), D, reset, NAND_temp(4));
NAND5: NAND_2 port map (NAND_temp(2), NAND_temp(6), NAND_temp(5));
NAND6: NAND_3 port map (NAND_temp(5), NAND_temp(3), reset, NAND_temp(6));

Q <= NAND_temp(5);

end struc;

-----
--2 Input NAND
-----
library ieee;
use ieee.std_logic_1164.all;

entity NAND_2 is
port (IN1  : in  std_logic ;
      IN2  : in  std_logic ;
      OUT1 : out std_logic);
end;

-----
architecture struc of NAND_2 is
begin

    OUT1 <= NOT(IN1 AND IN2);

end struc;

-----
--3 Input NAND
-----
library ieee;
use ieee.std_logic_1164.all;

entity NAND_3 is
port (IN1  : in  std_logic ;
      IN2  : in  std_logic ;
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
        IN3  : in   std_logic ;
        OUT1 : out  std_logic);
end;
-----
architecture struc of NAND_3 is
begin

        OUT1 <= NOT(IN1 AND IN2 AND IN3);

end struc;
```

Multiplicand 8-Bit Register:

```
-----
--
-- Library Name : DSD
-- Unit Name : Multiplicand
--
-----
-- Date : Mon Oct 27 13:32:59 2003
--
-- Author : Giovanni D'Aliesio
--
-- Description : Multiplicand is an 8-bit register
--               that is loaded when the LOAD_cmd is
--               received and cleared with reset.
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity Multiplicand is
port (reset : in std_logic ;
      A_in : in std_logic_vector (7 downto 0);
      LOAD_cmd : in std_logic ;
      RA : out std_logic_vector (7 downto 0));
end;

-----
architecture struc of Multiplicand is

component DFF
port (
reset : in std_logic;
clk : in std_logic;
D : in std_logic;
Q : out std_logic
);
end component;

begin

DFFs: for i in 7 downto 0 generate

        DFFReg:DFF port map (reset, LOAD_cmd, A_in(i), RA(i));

end generate;

end struc;
```

VHDL: Multiplier_Result

```
-----  
--  
-- Library Name : DSD  
-- Unit Name : Multiplier_Result  
--  
-----  
-----  
-- Date : Mon Oct 27 14:13:51 2003  
--  
-- Author : Giovanni D'Aliesio  
--  
-- Description : Multiplier_Result performs the  
-- following:  
-- > loads B_in into register upon  
-- receiving LOAD_cmd  
-- > loads Adder output into register  
-- upon receiving ADD_cmd  
-- > shifts register right upon  
-- receiving SHIFT_cmd  
--  
-----  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity Multiplier_Result is  
port (reset : in std_logic ;  
      clk : in std_logic ;  
      B_in : in std_logic_vector (7 downto 0);  
      LOAD_cmd : in std_logic ;  
      SHIFT_cmd : in std_logic ;  
      ADD_cmd : in std_logic ;  
      Add_out : in std_logic_vector (7 downto 0);  
      C_out : in std_logic ;  
      RC : out std_logic_vector (15 downto 0);  
      LSB : out std_logic ;  
      RB : out std_logic_vector (7 downto 0));  
end;  
  
-----  
architecture rtl of Multiplier_Result is  
signal temp_register : std_logic_vector(16 downto 0);  
signal temp_Add : std_logic;  
  
begin  
  
process (clk, reset)  
begin  
    if reset='0' then  
        temp_register <= (others =>'0'); -- initialize temporary register  
        temp_Add <= '0';  
  
    elsif (clk'event and clk='1') then  
        if LOAD_cmd = '1' then  
            temp_register (16 downto 8) <= (others => '0');  
            temp_register(7 downto 0) <= B_in; -- load B_in into register  
        end if;  
  
        if ADD_cmd = '1' then  
            temp_Add <= '1';  
        end if;  
  
        if SHIFT_cmd = '1' then  
            if temp_Add = '1' then
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
-- store adder output while shifting register right 1 bit
temp_Add <= '0';
temp_register <= '0' & C_out & Add_out & temp_register (7 downto 1);
else
  -- no add - simply shift right 1 bit
  temp_register <= '0' & temp_register (16 downto 1);
end if;
end if;

end if;
end process;

RB <= temp_register(15 downto 8);
LSB <= temp_register(0);
RC <= temp_register(15 downto 0);

end rtl;
```

VHDL: Adder

Full Adder Block:

```
-----  
--  
-- Library Name : DSD  
-- Unit Name : Full_Adder  
--  
-----  
-----  
-- Date : Wed Sep 24 12:50:50 2003  
--  
-- Author : Giovanni D'Aliesio  
--  
-- Description : Basic Full Adder Block  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity Full_Adder is  
port (X : in std_logic;  
      Y : in std_logic;  
      C_in : in std_logic;  
      Sum : out std_logic ;  
      C_out : out std_logic);  
end;  
  
-----  
architecture struc of Full_Adder is  
begin  
  
Sum <= X xor Y xor C_in;  
C_out <= (X and Y) or (X and C_in) or (Y and C_in);  
  
end struc;
```

8-Bit Ripple Carry Adder:

```
-----  
--  
-- Library Name : DSD  
-- Unit Name : RCA  
--  
-----  
-----  
-- Date : Wed Sep 24 12:50:50 2003  
--  
-- Author : Giovanni D'Aliesio  
--  
-- Description : RCA is an 8-bit ripple carry  
-- adder composed of 8 basic full  
-- adder blocks.  
--  
-----  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity RCA is  
port (RA : in std_logic_vector (7 downto 0);
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```

    RB      : in  std_logic_vector (7 downto 0);
    C_out   : out std_logic ;
    Add_out : out std_logic_vector (7 downto 0));
end;

-----
architecture struc of RCA is

signal c_temp : std_logic_vector(7 downto 0);

component Full_Adder
  port (
    X      : in  std_logic;
    Y      : in  std_logic;
    C_in   : in  std_logic;
    Sum    : out std_logic;
    C_out  : out std_logic
  );
end component;

begin

  c_temp(0) <= '0'; -- carry in of RCA is 0

Adders: for i in 7 downto 0 generate

-- assemble first 7 adders from 0 to 6
Low: if i/=7 generate
  FA:Full_Adder port map (RA(i), RB(i), c_temp(i), Add_out(i), c_temp(i+1));
end generate;

-- assemble last adder
High: if i=7 generate
  FA:Full_Adder port map (RA(7), RB(7), c_temp(i), Add_out(7), C_out);
end generate;

end generate;

end struc;
```

8-Bit Carry Select Adder (Composed of 4-Bit RCA):

```

-----
--
-- Library Name : DSD
-- Unit Name : RCA4
--
-----
-- Date      : Wed Sep 24 12:50:50 2003
--
-- Author    : Giovanni D'Aliesio
--
-- Description : RCA is an 4-bit ripple carry
--              adder composed of 8 basic full
--              adder blocks.
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity RCA4 is
port (C_in   : in  std_logic;
      RA     : in  std_logic_vector (3 downto 0);
      RB     : in  std_logic_vector (3 downto 0);
      C_out  : out std_logic ;
      Add_out : out std_logic_vector (3 downto 0));
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
end;

-----
architecture rtl of RCA4 is

signal c_temp : std_logic_vector(3 downto 1);

component Full_Adder
  port (
    X      : in  std_logic;
    Y      : in  std_logic;
    C_in   : in  std_logic;
    Sum    : out std_logic;
    C_out  : out std_logic
  );
end component;

begin

Adders: for i in 3 downto 0 generate

  Low: if i=0 generate
    FA:Full_Adder port map (RA(0), RB(0), C_in, Add_out(0), c_temp(i+1));
  end generate;

  Mid: if (i>0 and i<3) generate
    FA:Full_Adder port map (RA(i), RB(i), c_temp(i), Add_out(i), c_temp(i+1));
  end generate;

  High: if i=3 generate
    FA:Full_Adder port map (RA(3), RB(3), c_temp(i), Add_out(3), C_out);
  end generate;

end generate;

end rtl;

-----
--
-- Library Name : DSD
-- Unit Name : CSA8
--
-----
-----
-- Date : Wed Sep 24 12:50:50 2003
--
-- Author : Giovanni D'Aliesio
--
-- Description : CSA8 is an 8 bit carry select adder
--
-----
-----
library ieee;
use ieee.std_logic_1164.all;

entity CSA8 is
port (RA : in std_logic_vector (7 downto 0);
      RB : in std_logic_vector (7 downto 0);
      C_out : out std_logic ;
      Add_out : out std_logic_vector (7 downto 0));
end;

-----
architecture rtl of CSA8 is

signal c_temp : std_logic_vector(5 downto 0);
signal add_temp0 : std_logic_vector(3 downto 0);
signal add_temp1 : std_logic_vector(3 downto 0);
```


8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
component RCA4
  port (
    C_in      : in  std_logic;
    RA       : in  std_logic_vector(3 downto 0);
    RB       : in  std_logic_vector(3 downto 0);
    Add_out   : out std_logic_vector(3 downto 0);
    C_out    : out std_logic
  );
end component;

begin

  c_temp(0) <= '0';
  c_temp(2) <= '0';
  c_temp(3) <= '1';

  inst_RCA1: RCA4
    port map (
      C_in => c_temp(0),
      RA  => RA(3 downto 0),
      RB  => RB(3 downto 0),
      Add_out => Add_out(3 downto 0),
      C_out => c_temp(1)
    );
  inst_RCA2: RCA4
    port map (
      C_in => c_temp(2),
      RA  => RA(7 downto 4),
      RB  => RB(7 downto 4),
      Add_out => add_temp0,
      C_out => c_temp(4)
    );
  inst_RCA3: RCA4
    port map (
      C_in => c_temp(3),
      RA  => RA(7 downto 4),
      RB  => RB(7 downto 4),
      Add_out => add_temp1,
      C_out => c_temp(5)
    );

  Add_out (7 downto 4) <= add_temp0 when c_temp(1)='0' else
    add_temp1 when c_temp(1)='1' else
    "ZZZZ";

  C_out <= (c_temp(1) and C_temp(5)) or c_temp(4);

end rtl;
```

VHDL: Multiplier

```
-----  
--  
-- Library Name : DSD  
-- Unit Name : Multiplier  
--  
-- Description : Complete multiplier  
--  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
--library synplify; -- required for synthesis  
--use synplify.attributes.all; -- required for synthesis  
  
entity Multiplier is  
  port (  
    A_in : in std_logic_vector(7 downto 0 );  
    B_in : in std_logic_vector(7 downto 0 );  
    clk : in std_logic;  
    reset : in std_logic;  
    START : in std_logic;  
    RC : out std_logic_vector(15 downto 0 );  
    STOP : out std_logic);  
  
end Multiplier;  
  
use work.all;  
architecture rtl of Multiplier is  
  
  signal ADD_cmd : std_logic;  
  signal Add_out : std_logic_vector(7 downto 0 );  
  signal C_out : std_logic;  
  signal LOAD_cmd : std_logic;  
  signal LSB : std_logic;  
  signal RA : std_logic_vector(7 downto 0 );  
  signal RB : std_logic_vector(7 downto 0 );  
  signal SHIFT_cmd : std_logic;  
  
  component RCA  
    port (  
      RA : in std_logic_vector(7 downto 0 );  
      RB : in std_logic_vector(7 downto 0 );  
      C_out : out std_logic;  
      Add_out : out std_logic_vector(7 downto 0 )  
    );  
  end component;  
  
  component Controller  
    port (  
      reset : in std_logic;  
      clk : in std_logic;  
      START : in std_logic;  
      LSB : in std_logic;  
      ADD_cmd : out std_logic;  
      SHIFT_cmd : out std_logic;  
      LOAD_cmd : out std_logic;  
      STOP : out std_logic  
    );  
  end component;  
  
  component Multiplicand  
    port (  
      reset : in std_logic;  
      A_in : in std_logic_vector(7 downto 0 );
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
        LOAD_cmd : in  std_logic;
        RA       : out std_logic_vector(7 downto 0 )
    );
end component;

component Multiplier_Result
    port (
        reset      : in  std_logic;
        clk        : in  std_logic;
        B_in       : in  std_logic_vector(7 downto 0 );
        LOAD_cmd   : in  std_logic;
        SHIFT_cmd  : in  std_logic;
        ADD_cmd    : in  std_logic;
        Add_out    : in  std_logic_vector(7 downto 0 );
        C_out      : in  std_logic;
        RC         : out std_logic_vector(15 downto 0 );
        LSB        : out std_logic;
        RB         : out std_logic_vector(7 downto 0 )
    );
end component;

begin

inst_RCA: RCA
    port map (
        RA => RA(7 downto 0),
        RB => RB(7 downto 0),
        C_out => C_out,
        Add_out => Add_out(7 downto 0)
    );

inst_Controller: Controller
    port map (
        reset => reset,
        clk => clk,
        START => START,
        LSB => LSB,
        ADD_cmd => ADD_cmd,
        SHIFT_cmd => SHIFT_cmd,
        LOAD_cmd => LOAD_cmd,
        STOP => STOP
    );

inst_Multiplicand: Multiplicand
    port map (
        reset => reset,
        A_in => A_in(7 downto 0),
        LOAD_cmd => LOAD_cmd,
        RA => RA(7 downto 0)
    );

inst_Multiplier_Result: Multiplier_Result
    port map (
        reset => reset,
        clk => clk,
        B_in => B_in(7 downto 0),
        LOAD_cmd => LOAD_cmd,
        SHIFT_cmd => SHIFT_cmd,
        ADD_cmd => ADD_cmd,
        Add_out => Add_out(7 downto 0),
        C_out => C_out,
        RC => RC(15 downto 0),
        LSB => LSB,
        RB => RB(7 downto 0)
    );

end rtl;
```

VHDL: TestBench

```
-----  
--  
-- TESTBENCH  
--  
-- Author   : Giovanni D'Aliesio  
--  
-- Description : Testbench generates clk and reset  
--               signals as well as numerous multiplies.  
--               It multiplies A and B where A starts from  
--               0 to 255 and B starts from 255 down to 0.  
--               The inputs and the results are stored in  
--               a text file (bus_log.txt) for off-line  
--               comparison.  
--  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use std.textio.all;           --required for file I/O  
use ieee.std_logic_textio.all; --required for file I/O  
  
entity TESTBENCH is  
  
end TESTBENCH;  
  
architecture BEHAVIORAL of TESTBENCH is  
  
component Multiplier  
  port (  
    A_in  : in  std_logic_vector(7 downto 0 );  
    B_in  : in  std_logic_vector(7 downto 0 );  
    clk   : in  std_logic;  
    RC    : out std_logic_vector(15 downto 0 );  
    reset : in  std_logic;  
    START : in  std_logic;  
    STOP  : out std_logic  
  );  
end component;  
  
signal A_in_TB, B_in_TB : std_logic_vector(7 downto 0 );  
signal clk_TB, reset_TB, START_TB : std_logic;  
signal STOP_TB : std_logic;  
signal RC_TB : std_logic_vector(15 downto 0);  
  
begin  
  
-- instantiate the Device Under Test  
inst_DUT : Multiplier  
  port map (  
    A_in => A_in_TB,  
    B_in => B_in_TB,  
    clk => clk_TB,  
    reset => reset_TB,  
    RC => RC_TB,  
    START => START_TB,  
    STOP => STOP_TB);  
  
-- Generate clock stimulus  
STIMULUS_CLK : process  
begin  
  clk_TB <= '0';  
  wait for 10 ns;  
  clk_TB <= '1';  
  
end process;
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
wait for 10 ns;
end process STIMULUS_CLK;

-- Generate reset stimulus
STIMULUS_RST : process
begin
    reset_TB <= '0';
    wait for 50 ns;
    reset_TB <= '1';
    wait;
end process STIMULUS_RST;

-- Generate multiplication requests
STIMULUS_START : process

file logFile : text is out "bus_log.txt"; -- set output file name
variable L: line;
variable A_temp, B_temp, i : integer;

begin

    write(L, string("A B Result")); -- include heading in file
    writeline(logFile,L);
    A_temp := 0; -- start A at 0
    B_temp := 255; -- start B at 255
    i := 1;

    for i in 1 to 256 loop
        A_in_TB <= STD_LOGIC_VECTOR(to_unsigned(A_temp,8));
        B_in_TB <= STD_LOGIC_VECTOR(to_unsigned(B_temp,8));

        START_TB <= '0';
        wait for 100 ns;
        START_TB <= '1'; -- request the multiplier to start
        wait for 100 ns;
        START_TB <= '0';
        wait until STOP_TB = '1'; -- wait for the multiplier to finish
        hwrite(L, A_in_TB); -- insert hex value of A in file
        write(L, string(" "));
        hwrite(L, B_in_TB); -- insert hex value of B in file
        write(L, string(" "));
        hwrite(L, RC_TB); -- insert hex value of result in file
        writeline(logFile,L);
        A_temp := A_temp + 1; -- increment value of A (Multiplicand)
        B_temp := B_temp - 1; -- decrement value of B (Multiplier)
    end loop;
    wait;

end process STIMULUS_START;

end BEHAVIORAL;
```

VHDL: 32-Bit Multiplier

```
-----  
--  
-- Library Name : DSD  
-- Unit Name : Multiplier_Result  
--  
-----  
-----  
-- Date : Mon Oct 27 14:13:51 2003  
--  
-- Author : Giovanni D'Aliesio  
--  
-- Description : Multiplier_Result performs the  
-- following:  
-- > loads B_in into register upon  
-- receiving LOAD_cmd  
-- > loads Adder output into register  
-- upon receiving ADD_cmd  
-- > shifts register right upon  
-- receiving SHIFT_cmd  
--  
-----  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity Multiplier_Result is  
port (reset : in std_logic ;  
      clk : in std_logic ;  
      B_in : in std_logic_vector (31 downto 0);  
      LOAD_cmd : in std_logic ;  
      SHIFT_cmd : in std_logic ;  
      ADD_cmd : in std_logic ;  
      Add_out : in std_logic_vector (31 downto 0);  
      C_out : in std_logic ;  
      RC : out std_logic_vector (63 downto 0);  
      LSB : out std_logic ;  
      RB : out std_logic_vector (31 downto 0));  
end;  
  
-----  
architecture rtl of Multiplier_Result is  
signal temp_register : std_logic_vector(64 downto 0);  
signal temp_Add : std_logic;  
  
begin  
  
process (clk, reset)  
begin  
    if reset='0' then  
        temp_register <= (others =>'0'); -- initialize temporary register  
        temp_Add <= '0';  
  
    elsif (clk'event and clk='1') then  
        if LOAD_cmd = '1' then  
            temp_register (64 downto 32) <= (others => '0');  
            temp_register(31 downto 0) <= B_in; -- load B_in into register  
        end if;  
  
        if ADD_cmd = '1' then  
            temp_Add <= '1';  
        end if;  
  
        if SHIFT_cmd = '1' then  
            if temp_Add = '1' then
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
        -- store adder output while shifting register right 1 bit
        temp_Add <= '0';
        temp_register <= '0' & C_out & Add_out & temp_register (31 downto 1);
    else
        -- no add - simply shift right 1 bit
        temp_register <= '0' & temp_register (64 downto 1);
    end if;
end if;
end process;

RB <= temp_register(63 downto 32);
LSB <= temp_register(0);
RC <= temp_register(63 downto 0);

end rtl;
```

```
-----
--
-- Library Name : DSD
-- Unit Name : Multiplicand
--
-----
-- Date      : Mon Oct 27 13:32:59 2003
--
-- Author    : Giovanni D'Aliesio
--
-- Description : Multiplicand is an 8-bit register
--               that is loaded when the LOAD_cmd is
--               received and cleared with reset.
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity Multiplicand is
port (reset      : in  std_logic ;
      A_in       : in  std_logic_vector (31 downto 0);
      LOAD_cmd   : in  std_logic ;
      RA        : out std_logic_vector (31 downto 0));
end;

-----
architecture struc of Multiplicand is

component DFF
port (
    reset : in  std_logic;
    clk   : in  std_logic;
    D     : in  std_logic;
    Q     : out std_logic
);
end component;

begin

DFFs: for i in 31 downto 0 generate

    DFFReg:DFF port map (reset, LOAD_cmd, A_in(i), RA(i));

end generate;

end struc;

-----
-----
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
-----
-- Date       : Mon Oct 27 13:32:59 2003
--
-- Author      : Giovanni D'Aliesio
--
-- Description : DFF is an active high D flip flop
--               with asynchronous clear.
--
-----

library ieee;
use ieee.std_logic_1164.all;

entity DFF is
port (reset   : in  std_logic ;
      clk     : in  std_logic ;
      D       : in  std_logic ;
      Q       : out std_logic);
end;

-----

architecture behav of DFF is
begin

    process (clk, reset)
    begin
        if reset='0' then
            Q <= '0';    -- clear register

            elsif (clk'event and clk='1') then
                Q <= D;    -- load register
            end if;
        end process;
    end behav;

-----

--
-- Library Name : DSD
-- Unit Name : Controller
--
-----

-- Date       : Mon Oct 27 12:36:47 2003
--
-- Author      : Giovanni D'Aliesio
--
-- Description : Controller is a finite state machine
--               that performs the following in each
--               state:
--               IDLE > samples the START signal
--               INIT  > commands the registers to be
--                   loaded
--               TEST  > samples the LSB
--               ADD   > indicates the Add result to be stored
--               SHIFT > commands the register to be shifted
--
-----

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity Controller is
port (reset   : in  std_logic ;
      clk     : in  std_logic ;
      START   : in  std_logic ;
      LSB     : in  std_logic ;
```


8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```

    ADD_cmd   : out std_logic ;
    SHIFT_cmd : out std_logic ;
    LOAD_cmd  : out std_logic ;
    STOP      : out std_logic);
end;

-----
architecture rtl of Controller is

    signal temp_count : std_logic_vector(4 downto 0);

    -- declare states
    type state_typ is (IDLE, INIT, TEST, ADD, SHIFT);
    signal state : state_typ;

begin

    process (clk, reset)
    begin
        if reset='0' then
            state <= IDLE;
            temp_count <= "00000";

        elsif (clk'event and clk='1') then

            case state is

                when IDLE =>
                    if START = '1' then
                        state <= INIT;
                    else
                        state <= IDLE;
                    end if;

                when INIT =>
                    state <= TEST;

                when TEST =>
                    if LSB = '0' then
                        state <= SHIFT;
                    else
                        state <= ADD;
                    end if;

                when ADD =>
                    state <= SHIFT;

                when SHIFT =>
                    if temp_count = "11111" then -- verify if finished
                        temp_count <= "00000"; -- re-initialize counter
                        state <= IDLE; -- ready for next multiply
                    else
                        temp_count <= temp_count + 1; -- increment counter
                        state <= TEST;
                    end if;

            end case;

        end if;

    end process;

    STOP <= '1' when state = IDLE else '0';
    ADD_cmd <= '1' when state = ADD else '0';
    SHIFT_cmd <= '1' when state = SHIFT else '0';
    LOAD_cmd <= '1' when state = INIT else '0';

end rtl;
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
-----
--
-- Library Name : DSD
-- Unit Name : Full_Adder
--
-----
-----
-- Date : Wed Sep 24 12:50:50 2003
--
-- Author : Giovanni D'Aliesio
--
-- Description : Basic Full Adder Block
--
-----
-----
library ieee;
use ieee.std_logic_1164.all;

entity Full_Adder is
port (X : in std_logic;
      Y : in std_logic;
      C_in : in std_logic;
      Sum : out std_logic ;
      C_out : out std_logic);
end;

-----
architecture rtl of Full_Adder is
begin

Sum <= X xor Y xor C_in;
C_out <= (X and Y) or (X and C_in) or (Y and C_in);

end rtl;

-----
--
-- Library Name : DSD
-- Unit Name : RCA
--
-----
-----
-- Date : Wed Sep 24 12:50:50 2003
--
-- Author : Giovanni D'Aliesio
--
-- Description : RCA is an 8-bit ripple carry
-- adder composed of 8 basic full
-- adder blocks.
--
-----
-----
library ieee;
use ieee.std_logic_1164.all;

entity RCA is
port (RA : in std_logic_vector (31 downto 0);
      RB : in std_logic_vector (31 downto 0);
      C_out : out std_logic ;
      Add_out : out std_logic_vector (31 downto 0));
end;

-----
architecture rtl of RCA is

signal c_temp : std_logic_vector(31 downto 0);

component Full_Adder
port (
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```

        X      : in  std_logic;
        Y      : in  std_logic;
        C_in   : in  std_logic;
        Sum    : out std_logic;
        C_out  : out std_logic
    );
end component;

begin

    c_temp(0) <= '0'; -- carry in of RCA is 0

Adders: for i in 31 downto 0 generate

-- assemble first 31 adders from 0 to 31
    Low: if i/=31 generate
        FA:Full_Adder port map (RA(i), RB(i), c_temp(i), Add_out(i), c_temp(i+1));
    end generate;

-- assemble last adder
    High: if i=31 generate
        FA:Full_Adder port map (RA(31), RB(31), c_temp(i), Add_out(31), C_out);
    end generate;

end generate;

end rtl;

-----
--
-- Library Name : DSD
-- Unit Name : Multiplier
--
-- Description : Complete multiplier
--
-----

library ieee;
use ieee.std_logic_1164.all;
--library synplify; -- required for synthesis
--use synplify.attributes.all; -- required for synthesis

entity Multiplier_32 is
    port (
        A_in : in  std_logic_vector(31 downto 0 );
        B_in : in  std_logic_vector(31 downto 0 );
        clk  : in  std_logic;
        reset : in  std_logic;
        START : in  std_logic;
        RC    : out std_logic_vector(63 downto 0 );
        STOP  : out std_logic);
end Multiplier_32;

use work.all;
architecture rtl of Multiplier_32 is

    signal ADD_cmd : std_logic;
    signal Add_out : std_logic_vector(31 downto 0 );
    signal C_out   : std_logic;
    signal LOAD_cmd : std_logic;
    signal LSB     : std_logic;
    signal RA      : std_logic_vector(31 downto 0 );
    signal RB      : std_logic_vector(31 downto 0 );
    signal SHIFT_cmd : std_logic;

    component RCA
        port (
            RA      : in  std_logic_vector(31 downto 0 );

```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
        RB      : in  std_logic_vector(31 downto 0 );
        C_out   : out std_logic;
        Add_out : out std_logic_vector(31 downto 0 )
    );
end component;

component Controller
    port (
        reset    : in  std_logic;
        clk      : in  std_logic;
        START    : in  std_logic;
        LSB      : in  std_logic;
        ADD_cmd  : out std_logic;
        SHIFT_cmd : out std_logic;
        LOAD_cmd : out std_logic;
        STOP     : out std_logic
    );
end component;

component Multiplicand
    port (
        reset    : in  std_logic;
        A_in     : in  std_logic_vector(31 downto 0 );
        LOAD_cmd : in  std_logic;
        RA       : out std_logic_vector(31 downto 0 )
    );
end component;

component Multiplier_Result
    port (
        reset    : in  std_logic;
        clk      : in  std_logic;
        B_in     : in  std_logic_vector(31 downto 0 );
        LOAD_cmd : in  std_logic;
        SHIFT_cmd : in  std_logic;
        ADD_cmd  : in  std_logic;
        Add_out  : in  std_logic_vector(31 downto 0 );
        C_out    : in  std_logic;
        RC       : out std_logic_vector(63 downto 0 );
        LSB      : out std_logic;
        RB       : out std_logic_vector(31 downto 0 )
    );
end component;

begin

inst_RCA: RCA
    port map (
        RA => RA(31 downto 0),
        RB => RB(31 downto 0),
        C_out => C_out,
        Add_out => Add_out(31 downto 0)
    );

inst_Controller: Controller
    port map (
        reset => reset,
        clk => clk,
        START => START,
        LSB => LSB,
        ADD_cmd => ADD_cmd,
        SHIFT_cmd => SHIFT_cmd,
        LOAD_cmd => LOAD_cmd,
        STOP => STOP
    );

inst_Multiplicand: Multiplicand
    port map (
        reset => reset,
        A_in => A_in(31 downto 0),
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
        LOAD_cmd => LOAD_cmd,
        RA => RA(31 downto 0)
    );

inst_Multiplier_Result: Multiplier_Result
    port map (
        reset => reset,
        clk => clk,
        B_in => B_in(31 downto 0),
        LOAD_cmd => LOAD_cmd,
        SHIFT_cmd => SHIFT_cmd,
        ADD_cmd => ADD_cmd,
        Add_out => Add_out(31 downto 0),
        C_out => C_out,
        RC => RC(63 downto 0),
        LSB => LSB,
        RB => RB(31 downto 0)
    );
end rtl;
```

VHDL: 32-Bit Multiplier TestBench

```
-----  
--  
-- TESTBENCH  
--  
-- Author   : Giovanni D'Aliesio  
--  
-- Description : Testbench generates clk and reset  
--              signals as well as numerous multiplies.  
--              It multiplies A and B where A starts from  
--              0 to 255 and B starts from 255 down to 0.  
--              The inputs and the results are stored in  
--              a text file (bus_log.txt) for off-line  
--              comparison.  
--  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use std.textio.all;           --required for file I/O  
use ieee.std_logic_textio.all; --required for file I/O  
  
entity TESTBENCH_32 is  
  
end TESTBENCH_32;  
  
architecture BEHAVIORAL of TESTBENCH_32 is  
  
component Multiplier_32  
  port (  
    A_in  : in  std_logic_vector(31 downto 0 );  
    B_in  : in  std_logic_vector(31 downto 0 );  
    clk   : in  std_logic;  
    RC    : out std_logic_vector(63 downto 0 );  
    reset : in  std_logic;  
    START : in  std_logic;  
    STOP  : out std_logic  
  );  
end component;  
  
signal A_in_TB, B_in_TB : std_logic_vector(31 downto 0 );  
signal clk_TB, reset_TB, START_TB : std_logic;  
signal STOP_TB : std_logic;  
signal RC_TB : std_logic_vector(63 downto 0);  
  
begin  
  
-- instantiate the Device Under Test  
inst_DUT : Multiplier_32  
  port map (  
    A_in => A_in_TB,  
    B_in => B_in_TB,  
    clk => clk_TB,  
    reset => reset_TB,  
    RC => RC_TB,  
    START => START_TB,  
    STOP => STOP_TB);  
  
-- Generate clock stimulus  
STIMULUS_CLK : process  
begin  
  clk_TB <= '0';  
  wait for 10 ns;  
  clk_TB <= '1';  
  
end process;
```

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

```
    wait for 10 ns;
end process STIMULUS_CLK;

-- Generate reset stimulus
STIMULUS_RST : process
begin
    reset_TB <= '0';
    wait for 50 ns;
    reset_TB <= '1';
    wait;
end process STIMULUS_RST;

-- Generate multiplication requests
STIMULUS_START : process

file logFile : text is out "bus_log32.txt"; -- set output file name
variable L: line;
variable A_temp, B_temp, i : integer;

begin

    write(L, string("A B Result")); -- include heading in file
    writeline(logFile,L);
    A_temp := 1000000; -- start A at 1000000
    B_temp := 2000000; -- start B at 2000000
    i := 100000;

    for i in 100000 to 200000 loop
        A_in_TB <= STD_LOGIC_VECTOR(to_unsigned(A_temp,32));
        B_in_TB <= STD_LOGIC_VECTOR(to_unsigned(B_temp,32));

        START_TB <= '0';
        wait for 100 ns;
        START_TB <= '1'; -- request the multiplier to start
        wait for 100 ns;
        START_TB <= '0';
        wait until STOP_TB = '1'; -- wait for the multiplier to finish
        hwrite(L, A_in_TB); -- insert hex value of A in file
        write(L, string(" "));
        hwrite(L, B_in_TB); -- insert hex value of B in file
        write(L, string(" "));
        hwrite(L, RC_TB); -- insert hex value of result in file
        writeline(logFile,L);
        A_temp := A_temp + 1; -- increment value of A (Multiplicand)
        B_temp := B_temp - 1; -- decrement value of B (Multiplier)
    end loop;
    wait;

end process STIMULUS_START;

end BEHAVIORAL;
```

APPENDIX B: SIMULATION RESULT FILES

Simulation output for multiplier:
bus_log.txt:

| A | B | Result | A | B | Result | A | B | Result |
|----|----|--------|----|----|--------|----|----|--------|
| 00 | FF | 0000 | 57 | A8 | 3918 | AD | 52 | 376A |
| 01 | FE | 00FE | 58 | A7 | 3968 | AE | 51 | 370E |
| 02 | FD | 01FA | 59 | A6 | 39B6 | AF | 50 | 36B0 |
| 03 | FC | 02F4 | 5A | A5 | 3A02 | B0 | 4F | 3650 |
| 04 | FB | 03EC | 5B | A4 | 3A4C | B1 | 4E | 35EE |
| 05 | FA | 04E2 | 5C | A3 | 3A94 | B2 | 4D | 358A |
| 06 | F9 | 05D6 | 5D | A2 | 3ADA | B3 | 4C | 3524 |
| 07 | F8 | 06C8 | 5E | A1 | 3B1E | B4 | 4B | 34BC |
| 08 | F7 | 07B8 | 5F | A0 | 3B60 | B5 | 4A | 3452 |
| 09 | F6 | 08A6 | 60 | 9F | 3BA0 | B6 | 49 | 33E6 |
| 0A | F5 | 0992 | 61 | 9E | 3BDE | B7 | 48 | 3378 |
| 0B | F4 | 0A7C | 62 | 9D | 3C1A | B8 | 47 | 3308 |
| 0C | F3 | 0B64 | 63 | 9C | 3C54 | B9 | 46 | 3296 |
| 0D | F2 | 0C4A | 64 | 9B | 3C8C | BA | 45 | 3222 |
| 0E | F1 | 0D2E | 65 | 9A | 3CC2 | BB | 44 | 31AC |
| 0F | F0 | 0E10 | 66 | 99 | 3CF6 | BC | 43 | 3134 |
| 10 | EF | 0EF0 | 67 | 98 | 3D28 | BD | 42 | 30BA |
| 11 | EE | 0FCE | 68 | 97 | 3D58 | BE | 41 | 303E |
| 12 | ED | 10AA | 69 | 96 | 3D86 | BF | 40 | 2FC0 |
| 13 | EC | 1184 | 6A | 95 | 3DB2 | C0 | 3F | 2F40 |
| 14 | EB | 125C | 6B | 94 | 3DDC | C1 | 3E | 2EBE |
| 15 | EA | 1332 | 6C | 93 | 3E04 | C2 | 3D | 2E3A |
| 16 | E9 | 1406 | 6D | 92 | 3E2A | C3 | 3C | 2DB4 |
| 17 | E8 | 14D8 | 6E | 91 | 3E4E | C4 | 3B | 2D2C |
| 18 | E7 | 15A8 | 6F | 90 | 3E70 | C5 | 3A | 2CA2 |
| 19 | E6 | 1676 | 70 | 8F | 3E90 | C6 | 39 | 2C16 |
| 1A | E5 | 1742 | 71 | 8E | 3EAE | C7 | 38 | 2B88 |
| 1B | E4 | 180C | 72 | 8D | 3ECA | C8 | 37 | 2AF8 |
| 1C | E3 | 18D4 | 73 | 8C | 3EE4 | C9 | 36 | 2A66 |
| 1D | E2 | 199A | 74 | 8B | 3EFC | CA | 35 | 29D2 |
| 1E | E1 | 1A5E | 75 | 8A | 3F12 | CB | 34 | 293C |
| 1F | E0 | 1B20 | 76 | 89 | 3F26 | CC | 33 | 28A4 |
| 20 | DF | 1BE0 | 77 | 88 | 3F38 | CD | 32 | 280A |
| 21 | DE | 1C9E | 78 | 87 | 3F48 | CE | 31 | 276E |
| 22 | DD | 1D5A | 79 | 86 | 3F56 | CF | 30 | 26D0 |
| 23 | DC | 1E14 | 7A | 85 | 3F62 | D0 | 2F | 2630 |
| 24 | DB | 1ECC | 7B | 84 | 3F6C | D1 | 2E | 258E |
| 25 | DA | 1F82 | 7C | 83 | 3F74 | D2 | 2D | 24EA |
| 26 | D9 | 2036 | 7D | 82 | 3F7A | D3 | 2C | 2444 |
| 27 | D8 | 20E8 | 7E | 81 | 3F7E | D4 | 2B | 239C |
| 28 | D7 | 2198 | 7F | 80 | 3F80 | D5 | 2A | 22F2 |
| 29 | D6 | 2246 | 80 | 7F | 3F80 | D6 | 29 | 2246 |
| 2A | D5 | 22F2 | 81 | 7E | 3F7E | D7 | 28 | 2198 |
| 2B | D4 | 239C | 82 | 7D | 3F7A | D8 | 27 | 20E8 |
| 2C | D3 | 2444 | 83 | 7C | 3F74 | D9 | 26 | 2036 |
| 2D | D2 | 24EA | 84 | 7B | 3F6C | DA | 25 | 1F82 |
| 2E | D1 | 258E | 85 | 7A | 3F62 | DB | 24 | 1ECC |
| 2F | D0 | 2630 | 86 | 79 | 3F56 | DC | 23 | 1E14 |
| 30 | CF | 26D0 | 87 | 78 | 3F48 | DD | 22 | 1D5A |
| 31 | CE | 276E | 88 | 77 | 3F38 | DE | 21 | 1C9E |
| 32 | CD | 280A | 89 | 76 | 3F26 | DF | 20 | 1BE0 |
| 33 | CC | 28A4 | 8A | 75 | 3F12 | E0 | 1F | 1B20 |
| 34 | CB | 293C | 8B | 74 | 3EFC | E1 | 1E | 1A5E |
| 35 | CA | 29D2 | 8C | 73 | 3EE4 | E2 | 1D | 199A |
| 36 | C9 | 2A66 | 8D | 72 | 3ECA | E3 | 1C | 18D4 |
| 37 | C8 | 2AF8 | 8E | 71 | 3EAE | E4 | 1B | 180C |
| 38 | C7 | 2B88 | 8F | 70 | 3E90 | E5 | 1A | 1742 |
| 39 | C6 | 2C16 | 90 | 6F | 3E70 | E6 | 19 | 1676 |
| 3A | C5 | 2CA2 | 91 | 6E | 3E4E | E7 | 18 | 15A8 |
| 3B | C4 | 2D2C | 92 | 6D | 3E2A | E8 | 17 | 14D8 |

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

| | | |
|------------|------------|------------|
| 3C C3 2DB4 | 93 6C 3E04 | E9 16 1406 |
| 3D C2 2E3A | 94 6B 3DDC | EA 15 1332 |
| 3E C1 2EBE | 95 6A 3DB2 | EB 14 125C |
| 3F C0 2F40 | 96 69 3D86 | EC 13 1184 |
| 40 BF 2FC0 | 97 68 3D58 | ED 12 10AA |
| 41 BE 303E | 98 67 3D28 | EE 11 0FCE |
| 42 BD 30BA | 99 66 3CF6 | EF 10 0EF0 |
| 43 BC 3134 | 9A 65 3CC2 | F0 0F 0E10 |
| 44 BB 31AC | 9B 64 3C8C | F1 0E 0D2E |
| 45 BA 3222 | 9C 63 3C54 | F2 0D 0C4A |
| 46 B9 3296 | 9D 62 3C1A | F3 0C 0B64 |
| 47 B8 3308 | 9E 61 3BDE | F4 0B 0A7C |
| 48 B7 3378 | 9F 60 3BA0 | F5 0A 0992 |
| 49 B6 33E6 | A0 5F 3B60 | F6 09 08A6 |
| 4A B5 3452 | A1 5E 3B1E | F7 08 07B8 |
| 4B B4 34BC | A2 5D 3ADA | F8 07 06C8 |
| 4C B3 3524 | A3 5C 3A94 | F9 06 05D6 |
| 4D B2 358A | A4 5B 3A4C | FA 05 04E2 |
| 4E B1 35EE | A5 5A 3A02 | FB 04 03EC |
| 4F B0 3650 | A6 59 39B6 | FC 03 02F4 |
| 50 AF 36B0 | A7 58 3968 | FD 02 01FA |
| 51 AE 370E | A8 57 3918 | FE 01 00FE |
| 52 AD 376A | A9 56 38C6 | FF 00 0000 |
| 53 AC 37C4 | AA 55 3872 | |
| 54 AB 381C | AB 54 381C | |
| 55 AA 3872 | AC 53 37C4 | |
| 56 A9 38C6 | | |

Simulation output for 32-bit multiplier:

bus_log.txt:

| A | B | Result | A | B | Result |
|----------|----------|------------------|----------|----------|------------------|
| 000F4240 | 001E8480 | 000001D1A94A2000 | 000F4295 | 001E842B | 000001D1AE5B0307 |
| 000F4241 | 001E847F | 000001D1A959623F | 000F4296 | 001E842A | 000001D1AE6A449C |
| 000F4242 | 001E847E | 000001D1A968A47C | 000F4297 | 001E8429 | 000001D1AE79862F |
| 000F4243 | 001E847D | 000001D1A977E6B7 | 000F4298 | 001E8428 | 000001D1AE88C7C0 |
| 000F4244 | 001E847C | 000001D1A98728F0 | 000F4299 | 001E8427 | 000001D1AE98094F |
| 000F4245 | 001E847B | 000001D1A9966B27 | 000F429A | 001E8426 | 000001D1AEA74ADC |
| 000F4246 | 001E847A | 000001D1A9A5AD5C | 000F429B | 001E8425 | 000001D1AEB68C67 |
| 000F4247 | 001E8479 | 000001D1A9B4EF8F | 000F429C | 001E8424 | 000001D1AEC5CDF0 |
| 000F4248 | 001E8478 | 000001D1A9C431C0 | 000F429D | 001E8423 | 000001D1AED50F77 |
| 000F4249 | 001E8477 | 000001D1A9D373EF | 000F429E | 001E8422 | 000001D1AEE450FC |
| 000F424A | 001E8476 | 000001D1A9E2B61C | 000F429F | 001E8421 | 000001D1AEF3927F |
| 000F424B | 001E8475 | 000001D1A9F1F847 | 000F42A0 | 001E8420 | 000001D1AF02D400 |
| 000F424C | 001E8474 | 000001D1AA013A70 | 000F42A1 | 001E841F | 000001D1AF12157F |
| 000F424D | 001E8473 | 000001D1AA107C97 | 000F42A2 | 001E841E | 000001D1AF2156FC |
| 000F424E | 001E8472 | 000001D1AA1FBEBE | 000F42A3 | 001E841D | 000001D1AF309877 |
| 000F424F | 001E8471 | 000001D1AA2F00DF | 000F42A4 | 001E841C | 000001D1AF3FD9F0 |
| 000F4250 | 001E8470 | 000001D1AA3E4300 | 000F42A5 | 001E841B | 000001D1AF4F1B67 |
| 000F4251 | 001E846F | 000001D1AA4D851F | 000F42A6 | 001E841A | 000001D1AF5E5CDC |
| 000F4252 | 001E846E | 000001D1AA5CC73C | 000F42A7 | 001E8419 | 000001D1AF6D9E4F |
| 000F4253 | 001E846D | 000001D1AA6C0957 | 000F42A8 | 001E8418 | 000001D1AF7CDFC0 |
| 000F4254 | 001E846C | 000001D1AA7B4B70 | 000F42A9 | 001E8417 | 000001D1AF8C212F |
| 000F4255 | 001E846B | 000001D1AA8A8D87 | 000F42AA | 001E8416 | 000001D1AF9B629C |
| 000F4256 | 001E846A | 000001D1AA99CF9C | 000F42AB | 001E8415 | 000001D1AFAAA407 |
| 000F4257 | 001E8469 | 000001D1AAA911AF | 000F42AC | 001E8414 | 000001D1AFB9E570 |
| 000F4258 | 001E8468 | 000001D1AAB853C0 | 000F42AD | 001E8413 | 000001D1AFC926D7 |
| 000F4259 | 001E8467 | 000001D1AAC795CF | 000F42AE | 001E8412 | 000001D1AFD8683C |
| 000F425A | 001E8466 | 000001D1AAD6D7DC | 000F42AF | 001E8411 | 000001D1AFE7A99F |
| 000F425B | 001E8465 | 000001D1AAE619E7 | 000F42B0 | 001E8410 | 000001D1AFF6EB00 |
| 000F425C | 001E8464 | 000001D1AAF55BF0 | 000F42B1 | 001E840F | 000001D1B0062C5F |
| 000F425D | 001E8463 | 000001D1AB049DF7 | 000F42B2 | 001E840E | 000001D1B0156DBC |
| 000F425E | 001E8462 | 000001D1AB13DFFC | 000F42B3 | 001E840D | 000001D1B024AF17 |
| 000F425F | 001E8461 | 000001D1AB2321FF | 000F42B4 | 001E840C | 000001D1B033F070 |
| 000F4260 | 001E8460 | 000001D1AB326400 | 000F42B5 | 001E840B | 000001D1B04331C7 |
| 000F4261 | 001E845F | 000001D1AB41A5FF | 000F42B6 | 001E840A | 000001D1B052731C |
| 000F4262 | 001E845E | 000001D1AB50E7FC | 000F42B7 | 001E8409 | 000001D1B061B46F |

8-by-8 Bit Shift/Add Multiplier
Giovanni D'Aliesio

| | | | | | |
|----------|----------|------------------|----------|----------|------------------|
| 000F4263 | 001E845D | 000001D1AB6029F7 | 000F42B8 | 001E8408 | 000001D1B070F5C0 |
| 000F4264 | 001E845C | 000001D1AB6F6BF0 | 000F42B9 | 001E8407 | 000001D1B080370F |
| 000F4265 | 001E845B | 000001D1AB7EAE77 | 000F42BA | 001E8406 | 000001D1B08F785C |
| 000F4266 | 001E845A | 000001D1AB8DEFDC | 000F42BB | 001E8405 | 000001D1B09EB9A7 |
| 000F4267 | 001E8459 | 000001D1AB9D31CF | 000F42BC | 001E8404 | 000001D1B0ADF0 |
| 000F4268 | 001E8458 | 000001D1ABAC73C0 | 000F42BD | 001E8403 | 000001D1B0BD3C37 |
| 000F4269 | 001E8457 | 000001D1ABBB5AF | 000F42BE | 001E8402 | 000001D1B0CC7D7C |
| 000F426A | 001E8456 | 000001D1ABCAF79C | 000F42BF | 001E8401 | 000001D1B0DBEBF |
| 000F426B | 001E8455 | 000001D1ABDA3987 | 000F42C0 | 001E8400 | 000001D1B0EB0000 |
| 000F426C | 001E8454 | 000001D1ABE97B70 | 000F42C1 | 001E83FF | 000001D1B0FA413F |
| 000F426D | 001E8453 | 000001D1ABF8BD57 | 000F42C2 | 001E83FE | 000001D1B109827C |
| 000F426E | 001E8452 | 000001D1AC07FF3C | 000F42C3 | 001E83FD | 000001D1B118C3B7 |
| 000F426F | 001E8451 | 000001D1AC17411F | 000F42C4 | 001E83FC | 000001D1B12804F0 |
| 000F4270 | 001E8450 | 000001D1AC268300 | 000F42C5 | 001E83FB | 000001D1B1374627 |
| 000F4271 | 001E844F | 000001D1AC35C4DF | 000F42C6 | 001E83FA | 000001D1B146875C |
| 000F4272 | 001E844E | 000001D1AC4506BC | 000F42C7 | 001E83F9 | 000001D1B155C88F |
| 000F4273 | 001E844D | 000001D1AC544897 | 000F42C8 | 001E83F8 | 000001D1B16509C0 |
| 000F4274 | 001E844C | 000001D1AC638A70 | 000F42C9 | 001E83F7 | 000001D1B1744AEF |
| 000F4275 | 001E844B | 000001D1AC72CC47 | 000F42CA | 001E83F6 | 000001D1B1838C1C |
| 000F4276 | 001E844A | 000001D1AC820E1C | 000F42CB | 001E83F5 | 000001D1B192CD47 |
| 000F4277 | 001E8449 | 000001D1AC914FEF | 000F42CC | 001E83F4 | 000001D1B1A20E70 |
| 000F4278 | 001E8448 | 000001D1ACA091C0 | 000F42CD | 001E83F3 | 000001D1B1B14F97 |
| 000F4279 | 001E8447 | 000001D1ACAFD38F | 000F42CE | 001E83F2 | 000001D1B1C090BC |
| 000F427A | 001E8446 | 000001D1ACBF155C | 000F42CF | 001E83F1 | 000001D1B1CFD1DF |
| 000F427B | 001E8445 | 000001D1ACCE5727 | 000F42D0 | 001E83F0 | 000001D1B1DF1300 |
| 000F427C | 001E8444 | 000001D1ACDD98F0 | 000F42D1 | 001E83EF | 000001D1B1EE541F |
| 000F427D | 001E8443 | 000001D1ACECDAB7 | 000F42D2 | 001E83EE | 000001D1B1FD953C |
| 000F427E | 001E8442 | 000001D1ACFC1C7C | 000F42D3 | 001E83ED | 000001D1B20CD657 |
| 000F427F | 001E8441 | 000001D1AD0B5E3F | 000F42D4 | 001E83EC | 000001D1B21C1770 |
| 000F4280 | 001E8440 | 000001D1AD1AA000 | 000F42D5 | 001E83EB | 000001D1B22B5887 |
| 000F4281 | 001E843F | 000001D1AD29E1BF | 000F42D6 | 001E83EA | 000001D1B23A999C |
| 000F4282 | 001E843E | 000001D1AD39237C | 000F42D7 | 001E83E9 | 000001D1B249DAAF |
| 000F4283 | 001E843D | 000001D1AD486537 | 000F42D8 | 001E83E8 | 000001D1B2591BC0 |
| 000F4284 | 001E843C | 000001D1AD57A6F0 | 000F42D9 | 001E83E7 | 000001D1B2685CCF |
| 000F4285 | 001E843B | 000001D1AD66E8A7 | 000F42DA | 001E83E6 | 000001D1B2779DDC |
| 000F4286 | 001E843A | 000001D1AD762A5C | 000F42DB | 001E83E5 | 000001D1B286DEE7 |
| 000F4287 | 001E8439 | 000001D1AD856C0F | 000F42DC | 001E83E4 | 000001D1B2961FF0 |
| 000F4288 | 001E8438 | 000001D1AD94ADC0 | 000F42DD | 001E83E3 | 000001D1B2A560F7 |
| 000F4289 | 001E8437 | 000001D1ADA3EF6F | 000F42DE | 001E83E2 | 000001D1B2B4A1FC |
| 000F428A | 001E8436 | 000001D1ADB3311C | 000F42DF | 001E83E1 | 000001D1B2C3E2FF |
| 000F428B | 001E8435 | 000001D1ADC272C7 | 000F42E0 | 001E83E0 | 000001D1B2D32400 |
| 000F428C | 001E8434 | 000001D1ADD1B470 | 000F42E1 | 001E83DF | 000001D1B2E264FF |
| 000F428D | 001E8433 | 000001D1ADE0F617 | 000F42E2 | 001E83DE | 000001D1B2F1A5FC |
| 000F428E | 001E8432 | 000001D1ADF037BC | 000F42E3 | 001E83DD | 000001D1B300E6F7 |
| 000F428F | 001E8431 | 000001D1ADFF795F | 000F42E4 | 001E83DC | 000001D1B31027F0 |
| 000F4290 | 001E8430 | 000001D1AE0EBB00 | 000F42E5 | 001E83DB | 000001D1B31F68E7 |
| 000F4291 | 001E842F | 000001D1AE1DFC9F | 000F42E6 | 001E83DA | 000001D1B32EA9DC |
| 000F4292 | 001E842E | 000001D1AE2D3E3C | 000F42E7 | 001E83D9 | 000001D1B33DEACF |
| 000F4293 | 001E842D | 000001D1AE3C7FD7 | 000F42E8 | 001E83D8 | 000001D1B34D2BC0 |
| 000F4294 | 001E842C | 000001D1AE4BC170 | 000F42E9 | 001E83D7 | 000001D1B35C6CAF |
| | | | 000F42EA | 001E83D6 | 000001D1B36BAD9C |
| | | | 000F42EB | 001E83D5 | 000001D1B37AE87 |
| | | | 000F42EC | 001E83D4 | 000001D1B38A2F70 |

APPENDIX C: SYNTHESIS REPORT FILES

Synthesis Report File for RCA version with Behavioral DFF:

Performance Summary

Worst slack in design: 989.238

| Clock | Requested | Estimated | Requested | Estimated | |
|-------------------------|-----------|-----------|-----------|-----------|-------|
| Starting Clock | Frequency | Frequency | Period | Period | Slack |
| Type | | | | | |
| clk | 1.0 MHz | 92.9 MHz | 1000.000 | 10.762 | |
| 989.238 inferred | | | | | |
| load_cmd_inferred_clock | 1.0 MHz | 96.9 MHz | 1000.000 | 10.316 | |
| 989.684 inferred | | | | | |

Worst Paths Information

Path information for path number 1:

- Setup time: -0.420
= Required time: 1000.420

- Propagation time: 11.182
= Slack (critical) : 989.238

Starting point:

inst_Multiplier_Result.temp_register[8] / Q

Ending point:

inst_Multiplier_Result.temp_register[15] / D

The start point is clocked by clk [rising] on pin C
The end point is clocked by clk [rising] on pin C

Resource Usage Report for Multiplier

Mapping to part: xcv50bg256-4

Cell usage:

FDCE 17 uses
FDC 15 uses
FDP 1 use
keepbuf 1 use
GND 1 use
VCC 1 use

I/O primitives:

IBUF 18 uses
OBUF 17 uses

BUFGP 1 use

I/O Register bits: 8
Register bits not including I/Os: 25 (1%)

Global buffer usage summary
BUFGs + BUFGPs: 1 of 4 (25%)

Mapping Summary:
Total LUTs: 45 (2%)

Mapper successful!

Synthesis Report File for RCA version with Behavioral DFF Synthesized for Actel ACT3:

Performance Summary

Worst slack in design: 976.710

| Clock | Requested | Estimated | Requested | Estimated | |
|-------------------------|-----------|-----------|-----------|-----------|-------|
| Starting Clock Type | Frequency | Frequency | Period | Period | Slack |
| clk | 1.0 MHz | 42.9 MHz | 1000.000 | 23.290 | |
| 976.710 inferred | | | | | |
| load_cmd_inferred_clock | 1.0 MHz | 43.7 MHz | 1000.000 | 22.865 | |
| 977.135 inferred | | | | | |

Worst Paths Information

Path information for path number 1:

- Setup time: 0.000
 = Required time: 1000.000

- Propagation time: 23.290
 = Slack (critical) : 976.710

Starting point: inst_Multiplier_Result.temp_register[8] / q
 Ending point: inst_Multiplier_Result.temp_register[14] / d0
 The start point is clocked by clk [falling] on pin s00
 The end point is clocked by load_cmd_inferred_clock [falling] on pin s00

Synthesized design as a chip
 Resource Usage Report of Multiplier

Target Part: a1415a-3
 Combinational Cells: 44 of 96 (46%)
 Sequential Cells: 33 of 104 (32%)
 Total Cells: 77 of 200 (39%)
 Clock Buffers: 2
 IO Cells: 36

Details:

and2b: 2 comb:1
 and3: 1 comb:1
 buff: 2 comb:1
 cm8: 22 comb:1
 dfpl: 1 comb:2
 or2b: 1 comb:1
 xnor2: 4 comb:1
 xor2: 10 comb:1

dfc1b: 8 seq:1
 dfe3c: 4 seq:1
 dfm8a: 21 seq:1

clkbuf: 1 clock buffer
 inbuf: 18
 outbuf: 17

clkint: 1 clock buffer

keepbuf: 1

Found clock clk with period 1000.00ns
 Found clock load_cmd_inferred_clock with period 1000.00ns

Synthesis Report File for RCA version with Structural DFF:

Performance Summary

Worst slack in design: 989.238

| | Requested | Estimated | Requested | Estimated | |
|---------------------|-----------|-----------|-----------|-----------|---------|
| Clock | | | | | |
| Starting Clock Type | Frequency | Frequency | Period | Period | Slack |
| clk | 1.0 MHz | 92.9 MHz | 1000.000 | 10.762 | 989.238 |
| inferred | | | | | |

Worst Paths Information

Path information for path number 1:

- Setup time: -0.420
= Required time: 1000.420

- Propagation time: 11.182
= Slack (critical) : 989.238

Starting point: inst_Multiplier_Result.temp_register[8] / Q
Ending point: inst_Multiplier_Result.temp_register[15] / D
The start point is clocked by clk [rising] on pin C
The end point is clocked by clk [rising] on pin C

Resource Usage Report for Multiplier

Mapping to part: xcv50bg256-4

Cell usage:

FDCE 17 uses
FDC 7 uses
FDP 1 use
GND 1 use
VCC 1 use

I/O primitives:

IBUF 18 uses
OBUF 17 uses

BUFGP 1 use

I/O Register bits: 0
Register bits not including I/Os: 25 (1%)

Global buffer usage summary
BUFGs + BUFGPs: 1 of 4 (25%)

Mapping Summary:
Total LUTs: 77 (5%)

Mapper successful!

Synthesis Report File for CSA version with Behavioral DFF:

Performance Summary

Worst slack in design: 991.398

| | Requested | Estimated | Requested | Estimated | |
|---------------------|-----------|-----------|-----------|-----------|---------|
| Clock | | | | | |
| Starting Clock Type | Frequency | Frequency | Period | Period | Slack |
| clk | 1.0 MHz | 92.9 MHz | 1000.000 | 10.762 | 989.238 |
| inferred | | | | | |

8-by-8 Bit Shift/Add Multiplier
Giovanni D'Aliesio

```

clk                1.0 MHz      116.2 MHz    1000.000     8.602     991.398
inferred
load_cmd_inferred_clock  1.0 MHz      122.6 MHz    1000.000     8.156     991.844
inferred

```

Worst Paths Information

Path information for path number 1:

```

- Setup time:                -0.420
= Required time:             1000.420

- Propagation time:          9.022
= Slack (critical) :        991.398

```

```

Starting point:              inst_Multiplier_Result.temp_register[8] / Q
Ending point:                inst_Multiplier_Result.temp_register[12] / D
The start point is clocked by clk [rising] on pin C
The end point is clocked by  clk [rising] on pin C

```

Resource Usage Report for Multiplier

Mapping to part: xcv50bg256-4

Cell usage:

```

FDCE                17 uses
FDC                 15 uses
FDP                  1 use
keepbuf             1 use
GND                  1 use
VCC                  1 use

```

I/O primitives:

```

IBUF                 18 uses
OBUF                 17 uses

```

```

BUFGP                1 use

```

```

I/O Register bits:      8
Register bits not including I/Os: 25 (1%)

```

Global buffer usage summary
BUFGs + BUFGPs: 1 of 4 (25%)

Mapping Summary:
Total LUTs: 50 (3%)

Mapper successful!

Synthesis Report File for 32-Bit Multiplier with RCA version with Behavioral DFF:

Performance Summary

Worst slack in design: 973.758

| | Requested | Estimated | Requested | Estimated | |
|-------------------------|-----------|-----------|-----------|-----------|-------|
| Clock | Frequency | Frequency | Period | Period | Slack |
| Starting Clock | | | | | |
| Type | | | | | |
| ----- | | | | | |
| clk | 1.0 MHz | 38.1 MHz | 1000.000 | 26.242 | |
| 973.758 inferred | | | | | |
| load_cmd_inferred_clock | 1.0 MHz | 38.8 MHz | 1000.000 | 25.796 | |
| 974.204 inferred | | | | | |
| ===== | | | | | |

Worst Paths Information

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

Path information for path number 1:

| | |
|-------------------------------|--|
| - Setup time: | -0.420 |
| = Required time: | 1000.420 |
| | |
| - Propagation time: | 26.662 |
| = Slack (critical) : | 973.758 |
| | |
| Starting point: | inst_Multiplier_Result.temp_register[32] / Q |
| Ending point: | inst_Multiplier_Result.temp_register[63] / D |
| The start point is clocked by | clk [rising] on pin C |
| The end point is clocked by | clk [rising] on pin C |

Resource Usage Report for Multiplier_32

Mapping to part: xcv50bg256-4

Cell usage:

| | |
|---------|---------|
| FDCE | 70 uses |
| FDC | 36 uses |
| VCC | 2 uses |
| GND | 2 uses |
| FDP | 1 use |
| MUXCY_L | 4 uses |
| XORCY | 5 uses |
| keepbuf | 1 use |

I/O primitives:

| | |
|------|---------|
| IBUF | 66 uses |
| OBUF | 65 uses |

BUFG 1 use

BUFGP 1 use

| | |
|-----------------------------------|---------|
| I/O Register bits: | 32 |
| Register bits not including I/Os: | 75 (4%) |


Global buffer usage summary
BUFGs + BUFGPs: 2 of 4 (50%)

Mapping Summary:
Total LUTs: 142 (9%)

Mapper successful!

APPENDIX D: PLACE & ROUTE REPORT FILES


The following figures show how the design is mapped into the target device, namely the Xilinx XCV50. It is included here for illustrative purposes only since it was performed beyond the scope of this project and as such not much detail is included. The main goal of including these figures for each of the synthesized designs is such that the timing results and differences between designs becomes more apparent when viewing the physical structure. It can be clearly noted that due to the structure of the FPGA slice, the version of the design that uses a structural D flip-flop actually requires a lot more real estate than does its behavioral equivalent.

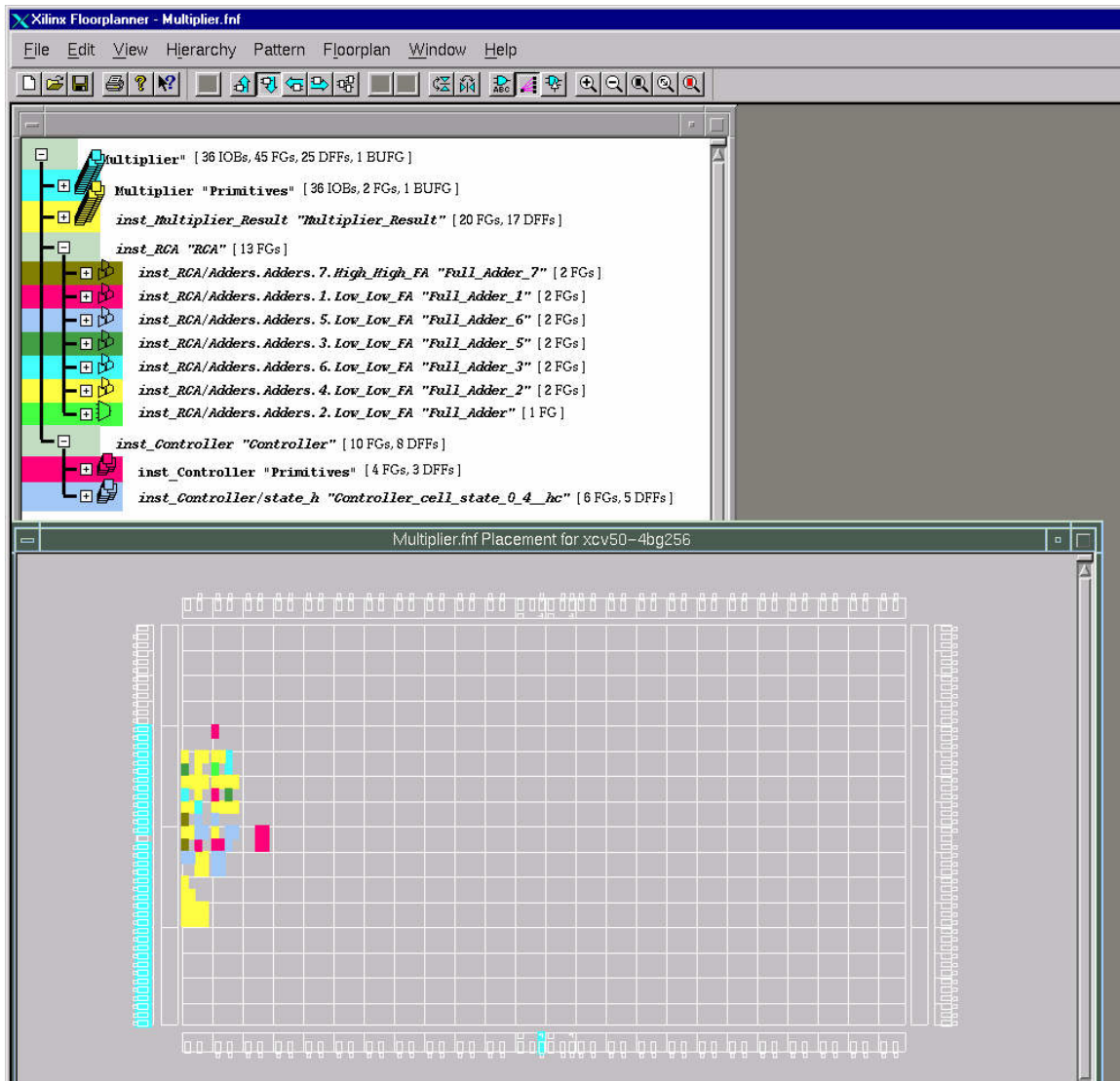

Mapped Design: 8-bit Multiplier with Ripple Carry Adder and behavioral D Flip-Flop


8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

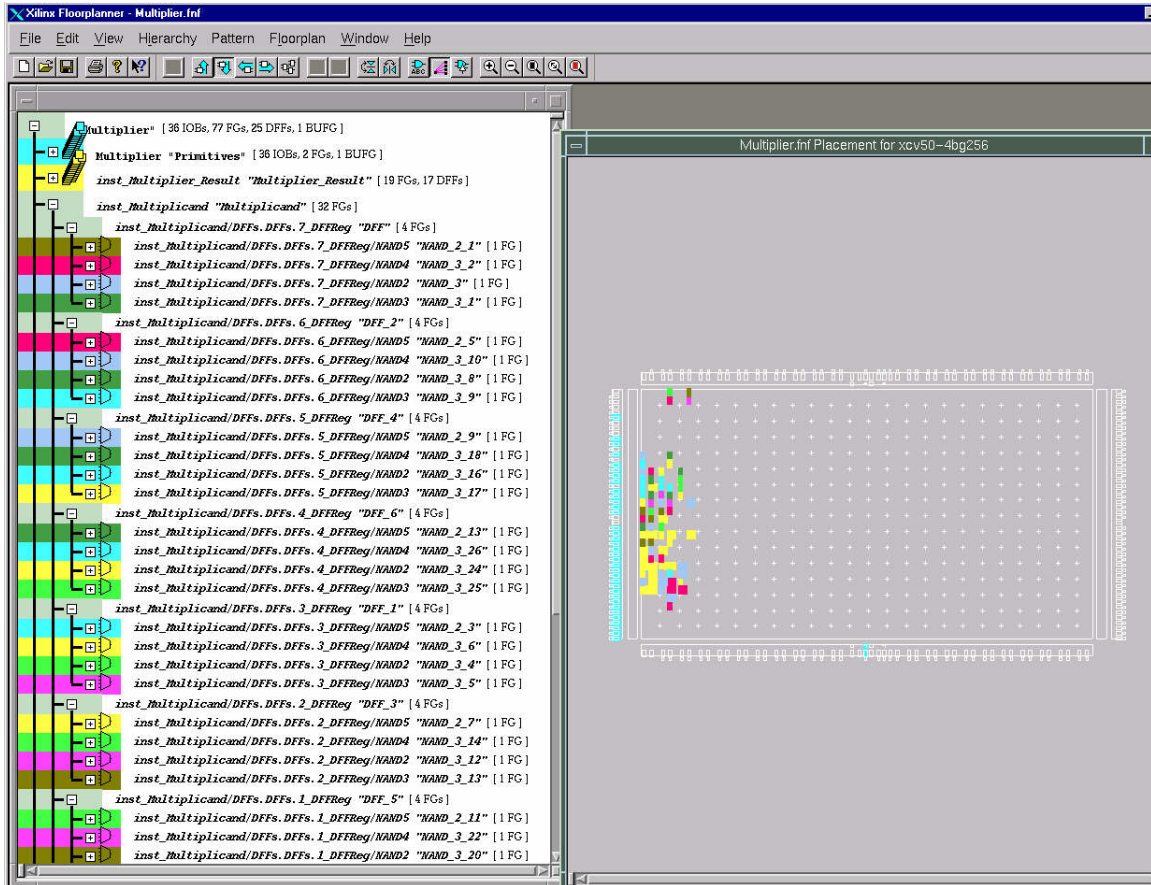

Mapped Design: 8-bit Multiplier with Ripple Carry Adder and structural D Flip-Flop

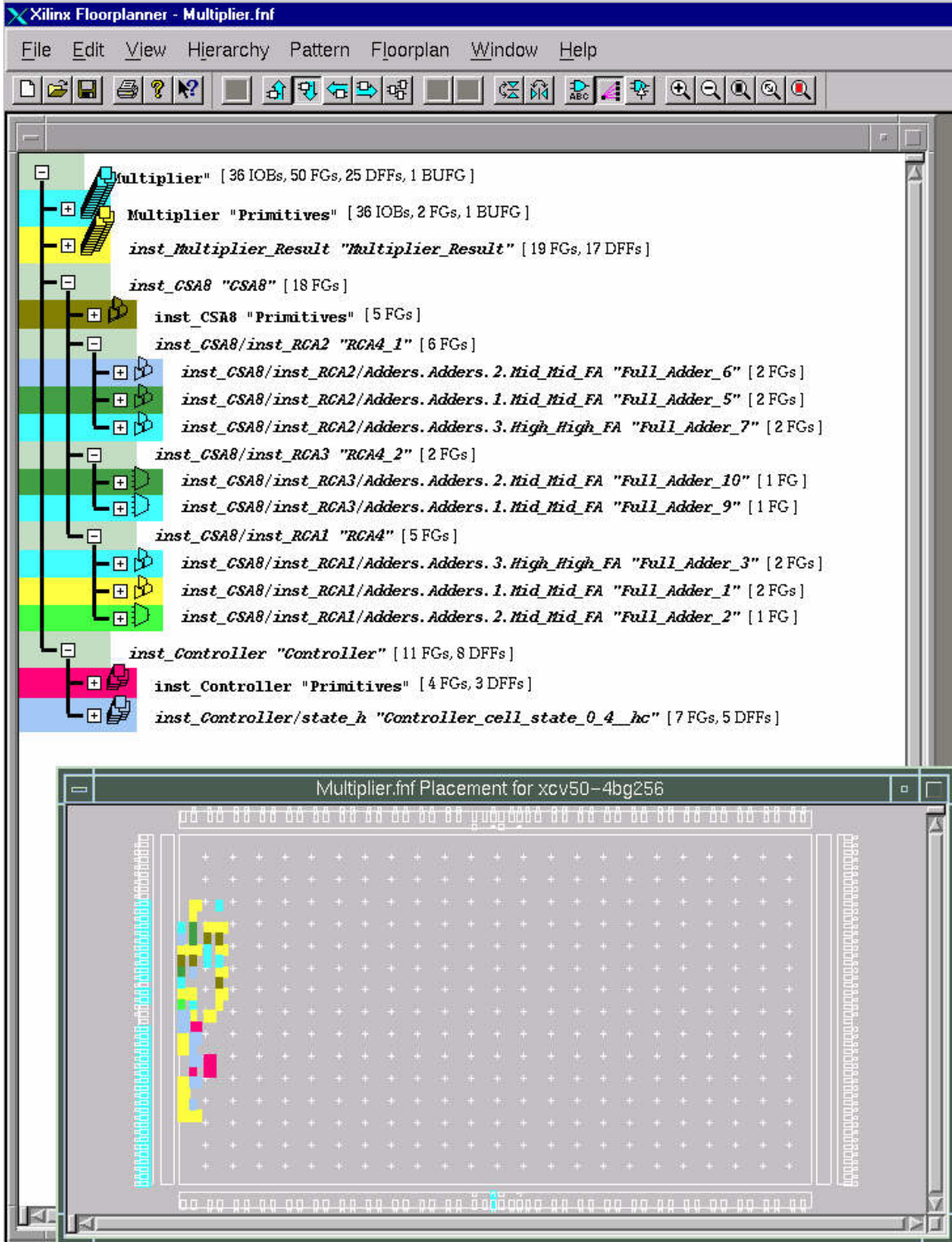
8-by-8 Bit Shift/Add Multiplier
Giovanni D'Aliesio



Mapped Design: 8-bit Multiplier with Carry Select Adder and behavioral D Flip-Flop

8-by-8 Bit Shift/Add Multiplier

Giovanni D'Aliesio

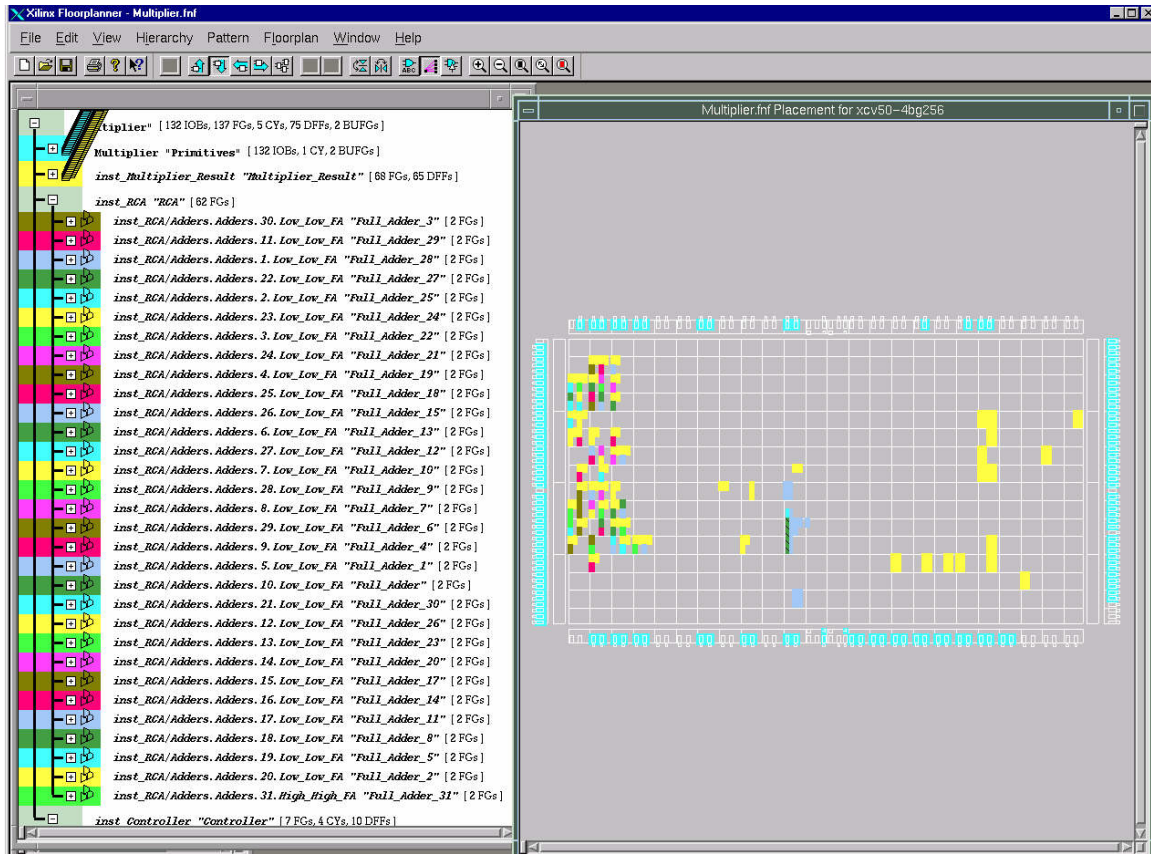

Mapped Design: 32-bit Multiplier with Ripple Carry Adder and behavioral D Flip-Flop