
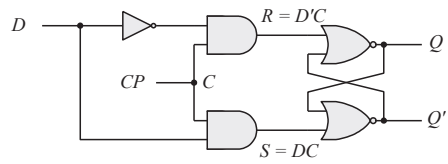


## CHAPTER 5


5.1 (a)

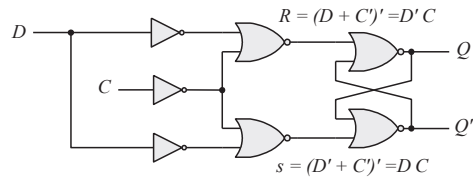


(b)



(c)

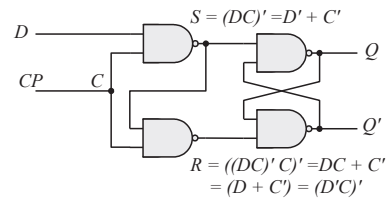


5.6

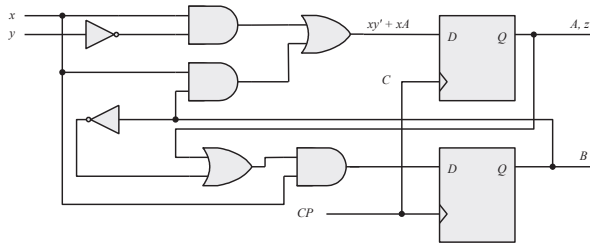

(b)  $A(t+1) = xy' + xB$   
 $B(t+1) = xA + xB'$   
 $z = A$


Present state		Inputs		Next state		Output	
A	B	x	y	A	B	z	
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	0
0	1	1	1	1	0	0	0
1	0	0	0	0	0	1	1
1	0	0	1	0	0	1	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	1
1	1	0	0	0	0	1	1
1	1	0	1	0	0	1	1
1	1	1	0	1	1	1	1
1	1	1	1	1	1	1	1

(c)

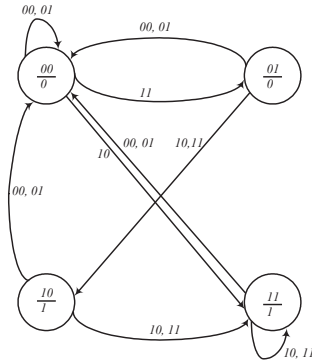

5.7

Present state	Inputs		Next state	Output
Q	x	y	Q	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

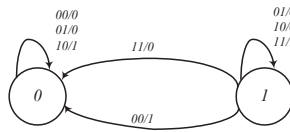

$S = x \oplus y \oplus Q$   
 $Q(t + 1) = xy + xQ + yQ$

5.8 A counter with a repeated sequence of 00, 01, 10.

Present state		Next state		FF Inputs	
A	B	A	B	$T_A$	$T_B$
0	0	0	0	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1


$$T_A = A + B$$

$$T_B = A' + B$$

Repeated sequence:

```

    00 → 01 → 10 →
  
```

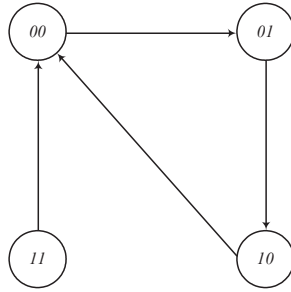

5.9


$$J_A = x \quad K_A = B$$

$$J_B = x \quad K_B = A'$$

$$A(t+1) = J_A A' + K_A A = xA' + B'A$$

$$B(t+1) = J_B B' + K_B B = xB' + AB$$


x	A	B	$xA' + B'A$	$xB' + AB$
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

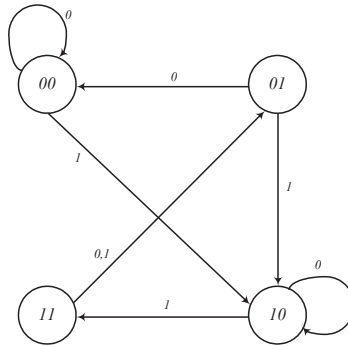

5.10 (a)  $J_A = Bx + B'y'$        $J_B = A'x$   
 $K_A = B'xy'$                $K_B = A + xy'$        $z = Axy + Bx'y'$

(b)


Present state		Inputs		Next state			FF Inputs		
A	B	x	y	A	B	z	$J_A$	$K_A$	$J_B$
0	0	0	0	1	0	0	1	0	0
0	0	0	1	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	1
0	0	1	1	0	1	0	0	0	1
0	1	0	0	0	1	1	0	0	0
0	1	0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	1	0	1
0	1	1	1	1	1	0	1	0	1
1	0	0	0	1	0	0	1	0	0
1	0	0	1	1	0	0	0	0	0
1	0	1	0	0	0	0	1	1	0
1	0	1	1	1	0	0	0	0	0
1	1	0	0	1	0	1	0	0	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	1	1	0	0

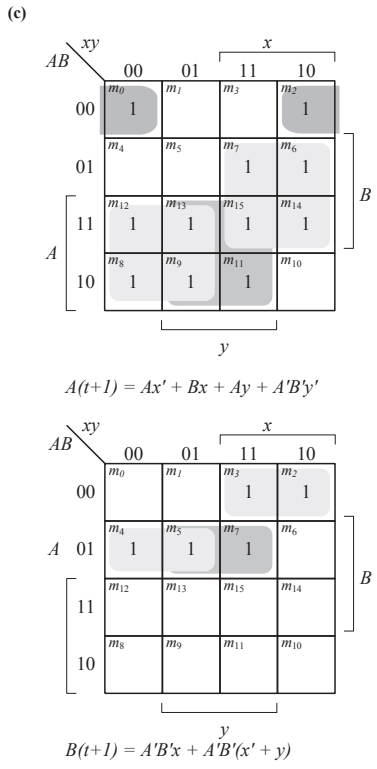

5.11

(a)  
 Present state: 00 00 01 00 01 11 00 01 11 10 00 01 11 10 10  
 Input: 0 1 0 1 1 0 1 1 1 0 1 1 1 1 0  
 Output: 0 0 1 0 0 1 0 0 0 1 0 0 0 0 1  
 Next state: 00 01 00 01 11 00 01 11 10 00 01 11 10 10 00  
 state:

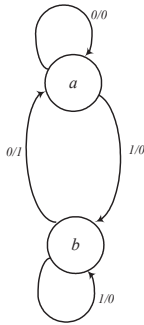(b)  
 State labels: a: 00, b: 10, c: 11, d: 01  
 c is equivalent to b  
 d is equivalent to c



(c)

input	state	next st	output
0	0	0	0
1	0	1	0
0	1	0	0
1	1	1	1

State machine: D-flop with direct input of the input to the original machine;  
 output logic:  $y = (\text{input}) \ \&\& \ (\text{state} == b)$

5.12

Present state	Next state		Output	
	0	1	0	1
a	f	b	0	0
b	d	a	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1



- 5.13 (a) State: *a f b c e d g h g g h a*  
 Input: 0 1 1 1 0 0 1 0 0 1 1  
 Output: 0 1 0 0 0 1 1 1 0 1 0
- (b) State: *a f b a b d g d g g d a*  
 Input: 0 1 1 1 0 0 1 0 0 1 1  
 Output: 0 1 0 0 0 1 1 1 0 1 0

5.14

	Present state ABCDE	Next state		Output	
		x=0	x=1	x=1	x=0
a	00001	00001	00010	0	0
b	00010	00100	01000	0	0
c	00100	00001	01000	0	0
d	01000	10000	01000	0	1
e	10000	00001	01000	0	1


5.15  $D_Q = Q'J + QK'$

Present state Q	Inputs J K		Next state Q	
	0	0 0		
0	0 1	0	Reset to 0	
0	1 0	1	Set to 1	
0	1 1	1	Complement	
1	0 0	1	No change	
1	0 1	0	Reset to 0	
1	1 0	1	Set to 1	
1	1 1	0	Complement	

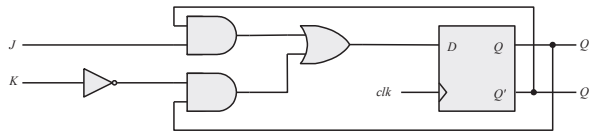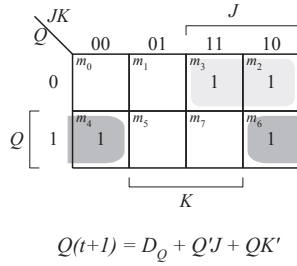


- 5.16 (a)  $D_A = Ax' + Bx$   
 $D_B = A'x + Bx'$

Present state		Input x	Next state	
A	B		A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

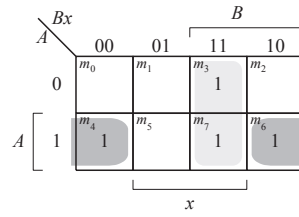

$$D_A = Ax' + Bx$$

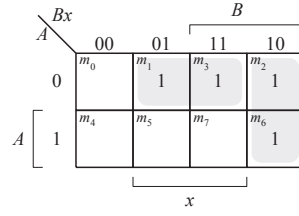


$$D_B = A'x + Bx'$$


(b)  $D_A = A'x + Ax'$

$$D_B = AB + Bx'$$

Present state		Input x	Next state	
A	B		A	B
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	1

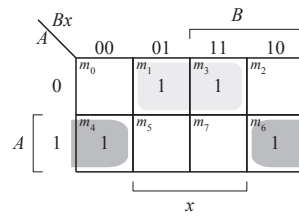


$$D_A = A'x + Ax'$$

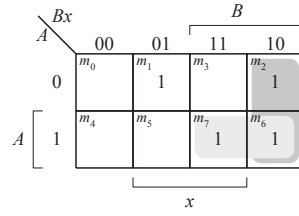


$$D_B = AB + Bx'$$

- 5.17 The output is 0 for all 0 inputs until the first 1 occurs, at which time the output is 1. Thereafter, the output is the complement of the input. The state diagram has two states. In state 0: output = input; in state 1: output = input'.

6.6 First stage of register:

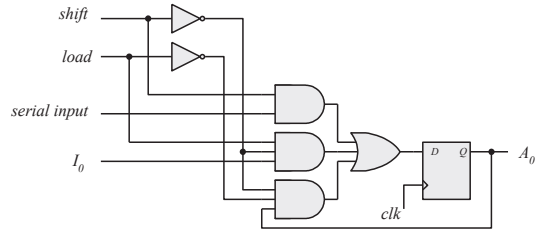

6.7 First stage of register:

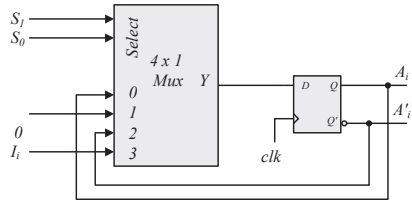

6.8  $A = 0010, 0001, 1000, 1100$ . Carry = 1, 1, 1, 0

6.9 (a) In Fig. 6.5, complement the serial output of shift register B (with an inverter), and set the initial value of the carry to 1.

(b)

Present state	Inputs		Next state	Output	FF inputs	
	Q	x y			Q	D
0	0	0	0	0	0	x
0	0	0	1	1	1	x
0	0	1	0	1	0	x
0	0	1	0	0	0	x
1	1	0	1	1	x	0
1	1	0	1	0	x	0
1	1	1	0	0	x	1
1	1	1	1	1	x	0

		$xy$		$x$	
$Q$		00	01	11	10
	$m_0$	$m_1$	$m_3$	$m_2$	
0			1		
$m_4$	$m_5$	$m_7$	$m_6$	$x$	
1		$x$	$x$	$x$	
		$y$		$J_Q = x'y$	

		$xy$		$x$	
$Q$		00	01	11	10
	$m_0$	$x$	$x$	$x$	$x$
0		$x$	$x$	$x$	
$m_4$	$m_5$	$m_7$	$m_6$	1	
1		$x$	$x$	$x$	
		$x$		$K_Q = xy' \oplus \oplus$	
		$D = Q \oplus x \oplus y$			



<b>6.16</b>	Q8 Q4 Q2 Q1 :	1010	1100	1110	Self correcting
	Next state:	1011	1101	1111	
	Next state:	0100	0100	0000	

1010 → 1011 → 0100


1100 → 1101 → 0100

1110 → 1111 → 0000


- 6.17** With  $E$  denoting the count enable in Fig. 6.12 and D-flip-flops replacing the J-K flip-flops, the toggling action of the bits of the counter is determined by:  $T_0 = E$ ,  $T_1 = A_0E$ ,  $T_2 = A_0A_1E$ ,  $T_3 = A_0A_1A_2E$ . Since  $D_A = A \oplus T_A$  the inputs of the flip-flops of the counter are determined by:  $D_{A0} = A_0 \oplus E$ ;  $D_{A1} = A_1 \oplus (A_0E)$ ;  $D_{A2} = A_2 \oplus (A_0A_1E)$ ;  $D_{A3} = A_3 \oplus (A_0A_1A_2E)$ .

- 6.18** When  $up = down = 1$  the circuit counts up.

	$up$	$down$	$x$	$y$	Operation
	0	0	0	0	No change
	0	1	0	0	Count down
	1	0	1	0	Count up
	1	1	0	0	No change

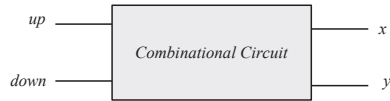

Add this to Fig. 6.13

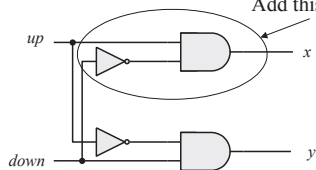

$$x = up (down)'$$

$$y = (up)'down$$

- 6.19 (b)** From the state table in Table 6.5:

$$D_{Q1} = Q_1'$$

$$D_{Q2} = \sum (1, 2, 5, 6)$$

$$D_{Q4} = \sum (3, 4, 5, 6)$$

$$D_{Q8} = \sum (7, 8)$$

$$\text{Don't care: } d = \sum (10, 11, 12, 13, 14, 15)$$

Simplifying with maps:

$$D_{Q2} = Q_2Q_1 + Q_8Q_2Q_1$$

$$D_{Q4} = Q_4Q_1 + Q_4Q_2 + Q_4Q_2Q_1$$

$$D_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$$