

Chapter 7


- 7.1 (a) $8\text{ K} \times 32 = 2^{13} \times 16$ $A = 13$ $D = 16$
 (b) $2\text{ G} \times 8 = 2^{31} \times 8$ $A = 31$ $D = 8$
 (c) $16\text{ M} \times 32 = 2^{24} \times 32$ $A = 24$ $D = 32$
 (d) $256\text{ K} \times 64 = 2^{18} \times 64$ $A = 18$ $D = 64$
 (e)

7.2 (a) 2^{13} (b) 2^{31} (c) 2^{26} (d) 2^{21}

7.3 Address: $563_{10} = 10_0011_0011_2$

Data word: $1,212_{10} = 0000_0100_1011_1100_2$

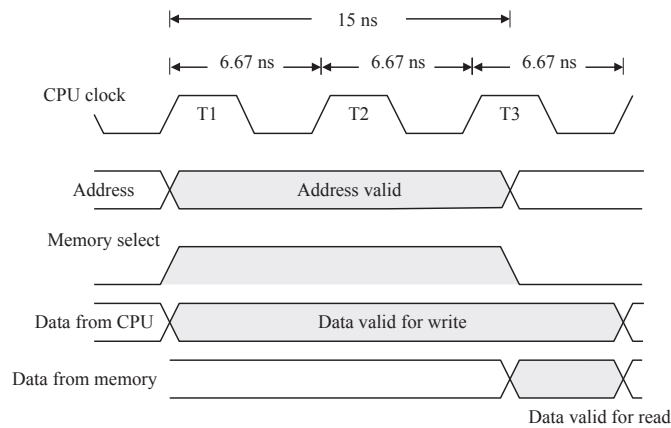7.4 $f_{\text{CPU}} = 150\text{ MHz}$, $T_{\text{CPU}} = 1/f_{\text{CPU}} = 6.67^{-9}\text{ Hz}^{-1}$



7.5


Pending

mdc 1/19/07 11:02 AM

Comment [1]: Spell check


- 7.7 (a) $16\text{ K} = 2^{14} = 2^7 \times 2^7 = 128 \times 128$
 Each decoder is 7×128
 Decoders require 256 AND gates, each with 7 inputs
- (b) $6,000 = 0101110_1110000$
 $x = 46 \quad y = 112$
- 7.8 (a) $256\text{ K} / 32\text{ K} = 8$ chips
- (b) $256\text{ K} = 2^{18}$ (18 address lines for memory); $32\text{ K} = 2^{15}$ (15 address pins / chip)
- (c) $18 - 15 = 3$ lines ; must decode with 3×8 decoder
- 7.9 $13 + 12 = 25$ address lines. Memory capacity = 2^{25} words.
- 7.10 $01011011 = 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad 7 \quad 8 \quad 9 \quad 10 \quad 11 \quad 12 \quad 13$
 $P_1 \quad P_2 \quad 0 \quad P_4 \quad 1 \quad 0 \quad 1 \quad P_8 \quad 1 \quad 0 \quad 1 \quad 1 \quad P_{13}$
- $P_1 = \text{Xor of bits (3, 5, 7, 9, 11)} = 0, 1, 1, 1, 1 = 0$ (Note: even # of 0s)
 $P_2 = \text{Xor of bits (3, 6, 7, 10, 11)} = 0, 0, 1, 0, 1 = 0$
 $P_4 = \text{Xor of bits (5, 6, 7, 12)} = 1, 0, 1, 1 = 1$ (Note: odd # of 0s)
 $P_8 = \text{Xor of bits (9, 10, 11, 12)} = 1, 0, 1, 1 = 1$
- Composite 13-bit code word: 0001 1011 1011 1
- 7.11 $11001001010 = 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad 7 \quad 8 \quad 9 \quad 10 \quad 11 \quad 12 \quad 13 \quad 14 \quad 15$
 $P_1 \quad P_2 \quad 1 \quad P_4 \quad 1 \quad 0 \quad 0 \quad P_8 \quad 1 \quad 0 \quad 0 \quad 1 \quad 0 \quad 1 \quad 0$
- $P_1 = \text{Xor of bits (3, 5, 7, 9, 11, 13, 15)} = 1, 1, 0, 1, 0, 0, 0 = 1$ (Note: odd # of 0s)
 $P_2 = \text{Xor of bits (3, 6, 7, 10, 11, 14, 15)} = 1, 0, 0, 0, 0, 1, 0 = 0$ (Note: even # of 0s)
 $P_4 = \text{Xor of bits (5, 6, 7, 12, 13, 14, 15)} = 1, 0, 0, 1, 0, 1, 0 = 1$
 $P_8 = \text{Xor of bits (9, 10, 11, 12, 13, 14, 15)} = 1, 0, 0, 1, 0, 1, 0 = 1$
- Composite 15-bit code word: 101 110 011 001 010
- 7.12 (a) $1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad 7 \quad 8 \quad 9 \quad 10 \quad 11 \quad 12$
 $0 \quad 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \quad 1 \quad 0$
- $C_1 (1, 3, 5, 7, 9, 11) = 0, 0, 1, 1, 1, 1 = 0$
 $C_2 (2, 3, 6, 7, 10, 11) = 0, 0, 1, 1, 0, 1 = 1$
 $C_4 (4, 5, 6, 7, 12) = 0, 1, 1, 1, 0 = 1$
 $C_8 (8, 9, 10, 11, 12) = 0, 1, 0, 1, 0 = 0$
- $C = 0110$
 Error in bit 6.
 Correct data: 0101 1010
- (b) $1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad 7 \quad 8 \quad 9 \quad 10 \quad 11 \quad 12$
 $1 \quad 0 \quad 1 \quad 1 \quad 1 \quad 0 \quad 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0$
- $C_1 (1, 3, 5, 7, 9, 11) = 1, 1, 1, 0, 0, 1 = 0$
 $C_2 (2, 3, 6, 7, 10, 11) = 0, 1, 0, 0, 1, 1 = 1$
 $C_4 (4, 5, 6, 7, 12) = 1, 1, 0, 0, 0 = 0$
 $C_8 (8, 9, 10, 11, 12) = 0, 0, 1, 1, 0 = 0$
- $C = 0010$

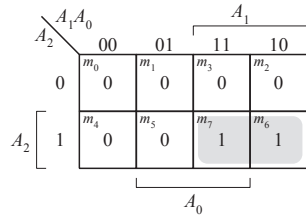7.21 Note: See truth table in Fig. 7.12(b).




$$F_1 = A_2A_1$$

$$F'_1 = A'_2 + A'_1$$

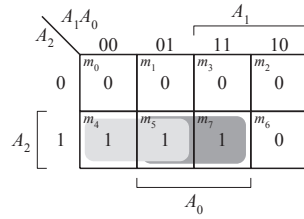


$$F_2 = A_2A'_1 + A_2A_0$$

$$F'_2 = A'_2 + A_1A'_0$$

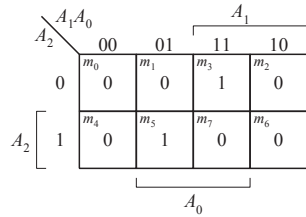

$$F_3 = A'_2A_1A_0 + A_2A'_1A_0$$

$$F'_3 = A'_0 + A'_2A'_1 + A_2A_1$$

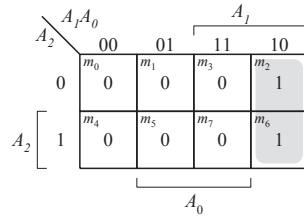

$$F_4 = A_1A'_0$$

$$F'_4 = A'_1 + A_0$$

Product term	Inputs $A_2A_1A_0$	Outputs $F_1F_2F_3F_4$
A_2A_1	1 1 1 -	1 - - -
A'_2	2 0 - -	- 1 - -
$A'_1A'_0$	3 - 1 0	- 1 - 1
$A'_2A_1A_0$	4 - 1 1	- - 1 -
$A_2A'_1$	5 1 0 1	- - 1 -
		<u> T C T T</u>

Alternative: F'_1, F'_2, F_3, F_4
(5 terms)

7.22

Decimal	w	x	y	z	b_7	b_6	b_5	b_4	b_3	b_2	b_1	b_0
0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	0	1	0	0	0	0	0	1
2	4	0	0	1	0	0	0	0	0	1	0	0
3	9	0	0	1	1	0	0	0	0	1	0	1
4	16	0	1	0	0	0	0	0	1	0	0	0
5	25	0	1	0	1	0	0	0	1	1	0	1
6	36	0	1	1	0	0	0	1	0	0	1	0
7	49	0	1	1	1	0	0	1	1	0	0	1
8	64	1	0	0	0	0	1	0	0	0	0	0
9	81	1	0	0	1	0	1	0	1	0	0	1
10	100	1	0	1	0	0	1	1	0	0	1	0
11	121	1	0	1	1	0	1	1	1	1	0	1
12	144	1	1	0	0	1	0	0	1	0	0	0
13	169	1	1	0	1	1	0	1	0	1	0	1
14	196	1	1	1	0	1	1	0	0	0	1	0
15	225	1	1	1	1	1	1	1	0	0	0	1

Note: $b_0 = z$, and $b_1 = 0$.
ROM would have 4 inputs and 6 outputs. A 4 x 8 ROM would waste two outputs.