

--Question 1

a) Using Boolean Algebra, minimize the following function (step by step):

i) $F(A, B, C) = A' + AB + (A' + B)(A + B')$;
ii) $F = BC + AC + A'B'C$ (4 marks)

b) List all possible prime implicants and essential prime implicants for Function F:

$F = \Sigma(0, 2, 6, 7, 10, 13, 14, 15)$ with don't care conditions $d = \Sigma(1, 3, 12)$.

Show groupings on a Karnaugh map accompanied with their algebraic forms. (3 marks)

c) A circuit of Fig. 1 has been designed by a inexperienced engineer. Re-design the circuit, by Express P and Q in Fig. 1 as function of A, B and C and then produce an optimized circuit. (3 marks)

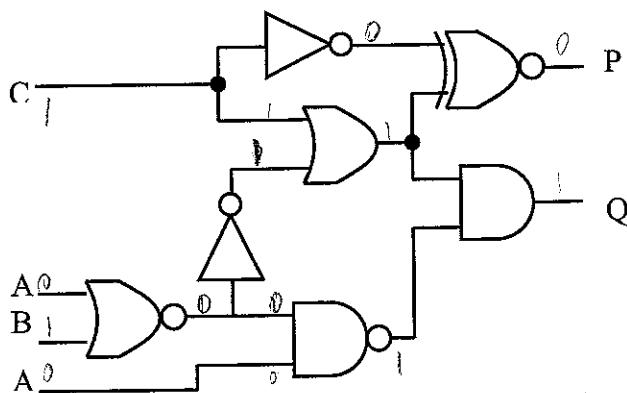


Fig. 1

--Question 2

2.1 Express function F

$F = AB + A'B'$ with:

- i) NAND-NAND ii) NOR-NOR iii) AND-OR-INV , iv) OR-AND-INV.
Show the different steps and the logic diagram. (6 marks)

2.2 Consider the circuit in Fig. 2. Draw the timing diagram of F when input A, goes from 0 to 1 → 0 → 1 → 0. Indicate all timings on the diagram. (4 Marks)
Assume delay of Inverter = 3 ns and delay of NAND = 5 ns

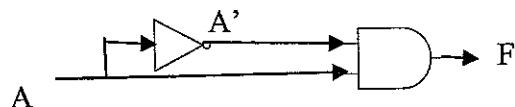


Fig. 2

--Question 3

a) Design a Circuit to give $F = A^3$.

A is a 2-bit unsigned binary number. $A = a_1a_0$.

(6 marks)

b) Use 2 to 4 decoder plus OR gates to implement F.

(4 marks)

--Question 4

- a) What is the difference between ROM, PROM, PAL, and the PLA. (2 marks)
b) A designed sequential circuit is to be implemented using **2 JK Flip Flops and a PLA**. The excitation equations are:

$$J_A = Bx' \quad K_A = Bx$$

$$J_B = x \quad K_B = (A \oplus x)$$

Where A and B are the present states and x is an external input. Implement the circuit, with a PLA. Give, personality matrix and showing your programming of the PLA by placing an • on the programmable nodes. (5 marks)

- c) Implement the following function F, using only 2 to 1 multiplexers:
$$F = A + B + ACD \quad (3 \text{marks})$$

Question 5

Design a synchronous counter that generates the odd numbers between 0 and 10.
(1,3,5,7,9) repeatedly and to generate an output of "1" corresponding to the number 9.

- 1) Draw the State Diagram.
- 2) Use binary state assignment, derive the State Transition Table.
- 3) Using D flip flops, derive the excitation equations.
- 4) Draw the sequential circuit diagram. (10 marks)

Question 6

The circuit in Figure 3 has been designed to perform certain function. Analyze the circuit. Derive the state transition table and state diagram including all inputs and outputs. (10 marks)

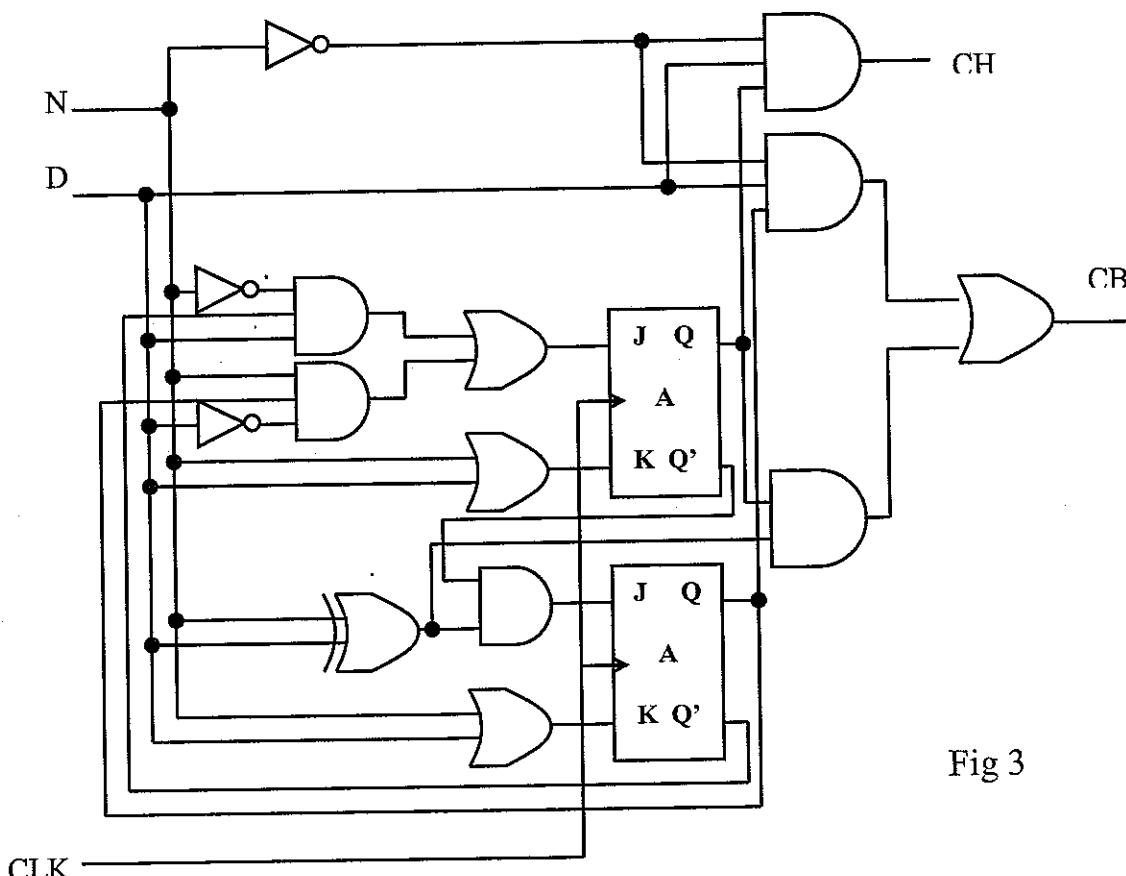


Fig 3

P1

Question 1:

$$\begin{aligned}
 2) i) F(A, B, C) &= \bar{A} + AB + (\bar{A} + B)(A + \bar{B}) \\
 &= \bar{A} + AB + \bar{A}\bar{B} + AB \\
 &= \bar{A}(1 + \bar{B}) + AB \\
 &= \bar{A} + AB \\
 &= (\bar{A} + A)(\bar{A} + B)
 \end{aligned}$$

$$\underline{F(A, B, C) = \bar{A} + B}$$

2/2

$$\begin{aligned}
 ii) F &= BC + AC + \bar{A}\bar{B}C \\
 &= (A + \bar{A})BC + (B + \bar{B})AC + \bar{A}\bar{B}C \\
 &= ABC + \bar{A}BC + A\bar{B}C + A\bar{B}C + \bar{A}\bar{B}C \\
 &= ABC + \bar{A}C(B + \bar{B}) + AC(B + \bar{B}) \\
 &= ABC + \bar{A}C + AC \\
 &= AC(B + 1) + \bar{A}C \\
 &= AC + \bar{A}C \\
 &= C(A + \bar{A})
 \end{aligned}$$

2/2

$$\underline{F = C}$$

5)

		A	B	C	D	00	01	11	10	
					00	01	11	10		
00		1	0				X			EPI ₁ : $\Sigma(0,1,2,3) = \bar{A}$
01			X				1	1	1	EPI ₂ : $\Sigma(12,13,14,15) =$
11		X	1	1		1	1	1	1	EPI ₃ : $\Sigma(2,6,10,14) =$
10		1	1	1	1	1	1	1	1	PI ₄ : $\Sigma(6,7,14,15) = P$
										PI ₅ : $\Sigma(2,3,6,7) = \bar{A}$

$$\underline{F = \bar{A}\bar{B} + AB + CD + \begin{cases} BC \\ \bar{A}C \end{cases}}$$

3/3

Q1 P2 CON3/2 Dec 20/0


C) $P = \bar{C} \odot (C + (\overline{A+B}))$
 $Q = (C + (\overline{\bar{A}+\bar{B}})) (A (\overline{\bar{A}+\bar{B}}))$

$$\begin{aligned}P &= \bar{C} \odot (A + B + C) \\&= \bar{C}(A + B + C) + C(\overline{A + B + C}) \\&= A\bar{C} + B\bar{C} + C(\overline{ABC}) \\P &= A\bar{C} + B\bar{C}\end{aligned}$$

$$\begin{aligned}Q &= (C + A + B)(\overline{A(\bar{A}\bar{B})}) \\&= (C + A + B)(\bar{A} + (\bar{A}\bar{B})) \\&= (A + B + C)(\bar{A} + A + B) \\&= (A + B + C)(1 + B)\end{aligned}$$

3/3

$$Q = A + B + C$$

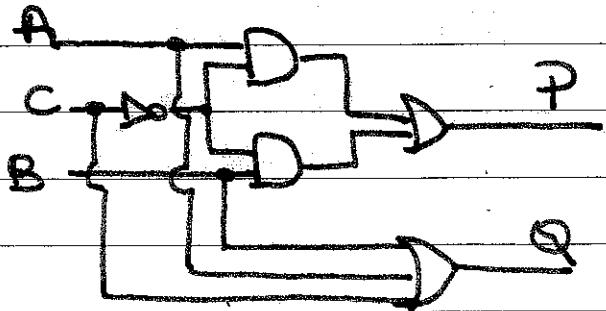


Question 2:

2.1) $F = AB + \overline{AB}$

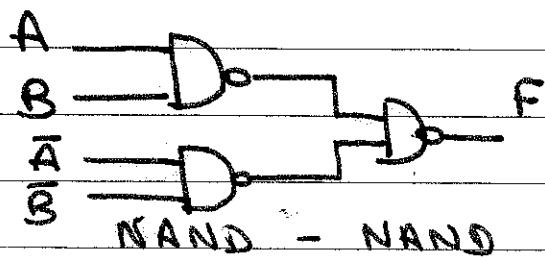i) $F = \overline{AB} + \overline{\overline{A}\overline{B}}$

$F = \overline{(AB)}(\overline{\overline{A}\overline{B}})$



ii) $F = \overline{AB} + \overline{\overline{A}\overline{B}}$


$$= (\overline{AB})(\overline{\overline{A}\overline{B}})$$

$$= (\bar{A} + \bar{B})(A + B)$$

$$= \overline{\overline{AB} + A\bar{B}}$$

$F = \overline{(A + \bar{B})} + \overline{(\bar{A} + B)}$

NOR - NOR

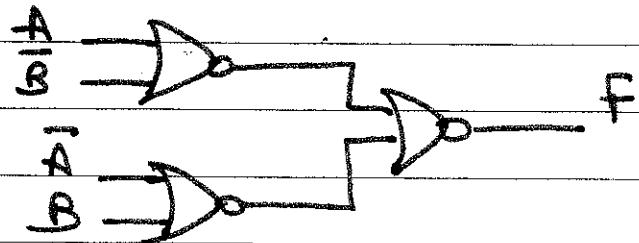

iii) $F = (\overline{A} + \bar{B}) + (\bar{A} + B)$


$$= (\bar{A} + \bar{B})(A + B)$$

$F = \overline{\overline{AB} + AB}$

C08N 312 P₂ C08N 312 Dec 2010


Q 2

AND-OR-INV

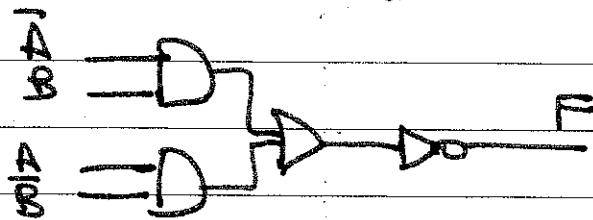

iii) $F = (\bar{A} + \bar{B}) + (\bar{A} + B)$

$F = (\bar{A} + \bar{B})(\bar{A} + B)$


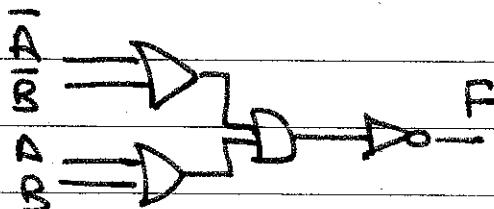


OR - AND - INV

2.2)



Before
Delay

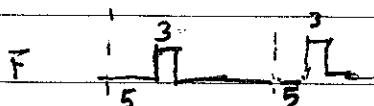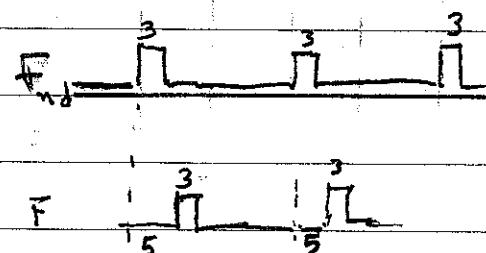

CSEN 312 Dec 2010

Question 3:

a) $F = A^3$

A	F
$a_1 a_0$	$b_4 b_3 b_2 b_1 b_0$
0 0	0 0 0 0 0
0 1	0 0 0 0 1
1 0	0 1 0 0 0
1 1	1 1 0 1 1



$$b_4 = a_1 a_0$$

$$b_3 = a_1$$


$$b_2 = 0$$

$$b_1 = b_4 = a_1 a_0$$

$$b_0 = a_0$$

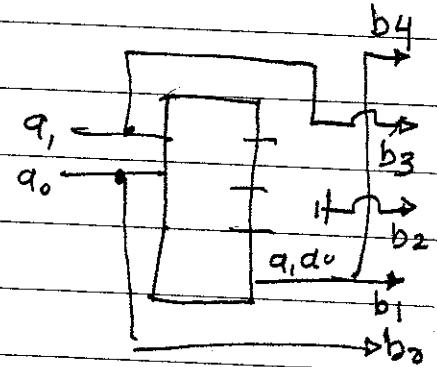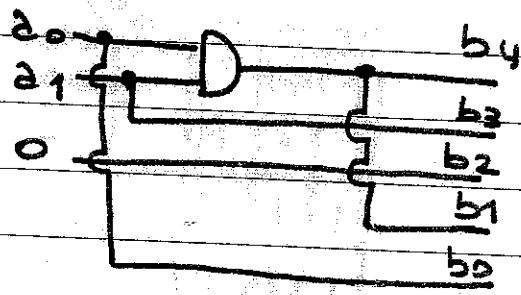

b)

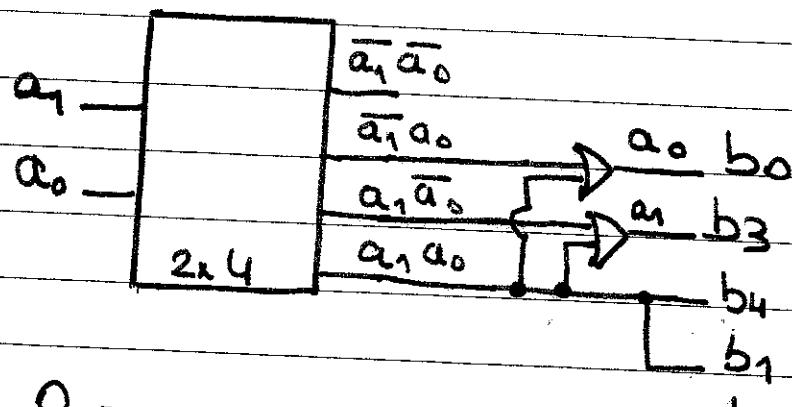

Q4 P₁ COEN 31 Dec 2010

Question 4

a) ROM: AND fixed OR fixed

ROM: AND fixed OR programmable


PAL: AND programmable OR fixed

PLA: AND programmable OR programmable

b) $J_A = Bx'$ $K_A = Bx$


$J_B = x$ $K_B = A \oplus x = A'x + Ax'$

			AND				OR			
A	B	x	A	B	x	J _A	J _B	K _A	K _B	
0	0	0	1	-	1	Bx	-	-	1	-
0	0	1	2	0	-	Ax	-	-	-	1
0	1	0	3	-	1	Bx	1	-	-	-
0	1	1	4	-	-	x	-	1	-	-
1	0	0	5	1	-	0	Ax	-	-	1
1	0	1					Bx	Ax	Bx	A \oplus x
1	1	0								
1	1	1								

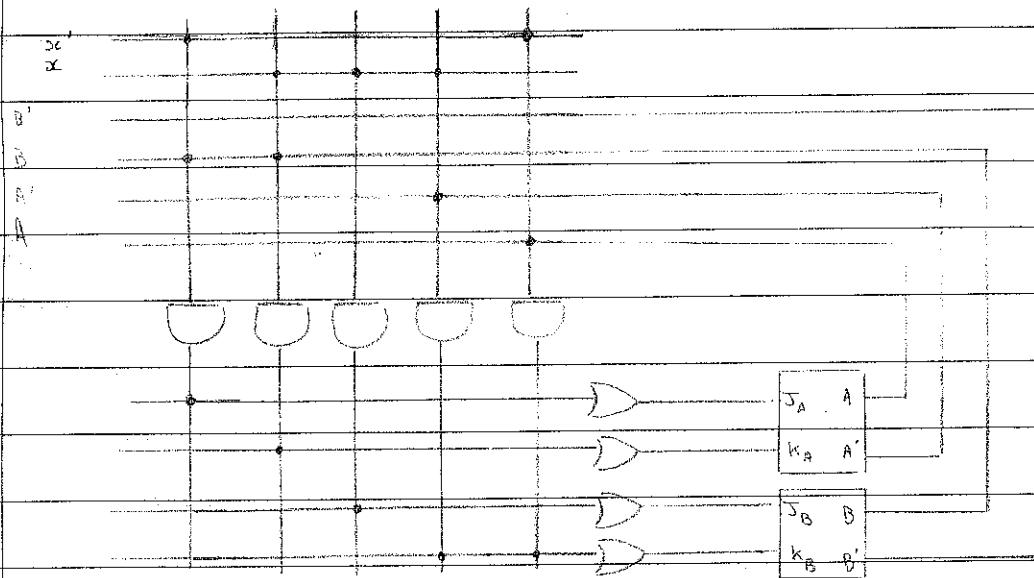

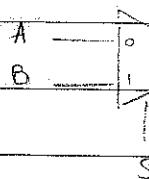Q4 P2 COEN 31 Dec 2010

$$c) F = A + B + ACD = B + A(1 + CD) = A + B$$




A	B	S	F	S' A + S B
0	0	0	0	0 0 0 1 1 0
0	0	1	0	0 0 1 1 0 0
0	1	0	0	1 0 1 0 0 0
0	1	1	1	1 0 1 1 0 0
1	0	0	1	0 0 0 0 1 0
1	0	1	0	0 0 1 0 0 0
1	1	0	1	1 0 0 1 0 0
1	1	1	1	1 0 1 1 1 0

$$\left. \begin{array}{l} \text{If } S=0 \quad F=A \\ \text{If } S=1 \quad F=B \end{array} \right\} F = A + B$$

Q5 P. COEN 312 Dec 2010

Question 5

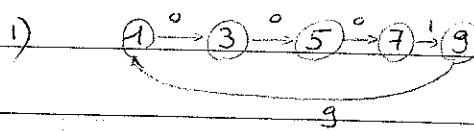

2) Present State

~~0, 2, 4, 6, 8~~

$m_3 \ m_2 \ m_1 \ m_0$

Next State
 $m_3' \ m_2' \ m_1' \ m_0'$

Output

X (representing even numbers &
numbers ≥ 10)

0 0 0 1	0 0 1 1	0
X X X X	X X X X	X
0 0 1 1	0 1 0 1	0
X X X X	X X X X	X
0 1 0 1	0 1 1 1	0
X X X X	X X X X	X
0 1 1 1	1 0 0 1	0
X X X X	X X X X	X
1 0 0 1	0 0 0 1	✓

Others don't care

$m_3 \ m_2 \ m_1 \ m_0$	00	01	11	10
00	X X X X			
01	0 0 X 0			
11	0 1 X X			
10	X X X X			

$$m_3^+ = D_3$$

$m_3 \ m_2 \ m_1 \ m_0$	00	01	11	10
00	X X X X			
01	0 1 X 0			
11	0 0 X X			
10	X X X X			

For a D flip flop

$$Q^+ = D$$

$m_3 \ m_2 \ m_1 \ m_0$	00	01	11	10
00	X X X X			
01	1 1 X 0			
11	0 0 X X			
10	X X X X			

$$m_2^+ = D_3$$

$$m_3^+ = m_2' m_1 = D_3$$

$$m_2^+ = m_2 m_1' + m_2' m_1 = m_2 \oplus m_1 = D_2$$

$$m_1^+ = m_3' m_1'$$

$$m_0^+ = 1$$

$$m_1^+$$

$m_3 \ m_2 \ m_1 \ m_0$	00	01	11	10
00	X X X X			
01	1 1 X 0			
11	0 0 X X			
10	X X X X			

$$x = m_2$$

$$m_0$$

~~Q3~~ P2 COEN 312 Dec 2010

4)



$m_0 D_0$

$m_1 D_1$
 m_1'

$m_2 D_2$
 m_2'

$m_3 D_3$
 m_3'

COEN 312 Dec 2010

Question 6:

$$\bar{J}_{A1} = \bar{N} \bar{Q}_{A2} D + N Q_{A2} \bar{D}$$

$$K_{A1} = N + D$$

$$\begin{aligned}\bar{K}_{A1} &= (\bar{N} + \bar{D}) \\ &= \bar{N} \bar{D}\end{aligned}$$

$$\bar{J}_{A2} = \bar{Q}_{A1} (N \oplus D)$$

$$K_{A2} = N + D$$

$$Q^+ = J \bar{Q} + \bar{K} Q$$

$$Q_{A1}^+ = \bar{J}_{A1} \bar{Q}_{A1} + \bar{K}_{A1} Q_{A1}$$

$$Q_{A1}^+ = (\bar{N} \bar{Q}_{A2} D + N Q_{A2} \bar{D}) \bar{Q}_{A1} + (\bar{N} \bar{D}) Q_{A1}$$

$$Q_{A2}^+ = \bar{J}_{A2} \bar{Q}_{A2} + \bar{K}_{A2} Q_{A2}$$

$$Q_{A2}^+ = (\bar{Q}_{A1} (N \oplus D)) \bar{Q}_{A2} + (\bar{N} \bar{D}) Q_{A2}$$

$$CH = Q_{A1}^+ D \bar{N}$$

$$CB = \bar{N} D Q_{A2}^+ + Q_{A1}^+ (N \oplus D)$$

Q6 - P2 COEN342 Dec 2010

Inputs Present State Next State Outputs.

N	D	Q_{A_1}, Q_{A_2}	$Q_{A_1} + Q_{A_2} +$	C _H	C _B
0	0	0 0	0 0	0	0
0	0	0 1	0 1	0	0
0	0	1 0	1 0	0	0
0	0	1 1	1 1	0	0
0	1	0 0	1 1	1	1
0	1	0 1	0 0	0	0
0	1	1 0	0 0	0	0
0	1	1 1	0 0	0	0
1	0	0 0	0 1	0	1
1	0	0 1	1 0	0	1
1	0	1 0	0 0	0	0
1	0	1 1	0 0	0	0
1	1	0 0	0 0	0	0
1	1	0 1	0 0	0	0
1	1	1 0	0 0	0	0
1	1	1 1	0 0	0	0

