

DIGITAL DESIGN COEN 312	Instructor: Drs. A. J. Al-Khalili & M. Nekili
Final exam. May 2000	Time Allowed 3:00 hrs.
No. of pages: 2	
No Calculators, books or notes are allowed	

Question 1

- a) Consider the circuit given in Fig. 1 below. Assume each gate, including the inverter has a 12 ns  $t_{pd}$ . The inputs are currently POR = 111. How does the OUT responds when Q makes a sudden change from HI to LO.
- b) A safe has 20-button keyboard. In order to unlock the safe, a teller must simultaneously press buttons 2,7,8,13, and 19. If extra buttons are pressed at the same time, the safe will not unlock. When a button is pressed, it can send a HI output to a logic circuit. Design a combinational circuit where HI output will represent the unlocked safe. Assume you have independent access to each digitized key.
- c) Prove the De Morgan Theorem.

 


Fig. 1 Circuit for timing Analysis of Q.1a

Question 2

- a) Design a full subtractor
- b) Implement a) above using 4→1 Multiplexers and minimal extra logic if required.
- c) Implement a) above using 3→8 decoder and minimal extra logic if required

Question 3

- a) What size of ROM is required to implement a BCD to 7-segment decoder.
- b) Design a BCD to 7-segment decoder. Given the content of the Rom IN A TABLE FORMAT. With each word as, abcdefg. Please refer to Fig. 2 below for the segment's destination. Assume that the illegal numbers will be displayed as E.

 


Fig. 2. 7-Segment Display of Q3

Question 4

- a) Design an adder that can add two BCD numbers.
- b) Give a circuit Diagram

Question 5

An engine needs to go through four strokes, all of equal duration.  
On the 1<sup>st</sup> stroke the inlet valve opens and outlet valve is closed.  
On the 2<sup>nd</sup> stroke the valve is closed.  
On the 3<sup>rd</sup> stroke a spark is delivered.  
On the 4<sup>th</sup> stroke the outlet valve is opened for the exhaust to vent.  
Then the first stroke comes again and the cycle repeats.

Design a controller for the system with a clock for the input and with 3 outputs:

O1 to open inlet

O2 to open outlet

O3 to ignore spark

Assume that if the control to open a valve is not asserted the valve closes (ie. Spring loaded).

Question 6

- a) Analyze the circuit given in Fig. 3 below fully (give excitation equations, transition table, state table and state diagram):
- b) Initially D0 has been set to "1" (for one clock period). Draw the timing diagram for y0, y1, y2 for 5 clock cycles. Assume each Flip flop has a delay of 10 ns.


 


Fig. 3. Circuit to be analyzed in Q.6.


## Solutions

### Question 1

a)

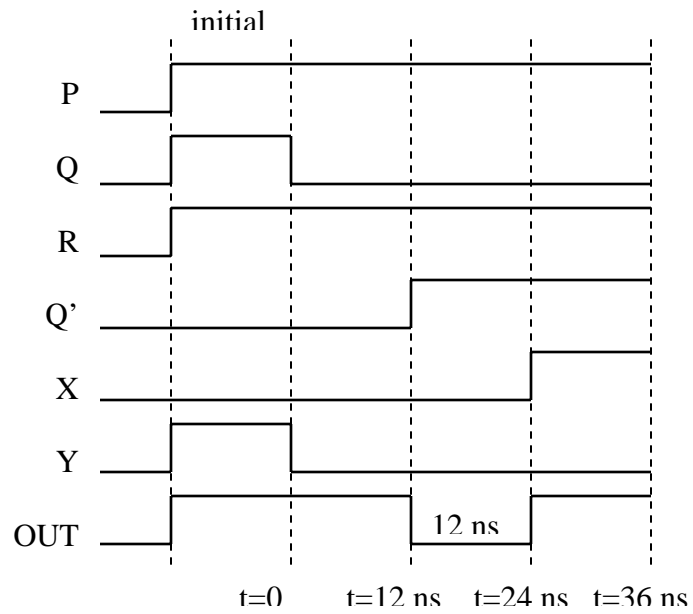

b)

 

c)  $(A.B)' = A' + B'$  By Truth Table

A	B	A.B	$(A.B)'$	A'	B'	$A' + B'$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

Equal

Question 2

a)  $B_{out} = a'B_{in} + a'b + bB_{in}$   
 $D = a \oplus b \oplus B_{in}$




a	b	$B_{in}$	D	$B_{out}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

		ab			
		00	01	11	10
$B_{in}$	0		1		1
	1	1		1	

D

		ab			
		00	01	11	10
$B_{in}$	0		1		
	1	1	1	1	

$B_{out}$

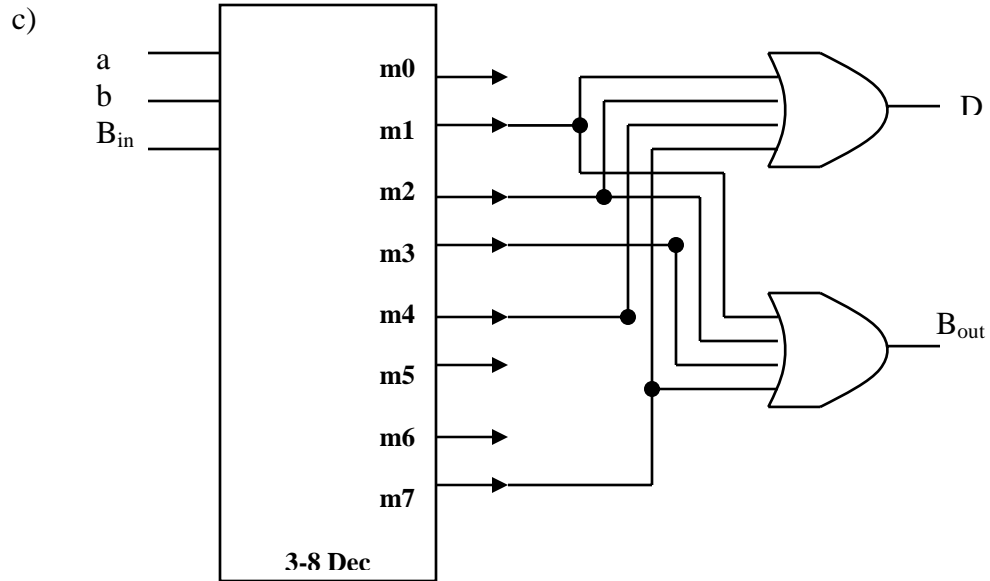  

Question 3

a) 10 words of 7 bits = 70 bits with error bits

Digit	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
E	1	0	1	0	1	0	0	1	1	1	1
	1	0	1	1	1	0	0	1	1	1	1
	1	1	0	0	1	0	0	1	1	1	1
	1	1	0	1	1	0	0	1	1	1	1
	1	1	1	0	1	0	0	1	1	1	1
	1	1	1	1	1	0	0	1	1	1	1

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	1	1	1	1
10	1	1	1	1

$$a = B + C + BD + B'D'$$

AB \ CD	00	01	11	10
00	1	1	0	1
01	1	0	0	1
11	1	1	0	0
10	1	0	0	0

$$b = (A' + B')(A' + C')(B' + C' + D)$$

AB \ CD	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	1	1	0	0
10	0	1	0	0

$$c = (A' + B')(A' + C')(B + C' + D)$$

		AB			
	CD	00	01	11	10
00		1	0	1	1
01		0	1	1	0
11		1	0	1	1
10		1	1	1	1

$$d = (A + B' + C + D)(A + B + C + D)(A + B' + C' + D')$$

		AB			
	CD	00	01	11	10
00		1	0	1	1
01		0	0	1	0
11		0	0	1	1
10		1	1	1	1

$$e = (A + C)(A + B' + C)(B + C + D')$$


		AB			
	CD	00	01	11	10
00		1	1	1	1
01		0	1	1	1
11		0	0	1	1
10		0	1	1	1

$$f = (A + B + D')(A + B + C)(A + C' + D')$$

		AB			
	CD	00	01	11	10
00		0	1	1	1
01		0	1	1	1
11		1	0	1	1
10		1	1	1	1

$$g = (A + B + C)(A + B' + C' + D')$$


ROM Implementation:

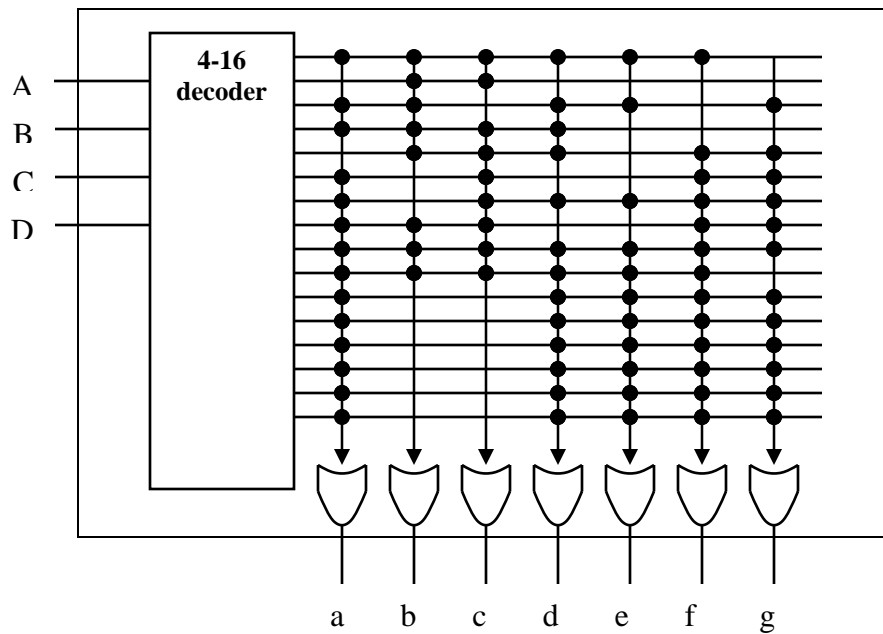

Question 4

Adding two BCD numbers, give a maximum of 19, i.e  $9 + 9 + 1 = 19$ .

Decimal	K	A B C D (BCD)	C	X3 X2 X1 X0 (Binary)
0	0	0 0 0 0	0	0 0 0 0
1	0	0 0 0 1	0	0 0 0 1
2	0	0 0 1 0	0	0 0 1 0
3	0	0 0 1 1	0	0 0 1 1
4	0	0 1 0 0	0	0 1 0 0
5	0	0 1 0 1	0	0 1 0 1
6	0	0 1 1 0	0	0 1 1 0
7	0	0 1 1 1	0	0 1 1 1
8	0	1 0 0 0	0	1 0 0 0
9	0	1 0 0 1	0	1 0 0 1
10	1	0 0 0 0	0	1 0 1 0
11	1	0 0 0 1	0	1 0 1 1
12	1	0 0 1 0	0	1 1 0 0
13	1	0 0 1 1	0	1 1 0 1
14	1	0 1 0 0	0	1 1 1 0
15	1	0 1 0 1	0	1 1 1 1
16	1	0 1 1 0	1	0 0 0 0
17	1	0 1 1 1	1	0 0 0 1
18	1	1 0 0 0	1	0 0 1 0
19	1	1 0 0 1	1	0 0 1 1

 


It can be seen that from 0-9 the two additions are equal. For numbers greater than 9, we had add a 6 (0110) to the binary addition to get the BCD addition.

From above Truth Table, we have:  
 $K = C + X_3X_2 + X_3X_1$ .

 **Question 5**


There are four states, are for each stroke, output are O1 O2 O3.



This is a simple counter  $S0 \rightarrow S1 \rightarrow S2 \rightarrow S3 \rightarrow S0 \rightarrow \dots$

Present state		Next state		Outputs								
y0	y1	y0 <sup>+</sup>	y1 <sup>+</sup>	O1	O2	O3						
0	0	0	1	1	0	0						
0	1	1	0	0	0	0						
1	0	1	1	0	1	1	1	0	0	0	1	0
1	1	0	0	0	1	0						

Use D FlipFlop  
 $y0^+ = D0 = y0 \oplus y1$   
 $y1^+ = D1 = y1'$   
 $O1 = y0'y1'$   
 $O2 = y0y1$   
 $O3 = y0 y1'$

 



**Question 6**

a) Excitation Equations

$$y0^+ = D0 = y2$$


$$y1^+ = D1 = y0$$

$$y2^+ = D2 = y1$$

$$\text{Output} = Z = y2$$

Transition Table and State Table

Present State			Next state			Output
y0	y1	y2	y0 <sup>+</sup>	y1 <sup>+</sup>	y2 <sup>+</sup>	Z
0	0	0	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	1	1	1	1	1

 

Timing Diagram

