

Answer all Questions.

Exam Duration 3 hour

Examiners : A. J. Al-Khalili and S. Das

No books / papers or electronic devices are allowed.

=====

### Question 1

For a) and b) below use Boolean Algebra.

a) Given F1 and F2 below, determine optimal  $(F1 \bullet F2)$  and  $(F1 + F2)$  (2 Marks)

$$F1 = AB + C'$$

$$F2 = A'C' + B'C'$$

b) Minimize the following Boolean Function: (2 Marks)

$$F(A,B,C,D) = ABC' + BC'D' + AC'D + ABC + BCD' + ACD'$$

c) Given  $F(A,B,C) = AB + AC' + BC$  (3 Marks)

i) Implement f in NOR-NOR format

ii) Implement f in AND-OR-INVERT format

Obtain optimum implementation.

### Question 2

a) **Design** a digital combinational circuit that implements (8 Marks)

$$F = (N-2)^2 \quad \text{where } N \text{ is an integer } 0 \leq N \leq 6$$

Show your design steps clearly starting with the Truth Table.

Draw the final circuit.

b) What size of a ROM is required for the implementation of F?

(2 Marks)

### Question 3

a) Using a 2 to 1 MUX implement AND, OR and XOR gates. (1 Marks)

b) Implement the Full Adder given below using minimum 2 to 1 MUXes only:

$$S(A,B,C) = A \oplus B \oplus C$$


$$C_{out}(A,B,C) = A \cdot B + C \cdot (A \oplus B) \quad (4 \text{ Marks})$$

c) Using a 4 to 1 MUX **implement F**

$$F(A,B,C,D) = A'B + A \cdot B \cdot D + A \cdot B' \cdot D' \quad (3 \text{ Marks})$$
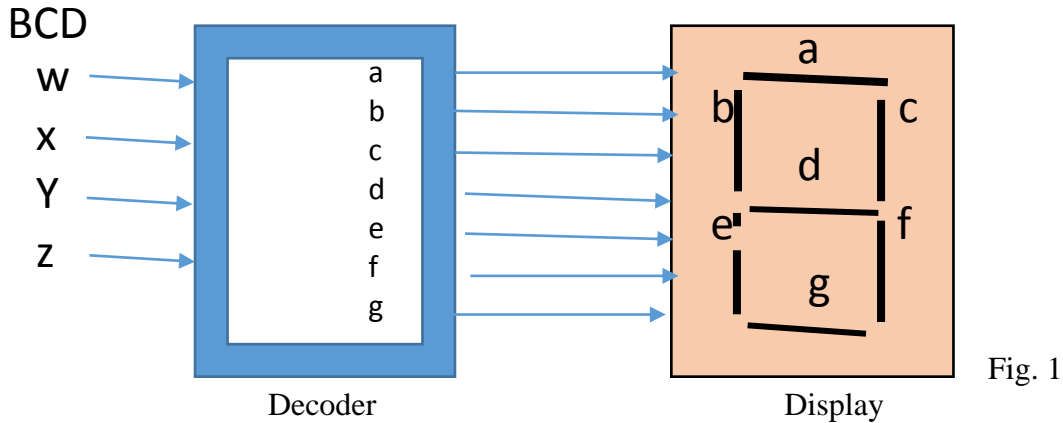
### Question 4

**Design** a Decoder that receives a BCD number and displays a **P** on a 7-segment display as shown in Fig. 1 below. If a non-BCD number appears at the input an **F** should be displayed. Start with a truth table and derive final output. Give final circuit diagram. (8 marks)



### Question 5

**Design** an UP/DOWN BCD counter, starting with a state diagram. Use T-Flip Flop for your implementation. (7 Marks)

### Question 6

- Analyze** the circuit given in Fig. 2 below fully (give excitation equations, transition table, state table and state diagram):
- Initially Do has been set to "1" (for one clock period). Draw the timing diagram for y0, y1, y2 for 5 consecutive clock cycles. Assume each Flip flop has a delay of 10 ns. (10 marks)

 


Fig. 2. Circuit to be analyzed in Q.6.