

## Question 1

$$A = a_3 a_2 a_1 a_0$$

$$B = b_3 b_2 b_1 b_0$$

| Decimal | Binary Sum<br><small>K 2<sup>3</sup> 2<sup>2</sup> 2<sup>1</sup> 2<sup>0</sup></small> | BCD Sum<br><small>C 5<sup>3</sup> 5<sup>2</sup> 5<sup>1</sup> 5<sup>0</sup></small> |
|---------|--|---|
| 0       | 0 0000   | 0 0000  |
| 1       | 0 0001   | 0 0001  |
| 2       | 0 0010   | 0 0010  |
| 3       | 0 0011   | 0 0011  |
| 4       | 0 0100   | 0 0100  |
| 5       | 0 0101   | 0 0101  |
| 6       | 0 0110   | 0 0110  |
| 7       | 0 0111   | 0 0111  |
| 8       | 0 1000   | 0 1000  |
| 9       | 0 1001   | 0 1001  |
| 10      | 0 1010   | 1 0000  |
| 11      | 0 1011   | 1 0001  |
| 12      | 0 1100   | 1 0010  |
| 13      | 0 1101   | 1 0011  |
| 14      | 0 1110   | 1 0100  |
| 15      | 0 1111   | 1 0101  |
| 16      | 1 0000   | 1 0110  |
| 17      | 1 0001   | 1 0111  |
| 18      | 1 0010   | 1 1000  |
| 19      | 1 0011   | 1 1001  |

⇒ Max BCD 4 digits

⇒ Max sum

(9+9=18)

⇒ Add A and B with a 4-bit binary adder



If the sum > 9, add 6

⇒ When C=1, Add 6 to the binary sum  
6 = 0110


|    |    |    |    |    |
|----|----|----|----|----|
|    | 00 | 01 | 11 | 10 |
| 00 |    |    |    |    |
| 01 |    |    |    |    |
| 11 | 1  | 1  | 1  | 1  |
| 10 |    |    | 1  | 1  |

$$C = K + Z_3 Z_2 + Z_3 Z_1$$

BCD adder

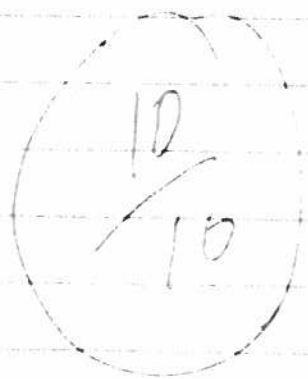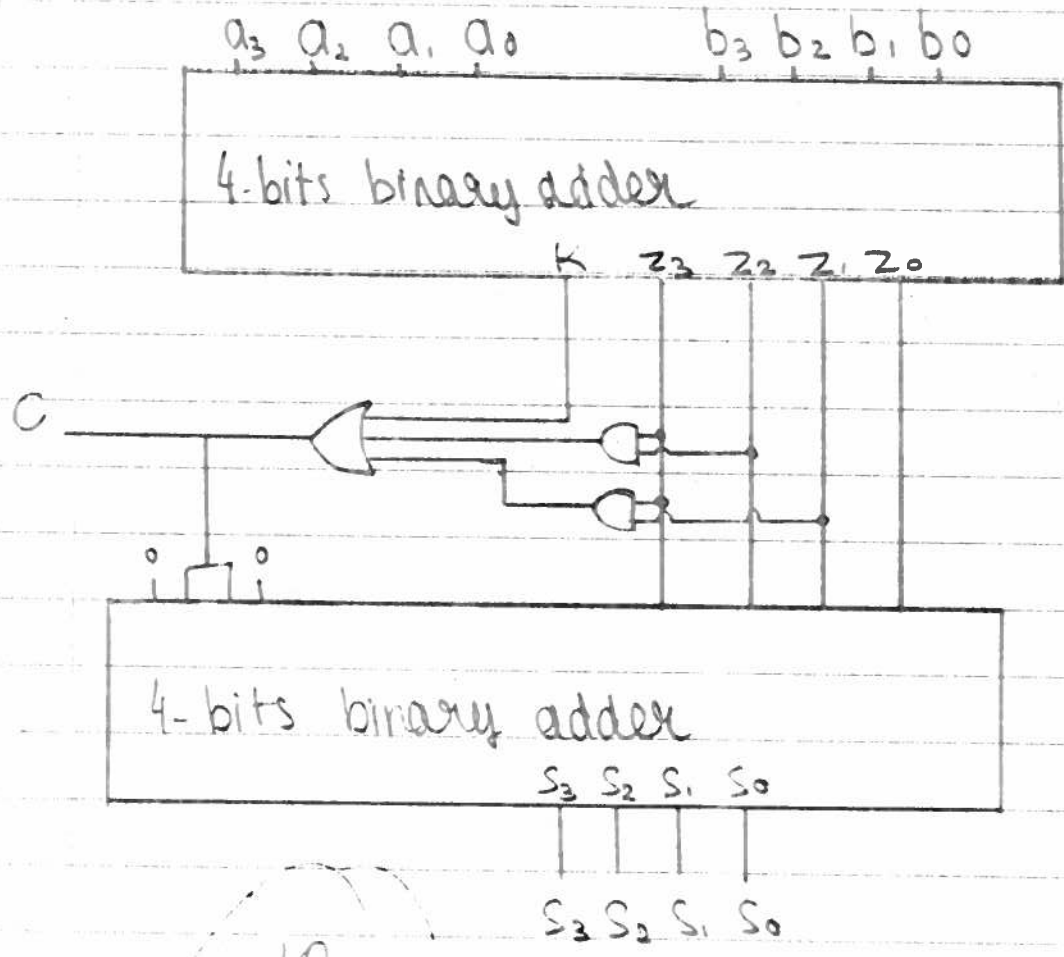

↳ no carry needed in the 2nd adder

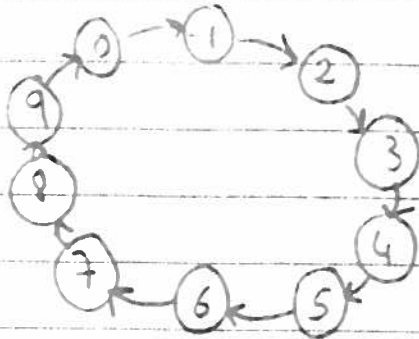
Question 2.

| Present state | Next state |       |       |       |
|---------------|------------|-------|-------|-------|
|               | $y_3$      | $y_2$ | $y_1$ | $y_0$ |
| 0             | 0          | 0     | 0     | 0     |
| 1             | 0          | 0     | 0     | 1     |
| 2             | 0          | 0     | 1     | 0     |
| 3             | 0          | 0     | 1     | 1     |
| 4             | 0          | 1     | 0     | 0     |
| 5             | 0          | 1     | 0     | 1     |
| 6             | 0          | 1     | 1     | 0     |
| 7             | 0          | 1     | 1     | 1     |
| 8             | 1          | 0     | 0     | 0     |
| 9             | 1          | 0     | 0     | 1     |
| 0             | 0          | 0     | 0     | 0     |

Next: don't care

| T Flip Flop: | $y_3^+$ | $y_2^+$ | $y_1^+$ | $y_0^+$ |
|--------------|---------|---------|---------|---------|
| 0 → 0        | 0       |         |         |         |
| 0 → 1        | 1       |         |         |         |
| 1 → 0        | 1       |         |         |         |
| 1 → 1        | 0       |         |         |         |

BCD counter

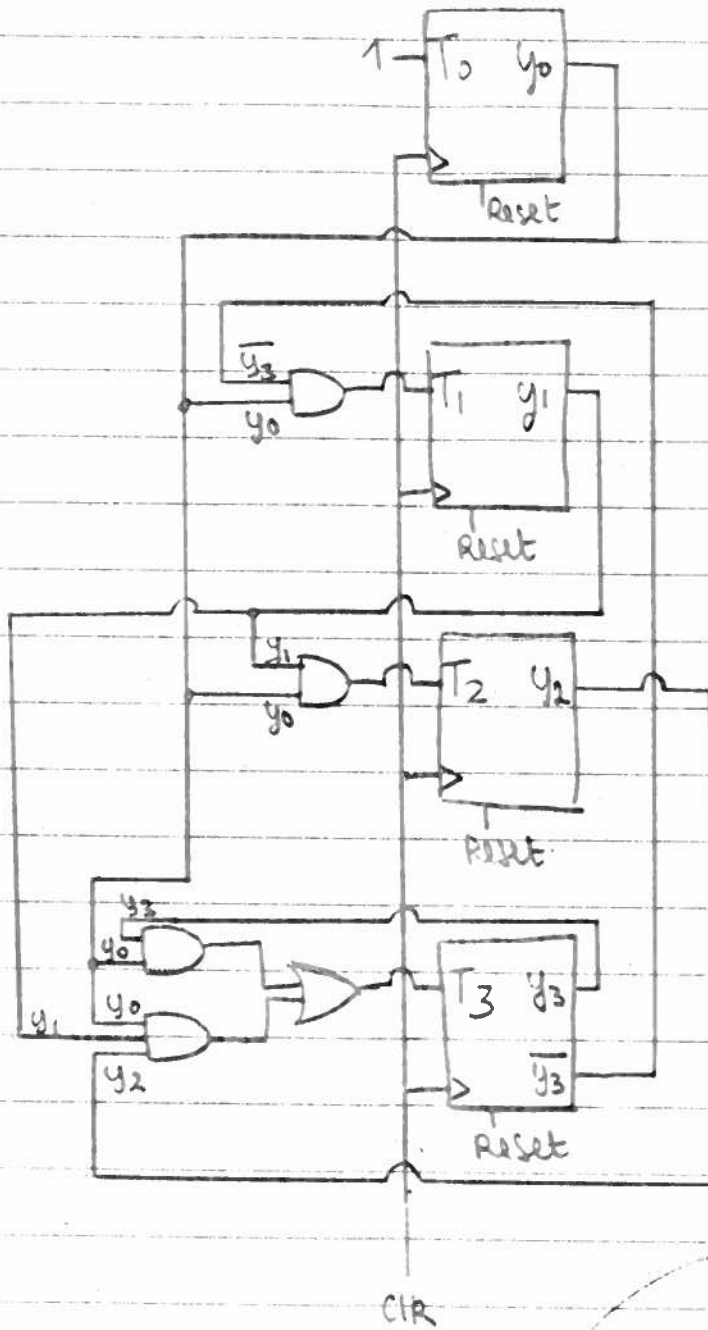

10/  
10

$y_3^+$

|                      |    |    |    |    |
|----------------------|----|----|----|----|
| $y_3 \backslash y_2$ | 00 | 01 | 11 | 10 |
| 00                   |    |    | 1  |    |
| 01                   |    |    | 1  |    |
| 11                   | X  | X  | X  | X  |
| 10                   |    | 1  | X  | X  |

$$T_3 = y_3 y_0 + y_2 y_1 y_0$$

$y_2^+$

|                      |    |    |    |    |
|----------------------|----|----|----|----|
| $y_3 \backslash y_2$ | 00 | 01 | 11 | 10 |
| 00                   |    |    | 1  |    |
| 01                   |    |    | 1  |    |
| 11                   | X  | X  | X  | X  |
| 10                   |    |    | X  | X  |

$$T_2 = y_1 y_0$$

$y_1^+$

|                      |    |    |    |    |
|----------------------|----|----|----|----|
| $y_3 \backslash y_2$ | 00 | 01 | 11 | 10 |
| 00                   |    | 1  | 1  |    |
| 01                   |    | 1  | 1  |    |
| 11                   | X  | X  | X  | X  |
| 10                   |    |    | X  | X  |

$$T_1 = \overline{y_3} y_0$$

$y_0^+$

|                      |    |    |    |    |
|----------------------|----|----|----|----|
| $y_3 \backslash y_2$ | 00 | 01 | 11 | 10 |
| 00                   | 1  | 1  | 1  | 1  |
| 01                   | 1  | 1  | 1  | 1  |
| 11                   | X  | X  | X  | X  |
| 10                   | 1  | 1  | X  | X  |

$$T_0 = 1$$

Question 3

a)  $N = N_2 N_1 N_0$      $M = M_2 M_1 M_0$

| K | $N_2$ | $N_1$ | $N_0$ |    | $M_2$ | $M_1$ | $M_0$ |
|---|-------|-------|-------|----|-------|-------|-------|
| 0 | 0     | 0     | 0     | 0  | 0     | 0     | 1     |
| 0 | 0     | 0     | 1     | 1  | 0     | 1     | 0     |
| 0 | 0     | 1     | 0     | 2  | 0     | 1     | 1     |
| 0 | 0     | 1     | 1     | 3  | 1     | 0     | 0     |
| 0 | 1     | 0     | 0     | 4  | 1     | 0     | 1     |
| 0 | 1     | 0     | 1     | 5  | 1     | 1     | 0     |
| 0 | 1     | 1     | 0     | 6  | 1     | 1     | 1     |
| 0 | 1     | 1     | 1     | 7  | X     | X     | X     |
| 1 | 0     | 0     | 0     | 8  | 0     | 1     | 0     |
| 1 | 0     | 0     | 1     | 9  | 0     | 1     | 1     |
| 1 | 0     | 1     | 0     | 10 | 1     | 0     | 0     |
| 1 | 0     | 1     | 1     | 11 | 1     | 0     | 1     |
| 1 | 1     | 0     | 0     | 12 | 1     | 1     | 0     |
| 1 | 1     | 0     | 1     | 13 | 1     | 1     | 1     |
| 1 | 1     | 1     | 0     | 14 | X     | X     | X     |
| 1 | 1     | 1     | 1     | 15 | X     | X     | X     |

$M_2$  K  $N_2$   $N_1$   $N_0$

| $N_2$ | $N_1$ | $N_0$ | 00 | 01 | 11 | 10 |
|-------|-------|-------|----|----|----|----|
| 00    |       |       |    |    | 1  |    |
| 01    | 1     | 1     | X  | 1  |    |    |
| 11    | 1     | 1     | X  | X  |    |    |
| 10    |       |       | 1  | 1  |    |    |

$M_2 = N_2 + N_1 N_2 + K N_0$   
 $= N_2 + N_0 (K + N_1)$

$M_1$  K  $N_2$   $N_1$   $N_0$


| $N_2$ | $N_1$ | $N_0$ | 00 | 01 | 11 | 10 |
|-------|-------|-------|----|----|----|----|
| 00    |       |       |    | 1  |    | 1  |
| 01    | 1     | 1     | X  | 1  |    |    |
| 11    | 1     | 1     | X  | X  |    |    |
| 10    | 1     | 1     | 1  | 1  |    |    |

$M_1 = \overline{N_1} (K + N_0) + K N_1 \overline{N_0}$

$M_0$


| $N_2$ | $N_1$ | $N_0$ | 00 | 01 | 11 | 10 |
|-------|-------|-------|----|----|----|----|
| 00    |       |       |    |    |    | 1  |
| 01    | 1     | 1     |    |    |    | 1  |
| 11    | 1     | 1     | X  | X  |    |    |
| 10    | 1     | 1     | 1  | 1  |    |    |

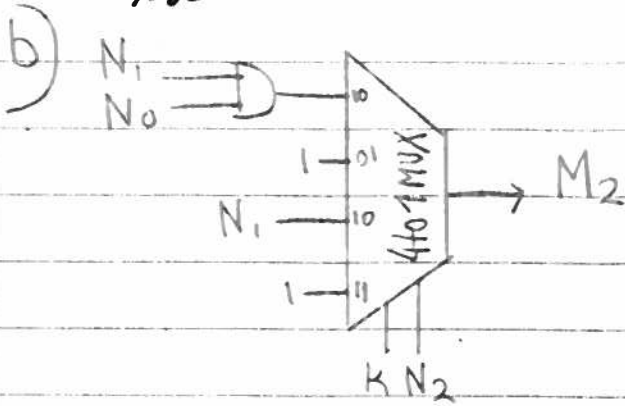
$M_0 = \overline{K N_0} + K N_0$   
 $= K \odot N_0$



↓

| $N_1 N_0$ \ $K N_2$ | 00 | 01 | 11 | 10 |
|---------------------|----|----|----|----|
| 00                  |    | 1  | 1  |    |
| 01                  |    | 1  | 1  |    |
| 11                  | 1  | X  | X  | 1  |
| 10                  |    | 1  | X  | 1  |

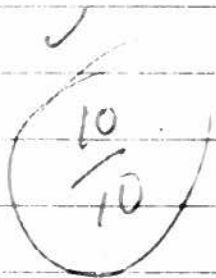

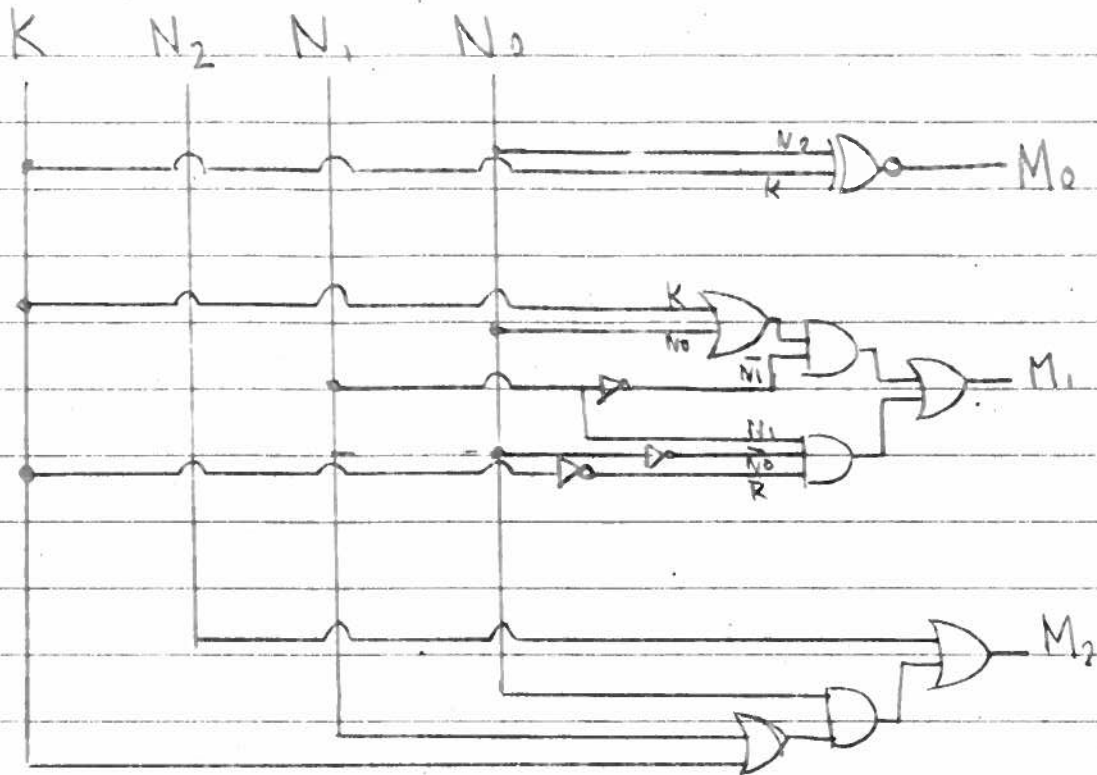



## Question 4

$$\begin{aligned}
 a) \quad f_1(a, b, c) &= \overline{a'c + b'c' + ab} \\
 &= \overline{(a+c')(b+c)(a'+b')} \\
 &= \overline{(ab+ac+bc'+a'b')} \\
 &= \overline{a'ba + a'ac + a'bc' + abb' + ab'c + b'bc'}
 \end{aligned}$$

$$\begin{aligned}
 f_2(a, b, c) &= a'b' + bc + ac' &= \overline{abc' + ab'c} \\
 & &= \overline{(a'bc')(ab'c)}
 \end{aligned}$$

$$\begin{aligned}
 &= \overline{a'b' + bc + ac'} \\
 &= \overline{(a'b')(bc)(ac')}
 \end{aligned}$$

$$= \overline{(a+b)(b+c')(a'+c)}$$

$$= \overline{(ab'+ac+bc')(a'+c)}$$

$$= \overline{aba' + ab'c + ac'a' + ac'c + bc'a' + bc'c}$$

$$\textcircled{2} \quad = \overline{ab'c + a'bc'}$$

$$= \overline{(ab'c)(a'bc')} = f_1(a, b, c)$$

$$\begin{aligned}
 b) \quad f(a, b, c, d) &= ac' + ab'd + a'b'c + a'cd' + b'c'd' \\
 &= ac'(b+b')(d+d') + ab'd(c+c') + a'b'c(d+d') + a'cd'(b+b')
 \end{aligned}$$

$$\begin{aligned}
 &= ab'd + ab'c'd + abc'd' + ab'c'd' + ab'cd' + ab'c'd + a'b'cd + a'acd' \\
 &\quad + a'b'cd' + a'b'cd' + ab'c'd' + a'b'c'd'
 \end{aligned}$$

$\textcircled{1/2}$

c)

|    |                 |                 |                 |                 |
|----|-----------------|-----------------|-----------------|-----------------|
|    | 00              | 01              | 11              | 10              |
| 00 | 0 <sub>00</sub> | 0 <sub>01</sub> | 0 <sub>11</sub> | 0 <sub>10</sub> |
| 01 | 0 <sub>01</sub> | 1 <sub>01</sub> | 1 <sub>11</sub> | 0 <sub>10</sub> |
| 11 | 0 <sub>11</sub> | 1 <sub>01</sub> | 1 <sub>11</sub> | 0 <sub>10</sub> |
| 10 | 0 <sub>10</sub> | 0 <sub>01</sub> | 0 <sub>11</sub> | 0 <sub>10</sub> |

$$f = \prod M(0, 1, 2, 3, 4, 6, 7, 9, 10, 11, 12, 14)$$

3/3

d)  $A = (TE \times TI \times H)'$   
 $\rightarrow$  if H means 'it is not a holiday'

if H means 'it is a holiday'

then  $A = (TE \cdot TI \cdot \bar{H})'$

2/2

Question 5


Sequence detector  
'1101' and '011' assuming no Read state

$S_0 = 0$


$S_1 = 11$

$S_2 = 110$

$S_3 = 01$

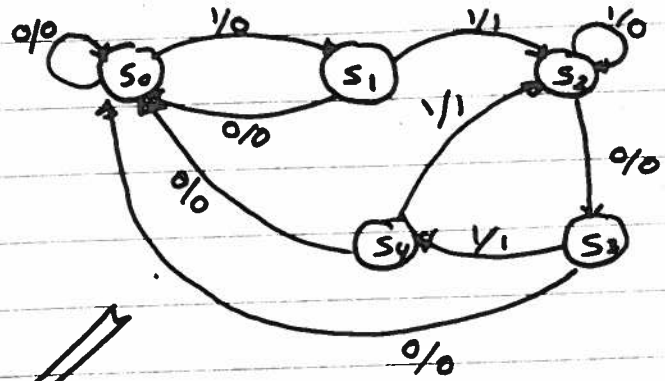

State Diagram

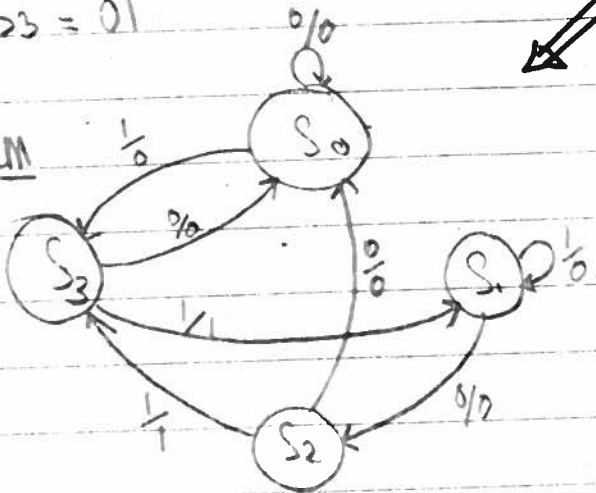

|                   |       |   |       |   |
|-------------------|-------|---|-------|---|
| $S_0$             | $S_0$ | 0 | $S_1$ | 0 |
| $\rightarrow S_1$ | $S_0$ | 0 | $S_2$ | 1 |
| $S_2$             | $S_3$ | 0 | $S_2$ | 0 |
| $S_3$             | $S_0$ | 0 | $S_4$ | 1 |
| $\rightarrow S_4$ | $S_0$ | 0 | $S_2$ | 1 |

$S_1$  &  $S_4$  are equal &  
 $S_4$  is replaced by  $S_1$

Transition table

| Present state | Next state |   | Output z |       |
|---------------|------------|---|----------|-------|
|               | $x=0$      | $x=1$                                   | $x=0$    | $x=1$ |
| $S$           | $y_1, y_0$ | $x=0 y_1^+ y_0^+ \quad x=1 y_1^+ y_0^+$ |          |       |
| $S_0$         | 0 0        | $S_0$ 00 $S_3$ 1 1                      | 0        | 0     |
| $S_1$         | 0 1        | $S_2$ 10 $S_1$ 0 1                      | 0        | 0     |
| $S_2$         | 1 0        | $S_0$ 00 $S_3$ 1 1                      | 0        | 1     |
| $S_3$         | 1 1        | $S_0$ 00 $S_1$ 0 1                      | 0        | 1     |

$y_0^+ = x$   
 $y_1^+ = \bar{x} \bar{y}_1 y_0 + x y_0$   
 $z = x y_1$


Using

D Flip-Flops

$$D = y^+$$

$$D_0 = x$$

$$D_1 = \bar{x} \bar{y}_1 y_0 + x y_0$$

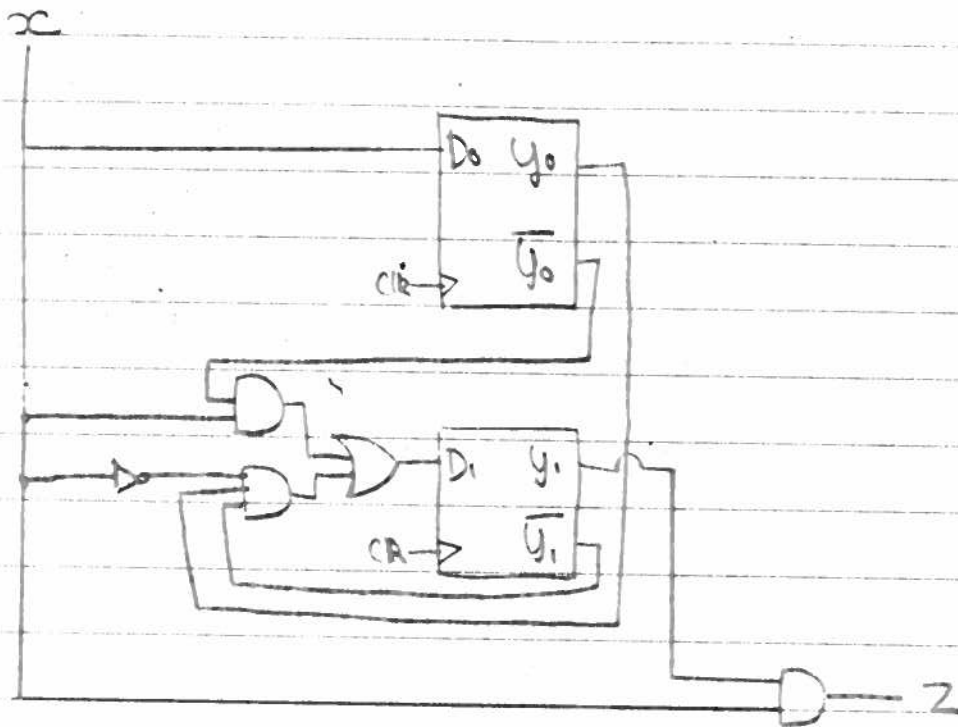

Question 6:

$D = y^+$

$D_1 = y_2 \bar{A}$


$D_2 = A + B + y_1$

$y_1^+ = y_2 \bar{A}$

$y_2^+ = A + B + y_1$

| Present State |   |       |       | Next State |         |
|---------------|---|-------|-------|------------|---------|
| A             | B | $y_1$ | $y_2$ | $y_1^+$    | $y_2^+$ |
| 0             | 0 | 0     | 0     | 0          | 0       |
| 0             | 0 | 0     | 1     | 1          | 0       |
| 0             | 0 | 1     | 0     | 0          | 1       |
| 0             | 0 | 1     | 1     | 1          | 1       |
| 0             | 1 | 0     | 0     | 0          | 1       |
| 0             | 1 | 0     | 1     | 1          | 1       |
| 0             | 1 | 1     | 0     | 0          | 1       |
| 0             | 1 | 1     | 1     | 1          | 1       |
| 1             | 0 | 0     | 0     | 0          | 1       |
| 1             | 0 | 0     | 1     | 0          | 1       |
| 1             | 0 | 1     | 0     | 0          | 1       |
| 1             | 0 | 1     | 1     | 0          | 1       |
| 1             | 1 | 0     | 0     | 0          | 1       |
| 1             | 1 | 0     | 1     | 0          | 1       |
| 1             | 1 | 1     | 0     | 0          | 1       |
| 1             | 1 | 1     | 1     | 0          | 1       |

State Diagram

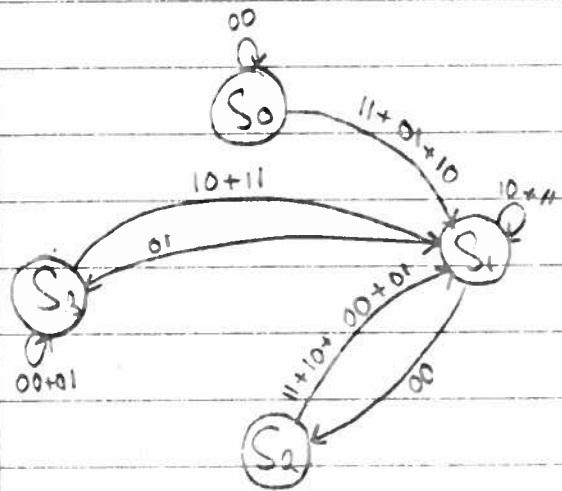

✓