

Question 1 (Use Boolean Algebra for Question 1)


1.a Simplify to obtain minimum SOP (2 marks)

$$F(W,X,Y,Z) = [XY \oplus (X + Y')][(W \odot (W + Y))]$$

1.b Simplify to obtain minimum SOP (2 marks)

$$F(a,b,c,d) = a'b'(c+d')(1+0) + ab(c'd+cd') + (a'b+0)cd$$

1.c Minimize the following circuit, draw final minimized circuit with minimum number of packages. You have single rails available to you. (3 marks)

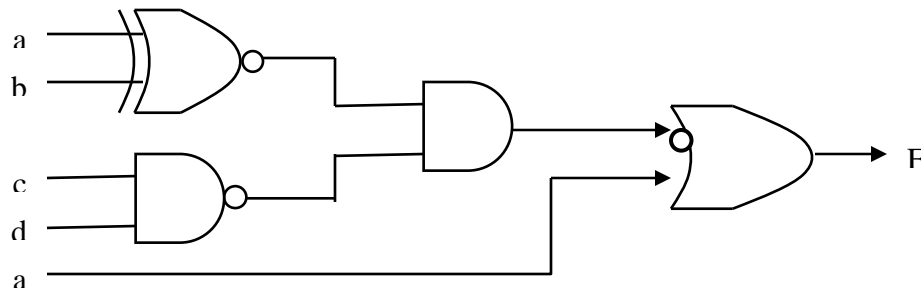**Question 2**2.a Give **minimal SOP** for $F(a,b,c,d)$ given by the following K-map (3 marks)
Identify the prime Implicants clearly.

		ab			
		00	01	11	10
cd	00	1	X	X	X
	01		1	1	
	11	1			1
	10	X	X	X	X

2.b Give the **POS** of $F(A,B,C,D) = (A + CD)(B + CD)$ (1 mark)2.c Give the **miniterm list** of $F(A,B,C,D) = B$ (1 mark)2.d Give the minimal **NOR-NOR** implementation of
 $F(A,B,C,D) = ABC + A(D + CB)$ (2 marks)**Question 3**3.1 a) Minimize $F(W,X,Y,Z) = C + AB' + AC'D$ using **Quine-McClusky's method**

b) Identify the Essential Prime Implicant (6 marks)

3.2 Draw the timing diagram for $F(A,B,C) = AB + (A'C)$ for the following consecutive inputs. $ABC = 010, 101, 010, 111$ (**follow these vectors in order given. Start from $ABC = 000$ **). Assume the following gate delays, AND = 3ns, OR gate = 4ns, and inverter = 2ns. (4 marks)


Solutions

Question 1

$$\begin{aligned}
 1.a \quad F(W,X,Y,Z) &= [XY \oplus (X + Y')] [W \odot (W + Y)] \\
 &= [XY(X + Y')' + (XY)' (X + Y')][W(W + Y) + W'(W + Y)'] \\
 &= [XY(X'Y) + (X' + Y')(X + Y')][W + W'(W'Y')] \\
 &= [0 + Y' + 0][W + Y'] \\
 &= Y'[W + Y'] = Y'
 \end{aligned}$$

$$\begin{aligned}
 1.b \quad F(a,b,c,d) &= a'b'(c + d')(1 + 0) + ab(c'd + cd') + (a'b + 1)cd \\
 &= a'b'c + a'b'd' + abc'd + abcd' + cd \\
 &= a'b'c + a'b'd' + abd + abc + cd
 \end{aligned}$$

$$\begin{aligned}
 1.c \quad F &= ((a \oplus b)' \cdot (cd)')' + a \\
 &= (a \oplus b + cd + a) \\
 &= a + b + cd \\
 &= ((a + b + c)(a + b + d))'' \\
 &= ((a + b + c)' + (a + b + d)')'
 \end{aligned}$$

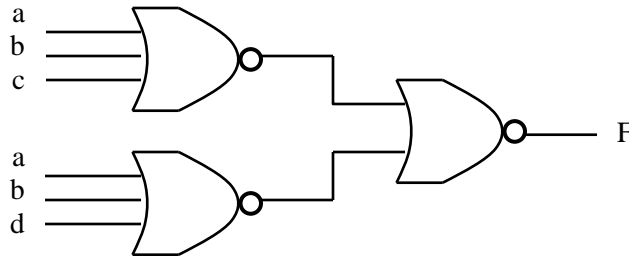

Question 2

2.a

AB \ CD	00	01	11	10
00	1	X	X	X
01		1	1	
11	1			1
10	X	X	X	X

$$\begin{aligned}
 2.b \quad F(A,B,C,D) &= (A + CD)(B + CD) \\
 &= (A + C)(A + D)(B + C)(B + D)
 \end{aligned}$$

$$2.c \quad F(A,B,C,D) = B$$

$$= \sum m(4,5,6,7,12,13,14,15)$$

	AB			
CD	00	01	11	10
00		1	1	
01		1	1	
11		1	1	
10		1	1	


$$2.d \quad F(A,B,C,D) = ABC + A(D + CB)$$

$$= ABC + AD + ABC$$

$$= ABC + AD$$

$$= A(BC + D)$$

$$= A(B + D)(C + D)$$

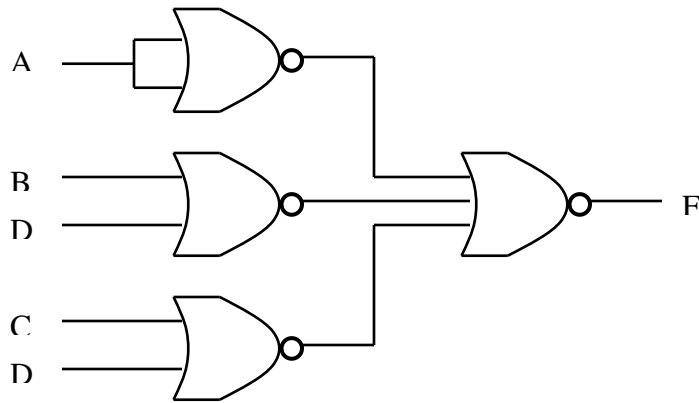

Question 3

$$3.1 \text{ a) } F(A,B,C,D) = C + AB' + AC'D$$


$$= \prod M(0, 1, 4, 5, 12)$$

	AB			
CD	00	01	11	10
00	0	0	0	1
01	0	0	1	1
11	1	1	1	1
10	1	1	1	1

0		0, 1, 4, 5 (1,4) *a	
1	0, 1 (1)		
4	0, 4 (4)		
5	1, 5 (4)		0, 1, 4, 5, 12
12	4, 5 (1)	*a	1 1 1 1
	4, 12 (8) *b	*b	1 1
		$F = a + b = (A + C)(B' + C + D)$	

3.1 b) Both a and b are essential PI

3.2 $F = AB + A'C$

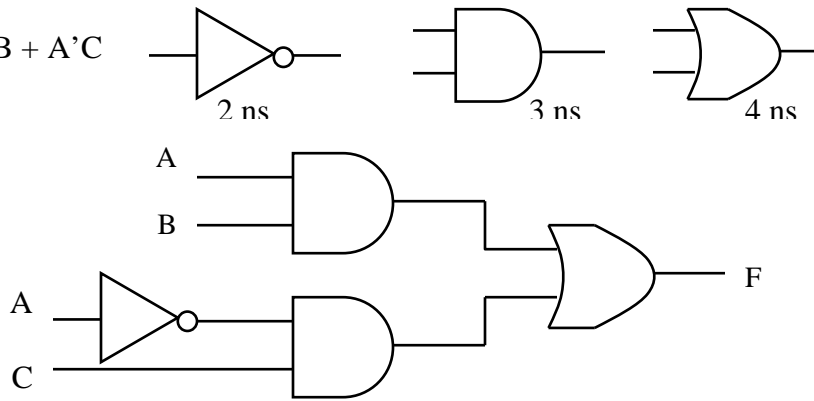

Longest delay = 2 + 3 + 4 = 9 ns, take period = 10

