

**Question 1 (Use Boolean Algebra for Question 1)**


- 1.a Simplify to obtain minimum SOP (3 marks)

$$F(A, B, C, D) = [AB \oplus C][(\overline{AB \odot D})']$$

- 1.b Simplify to obtain minimum SOP (2 marks)

$$F(A, B, C, D) = A'B'(C + C') + AB + (1 + 0)D$$

- 1.c Minimize the following circuit, draw final minimized circuit with minimum number of packages. You have single rails available to you. (3 marks)

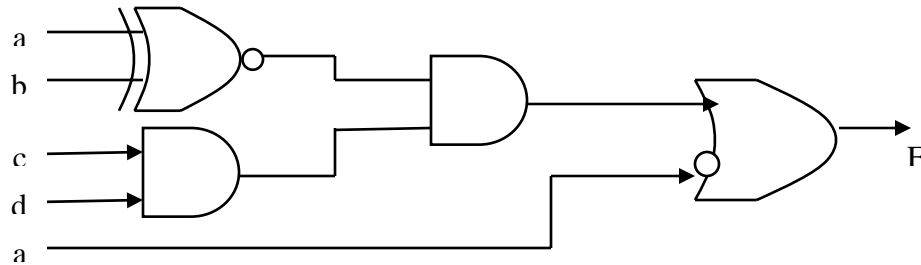**Question 2**

- 2.a Give
- minimal SOP**
- for
- $F(a,b,c,d)$
- given by the following K-map (2 marks)
- 
- Identify the prime Implicants clearly.

	ab					
		cd	00	01	11	10
00			X	X	X	X
01				1	X	
11			1			1
10			X	X	X	X


- 2.b Give minimal POS for
- $F(a,b,c,d)$
- given by the following K-map (3 marks)
- 
- Identify the Prime Implicants clearly

	ab					
		cd	00	01	11	10
00			X	X	X	X
01			1	1	X	
11						
10			X	X	X	X


- 2.c Give the **POS** of  $F(A,B,C,D) = (AB + BCD)(B + CD)$  (1 mark)  
 2.d Give the **minterm list** of  $F(A,B,C,D) = AB$  (1 mark)  
 2.e Give the **NOR-NOR** implementation of  $F(A,B,C,D) = ABC + CD + CB$  (2 marks)  
 2.f Give an all NAND implementation of  $F(A,B,C,D) = AB$  (1 mark)

Question 3

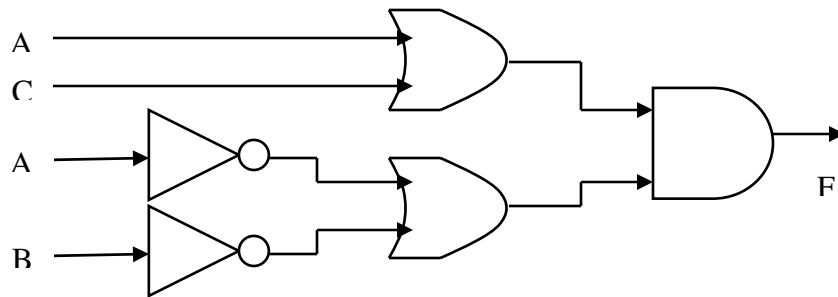- 3.a Draw the timing diagram for F, for the following consecutive inputs.  
 $ABC = 000, 100, 010$ , (\*\*follow these vectors in order given. Start from  $ABC = 000$ \*\*). Assume all gates have equal delay of 2 ns.



- 3.b Analyze the following circuit.

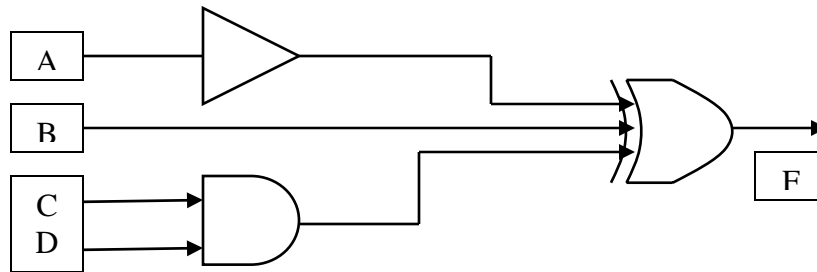


## Solutions

### Question 1

$$\begin{aligned}
 1.a \quad F(A,B,C,D) &= [AB \oplus C] [AB \odot D] \\
 &= [ABC' + (AB)'C][ABD' + (AB)'D]' \\
 &= [ABC' + (A' + B')C][((ABD')'((AB)'D)')] \\
 &= [ABC' + (A' + B')C][(A' + B' + D)(AB + D')] \\
 &= [ABC' + A'C + B'C][A'D' + B'D' + ABD] \\
 &= [ABC'D + A'CD' + A'B'CD' + A'B'CD' + B'CD'] \\
 &= ABC'D + A'CD' + B'CD'
 \end{aligned}$$

$$\begin{aligned}
 1.b \quad F(A,B,C,D) &= A'B'(C + C') + AB + (1 + 0)D \\
 &= A'B' + AB + D
 \end{aligned}$$
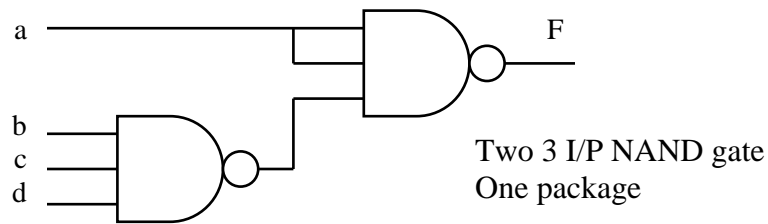
$$\begin{aligned}
 1.c \quad F(a,b,c,d) &= (a \oplus b)' (cd) + a' \\
 &= (ab + a'b')cd + a' \\
 &= abcd + a'b'cd + a' \\
 &= abcd + a' \\
 &= bcd + a' \\
 &= (bcd + a')'' \\
 &= ((bcd)' . a)'
 \end{aligned}$$



### Question 2

2.a

AB \ CD	00	01	11	10
00	X	X	X	X
01		1	X	
11	1			1
10	X	X	X	X

$= \sum m(4,5,12,13)$   
 $= BC'$

$= \sum m(2,3,10,11)$   
 $= B'C$

$$F = BC' + B'C$$

PI Implicants are  $BC'$  &  $B'C$

2.b

		AB				
		00	01	11	10	
CD	00	X	X	X	X	= $\prod M(8,9,10,11,12,13,14,15)$ = $A'$
	01	1	1	X	0	
	11	0	0	0	0	= $\prod M(2,3,6,7,10,11,14,15)$ = $C'$
	10	X	X	X	X	

$$F = C'A'$$


Both  $C'$  &  $A'$  are essential PI

2.c  $F(A,B,C,D) = (AB + BCD)(B + CD)$   
 $= B(A + CD)(B + CD)$   
 $= B(A + C)(A + D)(B + C)(B + D)$   
 $= B(A + C)(A + D)$


2.d  $F(A,B,C,D) = AB$

		AB				
		00	01	11	10	
CD	00	0	0	1	0	= $\sum m(12,13,14,15)$
	01	0	0	1	0	
	11	0	0	1	0	
	10	0	0	1	0	

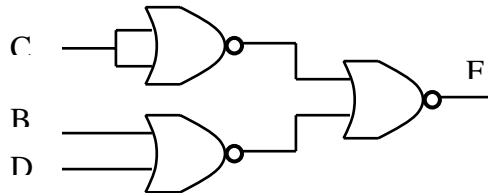2.e  $F(A,B,C,D) = ABC + CD + CB$   
 $= CB + CD$   
 $= C(B + D)$   
 $= [C(B + D)]''$   
 $= [C' + (B + D)]'$




2.f  $F(A,B,C,D) = AB = (AB)''$

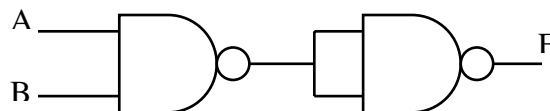

Question 3

3.a

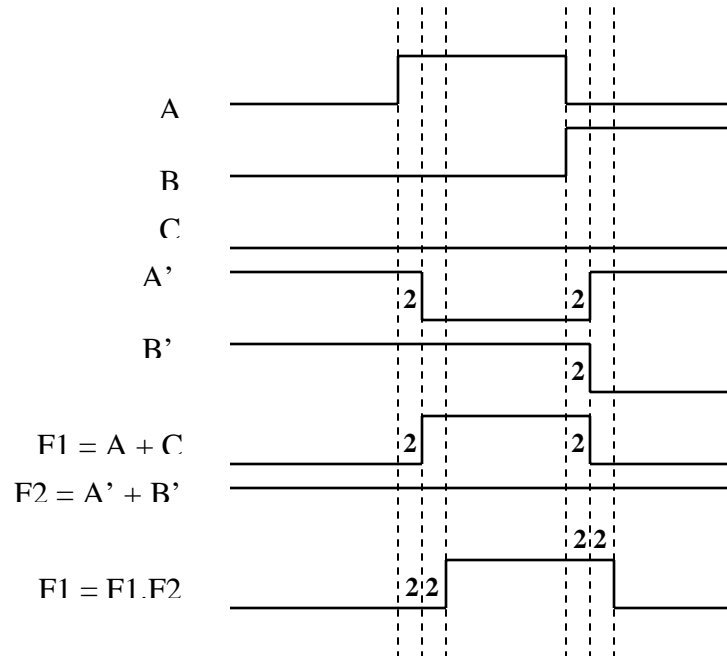

3.b

With inverter			With buffer		
A B C D	F1 F2 F	minterm	A B C D	F1 F2 F	minterm
0 0 0 0	1 0 1	0	0 0 0 0	0 0 0	0
0 0 0 1	1 0 1	1	0 0 0 1	0 0 0	1
0 0 1 0	1 0 1	2	0 0 1 0	0 0 0	2
0 0 1 1	1 1 0	3	0 0 1 1	0 1 1	3
0 1 0 0	1 0 0	4	0 1 0 0	0 0 1	4
0 1 0 1	1 0 0	5	0 1 0 1	0 0 1	5
0 1 1 0	1 0 0	6	0 1 1 0	0 0 1	6
0 1 1 1	1 1 1	7	0 1 1 1	0 1 0	7
1 0 0 0	0 0 0	8	1 0 0 0	1 0 1	8
1 0 0 1	0 0 0	9	1 0 0 1	1 0 1	9
1 0 1 0	0 0 0	10	1 0 1 0	1 0 1	10
1 0 1 1	0 1 1	11	1 0 1 1	1 1 0	11
1 1 0 0	0 0 1	12	1 1 0 0	1 0 0	12
1 1 0 1	0 0 1	13	1 1 0 1	1 0 0	13
1 1 1 0	0 0 1	14	1 1 1 0	1 0 0	14
1 1 1 1	0 1 0	15	1 1 1 1	1 1 1	15
$F1 = A'$ $F2 = CD$ $F = B \oplus F1 \oplus F2$			$F1 = A$ $F2 = CD$ $F = B \oplus F1 \oplus F2$		