

Question 1 (Use Boolean Algebra for Question 1)


1.a Simplify to obtain minimum SOP (2 marks)

$$F(A, B, C, D) = A'B'CD' + AC'D' + ABC' + AB'C + AB'C + BC'D$$

1.b Simplify to obtain minimum SOP (2 marks)

$$F(A, B, C, D) = A'B'(1 + C')' + A + (0 + D') + D$$

1.c Minimize the following circuit, Give minimum circuit in **NAND-NAND** Form. (3 marks)

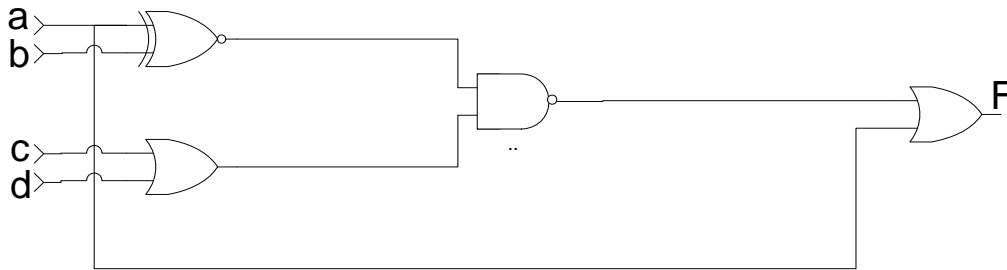

Question 2

a) Give **minimal POS** for F(a,b,c,d) given by the following K-map.

Identify the prime Implicants clearly. Identify the Essential Prime Implicants. Give the minimum AND-OR-NOT implementation. (4 marks).

		ab			
		00	01	11	10
cd	00	X	X	X	X
	01	1	1	X	
	11	1	1	1	
	10	X	1	1	X

b) Give **minimal NOR-NOR** implementation for F(a,b,c,d) given by the following K-map (2 marks).

		ab			
		00	01	11	10
cd	00		X	X	
	01		1	X	
	11	X			
	10	X	1	1	X

c) Using F1 determine minimum F (4 marks)

	ab			
cd	00	01	11	10
00	X	X	X	X
01	1	1	X	
11	1	1	1	
10	X	1	1	X


F1

	ab			
cd	00	01	11	10
00	X	X	X	X
01	1	1	X	1
11		1	1	
10	X	1	1	X

F

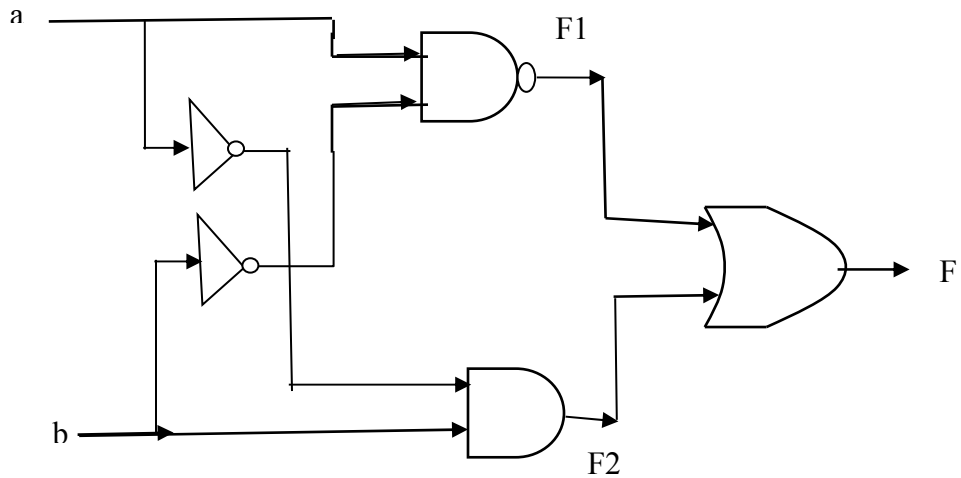Question 3

In the circuit below the delays are as follows:
 Delay of inverter = 2ns
 Delay of AND = 6ns
 Delay of NAND = 5ns
 Delay of OR = 8ns
 Input of the circuit goes from ab= 00 to 01 to 10 draw timing diagram for the circuit. (8 marks)



Midterm Solutions

COEN 312 Summer 2010

Q1 a)



$$\begin{array}{cccccc}
 A'B'CD' & + & AC'D' & + & ABC' & + & AB'C & + & AB'C & + & BC'D \\
 2 & & 8,12 & & 12, 13 & & 10,11 & & 10,11 & & 5,13 \\
 & & \downarrow & & & & & & & & \swarrow \\
 \dots & & & & ABC'(D+D') & \leftarrow & & & & & ABC' \text{ is deleted} \\
 2 \ \& \ 10,11 & & & A'B'CD' + AB'C = B'C(A+A'D) & & & & & & \\
 \text{Final Result: } & B'CD' & + & AC'D' & + & AB'C & + & BC'D & & &
 \end{array}$$

Q1 b)

$$\begin{aligned}
 F(A,B,C,D) &= A'B'(1+C')' + A + (0 + D') + D \\
 &= A'B'0 + A + D + D' \\
 &= 0 + A + 1 \\
 &= 1
 \end{aligned}$$

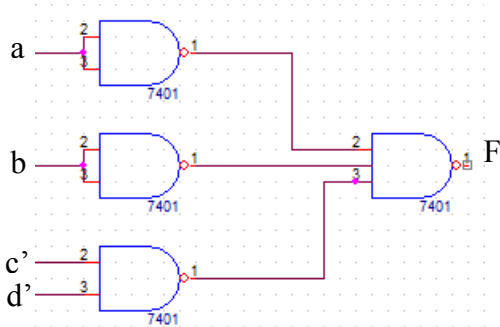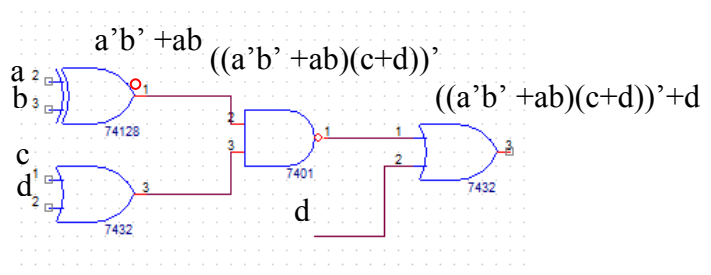Q1 c)

$$\begin{aligned}
 F &= (a'b' + ab)' + (c+d)' + d \\
 &= ab' + a'b + c'd' + d \\
 &= a + b + c'd'
 \end{aligned}$$



Assuming double rail $(a+b+c'd')' = (a'b'c'd')$

Alternate for Q1 a)

$$\begin{aligned}
 &= A'B'CD' + AC'D' + ABC' + AB'C + AB'C + BC'D \\
 &= A'B'CD' + (C'D' + BC' + B'C)A + BC'D \\
 &= A(CC'+B'C) + BC'D + A'B'CD' \\
 &= AC'D' + A'B'CD' + AB'C + BC'D \\
 &= AC'D' + B'CD' + AB'C + BC'D
 \end{aligned}$$

Q2 a)

i) Prime Implicant

$$\begin{aligned}
 PI_1 &= \sum_m(0,1,2,3,4,5,6,7) = A' \\
 PI_2 &= \sum_m(4,5,6,7,12,13,14,15) = B \\
 PI_3 &= \sum_m(0,2,4,6,8,10,12,14) = D'
 \end{aligned}$$

AB

<u>CD</u>	00	01	11	10
00	X	X	X	X
01	1	1	X	
11	1	1	1	
10	1	1	1	X


$$F = A' + B$$

ii) EPI = $PI_1 \& PI_2$

iii) $F' = AB'$

$$F = (AB')'$$

Assume double rail

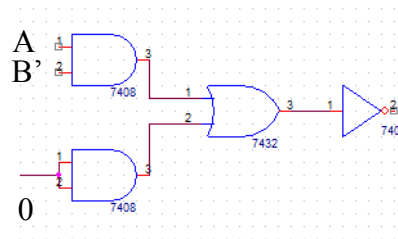

AB

<u>CD</u>	00	01	11	10
00	X	X	X	X
01			X	1
11				1
10	X			X

Q2 b)

$$F = B(C' + D')$$

$$F = (B+0)(C'+D')$$


$$F = ((B+0)' + (C'+D')')$$

AB

<u>CD</u>	00	01	11	10
00	0	X	X	0
01	0		X	0
11	X	0	0	0
10	X			X

$$F = (F_1F_2) + F_3$$

Assume double rail

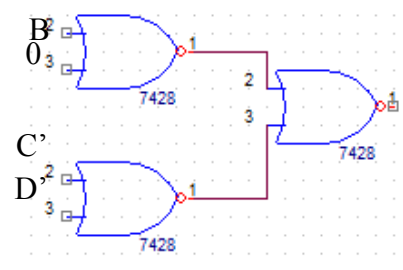

i.e. remove m_3 & add m_9 ; $F = F_1m_3' + m_0$

<u>AB</u>	00	01	11	10
CD	X	X	X	X
00	X	X	X	X
01	1	1	X	X
11	0	1	0	X
10	X	1		X

$$F_2 = B + C'$$

<u>AB</u>	00	01	11	10
CD	X	X	X	X
00	X	X	X	X
01	X	X	X	1
11	X	X	X	0
10	X	X	X	X

$$F_3 = C'$$

$$F = F(B+C') + C'$$

$$F = FB + C'$$

