

COEN 212:
DIGITAL SYSTEMS DESIGN I
Lecture 11: Registers and Counters

Instructor: Dr. Reza Soleymani, Office: EV-5.125,
Telephone: 848-2424 ext.: 4103.

Lecture 11:

Objectives of this lecture


- **In this lecture, we talk about:**
 - **Different types of Registers.**
 - **Implementation of registers and**
 - **Different Types of Counters.**
 - **Implementation of Counters.**
 - **Sample Applications.**

Lecture 11: Reading for this lecture


- **Digital Design by M. Morris R. Mano and Michael D. Ciletti, 6th Edition, Pearson, 2018:**
 - **Chapter 6**

Lecture 11: Registers:

- 4-bit register:

 


4-bit register with Load control

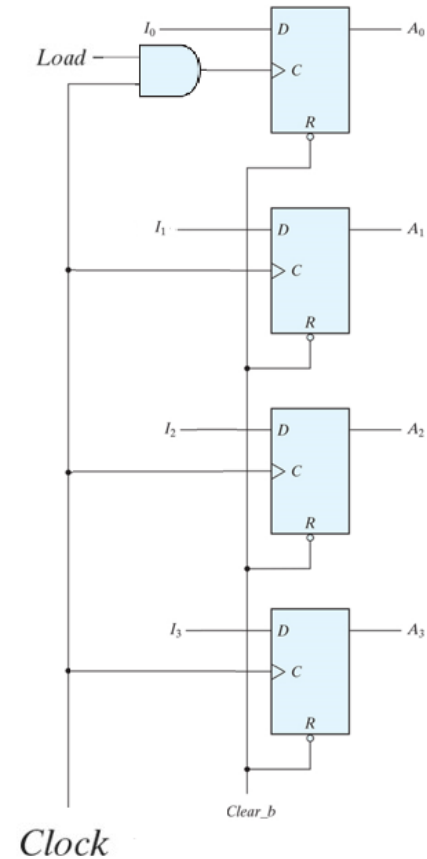


Lecture 11: Registers:

- MUX for Load Control:

 


- Implementation of the MUX:

 


Lecture 11: Registers:

- 4-bit register with Load:

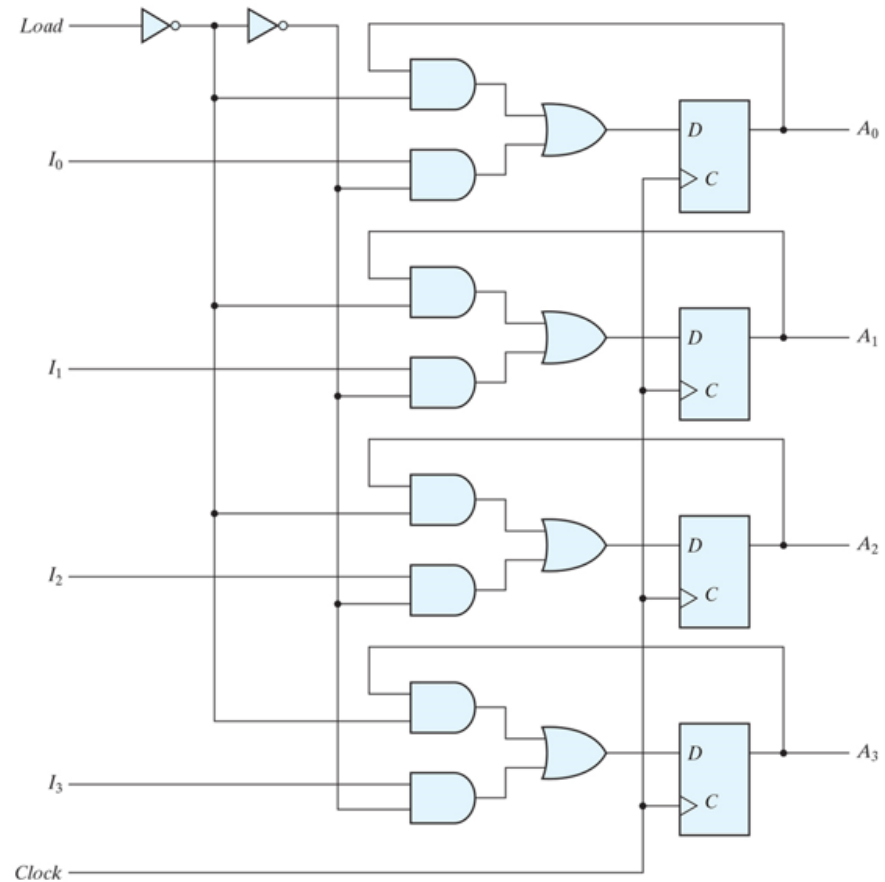


Lecture 11: Shift Registers:

- 4-bit Shift Register:

 


- Serial Transfer:

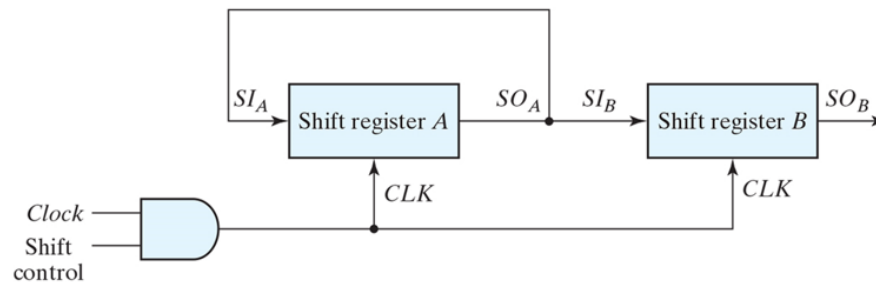

Lecture 11:

Register to Register Serial Transfer:

- Serial Transfer:

 


- Content of registers:

Timing Pulse	Shift Register A	Shift Register B
Initial value	1011	0010
After T_1	1101	1001
After T_2	1110	1100
After T_3	0111	0110
After T_4	1011	1011

Lecture 11: Serial Addition:

- Serial Adder:

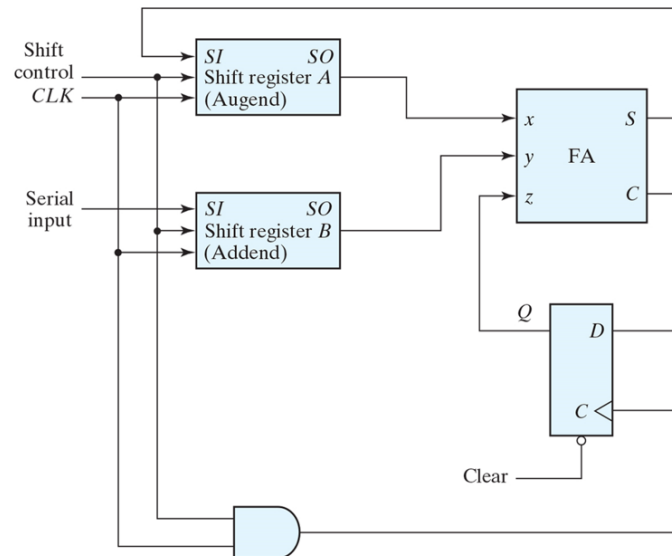

Lecture 11:

Serial Addition: JK FF Implementation

- State Transition Table:

Present state	Inputs		Next state	Output	FF Inputs	
Q	x	y	Q	S	J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

- FF input equations:

$$J_Q = xy$$
$$K_Q = x'y' = (x + y)'$$

The output equation:

$$S = x \oplus y \oplus Q$$

Lecture 11:

Universal Shift Register


- A Universal SR can:
 - Remain unchanged,
 - Load serially and shift right,
 - Load serially and shift left,
 - Load in parallel.

- We need 4 control signals (2 control bits):

Control bits		operation
s_1	s_0	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

Lecture 11: Universal Shift Register

- The circuit for Universal shift Register:

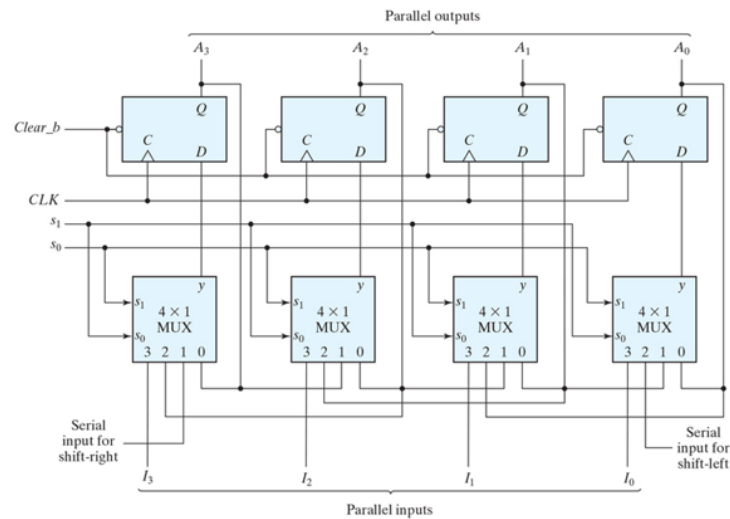

Lecture 11:


Counters:

- A counter is a register that changes in a certain order.
- Examples:
 - A binary counter counts from 0 to $2^n - 1$.
 - A BCD counter counts from 0 to 9 (0000 to 1001).
- There are two types of counters:
 - Ripple counters
 - Synchronous counters
- In a synchronous counter, state changes are dictated by a common clock.
- In a ripple counter, the output of one flip-flop has effect on the next state of the following flip-flop.

Lecture 11:

Binary Ripple Counter: with T FF


- A 4-bit ripple counter:

 

Lecture 11:

Binary Ripple Counter: with D FF


- A 4-bit ripple counter with D FFs:

 


Lecture 11:

BCD Ripple Counter:

- State Diagram of a BCD Ripple Counter:

 


Circuit Diagram:

 

Lecture 11: Synchronous Counters:


- State Diagram of a Synchronous Binary Counter:

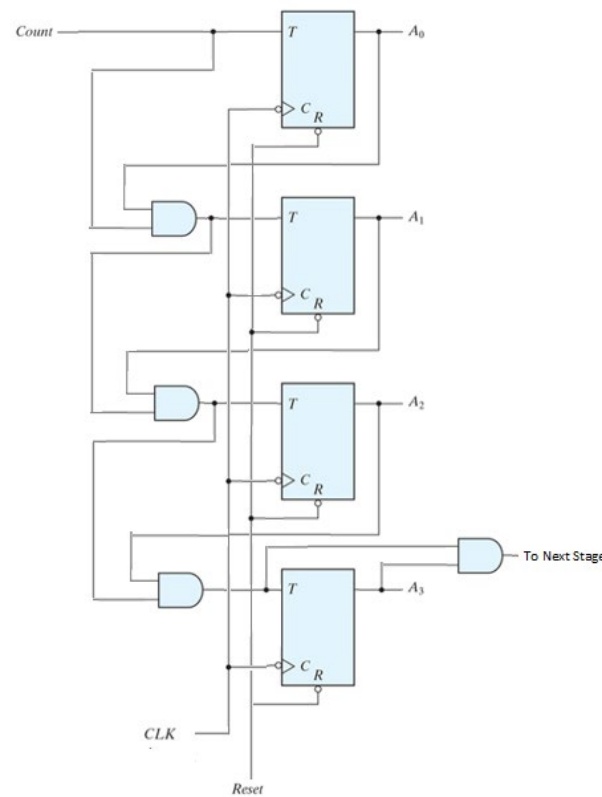

Lecture 11:

Up-Down counters:

- A 4-bit up/down counter:

 

Lecture 11:

Synchronous BCD counter:

- State transition table of a 4-bit up/down counter:

Present state				Next state				Output	FF inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	T_8	T_4	T_2	T_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

Lecture 11:

Synchronous BCD counter:

- K-map for T_2 :

		$Q_2 Q_1$		Q_2	
		00	01	11	10
$Q_8 Q_4$	00	m_0	m_1 1	m_3 1	m_2
	01	m_4	m_5 1	m_7 1	m_6
Q_8	11	m_{12} X	m_{13} X	m_{13} X	m_{14} X
	10	m_8	m_9	m_{11} X	m_{10} X
		Q_1		Q_4	

FF Input Equations:

$$T_1 = 1,$$

$$T_2 = Q_8' Q_1,$$

$$T_4 = Q_2 Q_1$$


$$T_8 = Q_8 Q_1 + Q_4 Q_2 Q_1$$

and the output equation: $y = Q_8 Q_1.$

Lecture 11:

Synchronous BCD counter:


- The circuit for a BCD Counter with T Flip-flops:

 

Lecture 11:

Counters with Parallel Load:

- Binary Counter with Parallel Load:

 

Lecture 11:

Counters with Unused States:

- Binary Counter with n flip-flops can have 2^n states.
- We may not need all these states.
- We have already seen the example of BCD counter that uses only 10 out of $2^4 = 16$ possible states.
- We can treat the unused states:
 - as don't care condition or
 - some specific next states. Since,
- **Example:** consider a counter following the sequence 000, 001, 010, 100, 101, 110. That is, the counter skips 011 and 111.

Lecture 11:

Counters with Unused States:

- **Example:** consider a counter following the sequence 000, 001, 010, 100, 101, 110. That is, the counter skips 011 and 111.
- The state table for this counter is:


Present state			Next state			Flip-flop inputs					
<i>A</i>	<i>B</i>	<i>C</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>J_A</i>	<i>K_A</i>	<i>J_B</i>	<i>K_B</i>	<i>J_C</i>	<i>K_C</i>
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

- We have $J_A = K_A = B$, $J_B = C$, $K_B = 1$, $J_C = B'$, and $K_C = 1$.


Lecture 11:

Counters with Unused States:

- The circuit diagram is:


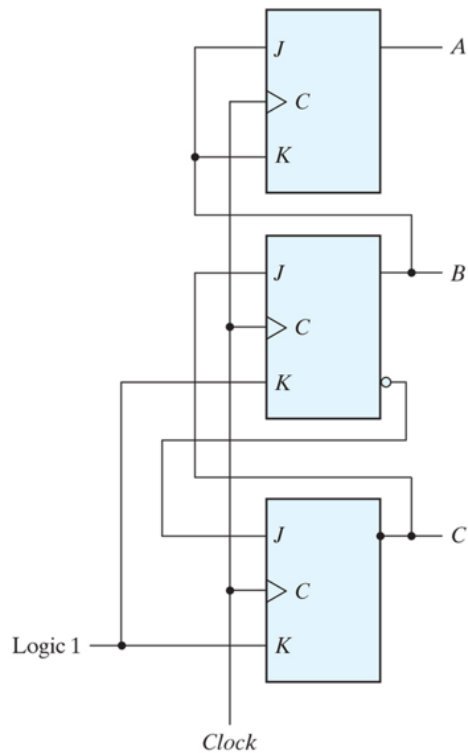


State Diagram:

 


Lecture 11: Ring Counter:

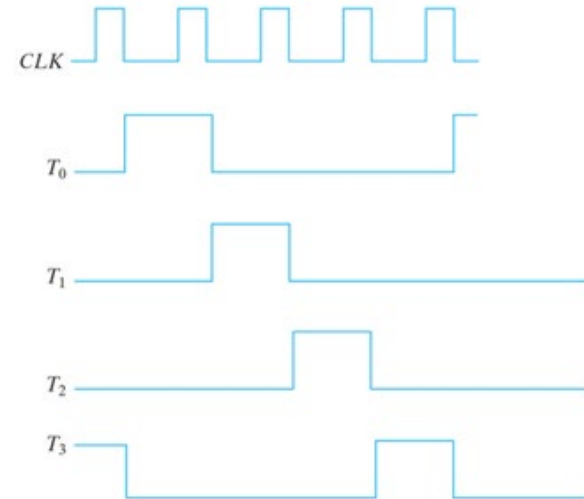 - A Ring Counter counts: 1000, 0100, 0010, 0001, 1000, ...
- At any time only one FF is on.
- It can be used to control a sequence of repetitive operations.
- A Ring Counter can be implemented by connecting the output of a shift register to its input.




Two FF implementation:

 

Lecture 11: Johnson Counter:

 - Schematic of
- switch-tail Ring Counter:



- A Johnson counter is a switch tail ring with outputs (or inverted outputs) of flip-flops combined (by AND) to form $2k$ timing signals.
- The rule for forming AND gate inputs is straightforward:
 - For all zero pattern the inverted outputs of the first and last flip-flop are used.
 - For all one pattern the regular outputs of the extreme flip-flops are used.
 - For other patterns, the first two alternating bits, either 01 or 10 are used.

Lecture 11: Johnson Counter:

- The count sequence for the 4-bit tail-switch ring counter:

Sequence number	(flip-flop outputs)				AND gate required for output
	<i>A</i>	<i>B</i>	<i>C</i>	<i>E</i>	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

- So, in this example: we use $A'E'$ for 0000, AE for 1111, AB' for 1000, BC' for 1100. Similarly $A'B$ for 0111 and $B'C$ for 0011 and so on.
- When Johnson counter goes to an unused state, it goes from one invalid state to another. To avoid this, we may disconnect the output of B flip-flop from the input D of C flip-flop and instead feed C flip-flop with $D_C = (A + C)B$.

Lecture 11:

Knowledge Check

- **Question 1:** Minimum number of Flip-flops needed to implement a counter that counts up to 25 is:
 - a) 25, b) 5, c) 6, d) 8
- **Question 2:** How many FF's do we need if we use ring counter:
 - a) 5, b) 8, c) 25, d) 12
- **Question 3:** Compared to parallel adder, a Serial adder:
 - a) is faster, b) is slower, c) needs more gates, d) both a and c