

COEN 212:
DIGITAL SYSTEMS DESIGN I
Lecture 12: Memory and Programmable Logic
Devices

Instructor: Dr. Reza Soleymani, Office: EV-5.125,
Telephone: 848-2424 ext.: 4103.

Lecture 12:

Objectives of this lecture

- **In this lecture, we talk about:**
 - **Random Access Memory (RAM),**
 - **Read Only Memory (ROM),**
 - **Memory Decoding,**
 - **Programmable Logic Array (PLA),**
 - **Programmable Array Logic (PAL).**

- **Revisiting Error Detection and Correction.**


Lecture 12: Reading for this lecture

- **Digital Design by M. Morris R. Mano and Michael D. Ciletti, 6th Edition, Pearson, 2018:**
 - **Chapter 7**

Lecture 12:

Random Access Memory (RAM):

- Block Diagram of RAM:

 

- If a RAM has k address lines it can point to 2^k words.
- Example:
 - $2^{10} = 1024 \approx 1000$. So, 10 address lines \rightarrow 1 k words.
 - $2^{20} \approx 10^6$. So, 20 address lines \rightarrow 1 M words.
 - If the width is 8, each word is called a byte.
- A read command (say read input high) puts the content of the location specified by the k address bits on the output lines.
- Write command allows the n bits placed on the input lines be written in the location addressed by the k addresses bits.

Lecture 12:

Random Access Memory (RAM):

- Example: Entries of a 1024×16 RAM:

Address	Content
000000000	1011011010011100
000000001	1100100111100010
000000010	0011110101111010
⋮	⋮
111111101	1001110100001001
111111110	0101111100011101
111111111	1010110011101011

- To Write:
 - Apply the address of the location to the address lines.
 - Apply the data to be written to the input lines.
 - Activate the write input.
- To Read:
 - Apply the address to the address lines.
 - Activate the write input. Data will be available on the output lines.

Lecture 12:

Random Access Memory (RAM):

- RAM with Chip Enable:


Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write
1	1	Read

- There are two types of RAM:
 - Static RAM (SRAM): value of bits are the state Latches.
 - Dynamic Ram (DRAM): value of bits are the changes on capacitors.
- DRAM: More dense, less power.
- SRAM: faster (shorter read and write time). uses a single transistor per bit instead of several transistors in SRAM, it is more dense (has more storage capacity) and also consumes less power.


Lecture 12:

Internal Construction of RAM:

 - A RAM consists a 2^k rows of n memory cells.
- Each memory cell has: An input, An output, A select (enable) input and a read/write input
- The logic diagram of a memory cell is:




- The block diagram is:

 


Lecture 12: Address Decoding:

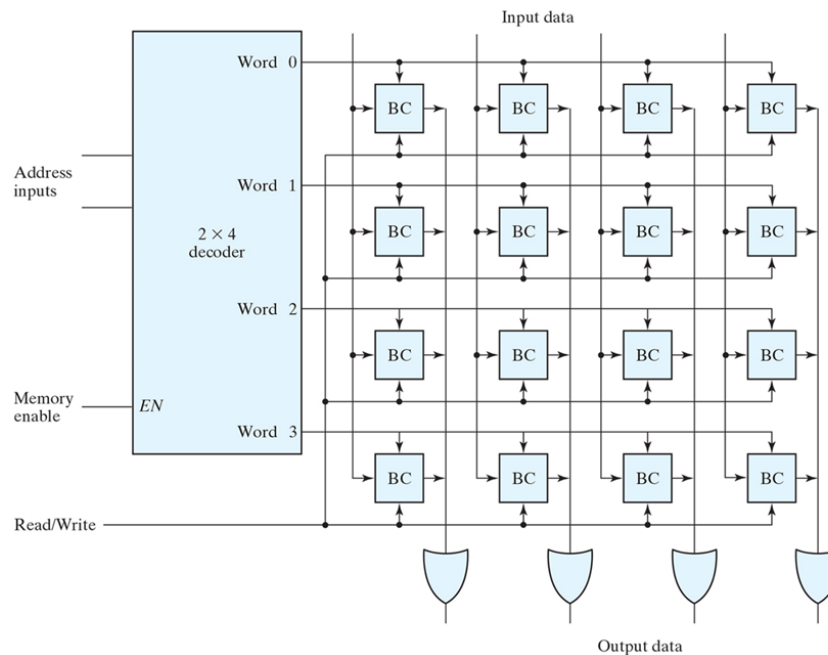
- To address 2^k memory locations (rows) we need a $k \times 2^k$ decoder.
- For example, a 4×4 RAM needs 2×4 decoder. Here, $k = 2$ and $2^k = 4$. Also, each word is 4 bits long.



To save space:
instead of:

 


we use:

 


Lecture 12: Read Only Memory (ROM):

 - The block diagram of $2^k \times n$ ROM is:



- Address Decoding for a 32×8 ROM

 

Lecture 12:


Logic Design using ROM:

- Using a $2^k \times n$ ROM: n functions each with k variables can be designed.

Truth Table:

Address	Content							
	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
00000	1	0	1	1	0	1	1	0
00001	0	0	0	1	1	1	0	1
00010	1	1	0	0	0	1	0	1
00011	1	0	1	1	0	0	1	0
⋮								
11100	0	0	0	0	1	0	0	1
11101	1	1	1	0	0	0	1	0
11110	0	1	0	0	1	0	1	0
11111	0	0	1	1	0	0	1	1

ROM Implementation:

 

Each OR output is function, e.g., $A_7(I_4, I_3, I_2, I_1, I_0) = \sum(0, 2, 3, \dots, 29)$


Lecture 12:

Logic Design using ROM:

- **Example:** Design a circuit that has a 3-bit input and its output is the square of its inputs.
- The truth table is:

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

Lecture 12: Logic Design using ROM:

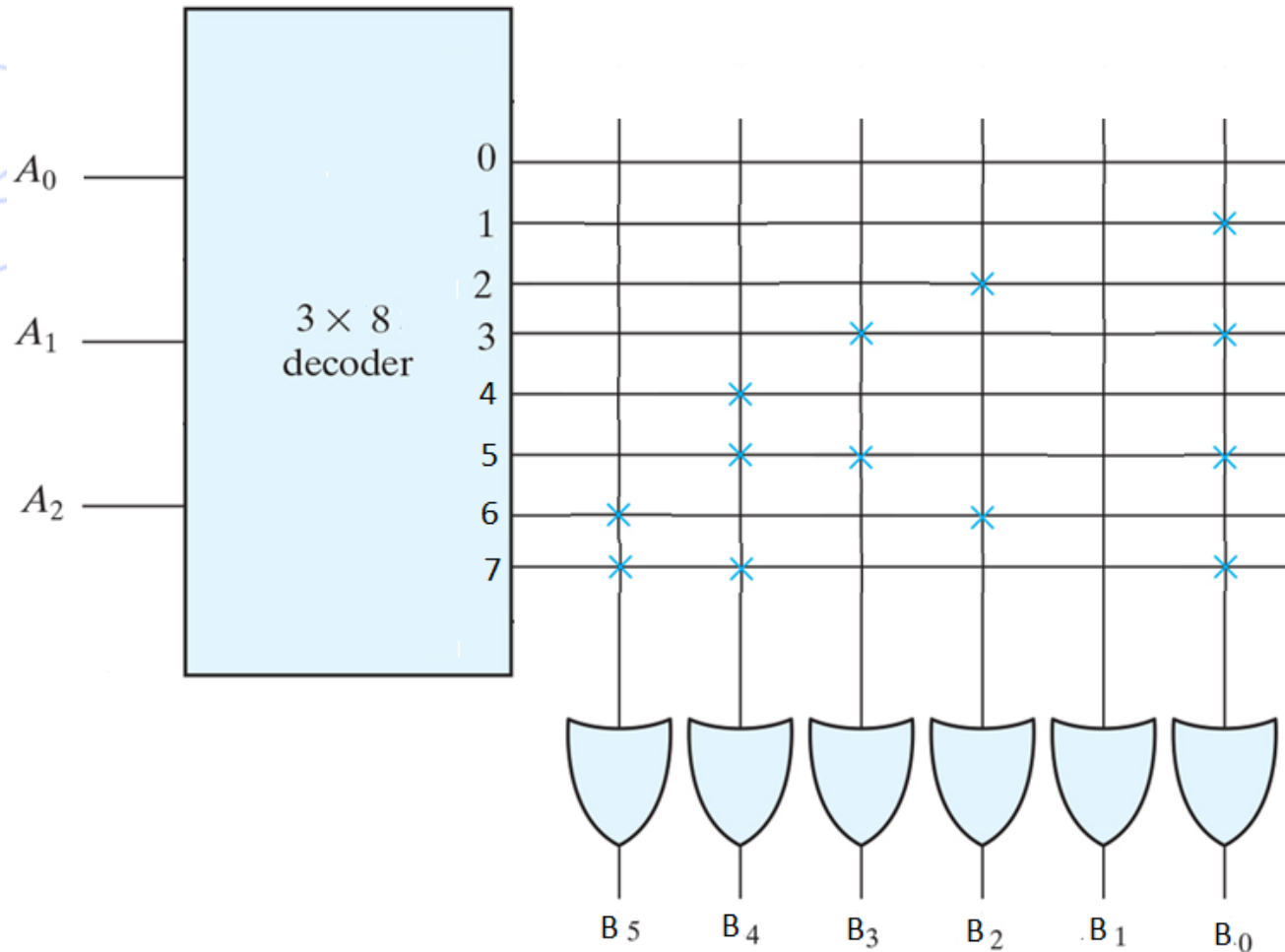

Lecture 12:

Different Types of ROM:


- **Different Types of ROM:**

- Mask Programmable ROM, or, simply ROM was programmed at the factory.
- PROM: Programmable ROM could be programmed by the user using a PROM programmer, using high voltage pulses. The process is irreversible, i.e., once the data is written it cannot be erased.
- EPROM: Erasable PROM. An EPROM can be erased using an ultraviolet source and programmed again.
- EEPROM (E²PROM): Electrically erasable PROM. This is similar to EPROM, but it can be erased using electric current.
- Flash memory: It is similar to EEPROM, but it has internal circuitry enabling to write and erase in specific locations without needing a special programmer.

Lecture 12:

Programmable Logic Devices (PLDs):

 
- There are three types of combinational PLDs:
 - PROM: in a PROM we have a set of fixed AND gates (forming the address decoder) and a set of programmable OR gates as we saw in previous examples.



- Programmable Logic Array (PLA): In a PLA both AND gates and OR gates are programmable.




- Programmable Array Logic (PAL): In a PAL the AND gates are programmable but the OR gates are fixed.

 

Lecture 12:

Programmable Logic Array (PLA):

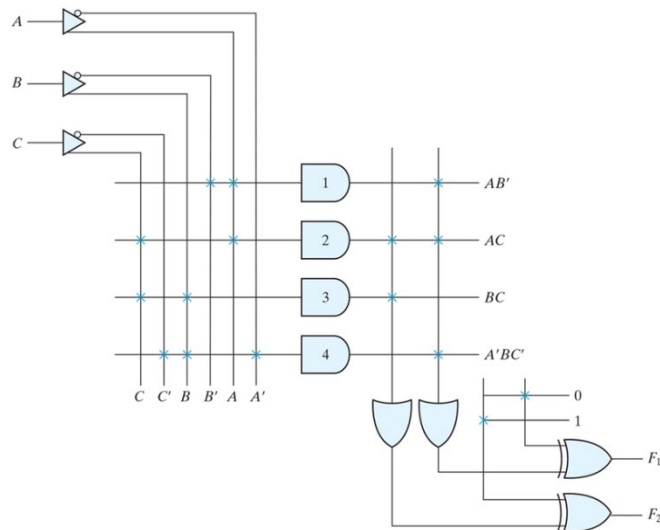- A PLA is similar to PROM. The difference is that in PLA all the minterms are not generate. Only the terms required for implementing a function are formed.
- Following diagram shows a PLA with 3 inputs and two outputs.



The connection here implement:

$$F_1 = AB' + AC + A'BC'$$

$$\text{and } F_2 = (AC + BC)$$

The Programming Table:

Product Term	Inputs			Outputs	
	A	B	C	(T) F ₁	(C) F ₂
AB'	1	0	–	1	–
AC	1	–	1	1	1
BC	–	1	1	–	1
A'BC'	0	1	0	1	–

Lecture 12: Programmable Logic Array (PLA):

- Example:** Design the following function using the PLA in the previous example:

$$F_1(A, B, C) = \sum (0,1,2,4) \quad \text{and} \quad F_2(A, B, C) = \sum (0,5,6,7)$$

Solution: $F_1 = (AB + AC + BC)'$ and $F_2 = AB + AC + A'B'C'$

		BC		B	
		00	01	11	10
A	0	m_0 1	m_1 1	m_3 0	m_2 1
	1	m_4 1	m_5 0	m_7 0	m_6 0

		BC		B	
		00	01	11	10
A	0	m_0 1	m_1 0	m_3 0	m_2 0
	1	m_4 0	m_5 1	m_7 1	m_6 1


The fuse map is:

Product term		Inputs			Outputs	
		A	B	C	(C)	(T)
					F_1	F_2
AB	1	1	1	-	1	1
AC	2	1	-	1	1	1
BC	3	-	1	1	1	-
$A'B'C'$	4	0	0	0	-	1

Lecture 12:

Programmable Array Logic (PAL):

- PAL is a programmable device with fixed OR gates and programmable AND gates.
- This PAL has 4 sections each with 3 programmable AND gates connected to a fixed OR gate. So, each function implemented can have at most 3 terms. If a function has more than 3 terms, we may implement it using two sections.

 

Lecture 12:

Programmable Array Logic (PAL):

- Example: implement functions:

$$w(A, B, C, D) = \sum(2, 12, 13), \quad x(A, B, C, D) = \sum(7, 8, 9, 10, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15) \text{ and } z(A, B, C, D) = \sum(1, 2, 8, 12, 13).$$

- Using K-map we find:

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$\text{and } z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

Lecture 12: Programmable Array Logic (PAL):


- z has more than 3 terms but since $ABC' + A'B'CD' = w$, we have:

$$z = w + AC'D' + A'B'C'D$$

- Using w as one of the AND inputs we have:

Product Term	AND Inputs					Outputs
	A	B	C	D	w	
1	1	1	0	–	–	$w = ABC' + A'B'CD'$
2	0	0	1	0	–	
3	–	–	–	–	–	$x = A + BCD$
4	1	–	–	–	–	
5	–	1	1	1	–	
6	–	–	–	–	–	$y = A'B + CD + B'D'$
7	0	1	–	–	–	
8	–	–	1	1	–	
9	–	0	–	0	–	$z = w + AC'D' + A'B'C'D$
10	–	–	–	–	1	
11	1	–	0	0	–	
12	0	0	0	1	–	

Lecture 12: Programmable Array Logic (PAL):

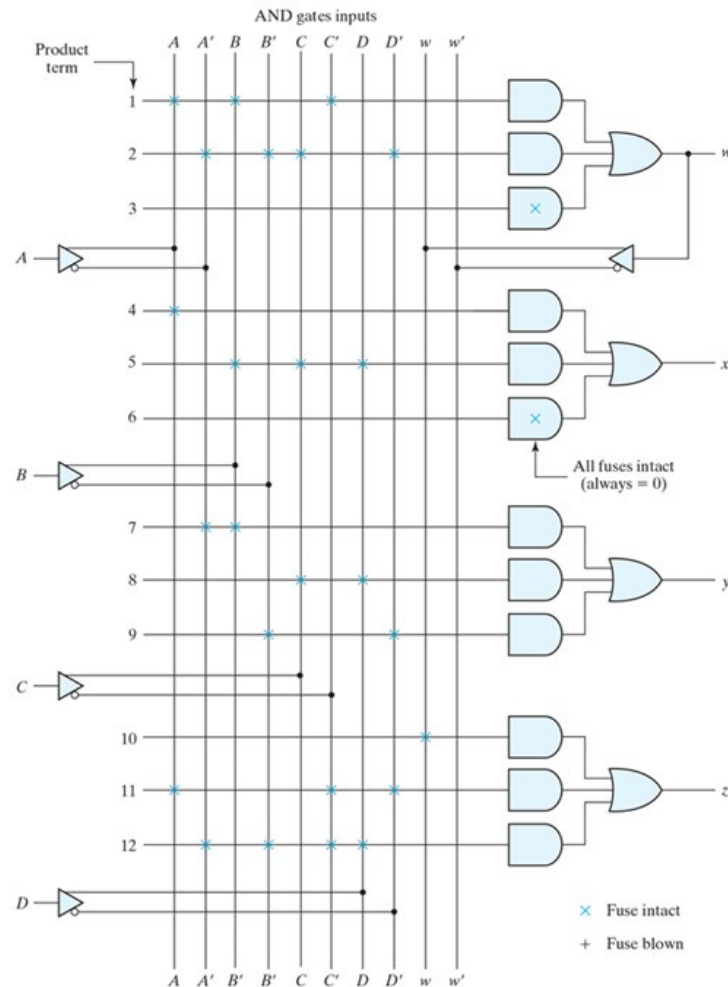

Lecture 12: Knowledge Check

- **Question 1:** Assume you implement three functions each with 6 inputs using ROM. What should be the size of the ROM
 - a) 1 k bytes, b) 1 kbits, c) 256 bits, d) 192 bits
- **Question 2:** In a PLA programmable gates are:
 - a) AND, b) OR, c) both, d) buffer/inverter.