
COEN 212:
DIGITAL SYSTEMS DESIGN I
Lecture 5.2: Hardware Description Language (HDL)

Instructor: Dr. Reza Soleymani, Office: EV-5.125,
Telephone: 848-2424 ext.: 4103.

Lecture 5.2: Objectives of this lecture

- **In this lecture, we see:**
 - **Basic Definitions.**
 - **Design Steps.**
 - **Simulation.**
 - **Timing.**

Lecture 5.2: Reading for this lecture

- **Digital Design by M. Morris R. Mano and Michael D. Ciletti, 6th Edition, Pearson, 2018:**
 - **Section 3.9**

Lecture 5.2: Hardware Description Language (HDL)

- HDL software is the tool for designing digital circuits.
- Developing a digital circuit using HDL consists of the following steps:
 - Design entry: creating an HDL based definition of the functionality of the circuit
 - Logic Simulation: verifying the functionality of the logic using a computer
 - Logic synthesis: deriving the list of physical components need to implement the circuit and their interconnection (a net list)
 - Timing Verification: to make sure that the fabricated circuit operates at the specified speed. In this stage, we need to take into consideration the gate delays.

Lecture 5.2: HDL: Module Definition

- Primitives: module, input, output, wire, and, or, not

// Description of the 3 gate circuit

module my_circuit (A, B, C, D, E);

output D, E;

input A, B, C;


wire w₁;

and G₁(w₁, A, B);

not G₂(E, C);

or G₃(D, w₁, E);

end module

 

Lecture 5.2:

HDL: Gate delays

- To simulate our circuit, we need to specify gate delays.
- Assume: propagation delays for G_1 , G_2 , and G_3 are 30 ns, 10 ns, and 20 ns, respectively.

```
// Verilog model with propagation delay
module my_circuit_prop_delay (A, B, C, D, E);
  output D, E;
  input A, B, C;
  wire w1;
  and #(30)G1(w1, A, B);
  not #(10)G2(E, C);
  or #(20)G3(D, w1, E);
end module
```

Lecture 5.2:


HDL: Simulation

- To simulate our circuit, we need to write a **testbench**.

```
// Test bench for my-circuit
Module t_my_circuit_prop_delay;
wire D, E;
reg A, B, C;
my_circuit_prop_delay M1(A, B, C, D, E);
initial
begin
A = 1'b0; B = 1'b0; C = 1'b0;
#100 A = 1'b1; B = 1'b1; C = 1'b1;
end
initial #200 $ finish;
end module
```

Lecture 5.2: HDL: Simulation

- The result of the simulation will be:

 

- Note that *D* is not defined for the first 20 ns, and *E* for the first 10 ns.


Lecture 5.2:

Boolean expressions in HDL

- Boolean expressions are defined using
 - & for AND
 - | for OR
 - ~ for NOT

using the keyword **assign**.

Example: For

 

The expression is:

assign $D = (A \& B) | \sim C$

Lecture 5.2:

Boolean expressions in HDL

- **Example:** write an HDL program implementing

$$E = A + BC + B'D$$

$$F = B'C + BC'D'$$

// Verilog model: My Boolean Circuit

module my_Boolean_Circuit (*E, F, A, B, C, D*);

output *E, F*;

input *A, B, C, D*;

assign $E = A|(B\&C)|(\sim B\&D)$;

assign $F = (\sim B\&C)|(B\&\sim C\&\sim D)$;

end module

Lecture 5.2: User-Defined Primitives

- **User-Defined Primitives (UDP):**
- Some basic logic operations, e.g., AND, OR, NOT are included in the language. We can add other primitives (UDP) using a table. These user-defined primitives can be later instantiated when designing more complex circuits.
- **Example:** Introduce a UDP implementing
- $X(A, B, C) = \sum(0, 2, 4, 6, 7)$

Lecture 5.2: User-Defined Primitives

```
// User Defined Primitive (UDP) example
primitive crctp (X,A,B,C);
output X;
input A,B,C;
// Truth Table for  $X(A,B,C)=\sum(0,2,4,6,7)$ 
Table
//A  B  C  :  X
0  0  0  :  1;
0  0  1  :  0;
0  1  0  :  1;
0  1  1  :  0;
1  0  0  :  1;
1  0  1  :  0;
1  1  0  :  1;
1  1  1  :  1;
end tabel
end primitive
```

Lecture 5.2: User-Defined Primitives

- The newly introduced primitive can then be instantiated using the following lines of code:
- `// Instantiate primitive`
- `module declare_crctp;`
- `reg x, y, z;`
- `wire w;`
- `crctp (w, x, y, z);`
- `end module`