

COEN 212:
DIGITAL SYSTEMS DESIGN I
Lecture 8: Common Combinational Logic Circuits
Decoders, Encoders, Multiplexers

Instructor: Dr. Reza Soleymani, Office: EV-5.125,
Telephone: 848-2424 ext.: 4103.

Lecture 8:

Objectives of this lecture


- In this lecture, we talk about:
 - Decoders.
 - Encoders.
 - Multiplexers.

Lecture 8: Reading for this lecture

- **Digital Design by M. Morris R. Mano and Michael D. Ciletti, 6th Edition, Pearson, 2018:**
 - **Chapter 4 (4.9 to 4.11)**


Lecture 8: Decoders:

- A 2-bit (2x4) Decoder:

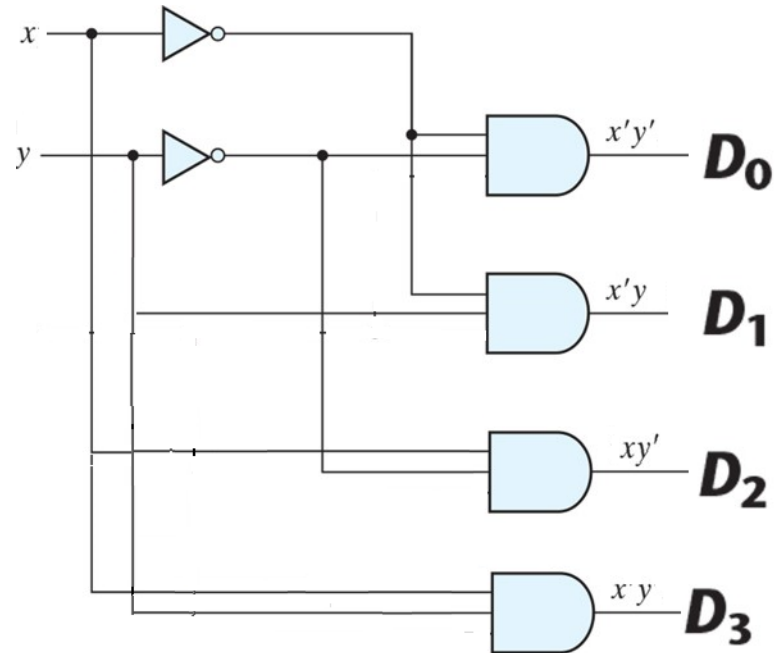

Lecture 8: Decoders, Encoders, Multiplexers:

- A 2-bit Decoder with ENABLE input:

 


Lecture 8: Decoders, Encoders, Multiplexers:

- Truth Table of Decoder:

E	x	y	D_0	D_1	D_2	D_3
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


- x and y cause the enable to appear on pins D_0, D_1, D_2, D_3 . This is what is termed a **demultiplexer**.

 

Lecture 8:

Decoders, Encoders, Multiplexers:

- **Expanding the decoders:** An n -bit decoder with can be implemented using two $n - 1$ -bit decoders.
- **Example:** Use two 2-input decoders to implement a 3-input decoder.

 

Lecture 8:


Combinational logic implementation using decoders:

- **Combination logic implementation using decoders:**
 - Outputs of a decoder represent the minterms of the input.
 - ORing these outputs we can implement any function.
- **Example:** Design a Full Adder.

x	y	z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \sum(1, 2, 4, 7)$$

$$C = \sum(3, 5, 6, 7)$$

 

Lecture 8: Encoders:

- **Truth Table for an Octal Encoder:**

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- **Implementation:**

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Lecture 8: Encoders:

- Everything is fine as long as one and only one input is high.
 - When the output is 000: is D_1 zero or one?
 - When the output is 011: is D_3 high or both D_3 and D_1 ?
 - Press 3 and 6 Simultaneously. Then $D_3 = D_6 = 1$ and $z = y = x = 1$.
But, 111 represents D_7 !
- Solution: Including extra logic
 - indicating whether any of the inputs is on or not.
 - A priority logic selecting one of the inputs when more than one input is high.

Lecture 8:

Encoder with priority Logic

- Example: a 4-input encoder:

D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

- Extra output $V = D_0 + D_1 + D_2 + D_3$.
- $V = 0$: no input. $V = 1$: input shown by (x, y) .
- When two inputs are high, the one with larger index is selected.

Lecture 8: Encoder with priority Logic

- K-map for x :


		D_2D_3		D_2		
		00	01	11	10	
D_0D_1	00	m_0 X	m_1 1	m_3 1	m_2 1	} D_1
	01	m_4	m_5 1	m_7 1	m_6 1	
11	m_{12}	m_{13} 1	m_{15} 1	m_{14} 1		
10	m_8	m_9 1	m_{11} 1	m_{10} X		
		D_3				

- K-map for y :

		D_2D_3		D_2		
		00	01	11	10	
D_0D_1	00	m_0 X	m_1 1	m_3 1	m_2	} D_1
	01	m_4 1	m_5 1	m_7 1	m_6	
11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14}		
10	m_8	m_9 1	m_{11} 1	m_{10}		
		D_3				


- So: $x = D_2 + D_3$ and $y = D_3 + D_1D_2'$.

- Implementation:

 


Lecture 8: Multiplexers

- **Example: 2-bit MUX**

 


- **Implementation:**

 

Lecture 8: Multiplexers

- **Example: 4-bit MUX**
- **Need $\log_2^4 = 2$ select inputs:**
- **Implementation:**

 


Lecture 8:

Boolean Function Design using MUX

- A Boolean function with n variables can be implemented using a multiplexer with 2^{n-1} inputs.
- It has $n - 1$ select lines.
- Connect the first $n - 1$ variables to the $n - 1$ select inputs.
- The remaining variables, say z , will be used for data inputs. Depending on the function, the inputs will receive $z, z', 1$, or 0 .
- Example: $F(x, y, z) = \sum(1,2,6,7)$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Truth Table

 

Implementation

Lecture 8:


Boolean Function Design using MUX

- Example: Design ($F(A, B, C, D) = \sum(1,3,4,11,12,13,14,15)$)
- $n = 4$ so $2^{n-1} = 2^{4-1} = 8$. We need an 8-to-1 MUX.

- Truth Table:


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Implementation

 

Lecture 8: Knowledge Check

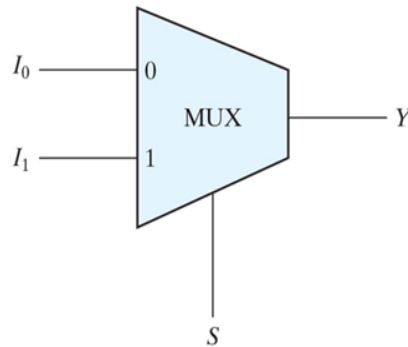- **Question 1:** In the circuit shown let $I_0 = 1$, $I_1 = 0$, and $S = 1$:



- The output will be?
 - a) 0, b) 1,
-
- **Question 2:** To design a function with inputs A, B, C, D, E, F, we need a multiplexer with:
 - a) 5 inputs, b) 8 inputs, c) 16 inputs, d) 4 inputs