

COEN 212:
DIGITAL SYSTEMS DESIGN I
Lecture 9: Sequential Circuits
Latches and Flip-flops

Instructor: Dr. Reza Soleymani, Office: EV-5.125,
Telephone: 848-2424 ext.: 4103.

Lecture 9: Objectives of this lecture


- In this lecture, we talk about:
 - Sequential Circuits.
 - Latches.
 - Flip-flops.

Lecture 9: Reading for this lecture


- **Digital Design by M. Morris R. Mano and Michael D. Ciletti, 6th Edition, Pearson, 2018:**
 - Chapter 5 (5.1 to 5.4)

Lecture 9: Sequential Circuits:

- A typical Sequential Circuit:

 

- Example:

 

- State Table:

Present state F^{n-1}	Next state		Output (F^n)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0	0	1	0	1
1	1	0	1	0

Lecture 9: Sequential Circuits:


- There are two types of sequential circuits:
 - The synchronous circuits,
 - The asynchronous circuits.
- In the synchronous circuits:
 - state and also outputs change at discrete times dictated by a clock.
- In an asynchronous sequential circuit:
 - the output of each gate is defined based on its input and gates delay. So, the state and outputs can change at any time.
 - The problem with asynchronous circuits is the possibility of encountering instability due to feedback.
- In this course, we mainly consider Synchronous Sequential Circuits.

Lecture 9:


Latches: SR-Latch

- SR Latch:
 - Has S (Set) and R (Reset) inputs and Q and Q' outputs.
 - Implemented using 2 NORs or 2 NANDs.

Symbol:

 

Implementation:

 

- Relationship between S, R, Q and Q' .

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(after $S = 1, R = 0$)

(after $S = 0, R = 1$)


(forbidden state)

Lecture 9:

Latches: SR-Latch with NAND

- SR latch implementation using NAND gates:

- Implementation:

 

Operation:


S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(after $S = 1, R = 0$)

(after $S = 0, R = 1$)

forbidden inputs (00)


 
- A Control or Enable input can be added.



C	S	R	Next state
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0, Q' = 1$ (reset state)
1	1	0	$Q = 1, Q' = 0$ (set state)
1	1	1	Indeterminate

Lecture 9: Latches: D-Latch

  - D-Latch: avoids indeterminate state by making $R = S'$



C	D	Next state
0	X	No change
1	0	$Q = 0, Q' = 1$ (reset)
1	1	$Q = 1, Q' = 0$ (set)

Lecture 9: Flip-flops

- Output of a Latches depends on the input level.
- Input levels fluctuation may cause erroneous operation.
- Flip-flops are edge triggered. So only change with the clock.
- Some Flip-flops respond to the Rising Edge of clock:




- while others change their state at the Falling Edge:




Lecture 9: Flip-flops

- There are two ways to implement edge-triggered flip-flops:
 - isolate the input from the output. The output change only after control (clock) signal has been removed.
 - make a flip-flop that only changes when level of its clock goes from 0 to 1 or from 1 to 0 and remains unchanged rest of the time.
- **Implementing edge-triggered D flip-flop:**

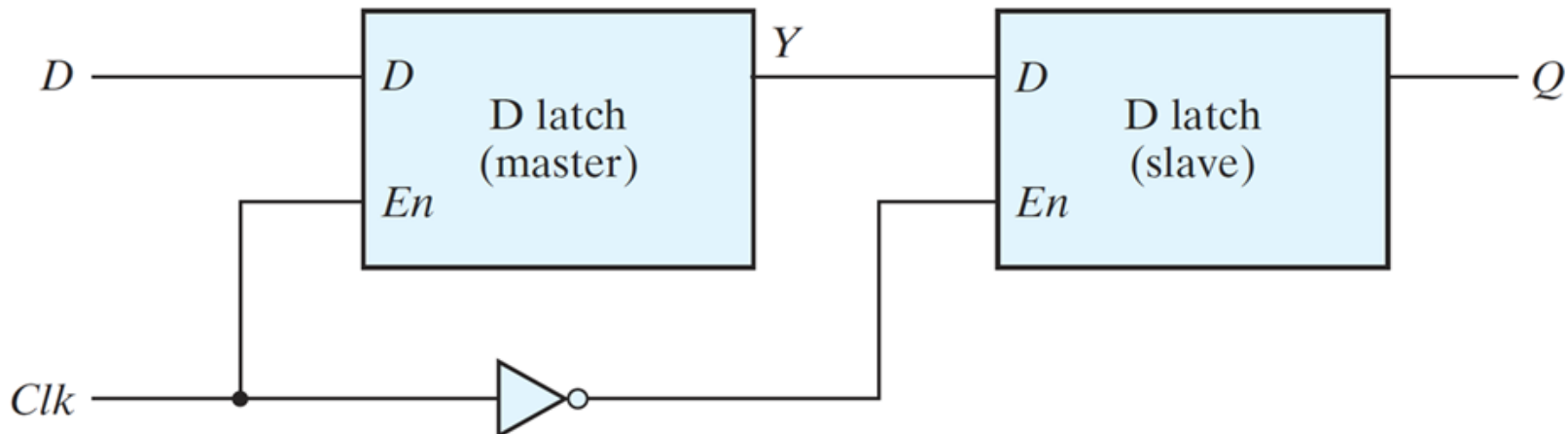

Lecture 9: D-Flip-flop

 
- Implementing D flip-flop using SR-Latch:




- as long as $\text{clk}=0$, $S = 1$ and $R = 1$ and output is unchanged.
- When clk goes to 1:
 - if $D = 0$ makes $R = 0$ and $Q' = 1$ and $Q = 0$,
 - if $D = 1$ the output of the lower most NAND will be 0 and $S = 0$.
 $Q = 1$, $Q' = 0$.
 - Any further change in D while $\text{clk}=1$ will have no effect on the output.

Lecture 9: D-Flip-flop

 - A rising (positive) edge triggered D-flip-flop is represented by the symbol:




- A falling (negative) edge triggered D-flip-flop is represented by the symbol:

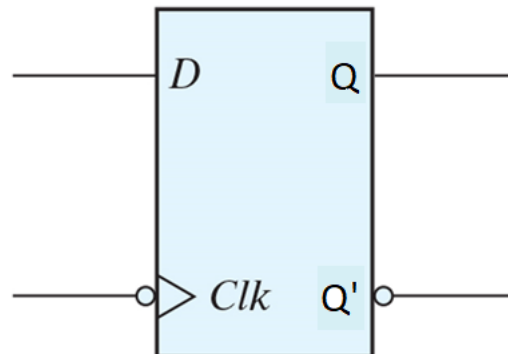

Lecture 9: JK-Flip-flop

- Truth Table for D
- as a function of J, K and Q:
- The K-map for D


J	K	Q	D
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 


$$D = JQ' + K'Q$$

Lecture 9: JK-Flip-flop

- The Circuit Diagram for the J-K FF is:

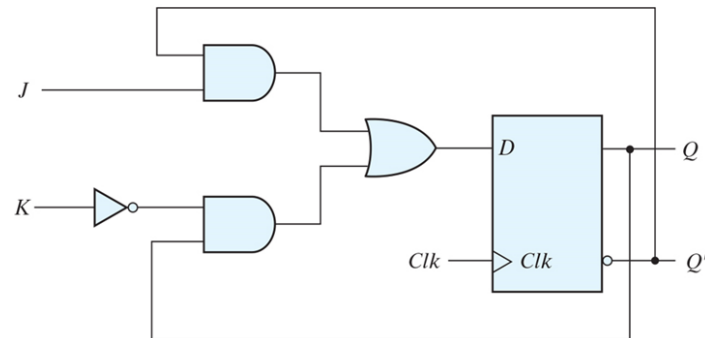


- and the symbol is:

 

Lecture 9: T-Flip-flop

- The Symbol for the T Flip-flop is:

 

- The T-FF changes its state (toggles) when $T = 1$:


T	Q	D	
0	0	0	no change
0	1	1	no change
1	0	1	toggle
1	1	0	toggle

Lecture 9: T-Flip-flop


- For implementation using D-FF, we have:

$$D = T \oplus Q.$$

- and the circuit diagram is:

 

- T-FF could also be implemented using JK-FF

 

Lecture 9:

Characteristic tables and equations:

- Characteristic tables (or equations) describe the operation of sequential circuits:
- For a JK flip-flop the characteristic table is:

J	K	$Q(t+1)$	
0	0	$Q(t)$	no change
0	1	0	reset
1	0	1	set
1	1	$Q'(t)$	invert

- And the Characteristic Function is:

$$Q(t+1) = JQ'(t) + K'Q(t)$$

where $Q(t)$ and $Q(t+1)$ are the state of the flip-flop, before and after the application of the clock signal.

Lecture 9:

Characteristic tables and equations:

- For D Flip-flop, we have:

D	$Q(t + 1)$
0	0
1	1

- So, the characteristic equation is:

$$Q(t + 1) = D$$

- For a T flip-flop the characteristic table is:


T	$Q(t + 1)$	
0	$Q(t)$	no change
1	$Q'(t)$	toggle (invert)

- And the Characteristic Function is:


$$Q(t + 1) = T \oplus Q(t) = T'Q(t) + TQ'(t)$$

Lecture 9: Flip-Flop with Direct Inputs:

- A flip-flop with a reset state:

 

- The symbol for D-FF with reset:

 

Lecture 9: Knowledge Check

- **Question 1:** In a JK FF $Q=1$, the input $J=1$, $K=1$ results in:
a) $Q=1$, b) $Q=0$, c) $Q'=0$, d) undefined state

- **Question 1:** In a T FF $Q=1$, applying a four bit stream 1010 results in:
a) $Q=1$, b) $Q=0$, c) $Q'=0$, d) $Q=10$