

Question 1--- Use Boolean algebra for Question 1.

1.a Simplify to obtain minimum SOP

(2 marks)


$$F(W,X,Y,Z) = [(X+Y') \oplus W] [(XY \ominus (W+Y))]$$

1.b Simplify to obtain minimum SOP

(3 marks)

$$F(a,b,c,d) = a'b'(c+d')(c'+d) + ab(c'd+cd') + (a'b+1)cd$$

1.c Minimize the following circuit, draw final minimized circuit with minimum number of packages. You have single rails available to you. (3 marks)

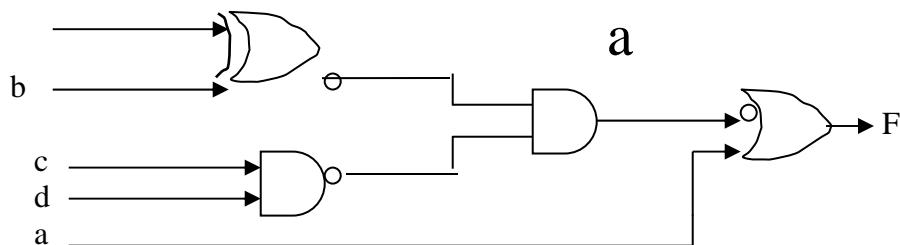**Question 2---**2.a Give **minimal SOP** for $F(a,b,c,d)$ given by the following K-map (3 marks)


Identify the Prime Implicants clearly. Which ones are essential? (1 mark)

2.b Give minimal POS for $F(a,b,c,d)$. (2 marks)

a\ b cd	00	01	11	10
00	1	X	X	X
01		1	1	
11	1			1
10	X	X	X	X

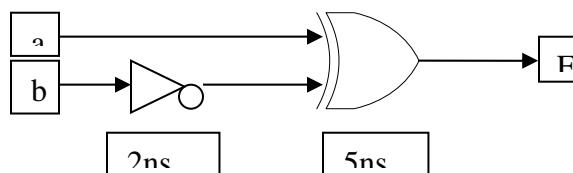2.c Give the **POS** of $F(A,B,C,D) = (A+B+CD)(B+CD)$ (2 marks)2.d Give the **minterm list** of $F(A,B,C,D) = AB$ (1 marks)2.e Give the **NOR-NOR** implementation of $F(A,B,C,D) = ABC+CD+CB$ (3 marks)**Question 3**Draw the **timing diagram** for $F(a,b) = b' \oplus a$ for the following consecutive inputs:

ab= 00, 10, 01, 11 (**follow these vectors in order given. Start from AB=00 **). Assume the following gate delays, INV.= 2ns , XOR gate = 5ns (5 marks)



SOLUTION Midterm exam, Feb.15th, 2006

Question 1


a)

$$\begin{aligned}
 F(w, x, y, z) &= [(x + \bar{y}) \oplus w] * [(xy) \square (w + x)] = [\overline{(x + y)}w + \bar{w}(x + \bar{y})] * [xy(w + y) + \bar{x}\bar{y}(w + y)] = \\
 &= [\bar{y}w + \bar{w}x + \bar{w}y] * [\cancel{wx\bar{y}} + xy + (\bar{x} + \bar{y})\bar{w}y] = [\bar{y}w + \bar{w}x + \bar{w}y] * [xy + \cancel{\bar{x}w\bar{y}} + \bar{w}y] = \\
 &= \underbrace{\bar{y}wxy}_0 + \underbrace{\bar{y}yw\bar{w}y}_0 + \underbrace{\bar{w}xxy}_{\bar{w}xy} + \underbrace{\bar{w}x\bar{w}y}_{\bar{w}\bar{w}y} + \underbrace{\bar{w}yxy}_0 + \underbrace{\bar{w}yw\bar{y}}_{\bar{w}y} = \bar{w}x(y + \bar{y}) + \bar{w}y = \bar{w}x + \bar{w}y
 \end{aligned}$$


b)

$$\begin{aligned}
 F(a, b, c, d) &= \bar{a}\bar{b}(c + \bar{d})(\bar{c} + d) + ab(\bar{c}d + c\bar{d}) + (\bar{a}b + 1)cd = \\
 &= (\bar{a}\bar{b}c + \bar{a}\bar{b}d)(\bar{c} + d) + ab\bar{c}d + abc\bar{d} + cd = \\
 &= \underbrace{\bar{a}\bar{b}cc}_0 + \cancel{\bar{a}\bar{b}cd} + \bar{a}\bar{b}cd + \underbrace{\bar{a}\bar{b}dd}_0 + ab\bar{c}d + abc\bar{d} + cd = \\
 &= \bar{a}\bar{b}cd + ab\bar{c}d + abc\bar{d} + cd = \bar{a}\bar{b}\bar{c}\bar{d} + ab\bar{c}d + c(ab\cancel{d} + d) = \\
 &= \bar{a}\bar{b}\bar{c}\bar{d} + ab\bar{c}d + abc + cd = \bar{a}\bar{b}\bar{c}\bar{d} + ab(\cancel{c}d + c) + cd = \\
 &= \bar{a}\bar{b}\bar{c}\bar{d} + abd + abc + cd
 \end{aligned}$$

c)

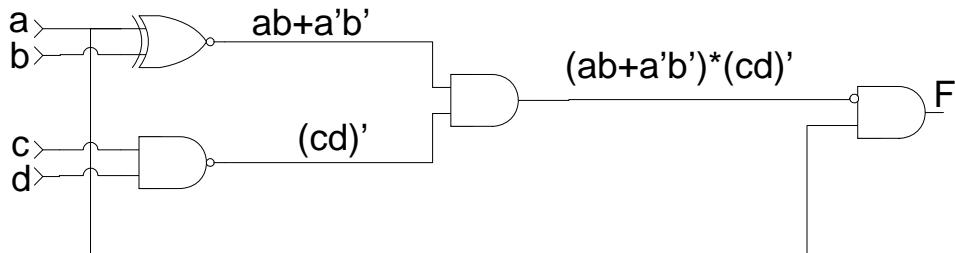


$$F = \overline{(\bar{a}b + \bar{a}\bar{b})\bar{c}\bar{d}} + a = (\bar{a}b + a\bar{b}) + \bar{c}\bar{d} + a = \bar{a}b + \cancel{a}\bar{b} + cd + a = \bar{a}b + cd + a = a + b + cd$$

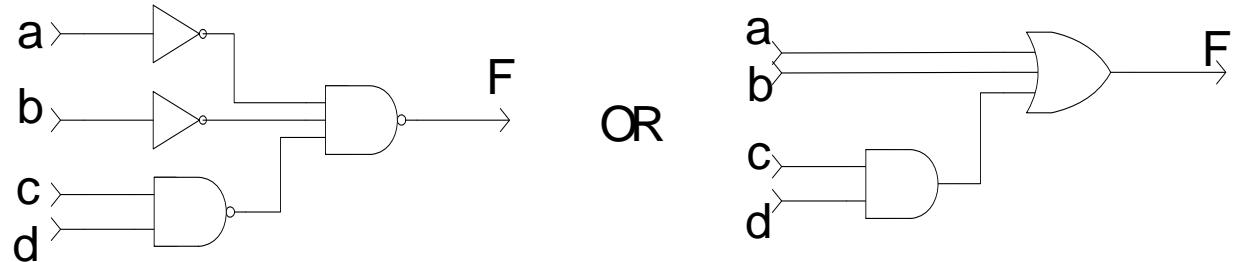

Question 2

a)

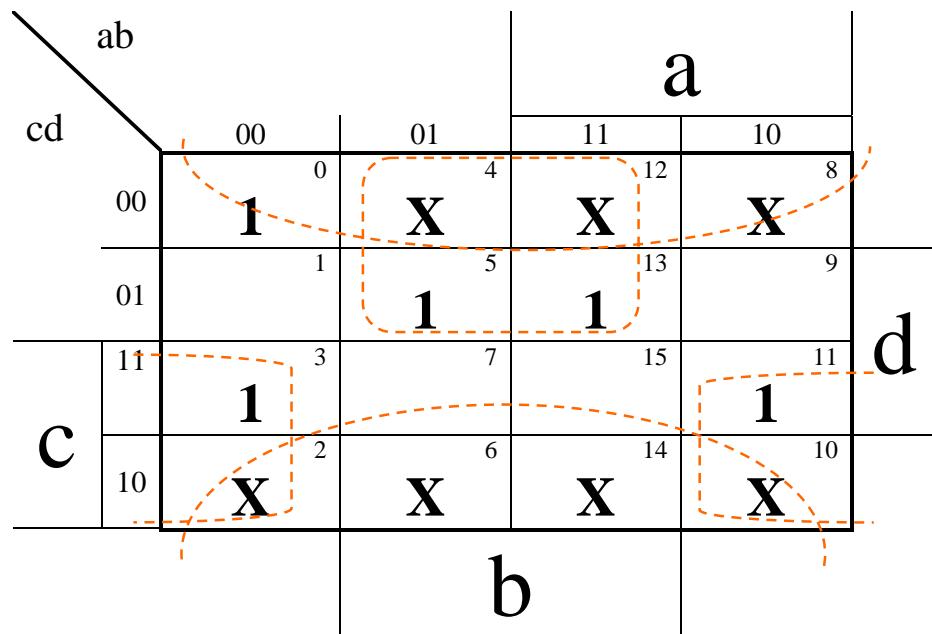

$$PI_1 = \bar{d} = \sum(0, 2, 4, 6, 8, 10, 12, 14)$$


$$PI_2 = b\bar{c} = \sum(4, 5, 12, 13)$$

$$PI_3 = \bar{b}c = \sum(2, 3, 10, 11)$$

All three PI are essential.

$$F = \bar{d} + b\bar{c} + \bar{b}c$$

b)

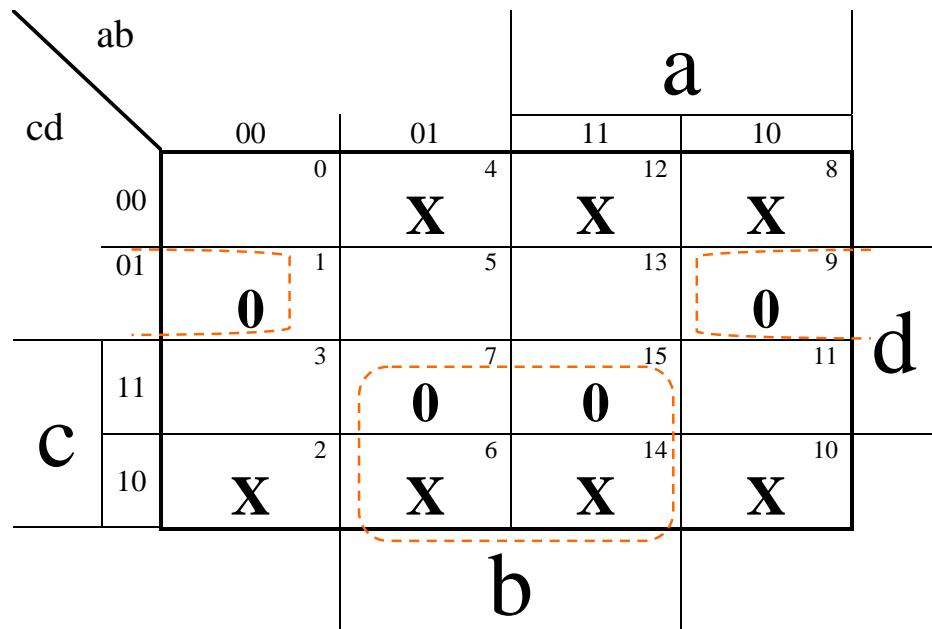

$$F = (b + c + \bar{d})(\bar{b} + \bar{c})$$

c) Applying distributive law:


$$F(A,B,C,D) = (A+BCD)(B+CD) = (A+B)(A+C)(A+D)(B+C)(B+D)$$

d) minterms of $F(A,B,C,D) = AB$:


		AB		A			
		00	01	11	10		
CD		00	0	4	12	8	
C	00	1	5	13	9		
	01	3	7	15	11		
B	11	2	6	14	10		
	10						

$F = \sum(12, 13, 14, 15)$


e) NOR-NOR of $F(A,B,C,D) = ABC + CD + CB = C(AB + D + B) = C(B + D) = \overline{\overline{C}} + \overline{\overline{(B + D)}}$

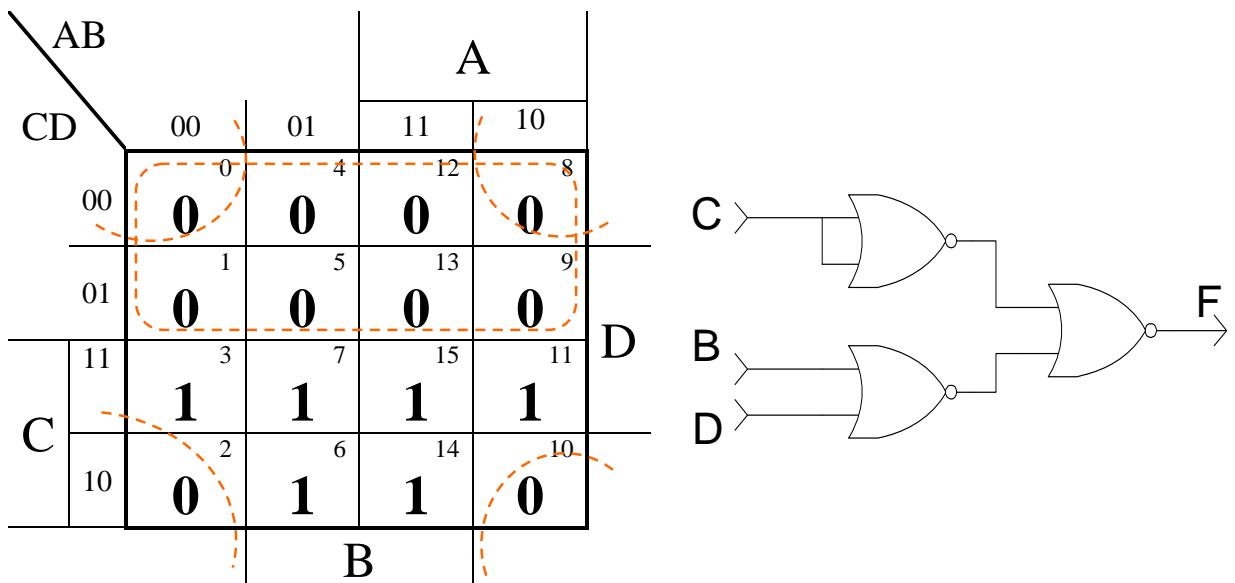

Question 3

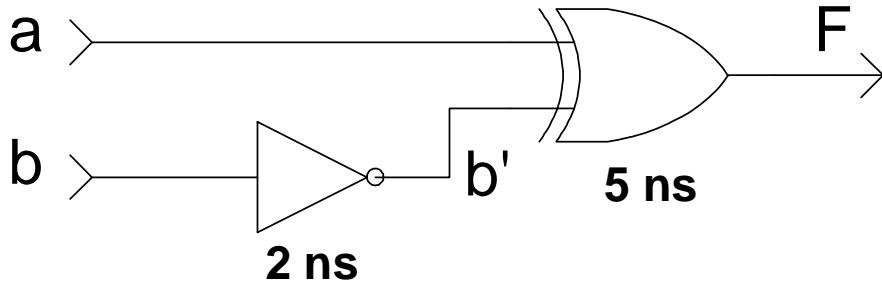

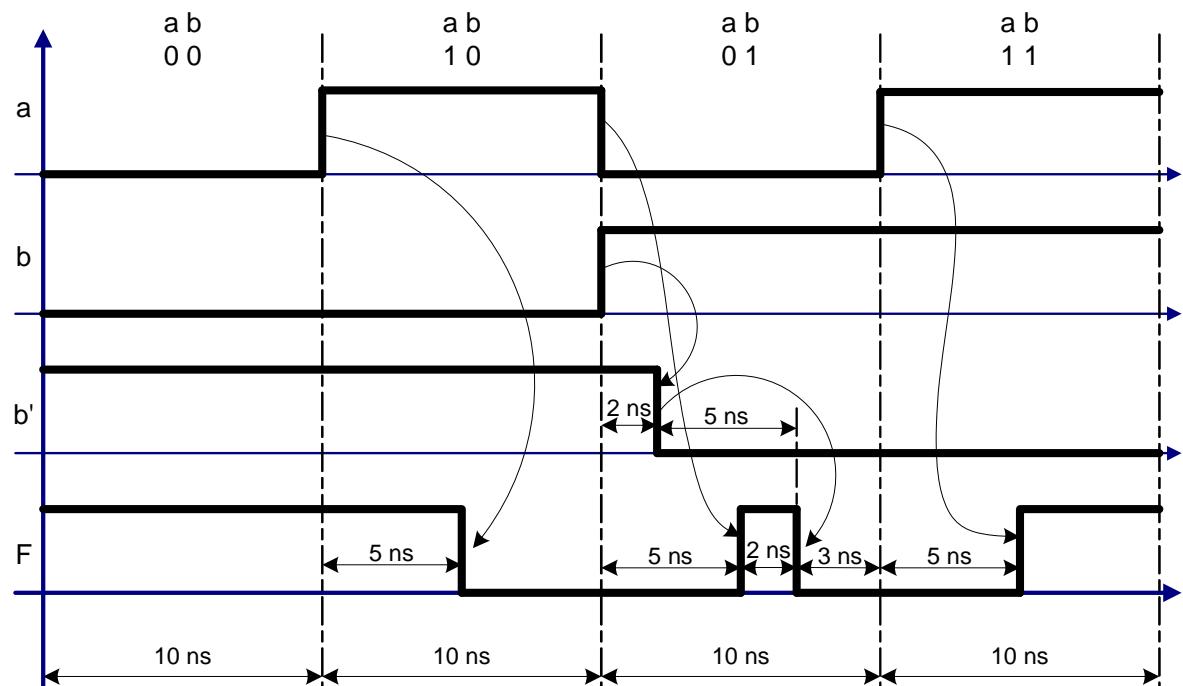Total delay is 7 ns => take period of 10 ns.



Edges that cause change in the output are shown with an arrow after delay of going through the gate.