

**Question 1****(Use Boolean Algebra for Question 1)**1.a Prove De Morgan's Theorem  $(AB)' = A' + B'$     (4 marks)

1.b Simplify to obtain minimum SOP    (2 marks)

$$F(A, B, C, D) = A'B' + AC'(C'+A') + BC' + AB'C + ABC + BC'D$$

1.c Simplify    (2 marks)

$$F(A, B, C, D) = A'B'(0 + C')' + A + (1 + D') + D$$

**Question 2**1) Give **minimal POS** for  $F(a,b,c,d)$  given by the following K-map. (1 Mark)a) Identify the **Prime Implicants clearly**.    (1 mark)b) Identify the **Essential Prime Implicants**.    (1 mark)c) Give the minimum **AND-OR-NOT** implementation.    (2 marks).

		ab			
	cd	00	01	11	10
00		X	X	X	X
01		1	1	X	
11		1			
10		X	1	1	X

**Question 3**3a) Give **minimal NOR-NOR** and **NAND NAND** implementation for  $F(a,b,c,d)$  given by the following K-map (2 marks).

		ab			
	cd	00	01	11	10
00			X	X	
01			1	X	
11		X			
10		X	1	1	X

3b) Using F given in K-map below determine minimum F1. (4 marks)

ab \ cd	00	01	11	10
00	X	X	X	X
01	1	1	X	
11	1	1	1	
10	X	1	1	X


F1

ab \ cd	00	01	11	10
00		X	X	X
01	1	1	X	1
11		1	1	
10	X	1	1	X

F

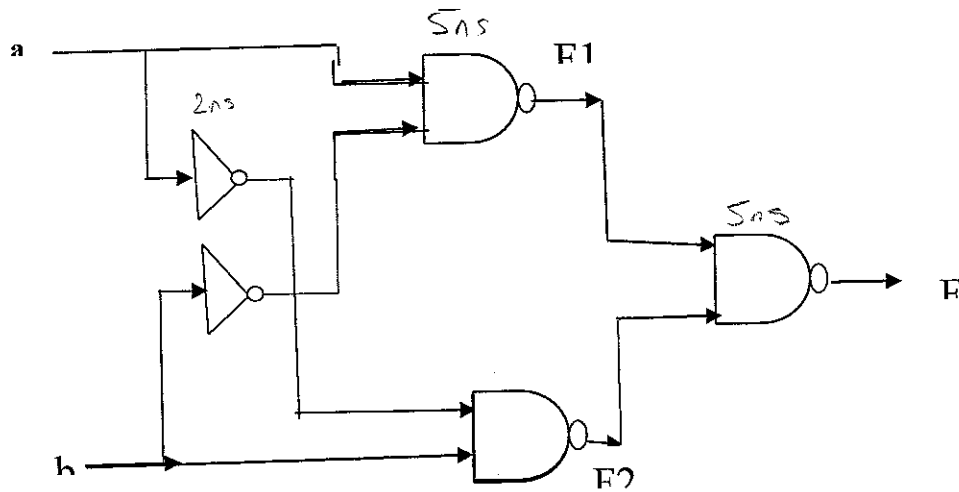**Question 4**

In the circuit below:  
 Delay of inverter = 2ns  
 Delay of NAND = 5ns  
 For change of input vector a b = 00 to 01 to 10,  
 draw timing diagram for the circuit. (6 marks)



Q1

Q1.a Prove  $\overline{AB} = \overline{A} + \overline{B}$

Since  $X \cdot \overline{X} = 0$  then  $(A \cdot B)(\overline{A} + \overline{B}) = A\overline{A}B + AB\overline{B}$   
 $= 0 \cdot B + A \cdot 0$   
 $= 0 + 0 = 0$

Q1.b

$$F(A, B, C, D) = \overline{A}\overline{B} + \underbrace{A\overline{C}(\overline{C} + \overline{A})}_{A\overline{C}} + \underbrace{B\overline{C} + A\overline{B}C + ABC + B\overline{C}D}_{B\overline{C}}$$

$$= \overline{A}\overline{B} + A\overline{C} + B\overline{C} + \underbrace{A\overline{B}C + ABC}_{AC}$$

$$= \overline{A}\overline{B} + A + B\overline{C} = \underbrace{\overline{A}\overline{B} + A}_{A + \overline{B}} + B\overline{C} = A + \overline{B} + \overline{C}$$

Q1.c

$$F(A, B, C, D) = \overline{A}\overline{B}(\overline{0 + \overline{C}}) + A + \overbrace{(1 + \overline{D})}^{=1} + D$$

$$= 1$$

POS  $F = (\bar{a} + b)(\bar{b} + \bar{c} + \bar{d})$

	ab	00	01	11	10
cd	00	X <sub>0</sub>	X <sub>4</sub>	X <sub>12</sub>	X <sub>8</sub>
	01	1 <sub>1</sub>	1 <sub>5</sub>	X <sub>9</sub>	0 <sub>3</sub>
	11	1 <sub>3</sub>	0 <sub>7</sub>	0 <sub>11</sub>	0 <sub>11</sub>
	10	X <sub>2</sub>	1 <sub>6</sub>	1 <sub>14</sub>	X <sub>10</sub>

F

PI  
 $\bar{d} = PI1 = \sum m(6, 14) + d(0, 2, 4, 8, 10, 12)$   
 $\bar{a}\bar{b} = PI2 = \sum m(1, 3) + d(0, 2)$   
 $\bar{a}\bar{c} = PI3 = \sum m(1, 5) + d(0, 4)$   
 $b\bar{c} = PI4 = \sum m(5) + d(4, 12, 13)$


	ab	00	01	11	10
cd	00	X <sub>0</sub>	X <sub>4</sub>	X <sub>12</sub>	X <sub>8</sub>
	01	1 <sub>1</sub>	1 <sub>5</sub>	X <sub>9</sub>	
	11	1 <sub>3</sub>	2 <sub>7</sub>	1 <sub>11</sub>	
	10	X <sub>2</sub>	1 <sub>6</sub>	1 <sub>14</sub>	X <sub>10</sub>

F

EPI = PI1, PI2, PI3

Assume double rail

$F = \overline{d\bar{b}} + bcd$

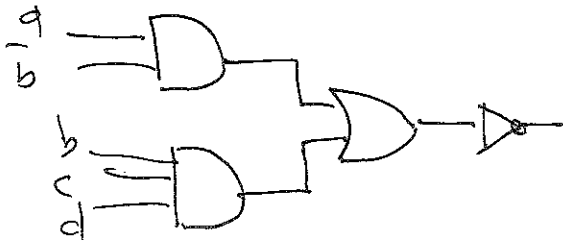

	ab	00	01	11	10
cd	00	X	X	X	X
	01			X	1
	11		1	1	1
	10	X			X


$\bar{F}$

Q3. a

assume double rail

	ab	00	01	11	10
cd	00	0	X	X	0
	01	0	1	X	0
	11	X	0	0	0
	10	X	1	1	X


$$F = b \cdot (\bar{c} + \bar{d})$$

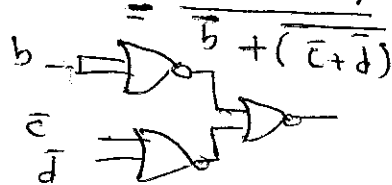

	ab	00	01	11	10
cd	00		X	X	
	01		1	X	
	11	X			
	10	X	1	1	X

$$F = b\bar{c} + c\bar{d}$$
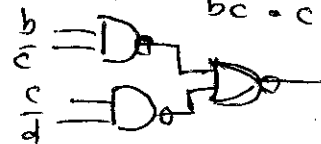
$$F = \overline{b\bar{c} \cdot c\bar{d}}$$



Q3 b

	ab	00	01	11	10
cd	00	X	X	X	X
	01	1	1	X	
	11	1	1	1	
	10	X	1	1	X

F1

	ab	00	01	11	10
cd	00	X	X	X	X
	01	1	1	X	1
	11	1	1	1	
	10	X	1	1	X

F

$$F1 = F \cdot \left\{ \begin{matrix} (\bar{c} + c) \\ \downarrow F_2 \end{matrix} + \begin{matrix} \bar{a} \\ \downarrow F_3 \end{matrix} \right.$$

	ab	00	01	11	10
cd	00	X	X	X	X
	01	1	1	X	
	11	1	1	1	X
	10	X	1	1	X

$\bar{a}$

	ab	00	01	11	10
cd	00	X	X	X	X
	01	1	1	X	0
	11	X	1	1	X
	10	X	1	1	X

$\bar{F}_3$


or  $(\bar{a} + b)$

Midterm Oct 13, 2001

MAJORITY

a	b	F
0	0	1
0	1	1
1	0	1
1	1	0

Q4

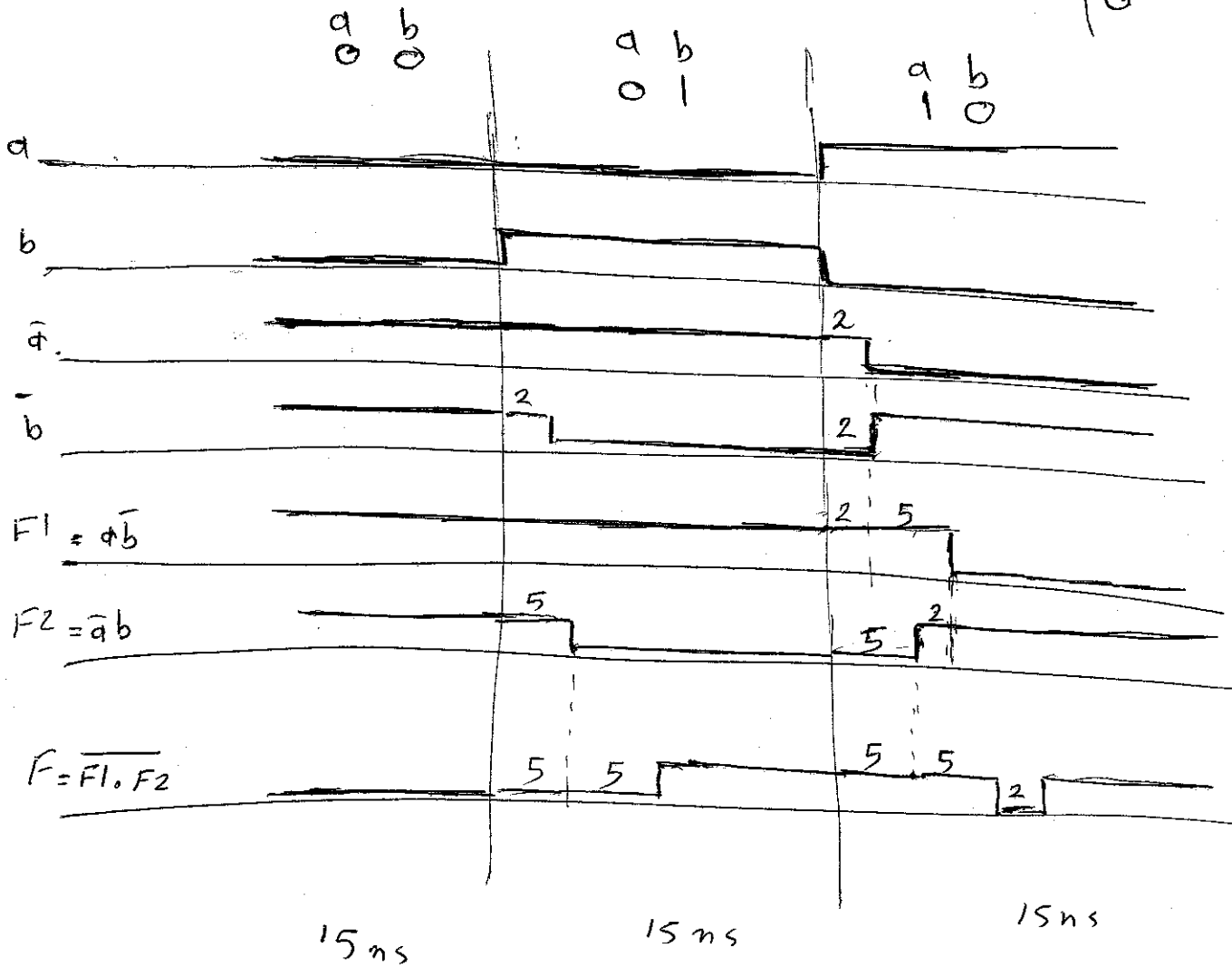

Critical Path =  $2 + 5 + 5 = 12 \text{ ns}$

Period is taken to be 15ns