

OLD EXAMS

COEN 312
DIGITAL DESIGN

3/5/2001

COEN 312 DIGITAL DESIGN

Final April 19, 2001

Answer all questions

No calculators, notes or books are allowed

Lecturers: A.J. Al-Khalili, M. Nekili, C. Taillefer

Time allowed 3:00 hours

Question 1 (10 Marks)

- (a) Given the function F' , determine the complement function F and minimize the total number of literals using Boolean algebra. (3 Marks)

$$F' = [(z + 0) \cdot (x' + y) + zxy' + z'(y + y'x) + z'x']'$$

- (b) Minimize the function Y using Karnaugh Maps. Present your answer as a product of sums (POS). List all the prime implicants. (4 Marks)


$$Y = \prod (3,5,7,8,12,13) + d(0,2,4)$$

- (c) Determine the minimized Boolean function Q defined in the following Truth Table. Use the Quine-McCluskey Tabular Method. (3 Marks)

A	B	C	Q
0	0	0	1
1	0	0	0
0	1	0	0
1	1	0	1
0	0	1	0
1	0	1	1
0	1	1	1
1	1	1	1

Question 2 (10 Marks)


 
- (d) Determine the timing diagram for the circuit below, where the inputs change simultaneously every 10ns from AB = 00 to AB = 11, then to AB = 00. Assume the AND gate has a propagation delay of 2ns and that the OR gate has a propagation delay of 1ns. Clearly label all the delays on the timing diagram. (3 Marks)



Question 2 (10 marks)

- (a) Convert the all-NOR multi-level combinational logic circuit to

 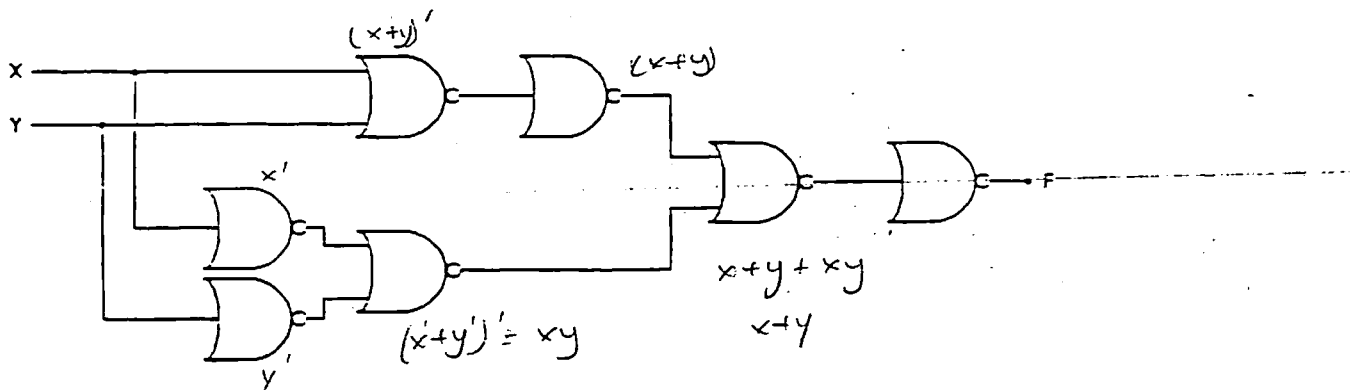- (i) a two-level AND-OR-Inverter circuit (2 Marks)
- (ii) a two-level all-NAND circuit (3 Marks)



Question 3 (10 Marks)

- (a) Design a 3-to-8 decoder using NOR gates only. Mark the minterms obtained. (3 Marks)
- (b) Use a 3-to-8 decoder plus minimal logic gates to implement the following functions: (3 Marks)

$$F(A, B, C) = \sum(0, 1, 2)$$

$$F(A, B, C) = \sum(4, 6, 7)$$

$$F(A, B, C) = \sum(2, 3, 5)$$

- (c) Use a 4-to-1 MUX plus minimal extra logic (if necessary) to implement the following function: (4 Marks)

$$F(A, B, C, D) = AB' + A'B'C' + A'BD$$

Question 4 (10 Marks)

- (a) Design a binary multiplier to multiply 2-bit binary numbers $A = a_1a_0$ and $E = b_1b_0$. (4 Marks)
-
- (b) Implement using a ROM by showing the patterns of "0"s and "1"s stored in the ROM as words and bits. (2 Marks)
- (c) Minimize and then implement using a PLA. (4 Marks)

Question 5 (10 Marks)

Design a synchronous sequential circuit, having one input x and one output z . Data is arriving serially on line x . The output $z=1$ if the total number of 0's received is an even number greater than zero, provided that two consecutive 1's have never occurred.

Question 6 (10 Marks)

Starting with all flip-flops outputs at the Low level, plot the timing diagram for the outputs q_0 , q_1 and Z over six clock periods for the circuit in the figure below. Assume that the JK flip-flops have a propagation delay of 10ns, the clock frequency is 10MHz, and the XOR gate has no delay.

