

Lecture 10, Feb. 7, 2007


## Subtraction

We saw in first lecture that subtracting  $B$  from  $A$  is equivalent to adding 2's complement of  $B$  to  $A$ .

So, an adder can be used to subtract two numbers if we invert each bit of the second number and add one to the result.

The following diagram shows how a single add/subtract circuit can be use for either

adding or subtracting two 4-bit numbers,

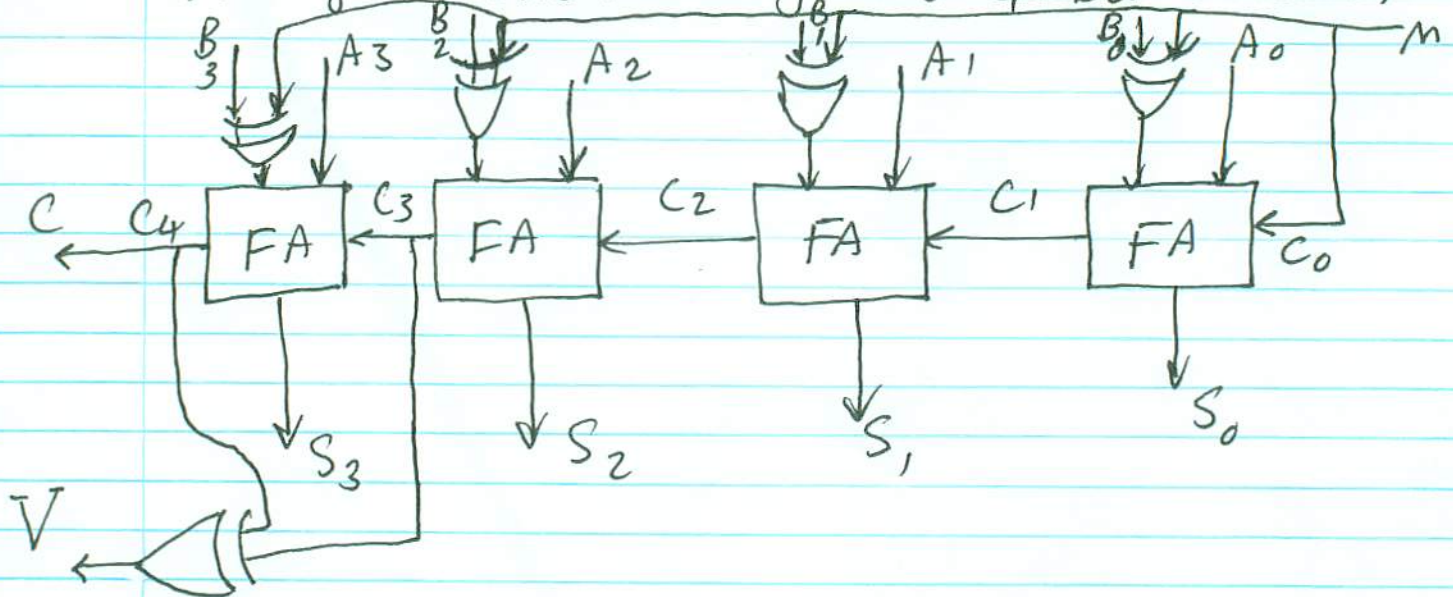

When  $M=0$ ,  $A$  and  $B$  are added

When  $M=1$ ,  $B$  is subtracted from  $A$ .

Note that when  $M=1$  the second input to Full adders are  $B_i \oplus 1 = B_i'$ , that is, each bit of  $B$  is inverted. Also  $M=C_0=1$  means that we add a 1 to  $B$  to get 2's complement.

The output  $V$  is used to show overflow. When  $V=1$ , there is an overflow. This means that the result of addition or subtraction does not fit in an  $n$  bit register.

Assume for example that we are adding two 8-bit signed numbers. This means:  
1 sign bit and 7 magnitude bits.

The range of numbers is from  $-127$  to  $+127$  (from  $1111111$  to  $0111111$ ).

But, when we add two numbers in this range, we may get a result that is not in the range.

For example if we add  $+60$  and  $+70$  we get  $+130$  or if we subtract  $70$  from  $-60$



we get  $-130$ , both being out of range.

$$\begin{array}{r} +60 \quad \begin{array}{c} \text{sign bit} \\ \downarrow \\ 00111100 \end{array} \\ +70 \quad 01000110 \\ \hline +130 \quad \underline{10000010} \quad \rightarrow -2 \end{array}$$

Notice that the sign bit indicates a minus and the seven remaining bits show 2.

Note that the sign bit becomes 1, when adding two positive numbers, if the carry from the previous bit is 1 since the carry from the last bit (when adding two positive numbers) is always zero (why?) then we have an overflow if

$$V = C_{n-1} \oplus C_n = 1$$
$$\begin{array}{r} -60 \quad \begin{array}{c} \text{sign bit} \\ \downarrow \\ 11000100 \end{array} \\ -70 \quad 10111010 \\ \hline -130 \quad \underline{10111010} \\ \quad \quad \quad \uparrow \\ \quad \quad \quad \text{overflow} \end{array}$$

Here, we get an overflow and a positive (instead of negative) number if the carry into

the last full adder is zero. Since the carry out of the last full adder is one (when adding two negative numbers), we have an overflow when  $V = C_{n-1} \oplus C_n = 1$ .

---

### BCD Adder

When we add two binary coded decimal (BCD) digits and a carry from a previous decimal digit addition we get a number between 0 and  $9 + 9 + 1 = 19$ . A 4-bit adder gives the appropriate output while the sum of two digits is less than 10. When the sum is 10 or more we need to have a carry and a 4-bit number representing the balance (the difference between the sum and 10).

For example when we add 6 (0110) and 7 (0111) we should get  $C = 1$  and 0011 or 1,0011 (13). But adding 0110 and 0111 with a 4-bit



we get 01101. We need to find a way to convert the output of a 4-bit adder to what we expect from a BCD adder.

The following table shows the output of the 4-bit adder and the BCD adder.

	<u>Binary Sum</u>					<u>BCD Sum</u>				
	K	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0		0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
<hr/>										
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	1	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

Note that  $C=1$  whenever  $K=1$  or  $Z_8=1$ .


But when  $Z_8=1$  and both  $Z_4$  and  $Z_2$  are zero  $C=0$ . So, we have a carry when

$K=1$  or  $Z_8=1$  and either  $Z_4$  or  $Z_2$  one

That is:

$$C = K + Z_8(Z_2 + Z_4) = K + Z_8Z_4 + Z_8Z_2$$

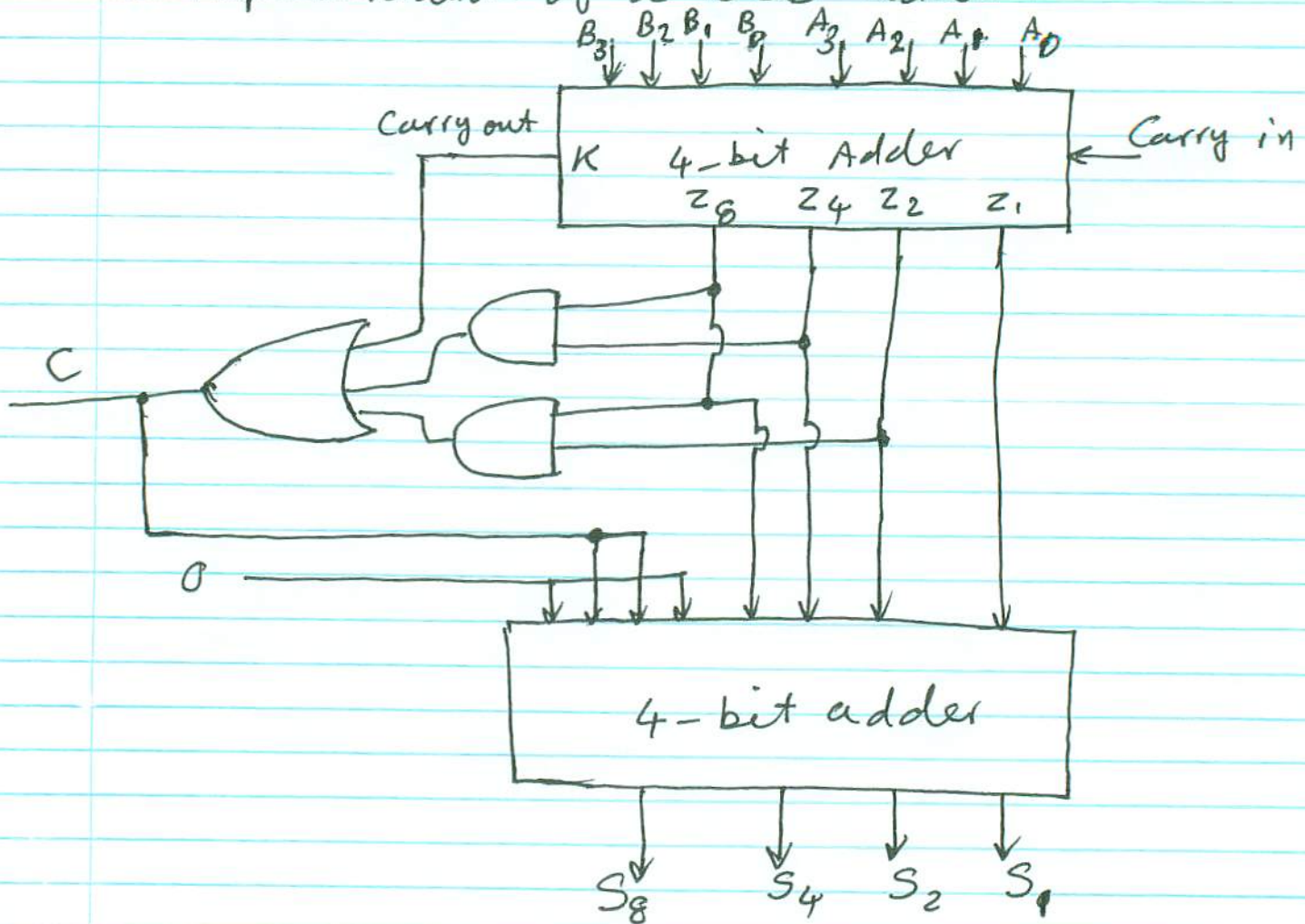When  $C=1$ , we need to add 6 (0110) to  $Z_8Z_4Z_2Z_1$  to get  $S_8S_4S_2S_1$ . Following is an implementation of a BCD adder.





## Binary Multiplication

Binary multiplication is done the same way we do decimal multiplication, i.e., we multiply the multiplicand by each bit of the multiplier to form a partial product. Then we shift each partial multiplication result and add them together.

As an example take the multiplication of  $B_1 B_0$  and  $A_1 A_0$ . That is we want to design a two bit multiplier.

$B_1 \quad B_0$

$A_1 \quad A_0$

---

$A_0 B_1 \quad A_0 B_0$

multiplying  $B_1 B_0$  by  $A_0$

$A_1 B_1 \quad A_1 B_0$

multiplying  $B_1 B_0$  by  $A_1$  and shifting the result.


---

$A_1 B_1 \quad A_0 B_1 + A_1 B_0 \quad A_0 B_0$

Adding two partial products.

$C_3 \quad C_2 \quad C_1 \quad C_0$

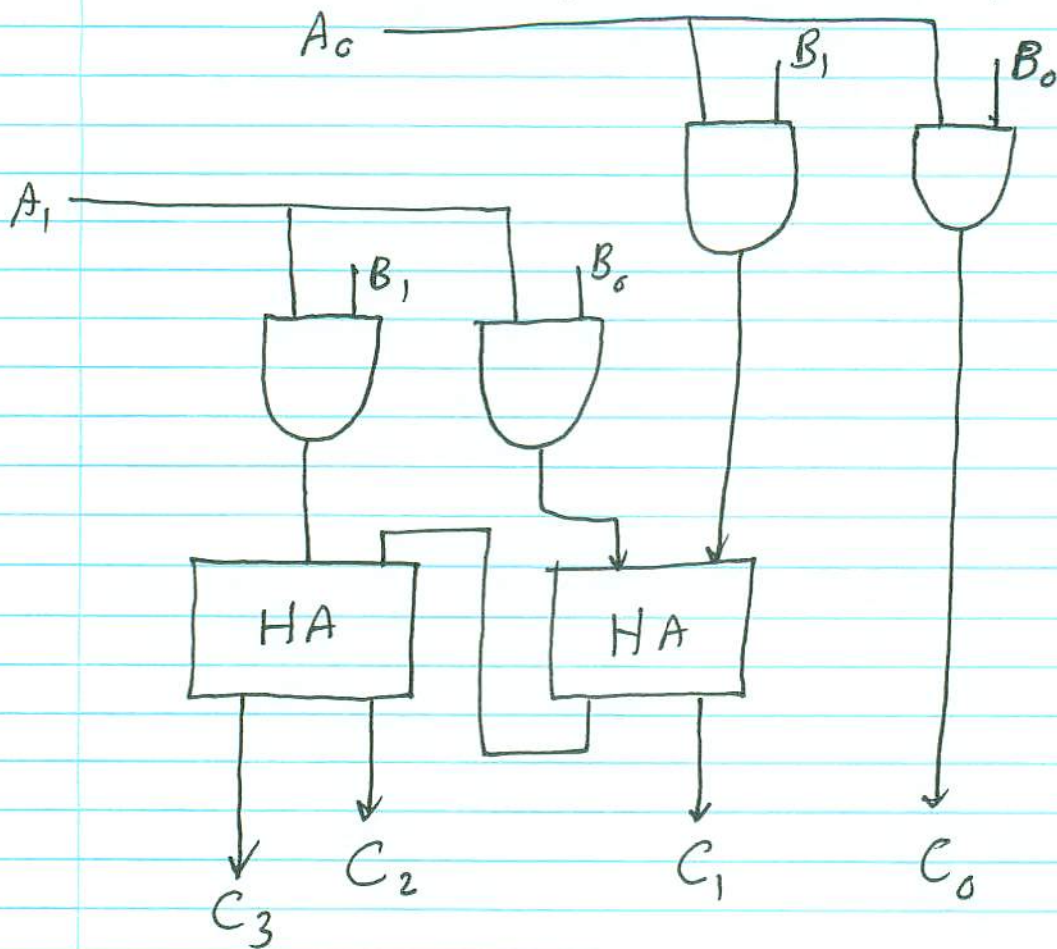The 2-bit multiplier can be implemented as,



4-bit by 3-bit multiplier

In this example we multiply  $B_3 B_2 B_1 B_0$

by  $A_2 A_1 A_0$

$$B_3 \quad B_2 \quad B_1 \quad B_0$$

$$A_2 \quad A_1 \quad A_0$$


---


$$A_0 B_3 \quad A_0 B_2 \quad A_0 B_1 \quad A_0 B_0$$

$$A_1 B_3 \quad A_1 B_2 \quad A_1 B_1 \quad A_1 B_0$$

$$A_2 B_3 \quad A_2 B_2 \quad A_2 B_1 \quad A_2 B_0$$


---


$$C_6 \quad C_5 \quad C_4 \quad C_3 \quad C_2 \quad C_1 \quad C_0$$



