

DATA TABLES

[To be cut out & pasted into the Report booklet]

DC CIRCUITS

INVERTER DATA

Inverter #1

Inverter #2

R ₁ =.....kΩ R ₂ = 100 kΩ Gain = -			R ₁ =.....kΩ R ₂ =.....kΩ Gain = -		
V _i volts	V _o volts	Gain	V _i volts	V _o volts	Gain

SUMMING-INVERTER DATA

#1

#2

R _a = kΩ R _b = kΩ			R _a = kΩ R _b = kΩ		
V _a volts	V _b volts	V _o volts	V _a volts	V _b volts	V _o volts

NON-INVERTER DATA

Non-Inverter #1

Non-Inverter #2

R ₁ = 100 kΩ R ₂ = 100 kΩ Gain = + 2			R ₁ =.....Ω R ₂ =.....Ω Gain = +		
V _i volts	V _o volts	Gain	V _i volts	V _o volts	Gain

VOLTAGE-FOLLOWER DATA

Input V _i volts			
Output V _o volts			

DIFFERENTIAL AMPLIFIER DATA

All 100kΩ Resistors, Gain = 1

V _a volts	V _b volts	V _o volts

TA Signature :

BLANK

AC CIRCUITS [Note: For the LPF, ‘cutoff frequency’ f_c is the frequency at which $A_v = \frac{1}{\sqrt{2}} = 0.707$, ie when $\omega CR = 1$. With $R_1 = R_2 = 2 \text{ k}\Omega$ and $C = 0.1 \mu\text{F}$, the ‘cutoff frequency’ $f_c = \frac{1}{2\pi CR} \approx 796 \text{ Hz}$. [Note that at 100 Hz, $A_v = 0.992 \approx 1$]

LOWPASS FILTER

Input $V_i = 2 \text{ volt RMS}$

f Hz	ω Radians/sec	Output V_o Volts RMS	$A_v = V_o/V_i$
100	628		
200	1257		
500	3142		
1000	6283		
2000	12566		
5000	31415		
10,000	62830		

TA Signature :

BLANK