

DATA TABLES

TRANSIENT RESPONSE DATA

Steps 1 to 3 :

(a) Values used for the series-RC circuit :

Nominal Value* of $R = \dots\dots\dots$ Ohms

Nominal Value of $C = 0.1 \mu\text{F}$

‘Theoretical’ Time Constant $\tau = RC = \dots\dots\dots$

*Neatly draw the circuit of the R –network which you used , to obtain the R value, in the space below.

(b) Values used for the series-RL circuit :

Nominal Value* of $R = \dots\dots\dots$ Ohms

Nominal Value of $L = 0.02 \text{ H}$

‘Theoretical’ Time Constant $\tau = L/R = \dots\dots\dots$

* Neatly draw the circuit of the R –network which you used , to obtain the R value, in the space below.

BLANK

Step 4 : Values used for the series-RLC circuit :

(c)

$$R_c(\text{nominal}) = 2\sqrt{0.02/0.1\mu} = 894.43 \Omega$$

Value of R used for 'OD' response, $R_{od} = \dots\dots\dots$ Ohms

Value of R used for 'CD' response, $R_{cd} = \dots\dots\dots$ Ohms

Value of R used for 'UD' response, $R_{ud} = \dots\dots\dots$ Ohms

TA Signature :

[Make sure to also obtain your TA's signature on the various time- and frequency- response printouts]

BLANK

FREQUENCY RESPONSE DATA

Step 5: Tables for Frequency Response Data (RC & RLC circuits)

Use a V_s magnitude in the 1 to 3 Volts RMS range

Series RC circuit

Attempt to keep V_s at a constant magnitude

[illegible]

Series RLC circuit

Attempt to keep V_s at a constant magnitude

[illegible]

TA Signature:

BLANK

DATA FOR Series-RLC RESONANT CIRCUIT, (Step 7)

[First locate the frequency at which V_c is a maximum and then 'descend' on both sides of the peak frequency. This will ensure proper plotting of the 'bandpass' curve]
Use a V_s magnitude in the 1 to 3 Volts RMS range

Attempt to maintain V_s at a constant level

First locate the frequency at which V_c reaches a maximum and enter the value here

f kHz	Input V_s Volts RMS	Output V_R Volts RMS	$M(\text{db}) = 20 \log \frac{V_c}{V_s}$
1			
1.5			
2			
2.5			
3			
4			
4.5			
5			
5.5			
6			

TA Signature :

BLANK