

PRE-LAB [To be completed and submitted before performing Lab # 3]

(Weight: 10%)


(1) A sinusoidal voltage signal has the peak-to-peak value V_{pp} and a frequency f Hz. On an oscilloscope display, the above signal appears to be ‘time-shifted’ by Δt sec with respect to another signal having the same frequency .

$V_{pp} = \dots\dots\dots$ Volts, $f = \dots\dots\dots$ Hz.,
 $\Delta t = \dots\dots\dots$ sec

For **your choice** of V_{pp} , f and Δt determine

- (a) the RMS value $V_{RMS} = \dots\dots\dots$ Volts
- (b) the Period $T = \dots\dots\dots$ sec
- (c) the radian frequency $\omega = \dots\dots\dots$ radians/sec
- (d) the ‘phase-shift’ between the two signals is $\theta = \dots\dots\dots$ degrees

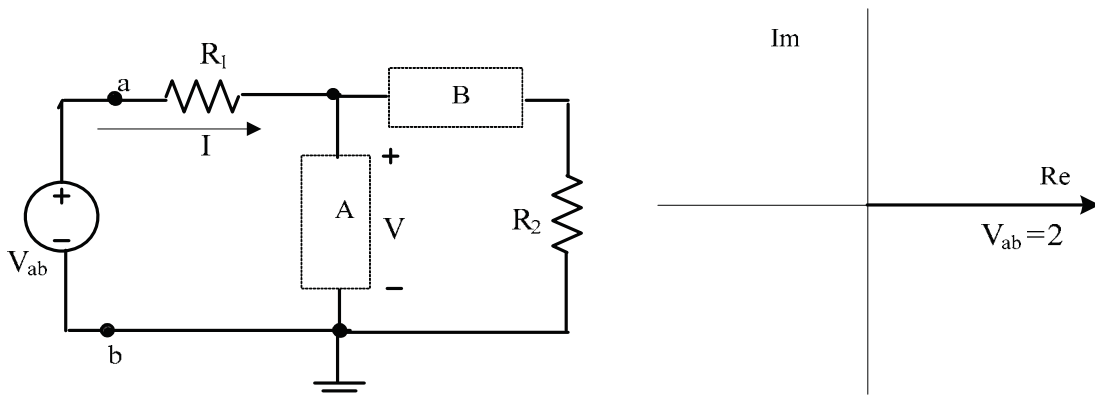(2): For the circuit shown $R_1 = 500\Omega$ and $R_2 = 1000\Omega$. The components A and B (within the dotted outlines) may be capacitors (C) in the range of 100–300 nF or inductors (L) in the range of 20-50 mH. The frequency of operation is in the range of 2000–5000Hz. and $V_{ab} = 2$ volts RMS.



Indicate the (L and/or C) component of **your choice** for A & B within the dotted outlines (with values) and the frequency $f = \dots\dots\dots$ Hz. and determine, by calculation,

- (a) the impedance (in polar form) connected to the source, $Z_{ab} = \dots \angle \dots$, Ohms
- (b) the phasor current $I = \dots\dots\dots$ A/mA
- (c) sketch the phasor diagram showing I and V , with V_{ab} as reference.

[Hint: Obtain V using KVL: $V = V_{ab} - IR_1$]

Show all calculations below (neatly!):

continued overleaf >>>>

(3) Assume that you have constructed the circuit setup of Figure 3.9, with frequency f adjusted to 4kHz. and that the measurements obtained from the printout (Step 6) were as follows: :

$V_1 = \dots\dots\dots$ volts [**choose** between 4 & 6 V RMS]

$V_2 = \dots\dots\dots$ volts [**choose** between 500mV & 800mV RMS] with V_2 lagging V_1 .

and the timeshift between the two waveforms is

$\Delta t = \dots\dots\dots$ μ s [**choose** between 20 & 40 μ s]

Determine :

(a) the magnitude of the unknown impedance $Z = (\dots\dots \dots j \dots\dots\dots) = \dots\dots \angle \dots\dots$ from the hypothetical values assumed above.

(b) the 'nature' of the impedance : Inductive / Capacitive (Circle the answer)

Show all calculations below (neatly!) :

