

**PRE-LAB (Weight: 20 %) SHOW RELEVANT CALCULATIONS ON A SEPARATE PAGE IF NECESSARY**

**PART (A):**

- (1) The circuit of an 'ideal' transformer with primary turns  $N_p = \dots\dots\dots$  and secondary turns  $N_s = \dots\dots\dots$  is connected on the secondary side to a load impedance  $Z_L = (\dots\dots + j \dots\dots)$  ohms.  
For values of  $N_p, N_s$  and  $Z_L = Z_s$  **selected by you**, (choose  $n$  between 1.5 and 2.5) determine:
- a) The transformation ratio  $n = \dots\dots\dots$
  - b) The impedance 'seen' on the primary side  $Z_p = \dots\dots\dots + \dots\dots\dots$
- (2) The above transformer and load are connected to a 60Hz voltage source whose no-load terminal voltage is  $V_g = 120$  voltsRMS, and 'internal' impedance  $Z_g$  is  $3\Omega$ . Determine
- a) The Average load power  $P = \dots\dots\dots$  Watts
  - b) The Reactive load Power  $Q = \dots\dots\dots$  VARs
  - c) The PF 'seen' by the source,  $PF = \dots\dots\dots$
  - d) The RMS load voltage  $V_L = \dots\dots\dots$  volts
  - e) The Power efficiency  $\eta = \dots\dots\dots$  %
  - f) The % Voltage Regulation =  $\dots\dots\dots = \dots\dots\dots$  %

**PART (B):**

- (1) A balanced 60 Hz three-phase Y-Y, 3-wire system is connected to measure power using the two-wattmeter method of Figure 4.6. The line-to-line voltage is 208 voltsRMS. The positive (non-zero) readings of the wattmeters are  $W_A = \dots\dots\dots$  Watts and  $W_C = \dots\dots\dots$  Watts.  
The line-current magnitude is  $I = \dots\dots\dots$  Amps.

For values of  $I, W_A$  and  $W_C$  **selected by you**, determine

- a) The total average power  $P = \dots\dots\dots$  Watts
  - b) The power-factor of the load  $PF = \dots\dots\dots$
  - c) The load impedance  $Z = \dots\dots \angle \dots\dots^\circ$  Ohms
- (2) A  $\Delta$ -connected balanced load has the value  $Z_\Delta = \dots\dots\dots + j \dots\dots\dots$  Ohms. is connected to a balanced Y-connected source and the line-current magnitude is  $I = \dots\dots\dots$  Amps. For values of  $Z_\Delta$  and  $I$  **selected by you**, determine :
- a) The impedance of an equivalent Y-connected load  
 $Z_Y = \dots\dots\dots + j \dots\dots\dots$  ohms
  - b) The Phase-voltage magnitude of the source  
 $V_{ph} = \dots\dots\dots$  Volts RMS