

ELECTRONICS-I (ELEC 311/1 BB)

Mid-Term Test (Summer 2013)

(No CRIB sheet allowed. Only ENCS approved calculator allowed)

Electrical and Computer Engineering Department

Instructor: Dr. R. Raut

June 16, 2013

Time: 70 minutes

(Answer ALL questions)

Please return the question paper with your answer book


Q.1: For the circuit in Fig.1, both diodes are identical. Find the value of R for which $V = 90$ mV. Assume $n=2$. *Hint: Use exponential model for the diodes.*

$$\frac{i_1}{i_2} = \exp\left(\frac{v_{D2} - v_{D1} + 0.09}{2 \times 0.025}\right)$$

$$= \exp(1.8) \approx 6.05$$

But $i_1 + i_2 = 10$ mA
Solving, $i_2 = 1.42$ mA
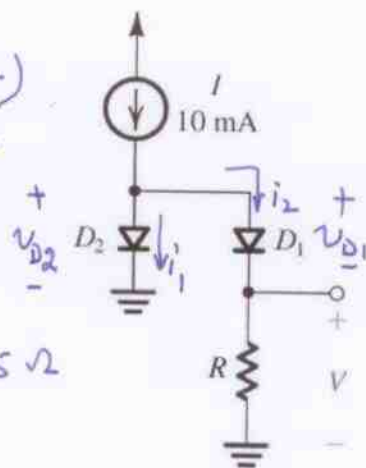
$$R = \frac{90 \text{ mV}}{1.42 \text{ mA}} \approx 63.45 \Omega$$



$$i_1 + i_2 = 10 \text{ mA}$$

$$V = 90 \text{ mV} = i_2 R$$

$$v_{D2} = v_{D1} + 90 \text{ mV}$$


$$i_1 = I_s \exp\left(\frac{v_{D1}}{nV_T}\right)$$

$$i_2 = I_s \exp\left(\frac{v_{D2} - 0.09}{nV_T}\right)$$

Figure 1

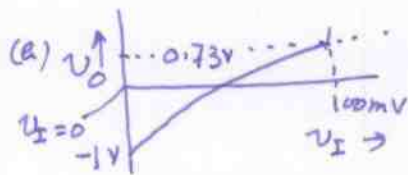Q.2: An electronic amplifier is characterized by the output-input relation $v_o = 2[0.5 - e^{-20v_i}]$.

- Show a graphical sketch of the transfer characteristic over $0 < v_i < 100$ mV.
- What will be the **small signal** gain of the amplifier at an operating input voltage of $V_i = 50$ mV?
- What is the associated output operating point for $V_i = 50$ mV?



$$(b) \left. \frac{\partial v_o}{\partial v_i} \right|_{v_i = 50 \text{ mV}} = -2(-20)e^{-20 \times 0.05} = 14.71 \text{ V/V}$$

$$(c) v_o = 2(0.5 - e^{-20 \times 0.05}) = 0.26 \text{ V}$$

Q.3: Figure 3 shows the equivalent circuit of a BJT amplifier. Obtain the voltage amplification $\frac{V_o}{V_i}$. Express the magnitude in dB. The various component values are given


as: $R_s = 100 \text{ ohms}$, $R_2 = 44\text{k ohms}$, $R_3 = 2.2\text{k ohms}$, $R_c = 3.3\text{k ohms}$, $R_L = 4.7\text{k ohms}$, $g_m = 0.05 \Omega^{-1} \text{ mhos}$.

Use $100 \mu = 0.1 \text{ k}\Omega$

$$V_a = V_s \frac{44\text{k} \parallel 2.2\text{k}}{1\text{k} + 44\text{k} \parallel 2.2\text{k}}$$

$$V_a = 0.95 V_s$$

$$\text{dB gain} = 20 \log_{10} | -92.1 | = 39.28 \text{ dB}$$

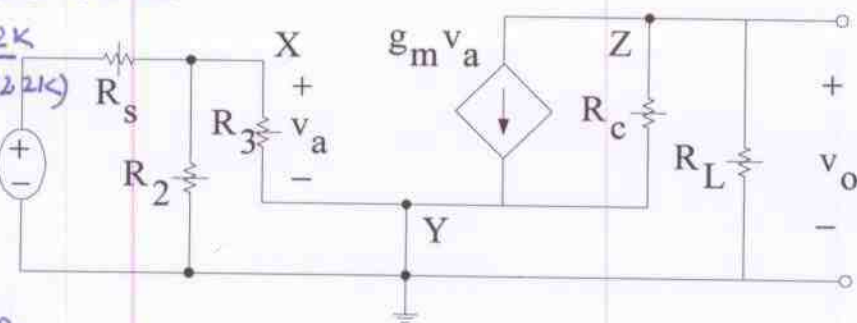

$$V_o = -0.05 \times (3.3\text{k} \parallel 4.7\text{k}) \times V_a$$

Then find $\frac{V_o}{V_s} \approx -92.1 \text{ V/V}$

Figure 3:

Q.4: Figure 4 shows a circuit for an ac voltmeter. The meter shows full scale deflection for a DC current of 1.5 mA. Design the resistance R so that an ac voltage v_i of 15 volts magnitude produces full deflection in the meter. The diode is ideal, and the system works like a half-wave rectifier. The meter has a resistance of 15Ω .

$$E_m = 15 \text{ V}$$

$$v_i = 15 \sin \omega t$$

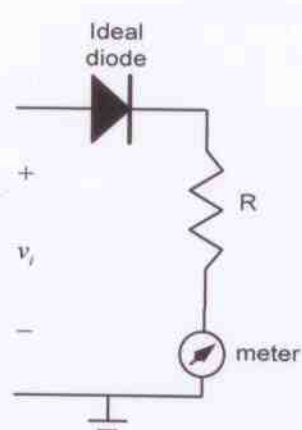


Figure 4

$$I_R = \frac{V_{DC}}{R + r_m} ; r_m = 15 \Omega$$

$$V_{DC} = \frac{E_m}{\pi} \text{ for a HWR system}$$

$$\text{So } \frac{E_m}{\pi} \cdot \frac{1}{R + 15} = 1.5 \text{ mA}$$

$$R + 15 = \frac{15}{\pi \times 1.5} \text{ k}\Omega$$

$$R = 3.168 \text{ k}\Omega$$