

# ELECTRONICS-I

ELEC 311

## Answers to past Final examinations

Yrs. 2005, 2006, 2007, 2008, 2009

Year	Q. No.	Q. No.	Q. No.
2005	1	2	3
2006	4	5	6
2007	7	8	9
2008	10	11	12
2009	13	14	15

Q1.  $A_{vo} = \frac{v_o}{v_i} = \frac{4}{9}$  ;  $R_i = \frac{v_i}{i_i} = 30 \Omega$   
 $R_o = -\frac{5}{6} \Omega$


Q2:  $R = 537 \Omega$  or lower  
 Load regulation =  $-5 \text{ mV/mA}$

Q3: (a)  $v_o = 0.871 \text{ volts (ac)}$   
 (b)  $v_o = 0.898 \text{ volts (ac)}$  } need to use iteration to find  $I_D$ , then  $r_d = V_T / I_D \dots$

Q4:  $R_B \approx 160 \text{ k}\Omega$  ;  $R_C \approx 7.7 \text{ k}\Omega$  are the initial design values for DC operation.

Q5:  $R_{in} = 21.79 \text{ k}\Omega$  ,  $R_{out} = 165 \Omega$  ;  $\frac{v_o}{v_{sig}}$  = close to 1 but less than (CC stage)  
 largest output signal level 5 V peak.

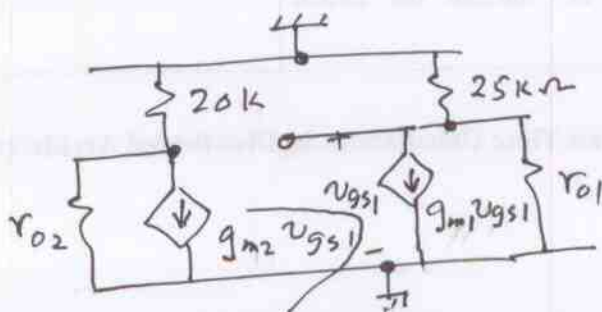Q6:  $R = 25 \text{ k}\Omega$  ;  $I_{D2} = 120 \mu\text{A}$




- Q1: (a)  $V_D = 0.664V$  ;  $I_D = I_R = 0.434mA$   
 (b)  $V_D = 0.66V$  ;  $I_D = 0.434mA$ .

- Q2: (a)  $C \approx 2562 \mu F$   
 (b)  $15.12V$   
 (c)  $\Delta t = \tau = 0.678 msec.$

- Q3: (a)  $V_E = -0.5V$  ;  $V_C = 4.5V$   
 (b)  $V_B = -0.5V$  ;  $> 2.4V$  (saturation..)  
 assuming  $V_{CE(sat)} = 0.2V$ .  
 (c) For cut-off,  $V_E = -1V$ ,  $V_C = 5V$   
 For saturation  $V_E = 1.9V$  ;  $V_C = 2.1V$

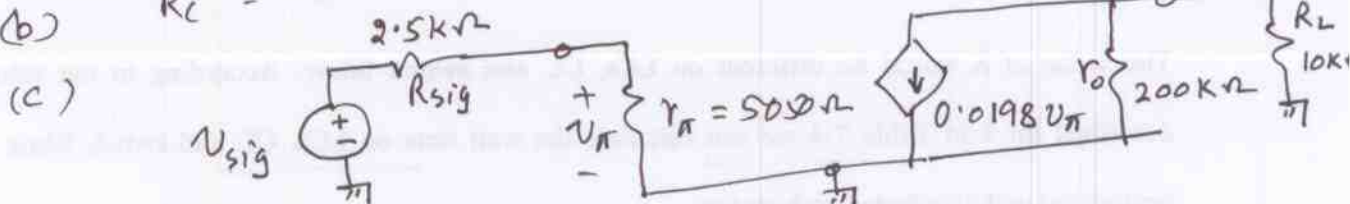- Q4: (a)  $R_E = 28.57 k\Omega$   
 (b)  $R_C = 20.2 k\Omega$



- (d)  $\frac{v_o}{v_{sig}} = -85.73 V/V$

- Q5: (a)  $R_{in} = 75.76 \Omega$   
 (b)  $v_o / v_{sig} = 9.68 V/V$   
 (c)  $v_{sig} \leq 50 mV$

Aug. 23, 2006


Final '06 (Answers)

p 2/2

Q6: (a)  $I_D = 1.697 \text{ mA}$

(b)  $\frac{v_o}{v_{sig}} = -3.55 \text{ V/V}$


ac equiv. ckt:

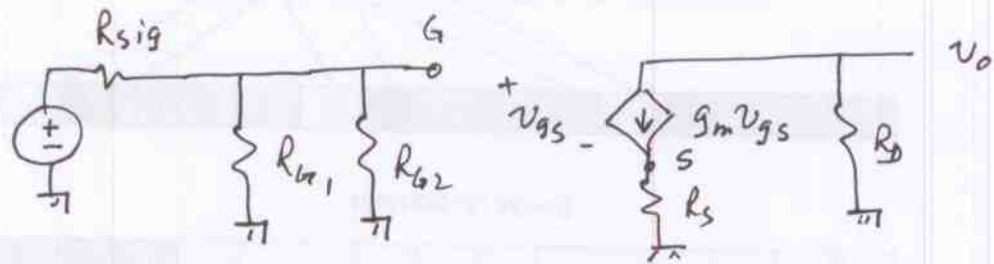

Final '07 (Answers)

Aug. 15, 2007

Q1:

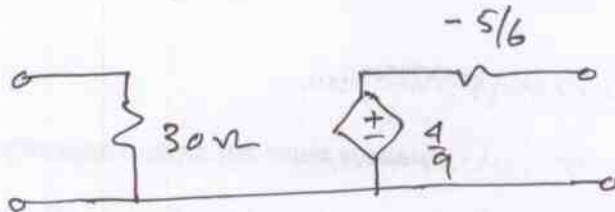

$R_i = 30 \Omega$ ;  $R_o = -\frac{5}{6} \Omega$ ;  $A_{vo} = \frac{4}{9} \text{ V/V}$

Q2:

Case I:  $v_o = 0.871 \text{ volts}$

Case II:  $v_o = 0.898 \text{ volts}$

Q3:

Same as Q.3, Final '06

Q4:

Same as Q 5, Final '06

Q5:

Same as Q 6, Final '06

Q6:

Same as Q.6, Final '05

Q1: (a)  $15.57 \text{ V}$

(b)  $474\% \rightarrow \frac{170.53}{360^\circ}$  for each diode


(c)  $I_{\text{AVG}} = 9.4 \text{ mA}$  (note:  $V_{\text{DC}} = \frac{2E_m}{\pi} - 1.4 \text{ V}$ )

Q2:  $V_E = -0.7 \text{ V}$ ;  $I_E = 0.93 \text{ mA}$   
 $I_B = 18.23 \text{ mA}$ ,  $I_C = 0.912 \text{ mA}$ ;  $V_C = 5.44 \text{ V}$

Q3: (a)  $V_C = 0.995 \text{ V}$

(b)  $V_B = 2 \text{ V}$

(c)  $R_{\text{in}} \approx 500 \Omega$

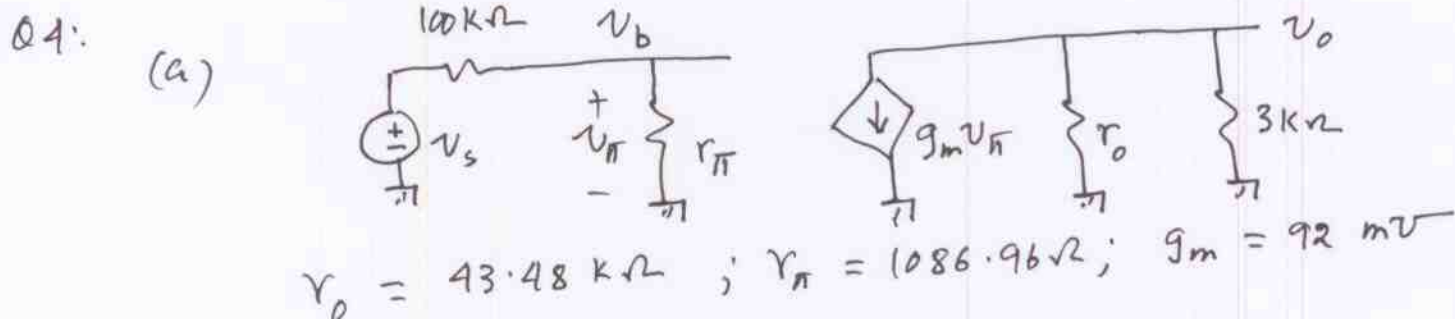


(b)  $\frac{v_o}{v_s} = -2.78 \text{ V/V}$

(c)  $v_s < 0.86 \text{ V}$

Q5:  $R_D = 5.33 \text{ k}\Omega$ ;  $R_S = 5.33 \text{ k}\Omega$ ;  $R_{G1} = 1.63 \text{ M}\Omega$   
 $R_{G2} = 3.37 \text{ M}\Omega$

Q6:

AC equivalent circuit model..

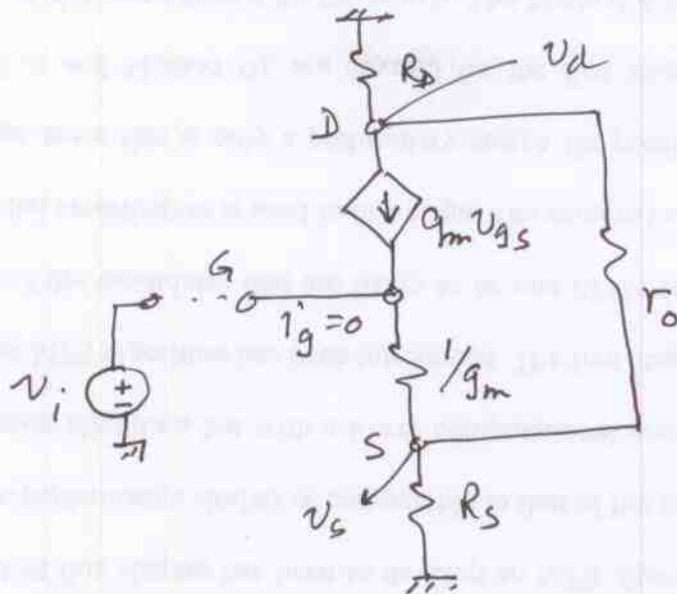

Assuming  $r_o \rightarrow \infty$  ,  $\frac{v_s}{v_i} = \frac{g_m R_s}{1 + g_m R_s}$  (a)

$\frac{v_d}{v_i} = - \frac{g_m R_D}{1 + g_m R_s}$  (b)

If  $r_o = \infty$  is not assumed

$\frac{v_s}{v_i} = + \frac{g_m g_D}{(g_D + g_D)(g_s + g_m + g_D) - g_D(g_m + g_D)}$  (a)

$\frac{v_d}{v_i} = - \frac{g_m(g_s + g_m + g_D) - g_m(g_m + g_D)}{(g_D + g_D)(g_s + g_m + g_D) - g_D(g_m + g_D)}$  (b)

<note:  $g_D = \frac{1}{r_o}$  ;  $g_D = \frac{1}{R_D}$  ;  $g_s = \frac{1}{R_s}$  >

Q1: (a)  $18.527 \text{ k}\Omega$

(b)  $I_Q = 149.85 \mu\text{A}$

$V_Q = 0.023 \text{ V}$  using given formula.

Q2: (a)  $R \approx 318 \Omega$

(b)  $6.47 \text{ V}$

Q3: (a)  $3.2 \text{ mF}$

(b)  $19.58 \text{ V}$

(c)  $12.84$

Q4: (a)  $28.575 \text{ k}\Omega$

(b)  $20.2 \text{ k}\Omega$


(c)  $-66.26 \text{ V/V}$

Q5: (a)  $97.5 \Omega$

(b)  $-17.91 \text{ V/V}$

(c)  $-86.73 \text{ V/V}$

Q6: (a)

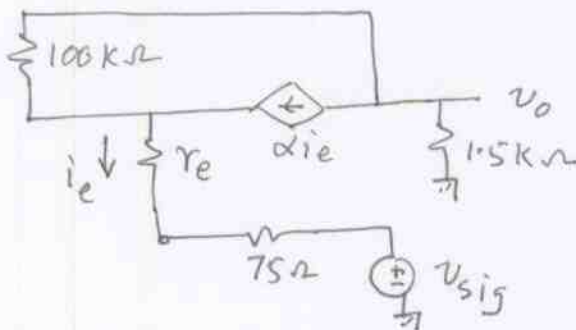

(b)  $9.7 \text{ V/V}$

(c)  $49.75 \text{ mV}$

Q7: (a)  $2.086 \text{ mA}$

(b)  $-12.12 \text{ V/V}$



BOOK No. \_\_\_\_\_

# CONCORDIA UNIVERSITY

NUMBER OF BOOKS USED \_\_\_\_\_ ADDITIONAL BOOK (to be placed inside back cover of first book)

FILL IN THE FOLLOWING:

NAME \_\_\_\_\_  
(Please Print) SURNAME GIVEN NAMES

SUBJECT \_\_\_\_\_  
(Course and Number)

COURSE GIVEN BY \_\_\_\_\_

EXAMINATION SUPERVISED \_\_\_\_\_

DATE WRITTEN \_\_\_\_\_

ELEC 311 Summer 2012

Final Exam

soln. - ~~part I~~

Q 1:

$$V_{GS2} = 0.7 \text{ V}, \quad V_{OV2} = 0.2 \text{ V}$$

$$I_2 = 0.5 \text{ mA} \cdot \left(\frac{4}{2}\right) \cdot V_{OV}^2 = 0.5 \times 2 \times 0.04 = 0.04 \text{ mA}$$

(a) So  $R_1 = \frac{1.8 - 0.7}{0.04} \text{ k}\Omega = \frac{1.1}{0.04} \text{ k}\Omega = 27.5 \text{ k}\Omega$

(b) At the edge of saturation,  $V_{D1} \approx V_{G1} = V_G$

$$V_{DS1} = V_{OV1} = V_{OV2} \quad (\because \text{gates are connected}) \\ = 0.2 \text{ V} = V_{D1} \quad (\because \text{source grounded})$$

$I_1 = I_2$   $\because$  identical transistors, identical  $V_{GS}$  values

So  $I_1 = 0.04 \text{ mA} = 40 \mu\text{A}$

$$R_2 = \frac{1.8 - 0.2}{0.04} \text{ k}\Omega = 40 \text{ k}\Omega$$

(c)  $I_1 \Big|_{\text{Early effect}} = I_1 \left(1 + \frac{V_{DS1}}{V_A}\right) \\ = 0.04 \text{ mA} \left(1 + \frac{0.2}{50}\right) = 40.16 \mu\text{A}$

\_\_\_\_\_ x \_\_\_\_\_

Q2: Using  $V_2 = V_1 + 2.303 n V_T \log_{10} (I_2/I_1)$


with  $I_2/I_1 = 10$ ,  $V_2 - V_1 = 100 \text{ mV}$ .

So  $100 \text{ mV} = 2.303 n \times 25 \text{ mV}$

$$n = \frac{4}{2.303} = 1.7368$$

~~Given  $V_2 = V_1 + 0.99 \log_{10} (I_2/I_1)$  Give ans.~~

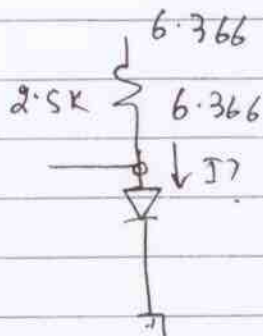For  $10 \text{ V peak}$ ;  $V_{DC} = \frac{10 \times 2}{n} = 6.366 \text{ V}$ .



Iteration :

Say  $V_D = 0.7 \text{ V}$ ,  $I = 1 \text{ mA}$

$$V_2 = 0.7 + 0.99 \log_{10} \left( \frac{I_2}{1} \right) = 0.7 + 0.99$$

$$\log_{10} (I_2) = \frac{V_2 - 0.7}{0.99}$$

$$(1) \quad I = \frac{6.366 - 0.7}{2.5 \text{ K}} = 2.266 \text{ mA}$$

$$V_2 = 0.7 + 0.99 \log_{10} (2.266) = 0.735$$

$$I(2) = \frac{6.366 - 0.735}{2.5 \text{ K}} = 2.252 \text{ mA} \quad \text{convergent}$$


$$V_2 = 0.7 + 0.99 \log_{10} (2.252) = 0.735 \text{ V}$$

Q2:  $I = 2.252 \text{ mA}$

$$r_d = \frac{25 \text{ mV}}{2.252 \text{ mA}} = 11.1 \Omega$$

$11.1 \Omega$

ac equivalent circuit:

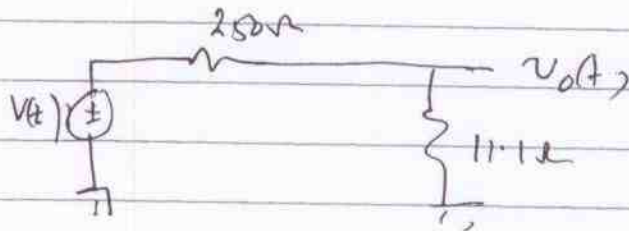

$$v_o(t) = \frac{11.1}{261.1} v_e(t)$$

$$v_o(t) |_{\text{peak}} = 0.425 \text{ V}$$


$$\text{So } v_o(t) = 0.425 \sin(\omega t)$$

----- X -----

Q3: Peak value at secondary winding =  $15 \times 1.414 = 21.21 \text{ V}$

Peak value at the filter capacitor =  $21.21 - 2V_{DO}$

$$= 21.21 - 1.6 = 19.61 \text{ V}$$

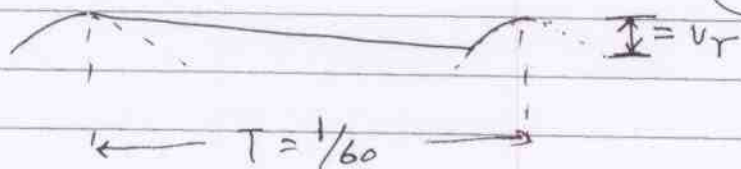

(a) Using charge conservation principle, the ripple  $V_r$  is given by:

$$C V_r = \text{charge up} \approx \frac{V_p}{R} \cdot \frac{T}{2} = \text{discharge}$$

$$C = \frac{V_p T}{R V_r} = \frac{19.61 \times 1/60}{200 \times 0.5}$$

$3.268 \text{ mF}$   
~~1.634 mF~~

$$Q3(b) = \frac{1}{2\pi} (6.4\theta_1 - 1.6 \times 3\pi) = -14.596 = -2.323V$$

3(b) From the symmetry of the rectified waveform, the output DC will be:

$$V_o|_{DC} = \frac{1}{\pi} \int_{\theta_1}^{\pi-\theta_1} (21.21 \sin \phi - 1.6) d\phi$$

$$= \frac{1}{\pi} \left[ 21.21 \cos \phi \Big|_{\pi-\theta_1}^{\theta_1} - 1.6 \phi \Big|_{\theta_1}^{\pi-\theta_1} \right]$$

$$= \frac{1}{\pi} \left[ 2 \times 21.21 \cos \theta_1 - 1.6 (\pi - 2\theta_1) \right]$$

$$= \frac{2 \times 21.21}{\pi} \cos \theta_1 - 1.6 \frac{\pi - 2\theta_1}{\pi}$$

$$V_{DC} = \frac{V_p + V_p - V_r}{2} = \frac{V_p - V_r}{2} = \frac{19.61 - 2.25}{2} = 19.36V$$

Subst.  $\theta_1$  value of 0.0755 rad.


$$V_o|_{DC} = 11.94 \text{ volts.}$$

3(c) The PIV rating for each diode should be  $V_s - V_D = 21.21 - 0.8 = 20.41 \text{ volts.}$

$$3(b) V_{DC} = \frac{V_p + V_p - V_r}{2} = 19.36V$$

Q4: We need to find the 'ac' parameters,  $g_m$ ,  $r_\pi$ ,  $r_o$ .  
DC bias current need be calculated.

The EB loop is :

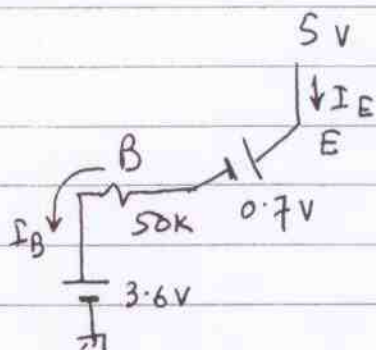

$$\text{Thus } 5V - 0.7V - 50k \times I_B - 3.6V = 0$$

$$\text{So } I_B = \frac{5 - 4.3}{50k} = 14 \mu A$$


$$\text{Then } I_C = 14 \mu A \times 80 = 1.12 \text{ mA}$$

$$g_m = \frac{1.12 \text{ mA}}{25 \text{ mV}} = 0.0448 \text{ S} = 44.8 \text{ mS}$$

$$\therefore r_\pi = \frac{\beta}{g_m} = \frac{80}{0.0448} = 1785.71 \Omega$$


$$r_o = \frac{50}{1.12} \text{ k}\Omega = 44.64 \text{ k}\Omega$$

The ac equivalent circuit is:

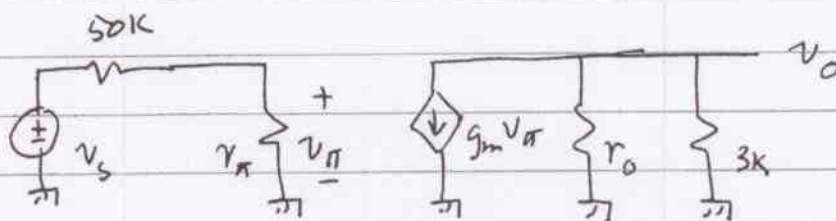

$$\begin{aligned} \frac{V_o}{V_s} &= -g_m \cdot \frac{r_\pi}{50k + r_\pi} \cdot r_o \parallel 3k = -0.0448 \times \frac{1785.71}{50k + 1785.71} \times (44.64k \parallel 3k) \\ &= -0.0448 \times \frac{1.786 \text{ k}}{51.786 \text{ k}} \times (44.64k \parallel 3k) = -4.34 \text{ V/V} \end{aligned}$$

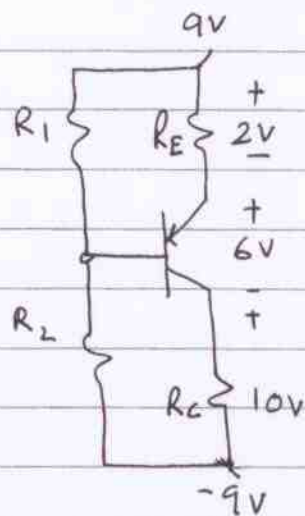Q5: The specified DC values on the schematic are:



$$\therefore I_{CQ} \approx 0.5 \text{ mA} \quad \text{and} \quad V_{RC} = 10 \text{ V} ; \quad R_C = \frac{10}{0.5} \text{ k}\Omega = 20 \text{ k}\Omega$$

$$I_{EQ} = \frac{\beta + 1}{\beta} I_{CQ} = \frac{100}{99} \times 0.5 \text{ mA} = \cancel{0.505 \text{ mA}} \quad 0.505 \text{ mA}$$

$$\text{Then } R_E = \frac{2 \text{ V}}{0.505 \text{ mA}} = \frac{2 \text{ V}}{0.505 \text{ mA}} = 3.96 \text{ k}\Omega$$

For  $R_1, R_2$  design, we find

$V_{BX}$  = Thev. voltage at base

$$= 9 \frac{R_2}{R_1 + R_2} - 9 \frac{R_1}{R_1 + R_2} = 9 \frac{R_2 - R_1}{R_1 + R_2}$$

$$R_{BX} = \text{Thev. equivalent resistance} = \frac{R_1 R_2}{R_1 + R_2}$$

Let  $R_2 = m R_1$  with  $m > 1$

$$V_{BX} = \frac{9(m-1)R_1}{(m+1)R_1} = \frac{9(m-1)}{m+1}$$

$$R_{BX} = \frac{m R_1}{m+1}$$

KVL @ the EB loop gives

$$7 \text{ V} - 0.7 \text{ V} - I_B \frac{m R_1}{m+1} = \frac{9(m-1)}{m+1}$$

Q5: But  $I_B = \frac{0.5 \text{ mA}}{99} = 5.05 \mu\text{A}$

So

$$6.3 = 5.05 \times 10^{-6} \times \frac{mR_1}{m+1} + 9 \frac{m-1}{m+1}$$

Let  $m = 2$

$$6.3 = 5.05 \times 10^{-6} \frac{2R_1}{3} + \frac{9}{3}$$

$$R_1 = \frac{3.3 \times 3}{2 \times 5.05 \times 10^{-6}} = 980.198 \text{ k}\Omega$$

$$R_2 = mR_1 = 1.96 \text{ M}\Omega \text{ (approx.)}$$


Basically,  $R_1 = \frac{6.3 - \frac{9(m-1)}{m+1}}{\frac{m}{m+1} \times 5.05 \times 10^{-6}}$

$$= \frac{6.3(m+1) - 9(m-1)}{m \times 5.05 \times 10^{-6}} \Omega$$

&  $R_2 = mR_1 \Omega$

∴

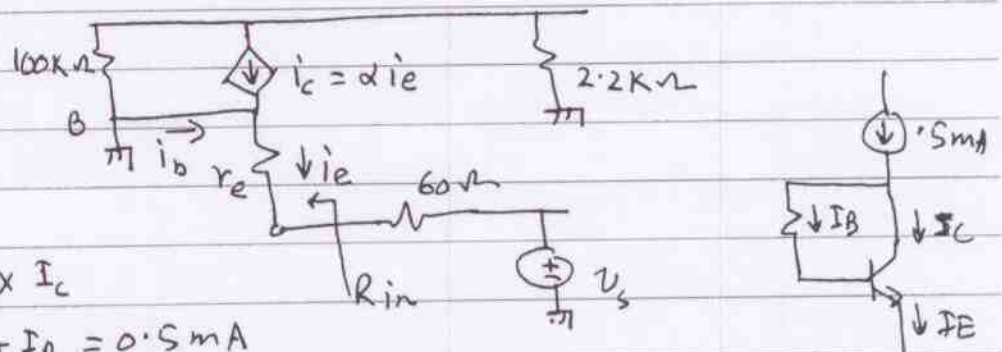Q6: This is a CB-BJT amplifier with an equivalent circuit as:



$$I_E = \frac{101}{100} \times I_C$$

$$= I_C + I_B = 0.5 \text{ mA}$$

$$\text{So } r_e = \frac{25 \text{ mV}}{0.5 \text{ mA}} = 50 \Omega$$



Q6: Since  $V_A$  is not given, we take  $r_o = \infty$

(a) By inspection,  $R_{in} = r_e = 50 \Omega$

(b) The output signal voltage

$$v_o = -\alpha i_e (100k\Omega \parallel 2.2k\Omega) \approx -\frac{100}{101} \times 2.2k\Omega \times i_e$$

$$\text{But } i_e = -\frac{v_s}{(60+50)\Omega}$$

$$\text{So } \frac{v_o}{v_s} = \frac{100}{101} \times 2.2k \times \frac{1}{110} = 19.8 \text{ V/V}$$

(c) For small signal approximation to be valid

$$v_{be} < 25 \text{ mV}$$

$$i_e v_s \frac{r_e}{60+r_e} < 25 \text{ mV}$$


$$v_s < 25 \times \frac{110}{50} \text{ mV} \rightarrow 25 \times 2.2 \text{ mV (peak)}$$

$$= 55 \text{ mV (peak)}$$

$$v_s \ll 55 \text{ mV (peak)}$$

Q7:

(a) Schematic

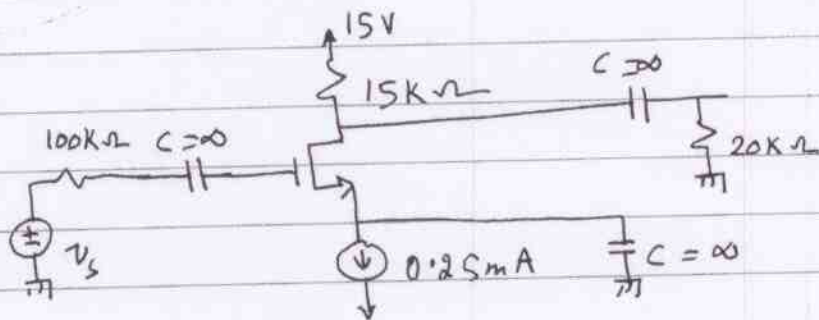

(b) For the voltage gain we need  $g_m = k_n \frac{W}{L} V_{ov} = 1.67 \text{ mA/V}$

$$I_D = 0.25 \text{ mA} = k_n \frac{W}{L} \frac{V_{ov}^2}{2} ; k_n \frac{W}{L} = \frac{0.5}{V_{ov}^2} \text{ mA/V}^2 = 5.55 \text{ mA/V}^2$$

$$r_o = 200k\Omega ; R_L = 15k\Omega \parallel 20k\Omega \parallel 200k\Omega ; v_o/v_s = -13.72 \text{ V/V}$$

Q8: Identical transistors; series connection.

→ So  $I_{D1} = I_{D2}$  & hence  $V_{GS1} = V_{GS2}$

For M2:

$$I_{D2} = \frac{1}{2} K \frac{W}{L} (V_{GS2})^2$$

$$V_{GS2} = 0 - V_1 - 1 \quad \text{while}$$

$$V_1 = -2.5 + I_{D2} \quad \text{where } I_{D2} \text{ is in mA.}$$

$$\text{So } I_{D2} = \frac{1}{2} \times 3 \times (0 - 1 + 2.5 - I_{D2})^2$$

Solve for  $I_{D2}$  - quadratic eqn.

→ accept  $I_{D2} = 0.78 \text{ mA}$

→ Then  $V_1 = -2.5 + 0.78 = -1.72 \text{ V} \rightarrow \text{Ans \# 1}$

$$V_{GS2} = 0 - V_1 - 1 = 1.72 - 1 = 0.72 \text{ V}$$

$$V_{GS1} = V_{GS2} = 0.72 \text{ V}$$

$$\text{Then } V_{GS2} = 2.5 - V_2 = 0.72 \text{ V}$$

$$V_2 = 2.5 - 0.72 = 1.78 \text{ V}$$

→  $V_2 = 2.5 - 1.72 = 0.78 \text{ V} \rightarrow \text{Ans \# 2}$