

**ELEC 312: ELECTRONICS – II : ASSIGNMENT-3**  
**Department of Electrical and Computer Engineering**  
**Winter – 2012-2013**

1. A series-series feedback circuit represented by Fig.1, and using an ideal transconductance amplifier operates with  $V_s = 100$  mV,  $V_f = 95$  mV, and  $I_o = 10$  mA. What are the corresponding values of  $A$  and  $\beta$ ? Include the correct units for each.

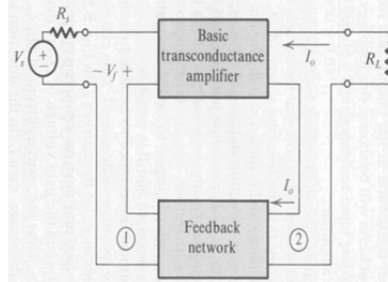


Figure 1:

**Hints:**

$$V_1 = V_s - V_f; V_f = \beta I_o \text{ hence, } \beta = V_f / I_o; A = I_o / V_1; A_F = I_o / V_s = A / (1 + A \beta).$$

2. For an amplifier connected in a negative feedback loop in which the output voltage is sampled (i.e., a shunt connection), measurement of the output resistance before and after the loop is connected shows a change by a factor of 80. Is the resistance with feedback higher or lower? What is the value of the loop gain  $A\beta$ ? If  $R_{of}$  is  $100 \Omega$ , what is  $R_o$  without feedback?

**Hints:**

$$R_o \text{ is lowered by amount of feedback i.e. } (1 + A \beta) = 80; A\beta = 79, R_o = R_{of} (1 + A \beta)$$

3. The shunt-shunt feedback amplifier in the Figure 3 has  $I = 1$  mA and  $V_{GS} = 0.8$  V. The MOSFET has  $V_t = 0.6$  V and  $V_A = 30$  V. For  $R_S = 10$  k $\Omega$ ,  $R_1 = 1$  M $\Omega$ , and  $R_2 = 4.7$  M $\Omega$ , find the voltage gain  $v_o/v_s$ , the input resistance  $R_{in}$  and the output resistance  $R_{out}$ . You need to figure out the *ac* parameters for the MOS device.

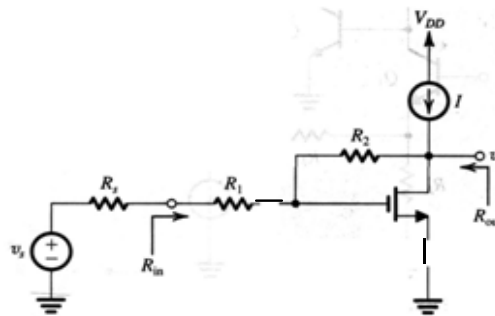
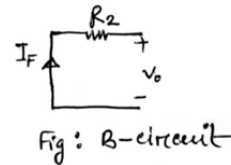
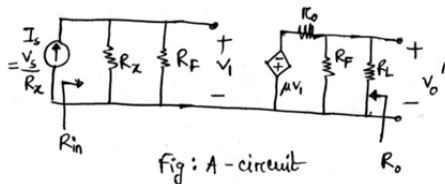


Figure 3:

**Hints:**

$$\underline{g_m} = 2I_D/V_{OV} \text{ and } r_o = V_A/I,$$

Shunt-shunt feedback. We use Y-parameter model for the feedback circuit.

Find  $y_{11}$ ,  $y_{22}$ ,  $y_{12}$  for  $R_1$ ,  $R_2$ . Remember  $\beta = y_{12}$ .

Draw loaded ac equivalent circuit. Use  $R_{11}(=1/y_{11})$  in shunt at input,  $R_{22}(=1/y_{22})$  in shunt at output.

$$\beta = I_F/V_o = -1/R_2, \text{ Let } R_x = R_s + R_1 \text{ and } \mu = g_m r_o, A = V_o'/I_s' = -[R_x || R_2][R_2 || r_o]g_m = -2.478E8;$$

$$A_F = V_o/I_s = A/(1+A\beta) = -4.612E6$$

$$\text{Thus } V_o/(I_s R_x) = V_o/V_1 = 1/(\beta R_x) = -R_2/(R_1 + R_s)$$

$$R_i' = (R_s + R_1) || R_2; R_{if} = R_i'/(1+A\beta) = 15473.2, R_{in} = R_{if} - R_s = 5473.2$$

$$R_o' = R_2 || r_o, R_{of} = R_o'/(1+A\beta) = 554.8 = R_o; v_o/v_s = -4.57$$

4. An op amp having a low-frequency gain of  $10^3$  and a single-pole transfer function with -3dB frequency of  $10^4$  rad/s is connected in a negative feedback loop via a feedback network having a transmission  $\beta(s)$  given by  $\beta(s) = \frac{\beta_o}{(1 + s/10^4)^2}$ . Find the value of  $\beta_o$  above which the closed-loop amplifier becomes unstable.

**Hints:**

$$A(s) = \frac{10^3}{1 + s/10^4}, \beta(s) = \frac{\beta_o}{(1 + s/10^4)^2}$$

$$\text{Ang}(A\beta) = -\tan^{-1}(\omega/10^4) - 2\tan^{-1}(\omega/10^4) = 3\tan^{-1}(\omega/10^4)$$

For  $180^\circ$ ,  $\omega_{180} = \sqrt{3} \times 10^4$ ; for  $|A\beta(\omega_{180})| < 1$ , Determine condition for  $\beta_o$  ( $=0.008$ )

5. A DC amplifier has an open-loop gain of 1000 and two poles, a dominant one at 1 kHz and a high-frequency one whose location can be controlled. It is required to connect this amplifier in a negative feedback loop that provides a dc closed-loop gain of 100 and a maximally flat response. The transfer function of the amplifier can be modeled as:

$$A(s) = \frac{1000}{(1 + s/\omega_1)(1 + s/\omega_2)}$$

In the above  $\omega_1$  is the dominant pole frequency. It is required that under feedback, the amplifier will have a maximally flat response according to the model

$$A_f(s) = \frac{1000\omega_1\omega_2}{s^2 + (\omega_p/Q_p)s + \omega_p^2}, \text{ with } Q_p = 0.707.$$

Calculate the required  $\omega_2$ .

**Hints:**

$$A(s) = \frac{1000}{(1 + s/\omega_1)(1 + s/\omega_2)};$$

$A_f(0) = 10^3/(1+10^3\beta) = 100$ , calculate  $\beta$  ( $\approx 0.009$ ).

Formulate the  $A_f(s)$  under feedback, and concentrate on the denominator polynomial  $D(s)$  in the form

$$s^2 + (\omega_p/Q_p)s + (\omega_p)^2$$

Compare it with

$$s^2 + s(\omega_1 + \omega_2) + (1 + A_o\beta)\omega_1\omega_2 = 0$$

$Q_p = \sqrt{[(1 + A_o\beta)\omega_1\omega_2]/(\omega_1 + \omega_2)}$ , calculate  $\omega_2$  Where,  $Q_p = 0.707$  and  $\omega_1 = 2\pi \times 1000$  rad/s.

Solve the quadratic eq. in  $\omega_2$ . Accept the value which is  $> 2\pi f_1$  (since  $f_1 = 1000$  Hz is the dominant pole)

$\omega_2 = 1.1278E5$  rad/s;  $f_2 = 17950.33$  Hz.