
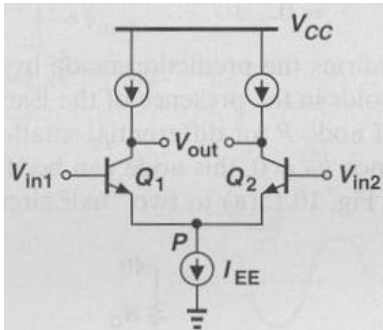


ELEC 312: ELECTRONICS – II ASSIGNMENT-Set #1
Department of Electrical and Computer Engineering
Winter -2013

- Find an expression for the differential gain of the following circuit, where ideal current sources are used as loads to maximize the gain. V_{in1} , V_{in2} may be assumed to be balanced differential signals.

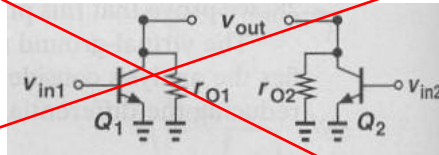**Hints:**


With ideal current sources, the Early effect in Q_1 and Q_2 cannot be neglected, and the half circuits must be visualized as depicted in the following figure:



see at the end


$$V_{out1} = g_m r_o V_{in1}, \quad V_{out2} = -g_m r_o V_{in2}, \quad \text{and hence } (V_{out1} - V_{out2}) / (V_{in1} - V_{in2}) = -g_m r_o$$

- The following figure illustrates an implementation of a differential amplifier with active load using complementary BJT devices. Calculate the differential voltage gain $V_{out}/(V_{in1} - V_{in2})$

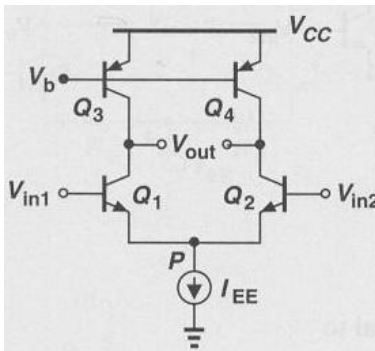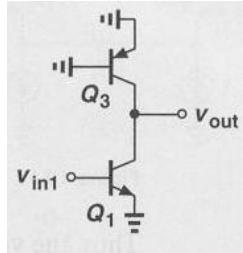**Hints:**


We will assume (since it is not stated otherwise) that the input signals are balanced-differential. Sp node P is at virtual ground.

Noting that each pnp device introduces a resistance of r_{OP} at the output nodes and drawing the half circuit as the bellow figure, we have (considering each half-circuit and combining differentially at the end)




$(V_{out1} - V_{out2}) / (V_{in1} - V_{in2}) = -g_m (r_{ON} // r_{OP})$. Where r_{ON} denotes the output impedance of the npn transistors.

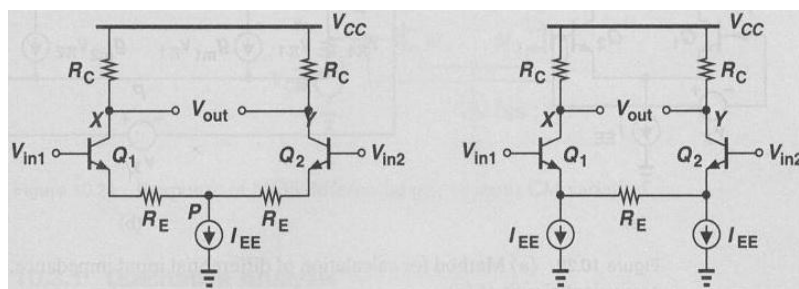3. Determine the gain of the emitter degenerated differential pairs shown in the following figure. Assume $V_A = \infty$.



Hints:

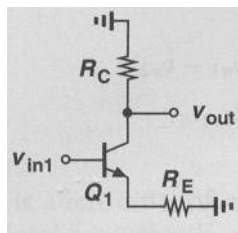
In the 1st figure, node P is a virtual ground, yielding the half circuit depicted in the following figure,



we have (like a CE amplifier with emitter load)


$$A_v = -R_C / (R_C + 1/g_m).$$

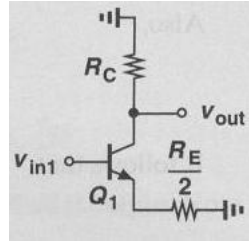In the 2nd figure, the line of symmetry passes through the “midpoint” of R_E . In other words, if R_E is regarded as two $R_E/2$ units in series, then the node between the units acts as a virtual ground as the following figure,




We have, $A_v = -R_C / (R_E/2 + 1/g_m)$.

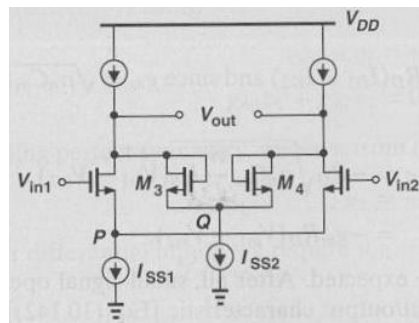4. Assuming $\lambda = 0$, compute the voltage gain of the following circuit. I_{SS2} is used to bias the transistors M_3 and M_4 . Consider all I-sources are identical.



Hints:

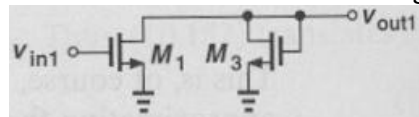Assume balanced differential operation. Identifying both nodes P and Q as virtual grounds, we construct the half circuit shown in the following figure,



And we have, $A_v = -g_{m1} / g_{m3}$

Q5: Use square law eqn. for M2

$$I_{out} = 100 \mu A = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_{THN})^2 = 300 \times 4 \times (V_{GS} - 0.5)^2 \mu A$$

$$\text{This gives } V_{GS} - 0.5 = \sqrt{\frac{100}{1200}} = \pm 0.289$$

$\therefore V_{GS}$ is required to be $> V_{THN}$ for M2 to conduct,

$$\text{we take } V_{GS} = 0.5 + 0.289 = 0.789 \text{ V}$$

$$\therefore V_{SS} = 0, \quad V_G = 0.789 \text{ V Then}$$

$$\text{Using M1, } \frac{V_{DD} - V_G}{R} = 100 \mu A; \quad R = \frac{1.5 - 0.789}{100} \text{ M}\Omega$$

$$\text{i) } \therefore R = 7110 \Omega \text{ or } 7.11 \text{ k}\Omega$$

ii) For proper operation, M2 should be in saturation.

$$\therefore V_D - V_S > V_{GS} - V_{THN} \rightarrow 0.289; \text{ but } V_S = V_{SS} = 0 \text{ V}$$

$$\therefore V_D = 0; \quad V_D > 0.289.$$


Lowest value of $V_D = 0.289 \text{ V}$.

$$\text{iii) } r_o = \frac{V_A}{I_{out}} = \frac{20}{100} \text{ M}\Omega = 200 \text{ k}\Omega$$

iv) Considering Early effect $I_{out} \sim (1 + \lambda V_{DS})$ with $\lambda = \frac{1}{|V_A|}$

$$\therefore \Delta I_{out} = \lambda \Delta V_{DS} = \frac{\Delta V_{DS}}{|V_A|} = \frac{\pm 0.5}{20} = \pm 0.025 \rightarrow \pm 2.5\%$$
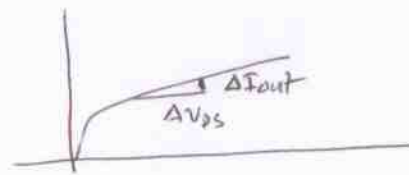
$$\underline{\text{Alt.}} \quad r_o = \frac{V_A}{I_{out}} = \frac{\Delta V_{DS}}{\Delta I_{out}} \text{ from the output characteristic}$$



$$\therefore \Delta I_{out} = \frac{\Delta V_{DS}}{r_o} = \pm \frac{0.5}{200 \times 10^3} \rightarrow \pm 2.5 \mu A$$

$$= \pm 0.000025 \text{ Amp} = \pm 2.5 \mu A$$

$$\frac{\Delta I_{out}}{I_{out}} = \frac{\pm 2.5}{100} \rightarrow \pm 2.5\%$$

Q6: Because of finite β we can write

$$I_{C1} = I_{in} - \frac{I_{B1}}{\beta} - \frac{I_{B2}}{\beta} = I_{in} - \frac{2}{\beta} I_B \quad \text{if } I_{B1} = I_{B2} = I_B \text{ (matched } Q_1, Q_2)$$

But $I_{C1} = \beta I_B$ as well.

$$\text{Thus, } \left(\beta + \frac{2}{\beta}\right) I_B = I_{in}$$

$$I_B = \frac{I_{in}}{\beta + \frac{2}{\beta}}$$

$$\text{Now } I_{out} = \beta I_B = \frac{\beta}{\beta + \frac{2}{\beta}} \cdot I_{in}$$

$$\text{So } \frac{I_{out}}{I_{in}} = \frac{\beta}{\beta + \frac{2}{\beta}}$$

$$\text{If } \beta = \beta_{min} = 50; \quad \frac{I_{out}}{I_{in}} = \frac{50}{50 + \frac{2}{50}} = 0.961$$

