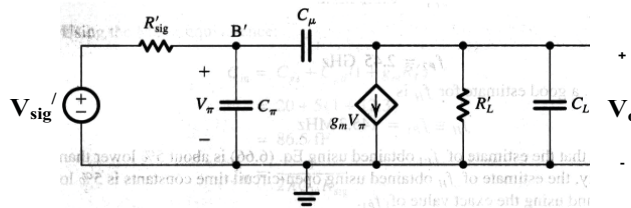


ELEC 312: ELECTRONICS – II : ASSIGNMENT-set 2
Department of Electrical and Computer Engineering
Winter 2013


1. A common-emitter amplifier that can be represented by the following equivalent circuit, has $C_\pi = 10$ pF, $C_\mu = 0.5$ pF, $C_L = 2$ pF, $g_m = 20$ mA/V, $\beta = 100$, $r_x = 200$ Ω , $R_L' = 5$ k Ω and $R_{sig} = 1$ k Ω . Find (i) the mid band gain A_M , (ii) the frequency of the zero f_Z , and (iii) the approximate values of the pole frequencies f_{P1} and f_{P2} . Hence estimate the 3-dB frequency f_H . Note that R'_{sig} is the equivalent Thevenin resistance looking towards the signal source and includes the effects of R_{sig} , r_x and r_π . For approximate estimates, you may use OCTC method.



Hints:

- (i) $A_M = -r_\pi(g_m R'_L)/(R_{sig} + r_x + r_\pi)$; (ii) $f_Z = g_m/(2\pi C_\mu)$ (iii) $f_{P1} = 1/[2\pi\{(C_\pi + C_\mu(1 + g_m R'_L))R'_{sig} + (C_L + C_\mu)R'_L\}]$; $f_{P2} = [(C_\pi + C_\mu(1 + g_m R'_L))R'_{sig} + (C_L + C_\mu)R'_L]/[2\pi\{C_\pi(C_L + C_\mu) + C_L C_\mu\}]R'_{sig}R'_L$; $f_{P1} \ll f_{P2}$ & $f_{P1} \ll f_Z$, hence $f_H \approx f_{P1}$
2. Analyze the high-frequency response of the CMOS amplifier shown below. The dc bias current is 100 μ A. For Q_1 , $\mu_n C_{ox} = 90$ μ A/V², $V_A = 12.8$ V, $W/L = 100$ μ m/1.6 μ m, $C_{gs} = 0.2$ pF, $C_{gd} = 0.015$ pF. For Q_2 , $C_{gd} = 0.015$ pF, $C_{gs} = 36$ fF and $|V_A| = 19.2$ V. Assume that the resistance of the input signal generator is negligibly small. Also, for simplicity assume that the signal voltage at the gate of Q_2 is zero. Find the low-frequency (i.e., at DC) gain, the frequency of the pole, and the frequency of the zero. You may use nodal analysis.

Note: fF=10⁻¹⁵ F, pF=10⁻¹² F.

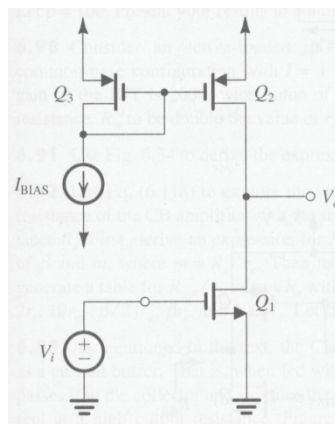

Hints:

DC gain = $-g_m(r_{o1} // r_{o2})$, where $g_m = \sqrt{2\mu_n C_{ox} I_D W/L}$, $r_o = V_A / I_D$ and
 Small-signal gain, $v_o / v_i = (g_m - sC_{gd1}) / [1 / r_{o1} + 1 / r_{o2} + s(C_L + C_{gd1})]$ where $C_L = C_{gd2}$
 $f_z = g_m / (2\pi C_{gd1})$; $f_p = (1/2\pi) [(1 / r_{o1} + 1 / r_{o2}) / (C_L + C_{gd1})]$

3. A CG amplifier is specified to have $C_{gs} = 2$ pF, $C_{gd} = 0.1$ pF, $C_L = 2$ pF, $g_m = 5$ mA/V, $\chi = 0.2$, $R_{sig} = 1$ k Ω and $R_L' = 20$ k Ω . Neglecting the effects of r_o , find the low-frequency gain v_o / v_{sig} , the frequencies of the poles f_{p1} and f_{p2} and hence an estimate of the 3-dB frequency f_H . For a CG amplifier you can use $g_{mb} = \chi g_m$. Use ac equivalent circuit.

Hints:

From the small-signal equivalent circuit,
 $v_o / v_i = [\{ 1 / (g_m + g_{mb}) \} / \{ R_{sig} + 1 / (g_m + g_{mb}) \}] (g_m + g_{mb}) R_L'$; $f_{p1} = 1 / [2\pi C_{gs} \{ R_{sig} // (1 / (g_m + g_{mb})) \}]$;
 $f_{p2} = 1 / [2\pi (C_{gd} + C_L) R_L']$. $f_{p2} \ll f_{p1}$, f_{p2} is the dominant pole and $f_H \approx f_{p2}$


4. (a) Consider a CS amplifier having $C_{gd} = 0.2$ pF, $R_{sig} = R_L = 20$ k Ω , $g_m = 5$ mA/V, $C_{gs} = 2$ pF, C_L (including C_{db}) = 1 pF, and $r_o = 20$ k Ω . Find (i) the low-frequency gain A_M , and (ii) estimate f_H using open-circuit time constants.

Hence determine the gain-bandwidth (GBW = mid-freq. gain *times* f_H).

Hints:

$A_M = g_m R_L'$; $f_H = 1 / (2\pi\tau_H)$ where $\tau_H = C_{gs}R_{gs} + C_{gd}R_{gd} + C_L R_L'$, $R_{gs} = R_{sig}$, $R_{gd} = R_{sig}(1 + g_m R_L') + R_L'$; $GBW = |A_M|f_H$

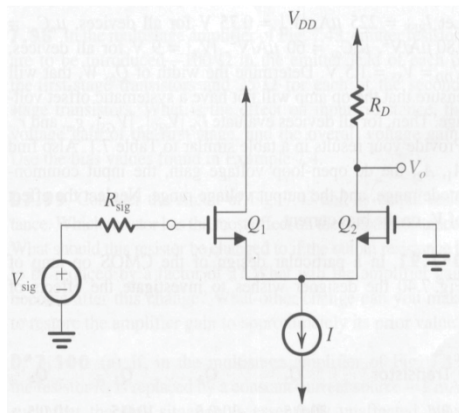5. Consider the following circuit for the case: $I = 200$ μ A and $V_{OV} = 0.25$ V, $R_{sig} = 200$ k Ω , $R_D = 50$ k Ω , $C_{gs} = C_{gd} = 1$ Pf (for both transistors). Find the dc (i.e., low-frequency) gain, the high-frequency poles, and an estimate of f_H . (hint: need to find g_m from I and V_{OV} data!).



Hints:

~~$V_{G1} = V_S \cdot [(2/g_m) / ((2/g_m) + R_S)]$, $I = V_{G1} / (2/g_m)$, $V_O = IR_D$ hence, $A_O = V_O / V_S = g_m R_D / (2 + g_m R_S)$; $f_{p1} = 1 / [2\pi R_S (C_{gs}/2 + C_{gd})]$; $f_{p2} = 1 / (2\pi R_D C_{gd})$~~ (See Later)





6.


(a) Consider a CS stage having $C_{gd} = 0.2 \text{ pF}$, $R_{sig} = 20 \text{ k}\Omega$, $g_m = 5 \text{ mA/V}$, $C_{gs} = 2 \text{ pF}$, and $r_o = 20 \text{ k}\Omega$.

(b) A CG stage is connected in totem-pole configuration with the CS transistor in (a) to create a cascode amplifier. The ac parameters of this stage are identical with those of the CS stage. Regarding the body-effect in the CG stage assume $\chi = 0.2$. Further $R_L = 20 \text{ k}\Omega$, and is shunted by a load capacitance $C_L = 1 \text{ pF}$. Show a schematic diagram of the system using NMOS transistors. Show the ac equivalent circuit.


Find (i) the low-frequency gain A_M , and (ii) estimate the gain-bandwidth of the system. You may use OCTC method to determine the dominant high frequency pole f_H of the system.

Hints:

For the cascade amplifier:

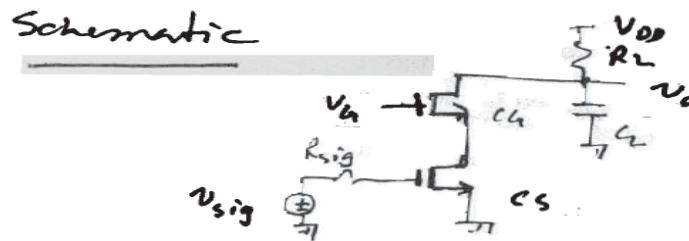


AC Equivalent circuit:

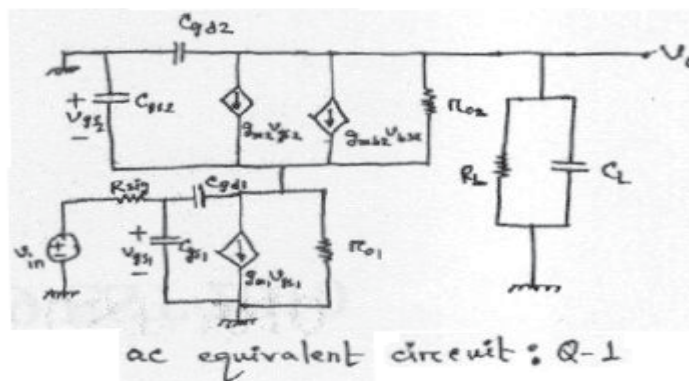

$$V_{gs2} = V_g - V_{s2} = 0 - V_{s2}$$

$$V_{bs2} = V_b - V_{s2} = 0 - V_{s2}$$

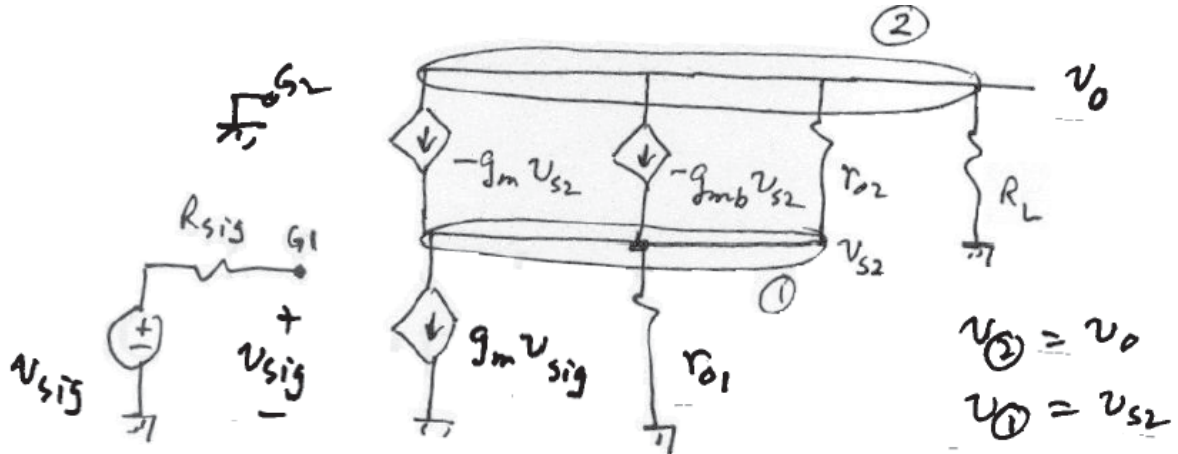For low frequency gain, ignore all C_{gs} and C_{gd}



Consider the 2- node system and derive V_o/V_{sig}

$$\begin{bmatrix} g_{01} + g_{02} & -g_{02} \\ -g_{02} & g_{02} + g_2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -g_m v_{sig} - (g_m + g_{mb})v_1 \\ (g_m + g_{mb})v_1 \end{bmatrix}$$

$$\frac{v_o}{v_{sig}} = - \frac{g_m (g_m + g_{mb} + g_0)}{(g_m + g_{mb})g_L + g_0(g_0 + 2g_L)}$$

Here $g_{01} = g_{02} = g_0 = \frac{1}{r_0}$

Using the values: $\frac{v_o}{v_{sig}} \approx -98.37 \text{ v/v}$

For Dominant pole calculation, note:


For C_{gd1} , the Miller effect amplifications are :

i) At input $(1 + K_1) C_{gd1}$, $K_1 = \frac{g_m}{g_m + g_{mb}} = \frac{1}{1.2} = 0.8$

ii) At output $(1 + \frac{1}{k_1}) C_{gd1} = (1 + 1.2) C_{gd1}$


C_{gd2} does not have miller effect

So the AC equivalent circuit is

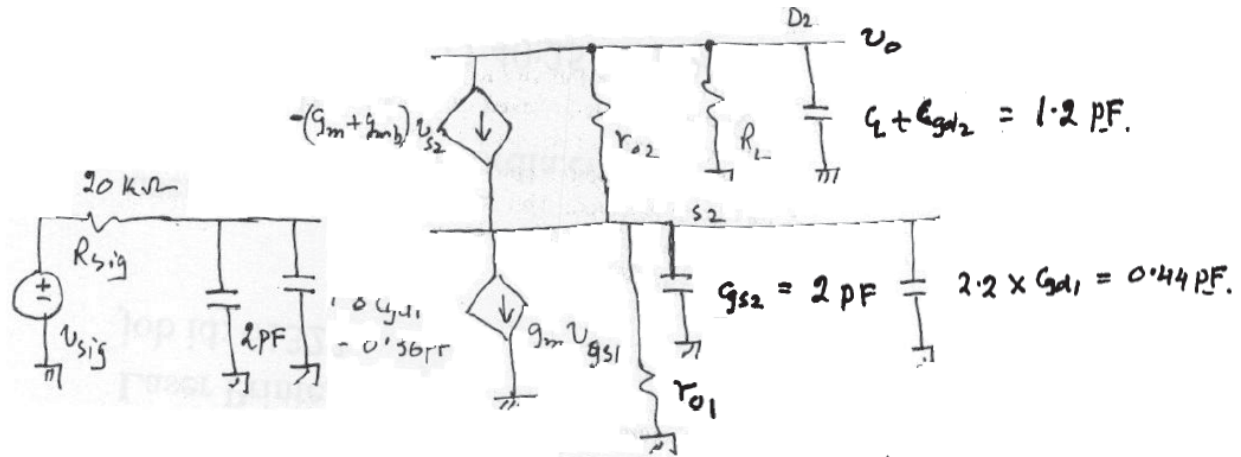

Ignoring r_{o1} and r_{o2} as was done in the class lecture.

CE-CB Cascade

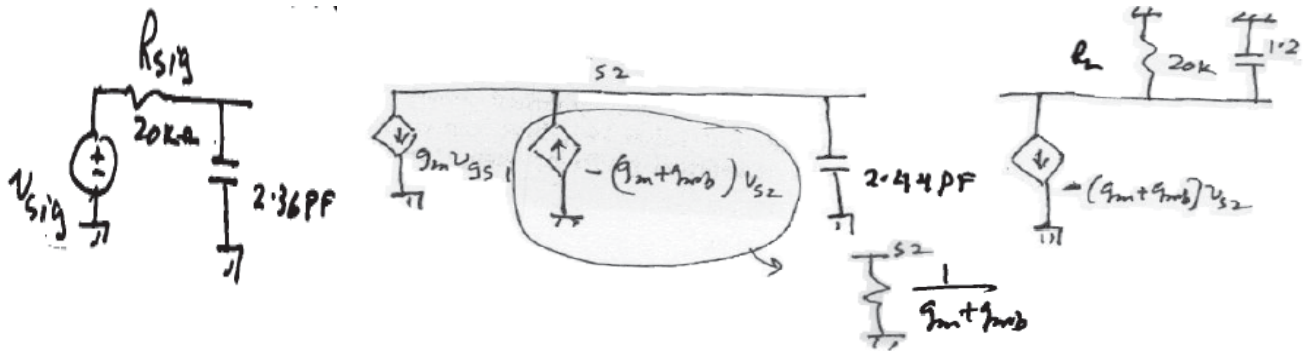

The time constants are:

$$\tau_1 = 2.36 \times 10^{-12} \times 20 \times 10^3 = 4.72 \times 10^{-8} \text{ sec}$$

$$\tau_2 = \frac{2.44 \times 10^{-12}}{1.2 \times 10^{-3}} = 4.07 \times 10^{-10} \text{ sec}$$

$$\tau_3 = 1.2 \times 10^{-12} \times 20 \times 10^3 \text{ sec}$$

τ_1, τ_3 are close enough, so dominant time constant principle may not apply




We will take $\tau_H = \tau_1 + \tau_2 + \tau_3 = f_H = \frac{1}{2\pi} \frac{1}{7.161 \times 10^{-8}} = 2.22 \text{ MHz}$

$$\text{GBW} = |-98.37| \times 2.2 \times 10^6 = 218.6 \text{ MHz}$$

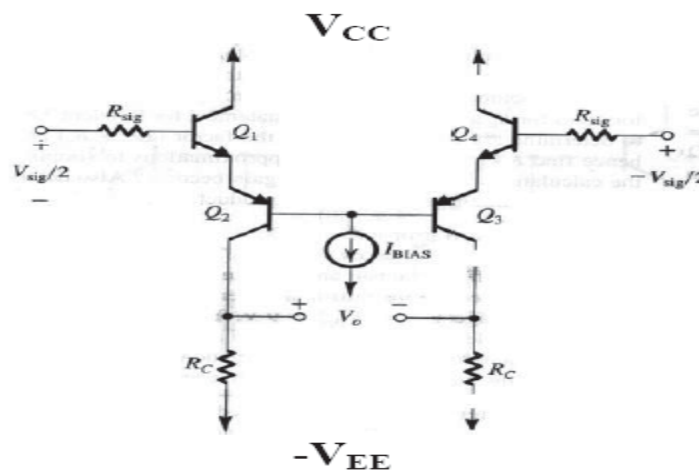7. For the following circuit, let the bias be such that each transistor is operating at $100\text{-}\mu\text{A}$ collector current. Let the BJTs have $h_{fe} = 200$, $f_T = 600 \text{ MHz}$, and $C_\mu = 0.2 \text{ pF}$, and neglect r_o and r_x . Also, $R_{sig} = RC = 50 \text{ k}\Omega$.

Show the ac equivalent circuit.


Find (i) the low-frequency gain, (ii) the high-frequency poles, and (iii) an estimate of the dominant high frequency pole f_H of the system. Now find the GBW (gain-bandwidth) of the system. You may use half-circuit technique.



Hints:

- ~~(i) $A_o = \alpha R_C / [(R_{sig} / (\beta + 1)) + 2r_o]$; where $\beta = h_{fe}$ (ii) $f_{P1} = 1 / [2\pi (R_{sig} \parallel 2r_x) (C_\pi / 2 + C_\mu)]$; $f_{P2} = 1 / [2\pi R_C C_\mu]$; where $2\pi f_1 = g_m / (C_\pi + C_\mu)$, calculate C_π from here. (iii) $f_H = \sqrt{(1/f_{P1})^2 + (1/f_{P2})^2}$; (iv) $\text{GBW} = |A_o| f_H$ (See Later)~~

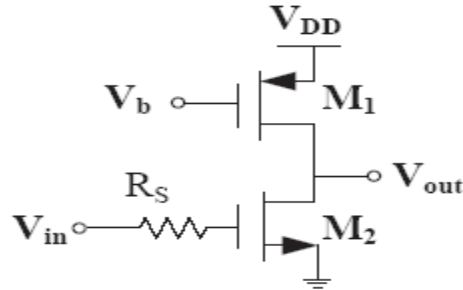
8. In the following circuit assume both transistors operate in saturation and $\lambda \neq 0$. For each transistor you can assume the parasitic capacitances as C_{gsi} , C_{gdi} , ($i=1,2$).



Draw the *ac* equivalent circuit, analyze and derive the expression for the dominant pole frequency.

Hints:

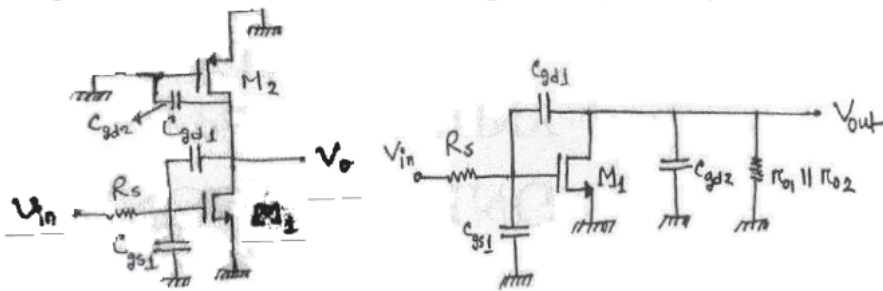Simplified circuit models for small signal analysis are given below:



~~Analyzing the small signal equivalent circuit we get,~~

~~$\omega_{P1} = 1 / \{ (1 + g_{m1}(r_{o1} || r_{o2})) C_{gd1} R_s + R_s C_{gs1} + (r_{o1} || r_{o2}) (C_{gd1} + C_{gd2}) \}$~~

~~$\omega_{P2} = \{ (1 + g_{m1}(r_{o1} || r_{o2})) C_{gd1} R_s + R_s C_{gs1} + (r_{o1} || r_{o2}) (C_{gd1} + C_{gd2}) \} / [R_s (r_{o1} || r_{o2}) (C_{gs1} C_{gd1} + C_{gd2} C_{gd1} + C_{gs1} C_{gd2})]$~~ (See Later)




5. $I = 200 \mu A = \mu_n C_{ox} \frac{W}{L} V_{ov}^2$ (square-law)

with $V_{ov} = 0.25$ $\mu_n C_{ox} \frac{W}{L} = 3.2 \times 10^{-3}$

$g_m = \mu_n C_{ox} \frac{W}{L} \cdot V_{ov} = 6.4 \times 10^{-3} \times 0.25 = 1.6 \times 10^{-3}$

Low freq. ac equiv:

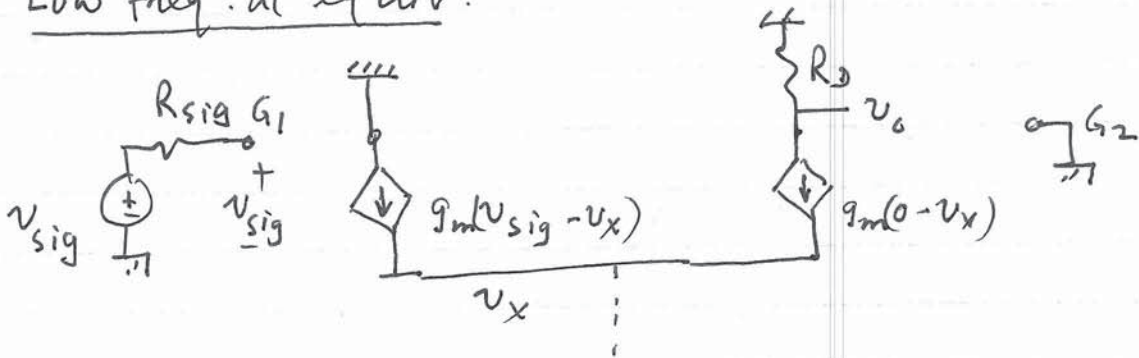


$v_o = g_m v_x R_D$, but $-g_m(v_{sig} - v_x) - g_m(-v_x) = 0$



gives $v_x = v_{sig} / 2$

$v_o = g_m R_D \frac{v_{sig}}{2}$; $v_o / v_{sig} |_{\text{Low freq.}} = \frac{g_m R_D}{2}$

H.F. equiv. cnt:

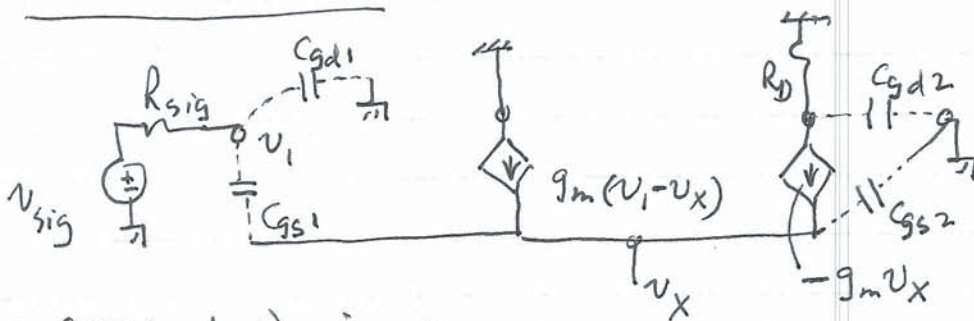

By OCTC technique:

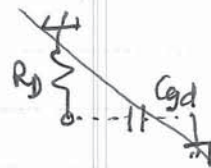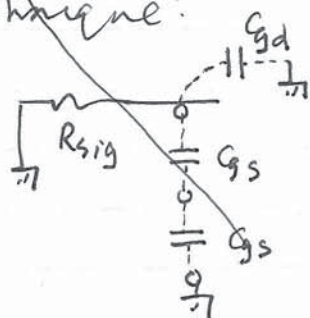


~~I-sources~~
→ ∞
resistance

5 (Cont.)

By OCTC technique:

1) For G_{d1} : $\tau_{gd1} = G_{d1} \cdot R_{sig}$

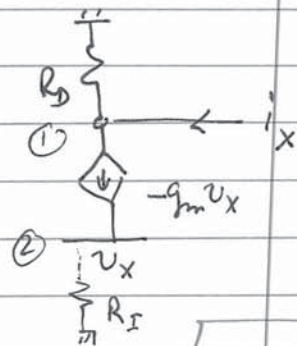2) For G_{d2} : $\tau_{gd2} = G_{d2} \cdot R_D$



By NAM
$$\begin{pmatrix} g_D & 0 \\ 0 & g_I \end{pmatrix} \begin{pmatrix} v_1 \\ v_x \end{pmatrix} = \begin{pmatrix} i_x + g_m v_x \\ -g_m v_x \end{pmatrix}$$

By basic rule:

$$\begin{bmatrix} g_D & -g_m \\ 0 & g_I + g_m \end{bmatrix} \begin{bmatrix} v_1 \\ v_x \end{bmatrix} = \begin{bmatrix} i_x \\ 0 \end{bmatrix}$$

$-i_x + \frac{v_1}{R_D} - g_m v_x = 0$

$\frac{v_x}{R_I} + g_m v_x = 0$


So $v_x = 0$;
Then $i_x = v_1 / R_D$; $\frac{v_1}{i_x} = R_D$.
 $\frac{g_m i_x}{g_D g_m} = \frac{i_x}{g_D}$ \uparrow R_{Ther} .

$\Delta = g_D g_I + g_D g_m$

if $g_I \rightarrow 0$
$$v_1 = \frac{1}{g_D g_m} \begin{bmatrix} i_x & -g_m \\ 0 & g_I + g_m \end{bmatrix} = \frac{g_m i_x}{g_D g_m} = \frac{i_x}{g_D}$$

$\frac{v_1}{i_x} = R_D \uparrow R_{Ther}$


3) For G_{s1}

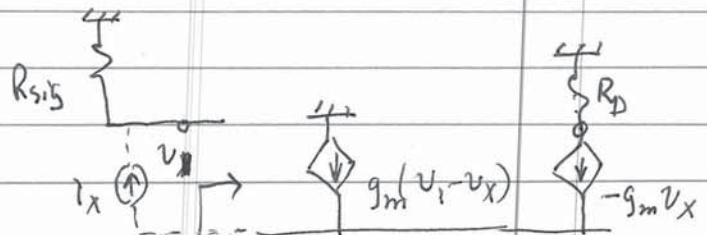

$$\begin{bmatrix} g_{sig} & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & g_D \end{bmatrix} \begin{bmatrix} v_1 \\ v_x \\ v_0 \end{bmatrix} = \begin{bmatrix} v_x \\ i_x \\ -i_x + g_m v_1 - g_m v_x - g_m v_x \\ +g_m v_x \end{bmatrix}$$

$$\begin{bmatrix} g_{sig} & 0 & 0 \\ -g_m & 2g_m & 0 \\ 0 & -g_m & g_D \end{bmatrix} \begin{bmatrix} v_1 \\ v_x \\ v_0 \end{bmatrix} = \begin{bmatrix} i_x \\ -i_x \\ 0 \end{bmatrix}$$

For G_{sig} by basic cut anal.

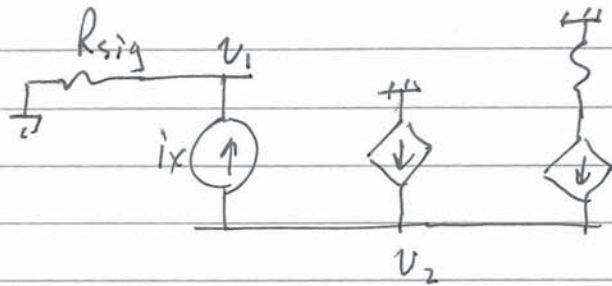

$$\text{At } v_1 : \frac{v_1}{R_{sig}} - i_x = 0 \quad ; \quad v_1 = i_x R_{sig}$$

$$\text{At } v_2 : +i_x - g_m(v_1 - v_2) - g_m(0 - v_2) = 0$$

$$i_x - g_m v_1 + g_m v_2 + g_m v_2 = 0$$

$$\frac{v_1}{R_{sig}} - g_m v_1 + 2g_m v_2 = 0.$$

$$v_1 \left(\frac{1}{R_{sig}} - g_m \right) + v_2 \cdot 2g_m = 0.$$

$$v_2 = -v_1 \left[\frac{1}{2R_{sig}g_m} - \frac{1}{2} \right] = -\frac{v_1}{2} \left[\frac{1}{R_{sig}g_m} - 1 \right]$$

$$v_1 - v_2 = v_1 + \frac{v_1}{2} \left(\frac{1}{R_{sig}g_m} - 1 \right)$$

$$= v_1 + \frac{v_1}{2} \left(\frac{1}{R_{sig}g_m} - 1 \right)$$

$$\frac{v_1 - v_2}{i_x} = \frac{v_1 + \frac{v_1}{2} \left(\frac{1}{R_{sig}g_m} - 1 \right)}{i_x} = R_{sig} \left[1 + \frac{1}{2R_{sig}g_m} - \frac{1}{2} \right]$$

$$= R_{sig} \left(\frac{1}{2} + \frac{1}{2R_{sig}g_m} \right)$$

$$= R_{sig} + \frac{R_{sig}}{2} \left(\frac{1}{R_{sig}g_m} - 1 \right)$$

$$= R_{sig} + \frac{1}{2g_m} - \frac{R_{sig}}{2} = \frac{R_{sig}}{2} + \frac{R_m}{2} = \frac{1}{2}(R_{sig} + R_m)$$

5 (cont.)

$$\Delta = g_{sig} \cdot 2g_m - g_D$$

$$v_i = \frac{1}{\Delta} \cdot \begin{vmatrix} i_x & 0 & 0 \\ -i_x & 2g_m & 0 \\ 0 & -g_m & g_D \end{vmatrix} = \frac{1}{\Delta} \cdot i_x \cdot 2g_m g_D$$

$$v_x = \frac{1}{\Delta} \begin{vmatrix} g_{sig} & i_x & 0 \\ -g_m & -i_x & 0 \\ 0 & 0 & g_D \end{vmatrix} = \frac{1}{\Delta} \left[\begin{matrix} i_x \cdot g_m g_D \\ -g_{sig} i_x g_D \end{matrix} \right]$$

$$= \frac{1}{\Delta} i_x g_D (g_m - g_{sig})$$


$$v_i - v_x = \frac{1}{\Delta} \cdot i_x \cdot \cancel{g_m g_D} = i_x \frac{g_{sig} g_D}{g_{sig} \cdot 2g_m \cdot g_D}$$

$$= \frac{1}{\Delta} \cdot i_x (2g_m g_D - g_m g_D + g_D g_{sig}) = i_x \frac{1}{2g_{sig}}$$

$$\frac{v_i - v_x}{i_x} = \frac{g_D (g_m + g_{sig})}{g_D \cdot 2g_m g_{sig}} = \frac{1}{2} \left(\frac{1}{g_{sig}} + \frac{1}{g_m} \right)$$

$$3) T_{gs1} = \frac{C_{gs1} \cdot R_{sig}}{2} = \frac{1}{2} (R_{sig} + R_m)$$

4) For g_{s2}

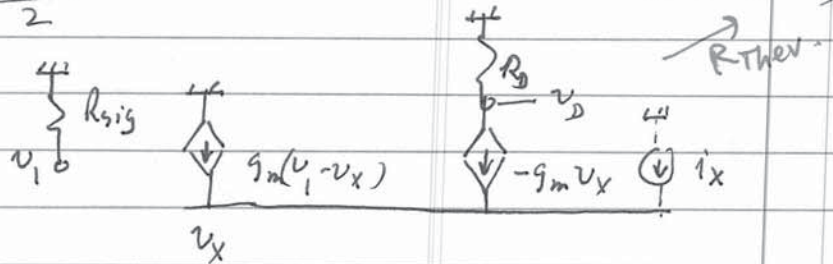

$$\begin{pmatrix} g_{sig} & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & g_D \end{pmatrix} \begin{pmatrix} v_i \\ v_x \\ v_D \end{pmatrix} = \begin{pmatrix} 0 \\ i_x + g_m v_i - g_m v_x - g_m v_x \\ g_m v_x \end{pmatrix}$$

$$\begin{pmatrix} g_{sig} & 0 & 0 \\ -g_m & 2g_m & 0 \\ 0 & -g_m & g_D \end{pmatrix} \begin{pmatrix} v_i \\ v_x \\ v_D \end{pmatrix} = \begin{pmatrix} 0 \\ i_x \\ 0 \end{pmatrix}$$

5 (cont.)

$$\Delta = \text{same as before} = g_{sig} \cdot 2g_m \cdot g_D$$

$$v_x = \frac{1}{\Delta} \cdot \begin{vmatrix} g_{sig} & 0 & 0 \\ -g_m & i_x & 0 \\ 0 & 0 & g_D \end{vmatrix} = \frac{1}{\Delta} \cdot g_{sig} \cdot i_x \cdot g_D = \frac{g_{sig} \cdot i_x \cdot g_D}{g_{sig} \cdot 2g_m \cdot g_D}$$

$$v_x = \frac{i_x}{2g_m} ; \quad \frac{v_x}{i_x} = \frac{1}{2g_m} = \frac{1}{2} R_m ; \quad R_m = \frac{1}{g_m}$$


Then:

R_{Ther}

$$\tau_{gs2} = C_{gs2} \cdot \frac{1}{2g_m} = \frac{C_{gs2} R_m}{2}$$

Calculate after substitutions.

By basic ckt anal.?

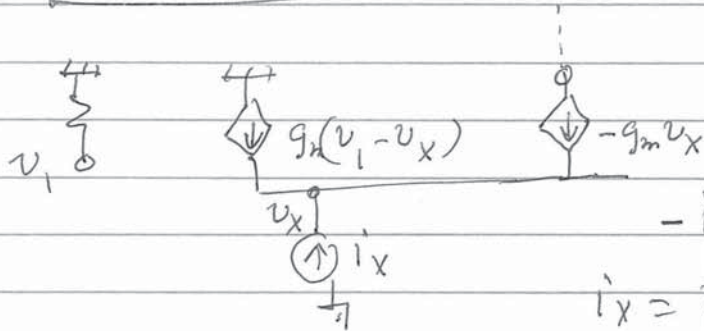

$$v_1 = 0$$


$$-i_x + g_m v_x + g_m v_x = 0$$

$$i_x = 2g_m v_x ; \quad \frac{v_x}{i_x} = \frac{1}{(2g_m)} = \frac{1}{2} R_m$$


R_{Ther}

7

Half circuit (see class lecture note)

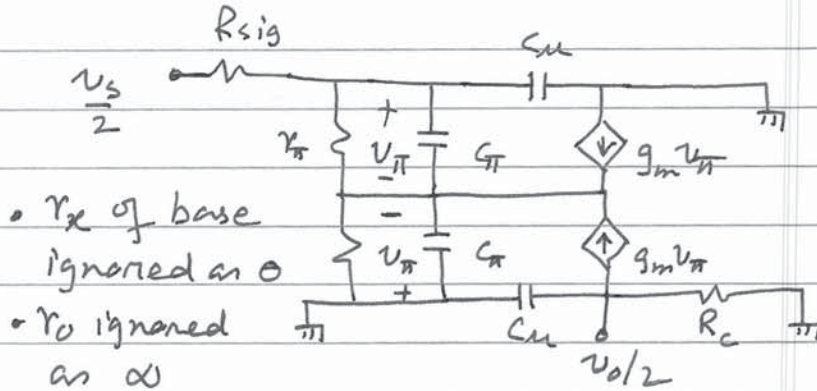

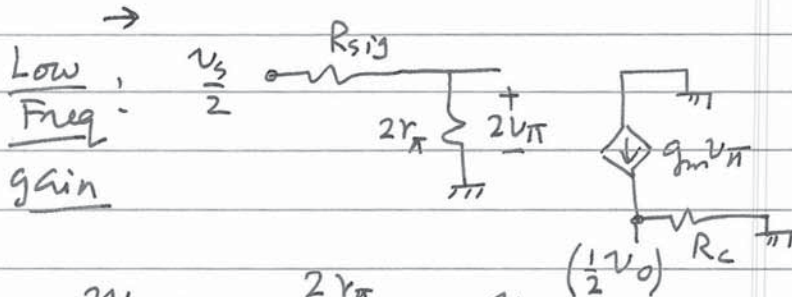- r_x of base ignored as ∞
- r_o ignored as ∞




$$2V_{\pi} = \frac{2r_{\pi}}{R_{sig} + 2r_{\pi}} \cdot \frac{v_s}{2} \quad ; \quad v_{\pi} = \frac{r_{\pi}}{R_{sig} + 2r_{\pi}} \cdot \frac{v_s}{2}$$

$$\frac{v_o}{2} = \frac{g_m r_{\pi} R_c}{R_{sig} + 2r_{\pi}} \cdot \frac{v_s}{2} \quad ; \quad \frac{v_o}{v_s} = \frac{R_c (h_{fe} + 1)}{R_{sig} + 2r_{\pi}} = A_{M}$$

subst. for r_{π} , R_{sig} ... etc.

HF. equiv. circ.

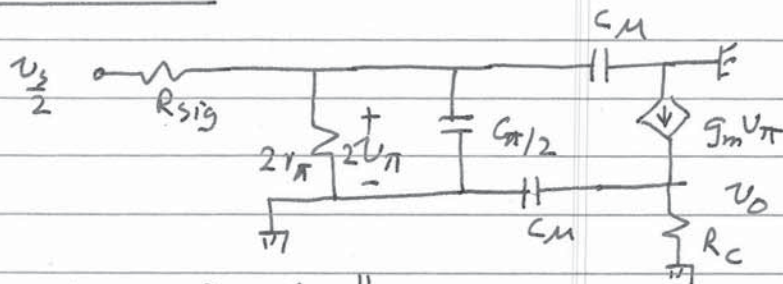

$$\tau_1 = (C_{\mu} + \frac{C_{\pi}}{2}) \cdot (2r_{\pi} \parallel R_{sig})$$

$$\tau_2 = C_{\mu} R_c$$

$$\omega_f = 2\pi \times 600 \times 10^6 = \frac{g_m}{C_{\pi} + C_{\mu}}$$

$$0.004 < g_m = \frac{I_c}{V_T} = \frac{0.1 \text{ mA}}{25 \text{ mV}} \quad ; \quad \text{find } C_{\pi} \because C_{\mu} = 0.2 \text{ pF.}$$

↓ 0.86 pF.

7


$$\omega_H = \frac{1}{\tau_1 + \tau_2}$$

$$GBW = A_M \omega_H \text{ rad/sec.}$$

X

8

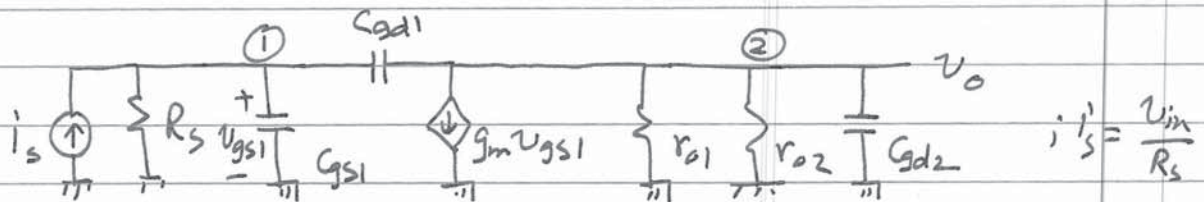AC equivalent circuit for nodal analysis:



$$\begin{bmatrix} g_s + s(C_{gs1} + C_{gd1}) & -sC_{gd1} \\ -sC_{gd1} & g_{o1} + g_{o2} + sC_{gd1} + sC_{gd2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i'_s \\ -g_m v_{gs1} \end{bmatrix}$$

$$\therefore v_{gs1} = v_1$$

$$\begin{bmatrix} g_s + s(C_{gs1} + C_{gd1}) & -sC_{gd1} \\ g_m - sC_{gd1} & g_{o1} + g_{o2} + s(C_{gd1} + C_{gd2}) \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i'_s \\ 0 \end{bmatrix}$$

A of the matrix:

$$D(s) = \{g_s + s(C_{gs1} + C_{gd1})\} \{g_{o1} + g_{o2} + s(C_{gd1} + C_{gd2})\} + sC_{gd1}(g_m - sC_{gd1})$$

Expanding:

$$D(s) = As^2 + Bs + C$$

$$A = C_{gs1} C_{gd1} + C_{gd1} C_{gd2} + C_{gs1} C_{gd2}$$

$$B = g_s (C_{gd1} + C_{gd2}) + C_{gs1} (g_{o1} + g_{o2}) + g_m C_{gd1} + C_{gd1} (g_{o1} + g_{o2})$$

$$C = g_s (g_{o1} + g_{o2})$$

$$\text{Dominant pole: } C/B$$