

# ELEC 312, Feb 2013, NT test (sol/hint)

Note Title

2/17/2013

Q1:


$$I_0 = I_{C2} = I_{S2} \exp(V_{BE2}/V_T) = 2 \text{ mA}$$

$$\therefore I_{S1} = 10^{-14} \text{ Amp} = 4 \text{ times } I_{S2}$$

$$I_{C1} = 4 I_{C2} = 8 \text{ mA}$$

$$\text{Then } I_{B1} = \frac{8 \text{ mA}}{100}, \quad I_{B2} = \frac{2 \text{ mA}}{100}$$
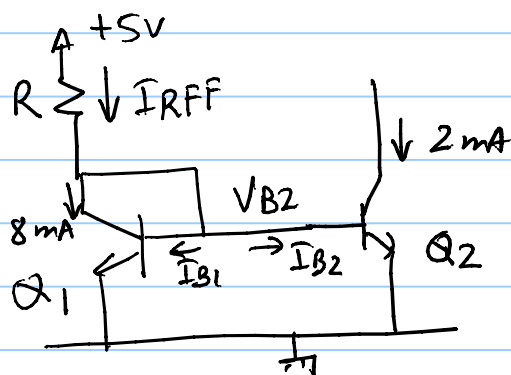
$$I_{REF} = I_{C1} + I_{B1} + I_{B2} = (8 + 0.08 + 0.02) \\ = 8.1 \text{ mA}$$



$$V_{BE2} = V_{B2} = V_T \ln\left(\frac{2 \text{ mA}}{0.25 \times 10^{-14} \text{ A}}\right) \\ = 0.025 \times 27.4 = 0.685 \text{ V}$$


$$\text{Then } \frac{5 \text{ V} - 0.685}{R} = I_{REF}$$

$$\text{Thus } R = 532.7 \text{ ohms}$$

\_\_\_\_\_ X \_\_\_\_\_

Q.2.

AC equivalent circuit is:

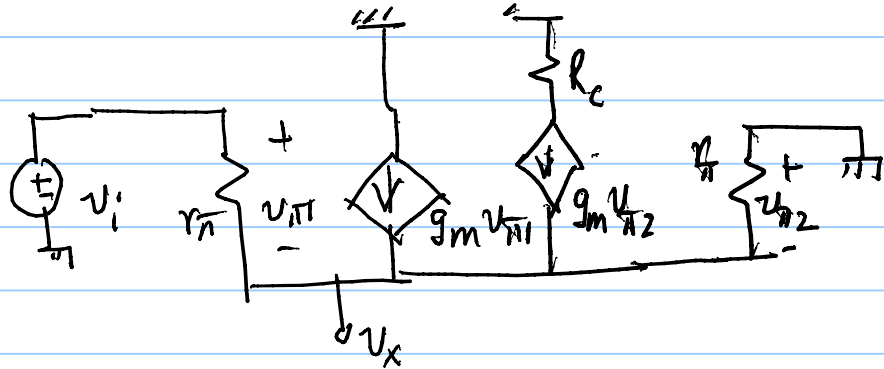

KCL

$$-(v_i - v_x)g_\pi - g_m(v_i - v_x)$$

$$-g_m(0 - v_x) + v_x g_\pi = 0$$

$$-(g_\pi + g_m)v_i + v_x(g_\pi + g_m + g_m + g_\pi) = 0$$

$$\text{So } v_x = + \frac{g_m + g_\pi}{2g_m + 2g_\pi} v_i = \frac{v_i}{2}$$


$$v_o = -g_m v_{\pi 2} R_c$$

$$= -g_m(0 - v_x) R_c = g_m R_c \frac{v_i}{2}$$

$$\text{So } \frac{v_o}{v_i} = \frac{g_m R_c}{2}$$




Q 4: The ac equivalent circuit is:

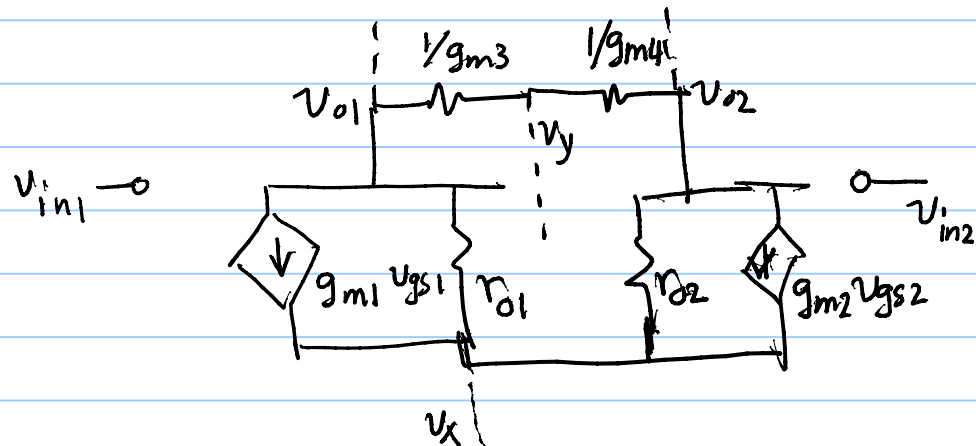

--- means open circuit i.e.  $R \rightarrow \infty$

Further, we used

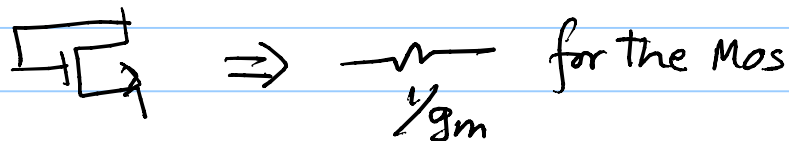

$$v_{out} = v_{o1} - v_{o2}$$

KCL @  $v_{o1}$  gives

$$g_{m1}(v_{in1} - v_x) + (v_{o1} - v_x)g_{o1} + (v_{o1} - v_y)g_{m3} = 0$$

where  $g_{o1} = \frac{1}{r_{o1}}$ , similarly,

@  $v_{o2}$  node, KCL is

$$g_{m2}(v_{in2} - v_x) + (v_{o2} - v_x)g_{o2} + (v_{o2} - v_y)g_{m4} = 0$$

Considering matched pair of transistors

$$g_{m1} = g_{m2}; \quad g_{o1} = g_{o2}; \quad g_{m3} = g_{m4}$$

By subtraction

Q4 (contd.)

$$g_{m1}(v_{in1} - v_{in2}) + g_{o1}(v_{o1} - v_{o2}) + g_{m3}(v_{o1} - v_{o2}) = 0$$

$$g_{m1}(v_{in1} - v_{in2}) + (g_{m3} + g_{o1})(v_{o1} - v_{o2}) = 0$$

$$\text{So } \frac{v_{o1} - v_{o2}}{v_{in1} - v_{in2}} = - \frac{g_{m1}}{g_{m3} + g_{o1}} = \frac{v_{out}}{v_{in1} - v_{in2}}$$