

Course	Number		Section
Electronics I I	ELEC 312		F
Examination	Date	Time	# of pages
Mid-Term Test	October 21, 2012	75 minutes	3
Instructor(s)			
Dr. R. Raut			
Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)			
Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes			
NO formula sheet is allowed. ONLY ENCS approved calculator is allowed.			
Special Instructions:			
<u>Write your ID#</u> on the front page of your answer book Attempt <u>all questions</u> . Show all steps clearly in neat and legible handwriting. Students are required to <u>return question paper</u> together with exam booklet(s).			

***** Some useful formulae*****

BJT:

$$r_e = \alpha / g_m \quad g_m = I_C / V_T \quad r_\pi = h_{fe} / g_m \quad h_{fe} = i_c / i_b \quad r_o = V_A / I_C$$

$$\alpha = \frac{h_{fe}}{h_{fe} + 1} \quad V_T = \frac{kT}{q} \approx 25mV \text{ at room temperature}$$

DIODE:

$$I = I_s \exp(v_{BE} / V_T)$$

MOSFET: $I_D = \mu C_{ox} \frac{W}{2L} (V_{GS} - V_{TH})^2$ (ignoring channel modulation effect, and assuming that the MOSFET is working in the saturation region)

$$g_m = \sqrt{\frac{2\mu C_{ox} W I_D}{L}}$$

Q.1: Consider the amplifier in Figure 1, built with MOS transistors. The transistor M3 functions as an active load for the transistors M1 and M2. M1 is a common source stage while M2 is a common gate stage.

- (a) Draw the small signal ac equivalent circuit for the system. Ignore the *body effect* for M2.
- (b) Produce the nodal admittance matrix for the system with a goal to find the small signal voltage gain v_o/v_i . You do not have to calculate the voltage gain.

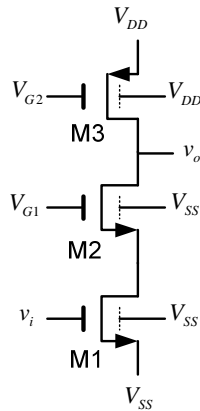


Figure 1:

Q.2: Figures 2(a)-(b) show the *schematics* of a basic and an improved current mirror respectively using MOSFET devices.

- (a) Draw the pertinent *ac equivalent* circuits for the two circuits.

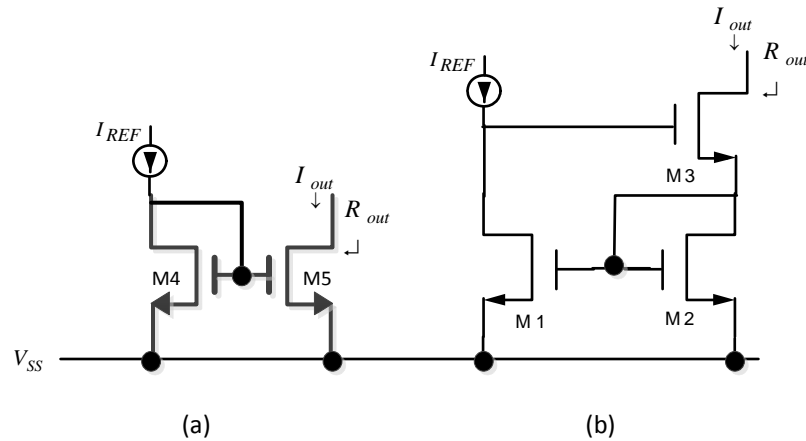


Figure 2:

Given (for all transistors), $\mu C_{ox} = 100 \mu A/V^2$, $W/L=10$, $V_{SS} = -5 V$, $V_{TH} = 0.8 V$, $V_{DD} = 5 V$, $V_{GS} - V_{TH} = 1 V$, and $V_A = 20 V$. Approximate analysis gives the output resistance of the mirror in Fig.2(b) as $R_{out} = g_m r_o^2$, where r_o is the output resistance of each MOSFET device.

- (b) Compare the numerical values of the output resistances of the mirrors in Figs. 2(a) and 2(b)

Q.3: The BJT differential amplifier in Figure 3 is supplied with a differential ac signal $v_D = v_1 - v_2$. The differential output signal is given by the expression

$$v_{o1} - v_{o2} = R_c I \left[\frac{\exp(-v_D/V_T)}{1 + \exp(-v_D/V_T)} - \frac{\exp(v_D/V_T)}{1 + \exp(v_D/V_T)} \right]$$

Where, V_T is the thermal voltage (~ 25 mV). The bias current I is arranged to be 5 mA

Determine the voltage gain $(v_{o1}-v_{o2})/v_D$, when (i) $v_D=10$ mV and (ii) $v_D= 1$ mV. How do these compare with the theoretical small signal voltage gain value of $|g_m R_c|$, where g_m is the trans-conductance of each BJT device, and R_c is the resistance at the collector.

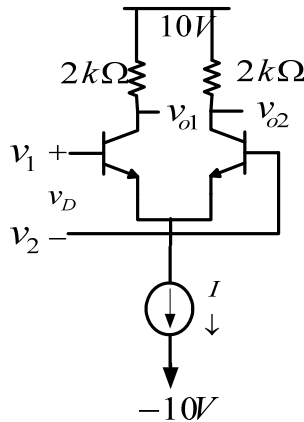


Figure 3:

Q.4. Figure 4 illustrates an implementation of a differential amplifier with active load using complementary BJT devices. The bias current I_{EE} is 2 mA. The early voltages are :

$$V_{AN} \text{ (for NPN BJT)} = 25 \text{ V, } V_{AP} \text{ (for PNP BJT)} = 50 \text{ V.}$$

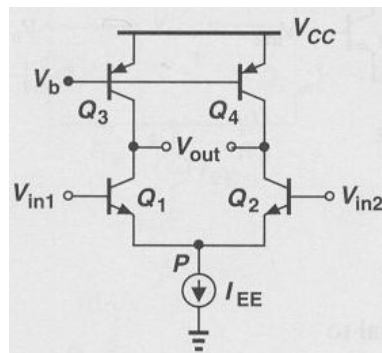



Figure 4:

- Draw the ac equivalent circuit for the differential amplifier. Assume that the source I_{EE} has an ac resistance of R_I .
- What will be the differential voltage gain $V_{out}/(V_{in1} - V_{in2})$ when V_{in1} and V_{in2} are *balanced differential signals*?

Q1.

(a) M3 has source and gate at DC ($= 0$ ac). So it acts as a current-source active load $= r_{o3}$
 M2 has gate at DC. So the $g_{m2} v_{gs2}$ source becomes $g_{m2} (0 - v_{s2}) = -g_{m2} v_{s2}$

The ac equivalent circuit is:

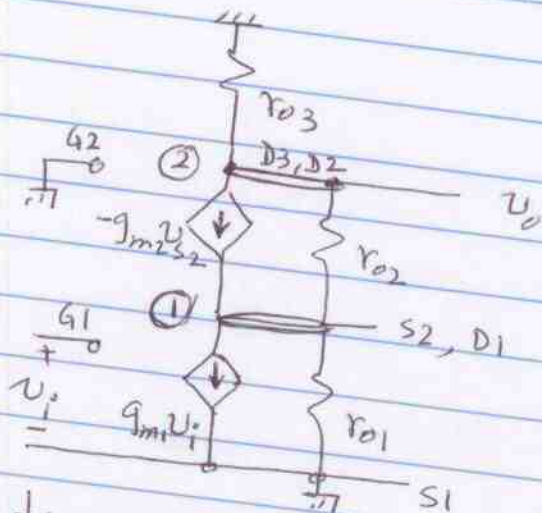

(b) This is a two node system with v_i is ~~an~~ input node. Since v_i does not have any component attached, we will exclude it in formulating the nodal admittance matrix (NAM). By inspection (and letting $g = 1/r$)

$$\begin{matrix} \textcircled{1} & \textcircled{2} \\ \begin{bmatrix} g_{o1} + g_{o2} & -g_{o2} \\ -g_{o2} & g_{o2} + g_{o3} \end{bmatrix} & \begin{bmatrix} v_{\textcircled{1}} \\ v_{\textcircled{2}} \end{bmatrix} = \begin{bmatrix} -g_{m1} v_i - g_{m2} v_{s2} \\ g_{m2} v_{s2} \end{bmatrix} \end{matrix}$$

But $v_{s2} = v_{\textcircled{1}}$. Substituting and moving on left side (ie. $g_{m2} v_{s2} = g_{m2} v_{\textcircled{1}} \rightarrow -g_{m2} v_{\textcircled{1}}$ on left)

$$\begin{bmatrix} g_{m2} + g_{o1} + g_{o2} & -g_{o2} \\ -g_{m2} - g_{o2} & g_{o2} + g_{o3} \end{bmatrix} \begin{bmatrix} v_{\textcircled{1}} \\ v_{\textcircled{2}} \end{bmatrix} = \begin{bmatrix} -g_{m1} v_i \\ 0 \end{bmatrix} \text{ (soln.)}$$


Q2:

For Fig. 2(a), it is a basic current mirror made from M4, M5. R_{out} for M5 is simply r_o of M5.


$$r_o = \frac{V_A}{I_{REF}}, \text{ so } I_{REF} \text{ need be found out.}$$

Q2.
For (a)

AC equiv. circuit of Fig 2(a) will be

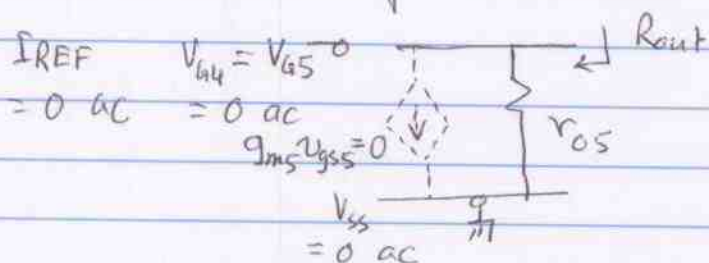

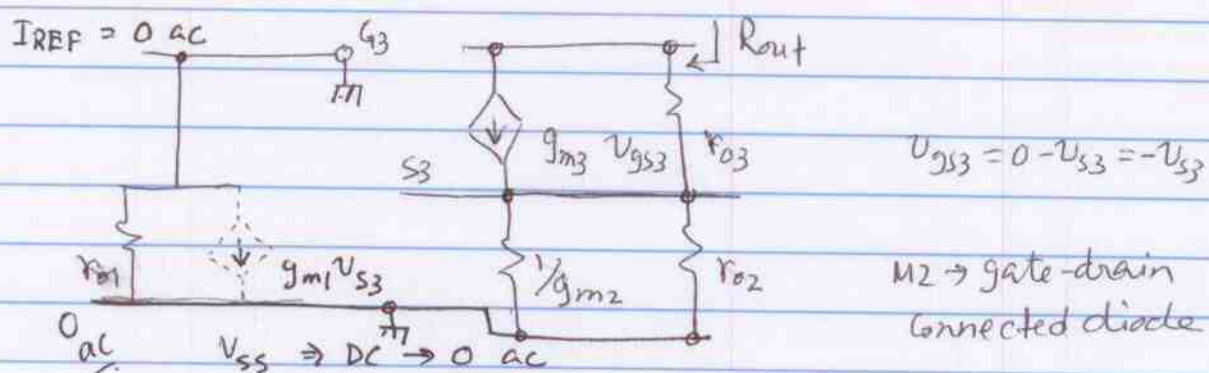For (b), remembering I_{REF} is a DC value i.e. zero 'ac' the ac equivalent circuit will be:



In Q 2(b) we can use $g_m = g_{m3} = g_{m2} = g_{m1}$ etc.

$$I_{REF} = \mu C_{ox} \frac{W}{2L} (V_{gs} - V_{TH})^2 = 100 \times \frac{10}{2} \times 1^2 = 500 \mu A$$

$$\text{So } r_o \text{ for all the MOSFET} = \frac{V_A}{I_{REF}} = \frac{20}{.5} \text{ k}\Omega$$

$$r_o = 40 \text{ k}\Omega$$

$$g_m = \sqrt{\frac{2\mu C_{ox} W}{L} I_D} \text{ Where } I_D = I_{out} = I_{REF}$$

Q2 (b) We take $I_{out} = I_{REF}$ since no specific data
(cont.) are given to make any difference. The data set
given implies all transistors are identical.

$$\begin{aligned} \text{So } g_m &= \sqrt{2 \times 100 \times 10 \times 500} && \leftarrow \text{given formula} \\ &\quad \downarrow \quad \downarrow \quad \downarrow \\ &\quad \mu\text{Cx} \quad \frac{W}{L} \quad I_D = I_{REF} = I_{out} \\ &= 1000 \mu\text{S} = 1 \text{ milli mho} \end{aligned}$$

$$\text{So } R_{out} \text{ for Fig 2b) circuit is } = 1 \times 10^3 \times 40 \times 10^3 \times 40 \times 10^3$$

(by given formula)

$$\text{So } R_{out} \Big|_{2b} = 1600 \text{ k}\Omega = 1.6 \text{ M}\Omega$$

$$\text{Comparison: } \left. \begin{aligned} R_{out} \Big|_{2a} &= r_o = 40 \text{ k}\Omega \\ R_{out} \Big|_{2b} &= 1.6 \text{ M}\Omega \end{aligned} \right\}$$

Q3: $g_m R_c = \frac{I_c}{V_T} \cdot R_c = \frac{I/2}{V_T} R_c = \frac{2.5 \text{ mA}}{25 \text{ mV}} \times 2000$

$g_m R_c = 200 \text{ V/V} \rightarrow \text{Small signal gain.}$

(i) For $v_D = 10 \text{ mV}$

$\exp(v_D/V_T) = \exp(10/25) = 1.4918$

$\exp(-v_D/V_T) = 0.6703$

Then $\frac{\exp(-v_D/V_T)}{1 + \exp(-v_D/V_T)} = \frac{0.6703}{1 + 0.6703} = 0.401$

$\frac{\exp(v_D/V_T)}{1 + \exp(v_D/V_T)} = \frac{1.4918}{2.4918} = 0.5987$

Then $v_{O1} - v_{O2} = 2000 \times 5 \times 10^{-3} [0.401 - 0.5987]$
 $= -1.977$

Gain = $-\frac{1.977}{10 \text{ mV}} = -197.7 \text{ V/V}$

(ii) For $v_D = 1 \text{ mV}$

$\exp(v_D/V_T) = \exp(1/25) = 1.04$

$\exp(-v_D/V_T) = 0.96$

$\frac{\exp(-v_D/V_T)}{1 + \exp(-v_D/V_T)} = \frac{0.96}{1.96} = 0.489$

$\frac{\exp(v_D/V_T)}{1 + \exp(v_D/V_T)} = \frac{1.04}{2.04} = 0.509$

Q3: Case $v_D = 1 \text{ mV}$

$$\text{(cont.) } v_{o1} - v_{o2} = 2000 \times 5 \times 10^{-3} [0.489 - 0.509]$$
$$= -0.2 \text{ V}$$

$$\text{Gain} = - \frac{0.2}{1 \text{ mV}} = -200 \text{ v/v.}$$


For $v_D = 1 \text{ mV}$ which is $\ll V_T$, the gain $\rightarrow -200$ exactly matches with that given by the formula $|g_m R_c|$ in magnitude.

For $v_D = 10 \text{ mV}$ which is $< V_T$, the gain is $\rightarrow -197.7$ very close to the theoretical value $|g_m R_c| \rightarrow +200$.

Q4

Q_3, Q_4 have emitters connected to DC (V_{CC}) and bases connected to DC (V_B). These are functioning like current source active loads.

(a) The ac equivalent circuit is:

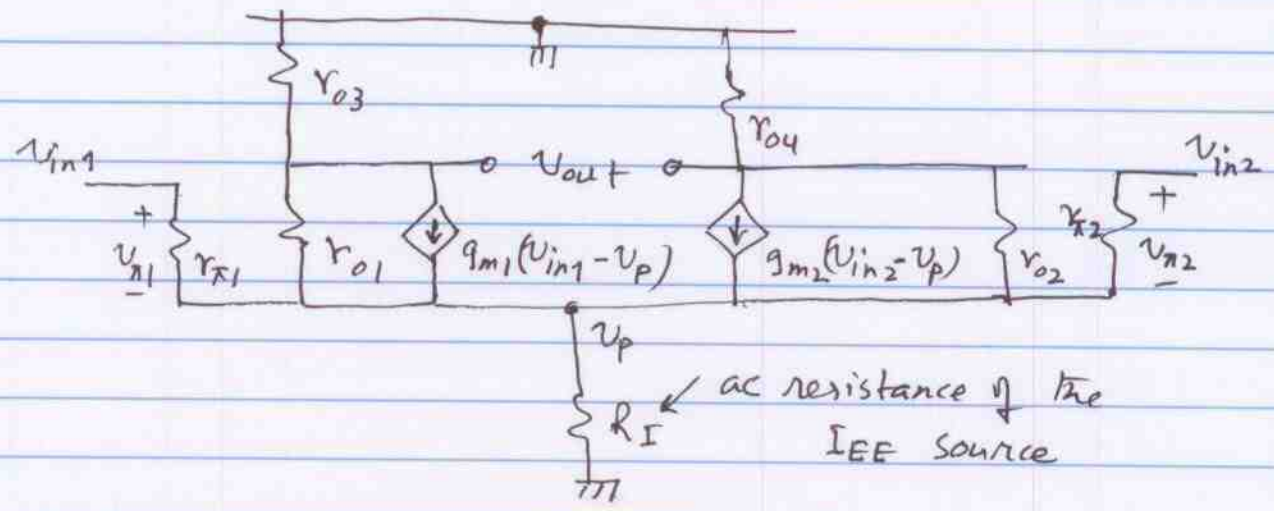


(b) When v_{in1}, v_{in2} are balanced differential signals, $v_p = 0$ (see lecture note derivation)

Each half of the circuit behaves as a CE-BJT amplifier.

Then
$$v_{o1} = -g_{m1}(v_{in1}) \cdot r_{o1} \parallel r_{o3}$$

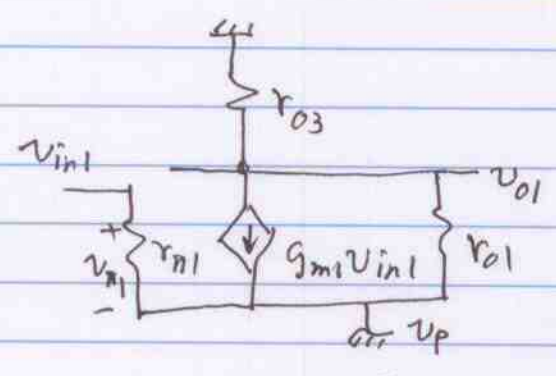Similarly,
$$v_{o2} = -g_{m2}(v_{in2}) \cdot r_{o2} \parallel r_{o4}$$



Assuming the BJTs are matched by pairs (i.e. $Q_3 \cong Q_4, Q_1 \cong Q_2$)

$$v_{out} = v_{o1} - v_{o2} = -g_{mn} \cdot r_{on} \parallel r_{op} v_{in1} + g_{mn} r_{on} \parallel r_{op} v_{in2}$$

Q4 (contd.)

$$\text{Note: } r_{o1} = r_{o2} = r_{on} \\ r_{o3} = r_{o4} = r_{op} \\ g_{m1} = g_{m2} = g_{mn}$$

$$V_{out} = V_{o1} - V_{o2} \\ = -g_{mn} r_{on} \parallel r_{op} (V_{in1} - V_{in2})$$

$$\therefore \frac{V_{out}}{V_{in1} - V_{in2}} = -g_{mn} \cdot r_{on} \parallel r_{op}$$

In the above

$$r_{o1} = r_{o2} = r_{on}; \quad r_{o3} = r_{o4} = r_{op},$$

$$g_{m1} = g_{m2} = g_{mn}$$

From the given data: $I_{C1} = I_{C2} = I_{EE}/2 = 1\text{mA}$

$$r_{op} = \frac{V_{AP}}{I_C} = \frac{5\text{V}}{1\text{mA}} = 50\text{K}\Omega$$

$$r_{on} = \frac{V_{AN}}{I_C} = \frac{2.5\text{V}}{1\text{mA}} = 25\text{K}\Omega$$

$$g_{mn} = \frac{1\text{mA}}{25\text{mV}} = 0.04\text{mA/V}$$

$$\text{Voltage gain} = -0.04 \times 25\text{K}\Omega \parallel 50\text{K}\Omega = -666.67\text{V/V}$$