

Electronics -II (ELEC 312), Winter 2009 class
Mid-term test (March 6, 2009)

(Time: 45 minutes Instructor: Dr. R. Raut)

Student ID#

Name:

Q.1: Consider the amplifier in Figure 1, built with MOS transistors. The transistor M3 functions as an active load for the transistors M1 and M2. M1 is a common source stage while M2 is a common gate stage.

(a) Draw the small signal ac equivalent circuit for the system. Ignore the body effect for M2.

(b) Set up the nodal admittance matrix for the system with a goal to find the small signal voltage gain v_o/v_i . You DO NOT have to find the voltage gain.

Setting up of nodal admittance matrix (say $g = \frac{1}{r}$)

$$\begin{matrix} ① & ② \\ \left[\begin{array}{cc} g_{o1} + g_{o2} & -g_{o2} \\ -g_{o2} & g_{o2} + g_{o3} \end{array} \right] \left[\begin{array}{c} v_1 \\ v_2 \end{array} \right] \\ = \left[\begin{array}{c} -g_{m1}v_i - g_{m2}v_x \\ g_{m2}v_x \end{array} \right] \end{matrix}$$

$$B_{nt} \quad v_x = v_1, \quad v_2 = v_o$$

$$so \quad -g_{m2}v_x = -g_{m2}v_1$$


Transferring sides

$$\left[\begin{array}{cc} g_{m2} + g_{o1} + g_{o2} & -g_{o2} \\ g_{o2} + g_{o3} & -g_{m2} - g_{o2} \end{array} \right] \left[\begin{array}{c} v_1 \\ v_o \end{array} \right] = \left[\begin{array}{c} -g_{m1}v_i \\ 0 \end{array} \right]$$

Ans (b)

Figure 1:

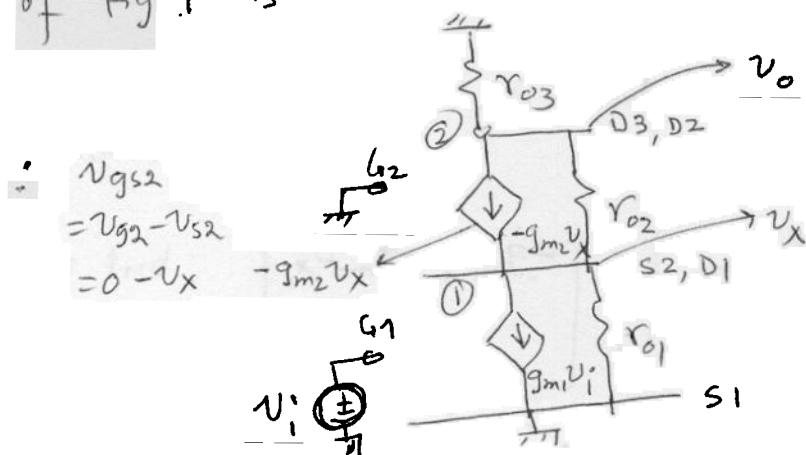
M3 has source and gate at DC, drain connected to drain of M2
 M3 functions as r_{o3} for ac signal. The ac equivalent of Fig 1 is



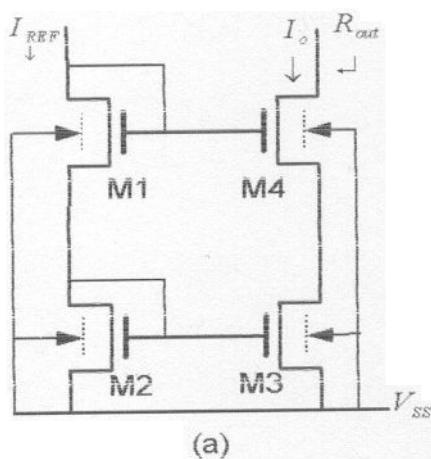
Q.2: Figures 2(a)-(b) show the Cascode and the Wilson current mirror respectively, using NMOS transistors. The bias currents are set as $I_{REF} = I_o = 20$ micro amp. Given that $V_A = 20$ volts, $K_n = 100$ micro amp./V², $W/L = 10$, $g_m = \sqrt{\frac{2K_n I_{BLAS} W}{L}}$, $g_{mb} = 0.2 g_m$ for all the transistors, compare the output resistances that the two mirrors present to an outside circuit. The expressions for the output resistances are (approximately):

$$(\text{Cascode}) R_{out} = (g_{m4} + g_{mb4}) r_{o3} r_{o4},$$

$$(\text{Wilson}) R_{out} = \frac{g_{m1} g_{m3}}{g_{m2}} r_{o1} r_{o3}$$



(a)

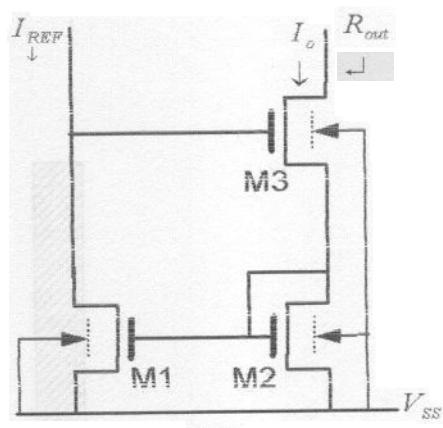

(b)

Figure 2:

Using $g_m = \sqrt{\frac{2K_n I_{BLAS} W}{L}}$ for M4 in Fig (a) $I_{BLAS} = I_o = 20 \times 10^{-6}$

$$g_{m4} = \sqrt{2 \times 100 \times 10^{-6} \times 20 \times 10^{-6}} \times 10 = 0.0002 \text{ mho}$$

$$g_{mb4} = 0.2 g_{m4} = 0.00004 \text{ mho}$$

$$r_{o3} = \frac{V_A}{I_{BLAS}} = \frac{20}{20 \times 10^{-6}} = 1 \times 10^6 = r_{o4} \quad (\because \text{same } I_{BLAS})$$

$$\text{So } R_{out} |_{\text{Cascode}} = (0.0002 + 0.00004) \times 1 \times 10^6 \times 1 \times 10^6 = 800 \text{ m}\Omega$$

For Fig (b)

$$r_{o1} = r_{o3} = 1 \times 10^6$$

$$g_{m1} = g_{m3} = g_{m2} = 0.0002$$

(All transistors are matched)

$$R_{out} |_{\text{Wilson}} = \frac{0.0002 \times 0.0002}{0.0002} \times 10^6 \times 10^6 = 200 \text{ m}\Omega$$

So $R_{out} |_{\text{Cascode}} > R_{out} |_{\text{Wilson}}$

Q.3 The BJT differential amplifier is supplied with a differential ac signal $v_D = v_1 - v_2$. The differential output signal is given by the expression

$$v_{o1} - v_{o2} = R_c I \left[\frac{\exp(-v_D/V_T)}{1 + \exp(-v_D/V_T)} - \frac{\exp(v_D/V_T)}{1 + \exp(v_D/V_T)} \right]$$

Where V_T is the thermal voltage (~ 25 mV). The bias current I is arranged to be 2 mA, and $R_C = 2000$ ohms.


Determine the voltage gain $(v_{o1} - v_{o2})/v_D$, when (i) $v_D = 20$ mV and (ii) $v_D = 2$ mV. How do these compare with the theoretical small signal voltage gain value of $|g_m R_C|$, where g_m is the transconductance of each BJT device.

ii) For $v_D = 2$ mV
 $\exp\left(\frac{v_D}{V_T}\right) = 1.083$

$$\exp\left(-\frac{v_D}{V_T}\right) = 0.923$$

$$\text{So } v_{o1} - v_{o2}$$
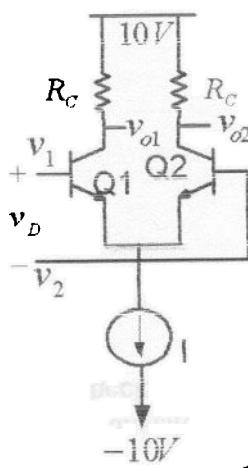
$$= 4 \left[\frac{0.923}{1.923} - \frac{1.083}{2.083} \right] \\ = -0.1598$$



(ii)

$$\begin{aligned} \text{Voltage gain} &= \frac{v_{o1} - v_{o2}}{v_D} \\ &= -\frac{0.1598}{2 \times 10^{-3}} \\ &= -79.89 \text{ V/V} \end{aligned}$$

Small Signal voltage gain = $|g_m R_C|$ where

$$g_m = \frac{1 \text{ mA}}{25 \text{ mV}} = 0.04$$

$$\text{Small Signal gain} = \frac{0.04 \times 2 \times 10^3}{3} = 80$$

i) For $v_D = 20$ mV, $\exp\left(\frac{v_D}{V_T}\right) = \exp\left(\frac{20}{25}\right) = 2.225$
 $\text{So } \exp\left(-\frac{v_D}{V_T}\right) = 1/2.225 = 0.449$

$$\frac{\exp\left(-\frac{v_D}{V_T}\right)}{1 + \exp\left(-\frac{v_D}{V_T}\right)} = \frac{0.449}{1.449} = 0.31$$

$$\frac{\exp\left(\frac{v_D}{V_T}\right)}{1 + \exp\left(\frac{v_D}{V_T}\right)} = \frac{2.225}{3.225} = 0.689$$

$$v_{o1} - v_{o2} = 2 \times 10^3 \times 2 \times 10^{-3} \times [0.31 - 0.689] = -1.516$$

$$\text{Voltage gain} = \frac{v_{o1} - v_{o2}}{v_D} = \frac{-1.516}{20 \times 10^{-3}} = -75.8 \text{ V/V}$$

Comparison: $|\text{Small signal gain}| = 80 \text{ V/V}$
 $|\text{gain for } v_D = 2 \text{ mV}| = 79.89 \text{ V/V}$
 $|\text{gain for } v_D = 20 \text{ mV}| = 75.8 \text{ V/V}$