

Course	Number	Section	
Electronics I I	ELEC 312	W	
Examination	Date	Time	# of pages
Mid-Term Test	February 17, 2012	45 minutes	3
Instructor(s)			
Dr. R. Raut			
Materials allowed: <input checked="" type="checkbox"/> No <input type="checkbox"/> Yes (Please specify)			
Calculators allowed: <input type="checkbox"/> No <input checked="" type="checkbox"/> Yes			
NO formula sheet is allowed. ONLY ENCS approved calculator is allowed.			
Special Instructions:			
Write your ID# on the front page of your answer book Attempt <u>all</u> questions. Show all steps clearly in neat and legible handwriting. Students are required to <u>return question paper</u> together with exam booklet(s).			

***** Some useful formulae*****

BJTs

$$r_e = \alpha / g_m \quad g_m = I_C / V_T \quad r_\pi = h_{fe} / g_m \quad h_{fe} = i_c / i_b \quad r_o = V_A / I_C$$

$$\alpha = \frac{h_{fe}}{h_{fe} + 1} \quad V_T = \frac{kT}{q} \approx 25mV \text{ at room temperature}$$

Diodes

$$I = I_s \exp(v_{BE} / V_T)$$

Q.1: Consider the basic current mirror in Figure 1. Design R , so that $I_o = 2 \text{ mA}$. Given $V_{CC} = 5 \text{ Volts}$, $\beta = 100$, $I_{S2} = 10^{-14} \text{ Amp.}$, $I_{S1} = 0.25 \times 10^{-14} \text{ Amp.}$ I_S is the scale current (i.e., reverse saturation current for the respective EB junctions of the transistors).

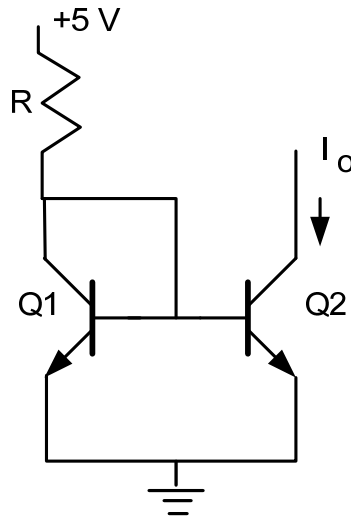


Figure 1:

Q.2: The BJT differential amplifier in Fig.2 is supplied with a differential ac signal $v_D = v_1 - v_2$. The differential output signal is given by the expression

$$v_{o1} - v_{o2} = R_c I \left[\frac{\exp(-v_D / V_T)}{1 + \exp(-v_D / V_T)} - \frac{\exp(v_D / V_T)}{1 + \exp(v_D / V_T)} \right]$$

Where V_T is the thermal voltage ($\sim 25 \text{ mV}$). The bias current I is arranged to be 2 mA

Calculate the voltage gain $(v_{o1} - v_{o2}) / v_D$, when (i) $v_D = 30 \text{ mV}$ and (ii) $v_D = 2 \text{ mV}$. How do these compare with the theoretical small signal voltage gain value of $|g_m R_c|$, where g_m is the trans-conductance of each BJT device.


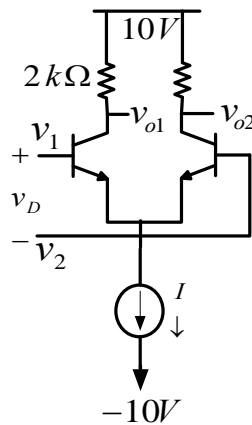


Figure 2:

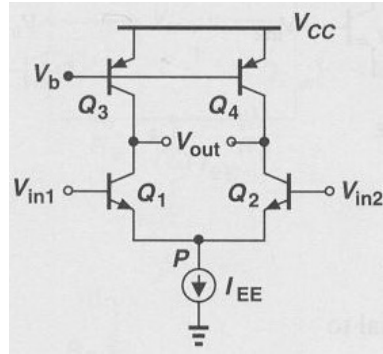Q.3: The following figure illustrates an implementation of a differential amplifier with current-source active load using complementary BJT devices. The current $I_{EE} = 2 \text{ mA}$. The early voltages are :

$$V_{AN} \text{ (for NPN BJT)} = 25 \text{ V}, V_{AP} \text{ (for PNP BJT)} = 50 \text{ V}.$$



The signals V_{in1} and V_{in2} are balanced differential. Calculate the differential voltage gain $V_{out}/(V_{in1} - V_{in2})$?

***** Some useful formulae*****

BJTs

$$r_e = \alpha / g_m \quad g_m = I_C / V_T \quad r_\pi = h_{fe} / g_m \quad h_{fe} = i_c / i_b \quad r_o = V_A / I_C$$

$$\alpha = \frac{h_{fe}}{h_{fe} + 1} \quad V_T = \frac{kT}{q} \approx 25 \text{ mV} \text{ at room temperature}$$

Diodes

$$I = I_s \exp(v_{BE} / V_T)$$
