

ELEC 312: ELECTRONICS – II : ASSIGNMENT-3
Department of Electrical and Computer Engineering
Fall – 2012-2013

1. A series-series feedback circuit represented by Fig.1, and using an ideal transconductance amplifier operates with $V_s = 100 \text{ mV}$, $V_f = 95 \text{ mV}$, and $I_o = 10 \text{ mA}$. What are the corresponding values of A and β ? Include the correct units for each.

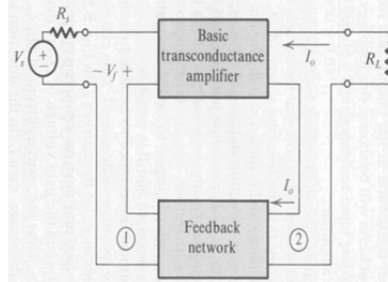


Figure 1:

Hints:

$$V_1 = V_s - V_f; V_f = \beta I_o \text{ hence, } \beta = V_f / I_o; A = I_o / V_1; A_F = I_o / V_s = A / (1 + A \beta).$$

2. For an amplifier connected in a negative feedback loop in which the output voltage is sampled (i.e., a shunt connection), measurement of the output resistance before and after the loop is connected shows a change by a factor of 80. Is the resistance with feedback higher or lower? What is the value of the loop gain $A\beta$? If R_{of} is 100Ω , what is R_o without feedback?

Hints:

$$R_o \text{ is lowered by amount of feedback i.e. } (1 + A \beta) = 80; A\beta = 79, R_o = R_{of} (1 + A \beta)$$

3. The shunt-shunt feedback amplifier in the Figure 3 has $I = 1 \text{ mA}$ and $V_{GS} = 0.8 \text{ V}$. The MOSFET has $V_t = 0.6 \text{ V}$ and $V_A = 30 \text{ V}$. For $R_S = 10 \text{ k}\Omega$, $R_1 = 1 \text{ M}\Omega$, and $R_2 = 4.7 \text{ M}\Omega$, find the voltage gain v_o/v_s , the input resistance R_{in} and the output resistance R_{out} . You need to figure out the *ac* parameters for the MOS device.

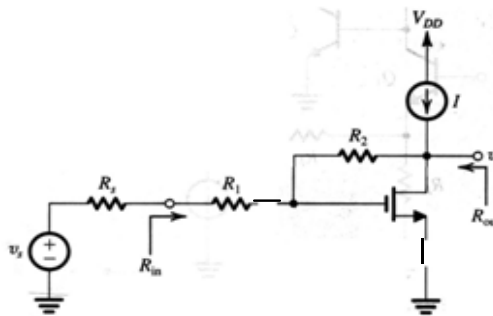
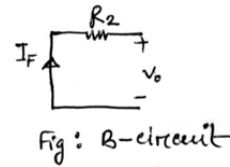
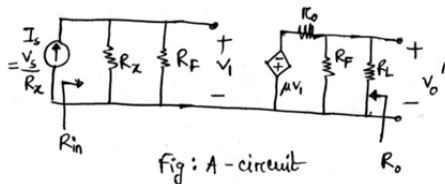


Figure 3:

Hints:

$$\underline{g_m} = 2I_D/V_{OV} \text{ and } r_o = V_A/I_A,$$

Shunt-shunt feedback. We use Y-parameter model for the feedback circuit.

Find y_{11} , y_{22} , y_{12} for R_1 , R_2 . Remember $\beta = y_{12}$.

Draw loaded ac equivalent circuit. Use $R_{11}(=1/y_{11})$ in shunt at input, $R_{22}(=1/y_{22})$ in shunt at output.

$$\beta = I_F/V_o = -1/R_2, \text{ Let } R_x = R_s + R_1 \text{ and } \mu = g_m r_o, A = V_o'/I_s' = -[R_x || R_2][R_2 || r_o]g_m;$$

$$A_F = V_o/I_s = A/(1+A\beta),$$

$$\text{Thus } V_o/(I_s R_x) = V_o'/V_1 = 1/(\beta R_x) = -R_2/(R_1 + R_s)$$

$$R_i' = (R_s + R_1) || R_2; R_{if} = R_i'/(1+A\beta), R_{in} = R_{if} - R_s$$

$$R_o' = R_2 || r_o, R_{of} = R_o'/(1+A\beta)$$

4. An op amp having a low-frequency gain of 10^3 and a single-pole transfer function with -3dB frequency of 10^4 rad/s is connected in a negative feedback loop via a feedback network having a transmission $\beta(s)$ given by $\beta(s) = \frac{\beta_o}{(1 + s/10^4)^2}$. Find the value of β_o above which the closed-loop amplifier becomes unstable.

Hints:

$$A(s) = \frac{10^3}{1 + s/10^4}, \beta(s) = \frac{\beta_o}{(1 + s/10^4)^2}$$

$$\text{Ang}(A\beta) = -\tan^{-1}(\omega/10^4) - 2\tan^{-1}(\omega/10^4) = 3\tan^{-1}(\omega/10^4)$$

For 180° , $\omega_{180} = \sqrt{3} \times 10^4$; for $|A\beta(\omega_{180})| < 1$, Determine condition for β_o

5. A DC amplifier has an open-loop gain of 1000 and two poles, a dominant one at 1 kHz and a high-frequency one whose location can be controlled. It is required to connect this amplifier in a negative feedback loop that provides a dc closed-loop gain of 100 and a maximally flat response. The transfer function of the amplifier can be modeled as:

$$A(s) = \frac{1000}{(1 + s/\omega_1)(1 + s/\omega_2)}$$

In the above ω_1 is the dominant pole frequency. It is required that under feedback, the amplifier will have a maximally flat response according to the model

$$A_f(s) = \frac{1000\omega_1\omega_2}{s^2 + (\omega_p/Q_p)s + \omega_p^2}, \text{ with } Q_p = 0.707.$$

Calculate the required ω_2 .

Hints:

$$A(s) = \frac{1000}{(1 + s/\omega_1)(1 + s/\omega_2)};$$

$A_f(0) = 10^3/(1+10^3\beta) = 100$, calculate β .

Formulate the $A_f(s)$ under feedback, and concentrate on the denominator polynomial $D(s)$ in the form

$$s^2 + (\omega_p/Q_p)s + (\omega_p)^2$$

Compare it with

$$s^2 + s(\omega_1 + \omega_2) + (1 + A_o\beta)\omega_1\omega_2 = 0$$

$Q_p = \sqrt{[(1 + A_o\beta)\omega_1\omega_2]/(\omega_1 + \omega_2)}$, calculate ω_2 Where, $Q_p = 0.707$ and $\omega_1 = 2\pi \times 1000$ rad