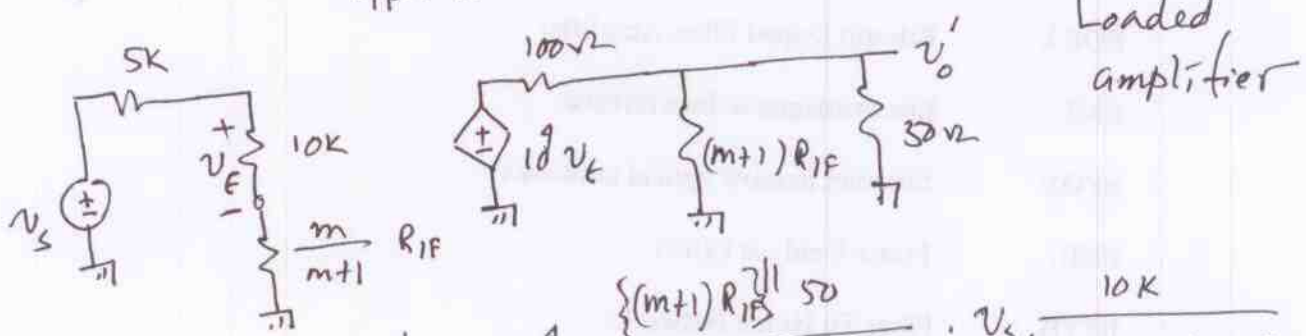


It is a series shunt feedback case. R_{1F}, R_{2F} are the feedback resistors.

$h_{11} = R_{11} = R_{1F} \parallel R_{2F}$; say $R_{2F} = m \cdot R_{1F}$. Then
 $h_{11} = R_{11} = \frac{m R_{1F}}{m+1}$

$h_{22} = \frac{1}{R_{1F} + R_{2F}} \rightarrow R_{22} = R_{1F} + R_{2F} = (m+1) R_{1F}$

$h_{12} = \beta = \frac{R_{1F}}{R_{1F} + R_{2F}} = \frac{1}{m+1}$



$v_o' / v_s = ?$ $v_o' = 10^4 \cdot \frac{\{(m+1) R_{1F} \parallel 50\}}{100 + \{(m+1) R_{1F} \parallel 50\}} \cdot v_s \cdot \frac{10K}{15K + \frac{m}{m+1} R_{1F}}$

$v_o' / v_s = 10^4 \times \frac{\{(m+1) R_{1F} \parallel 50\}}{100 + \{(m+1) R_{1F} \parallel 50\}} \cdot \frac{10,000}{15,000 + \frac{m}{m+1} R_{1F}}$

$= A_{loaded}$

Loaded amplifier

$$A_{\text{rounded}} \beta = 10^9 \times \frac{\{(m+1)R_{IF}\}'' 50}{100 + \{(m+1)R_{IF}\}'' 50} \cdot \frac{10,000}{15,000 + \frac{m}{m+1} R_{IF}} \cdot \frac{1}{m+1}$$

$$\frac{A_{\text{rounded}}}{1 + A_{\text{rounded}} \beta} = \frac{F \cdot \frac{1}{m+1}}{1 + \frac{F}{m+1}}$$

Where $F = 10^9 \times \frac{\{(m+1)R_{IF}\}'' 50}{100 + (m+1)R_{IF}'' 50} \cdot \frac{10,000}{15,000 + \frac{m}{m+1} R_{IF}}$

$$R_{IF}'' 50 = \frac{R_{IF} \times 50}{R_{IF} + 50}$$

$$(m+1)R_{IF}'' 50 = \frac{(m+1)R_{IF} \times 50}{(m+1)R_{IF} + 50}$$

Use Maple program.

Solve for $\frac{F}{1 + F\beta} = \frac{F}{1 + \frac{F}{m+1}}$
 $= 10$ relating m and R_{IF}

R_{IF}	m	$R_{2F} = m R_{IF}$
100	9.047	
500	9.047 9.047	
10	9.06	
1000	9.07	

$R_{2F} \approx 9 R_{IF}$
 $\& R_{2F} + R_{IF} \approx '10' \text{ units}$