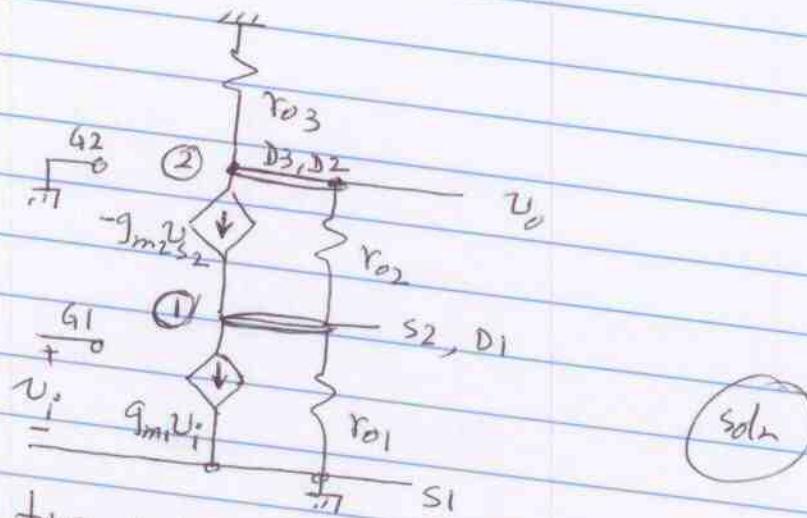


Q1.

(a)

M<sub>3</sub> has source and gate at DC ( $= 0$  ac). So it acts as a current-source active load  $= r_{o3}$ . M<sub>2</sub> has gate at DC. So the  $g_{m2}v_{gs2}$  source becomes  $g_{m2}(0 - v_{s2}) = -g_{m2}v_{s2}$ .

The ac equivalent circuit is:



(b) This is a two node system with  $v_i$  as input node. Since  $v_i$  does not have any component attached, we will exclude it in formulating the nodal admittance matrix (NAM). By inspection (and letting  $g = \frac{1}{r}$ )

$$\begin{bmatrix} g_{o1} + g_{o2} & -g_{o2} \\ -g_{o2} & g_{o2} + g_{o3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -g_{m1}v_i - g_{m2}v_{s2} \\ g_{m2}v_{s2} \end{bmatrix}$$

(1) (2)

But  $v_{s2} = v_1$ . Substituting and moving on left side (i.e.  $g_{m2}v_{s2} = g_{m2}v_1 \rightarrow -g_{m2}v_1$  on left)

$$\begin{bmatrix} g_{m2} + g_{o1} + g_{o2} & -g_{o2} \\ -g_{m2} - g_{o2} & g_{o2} + g_{o3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -g_{m1}v_i \\ 0 \end{bmatrix}$$

SOLN.

Q2:


For Fig. 2(a), it is a basic current mirror made from M<sub>4</sub>, M<sub>5</sub>. R<sub>out</sub> for M<sub>5</sub> is simply  $r_o$  of M<sub>5</sub>.

$$r_o = \frac{V_A}{I_{REF}}, \text{ so } I_{REF} \text{ need be found out.}$$


Q2.

For 2(a)

AC equiv. circuit of Fig 2(a) will be

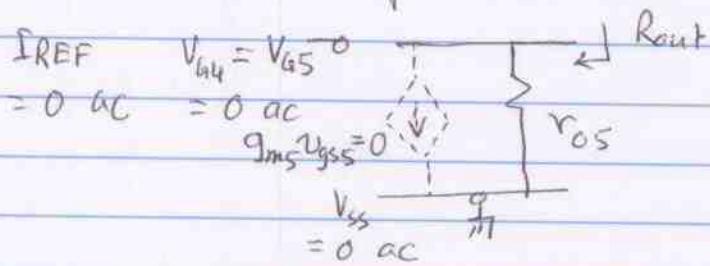

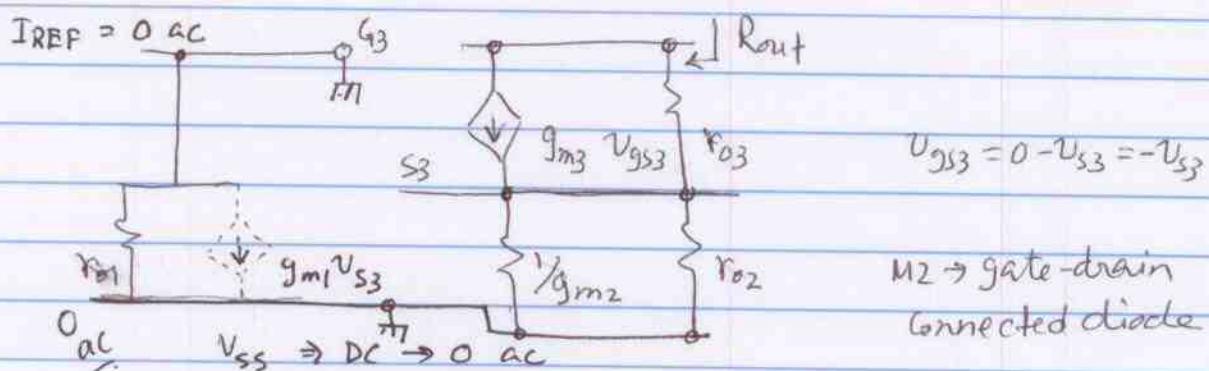For (b), remembering  $I_{REF}$  is a DC value i.e. zero 'ac' the ac equivalent circuit will be:



In Q 2(b) we can use  $g_m = g_{m3} = g_{m2} = g_{m1}$  etc.

$$I_{REF} = \mu C_{ox} \frac{W}{2L} (V_{GS} - V_{TH})^2 = 100 \times \frac{10}{2} \times 1^2 = 500 \mu A$$

$$\text{So } r_o \text{ for all the MOSFET} = V_A / I_{REF} = \frac{20}{5} \text{ k}\Omega$$

$$r_o = 40 \text{ k}\Omega$$

$$g_m = \sqrt{\frac{2\mu C_{ox} W}{L} I_D} \quad \text{Where } I_D = I_{out} = I_{REF}$$

Q2 (b) We take  $I_{out} = I_{REF}$  since no specific data  
(cont.) are given to make any difference. The data set given implies all transistors are identical.

$$\text{So } g_m = \sqrt{2 \times 100 \times 10 \times 500} \quad \leftarrow \text{given formula}$$

$\downarrow \quad \downarrow \quad \downarrow$

$$m_{ox} \quad \frac{W}{L} \quad I_D = I_{REF} = I_{out}$$

$$= 1000 \mu \text{S} = 1 \text{ milli mho}$$

$$\text{So } R_{out} \text{ for Fig 2(b) circuit is } = 1 \times 10^{-3} \times 40 \times 10^3 \times 90 \times 10^3 \quad (\text{by given formula})$$

$$\text{So } R_{out} \Big|_{2b} = 1600 \text{ k}\Omega = 1.6 \text{ M}\Omega$$

Comparison:  $R_{out} \Big|_{2a} = r_o = 40 \text{ k}\Omega \quad \Big\}$

$$R_{out} \Big|_{2b} = 1.6 \text{ M}\Omega \quad \Big\}$$

$$\text{Q3: } g_m R_c = \frac{I_c}{V_T} \cdot R_c = \frac{I_{12}}{V_T} R_c = \frac{2.5 \text{ mA}}{25 \text{ mV}} \times 2000$$

$$g_m R_c = 200 \text{ v/v} \rightarrow \text{small signal gain.}$$

(i) For  $V_D = 10 \text{ mV}$

$$\exp(V_D/V_T) = \exp(10/25) = 1.4918$$

$$\exp(-V_D/V_T) = 0.6703$$

Then

$$\frac{\exp(-V_D/V_T)}{1 + \exp(-V_D/V_T)} = \frac{0.6703}{1 + 0.6703} = 0.401$$

$$\frac{\exp(V_D/V_T)}{1 + \exp(V_D/V_T)} = \frac{1.4918}{2.4918} = 0.5987$$

$$\text{Then } V_{O1} - V_{O2} = 2000 \times 5 \times 10^{-3} [0.401 - 0.5987] \\ = -1.977$$

$$\text{Gain} = -\frac{1.977}{10 \text{ mV}} = -197.7 \text{ v/v}$$

(ii) For  $V_D = 10 \text{ mV}$

$$\exp(V_D/V_T) = \exp(1/25) = 1.04$$

$$\exp(-V_D/V_T) = 0.96$$

$$\frac{\exp(V_D/V_T)}{1 + \exp(-V_D/V_T)} = \frac{0.96}{1.96} = 0.489$$

$$\frac{\exp(V_D/V_T)}{1 + \exp(V_D/V_T)} = \frac{1.04}{2.04} = 0.509$$

Q3: Case  $V_D = 1 \text{ mV}$

$$\text{(cont.) } V_{O1} - V_{O2} = 2000 \times 5 \times 10^{-3} [0.489 - .509] \\ = -0.2 \text{ V}$$

$$\text{Gain} = -\frac{0.2}{1 \text{ mV}} = -200 \text{ v/V.}$$


For  $V_D = 1 \text{ mV}$  which is  $\ll V_T$ , the gain  $\rightarrow -200$   
exactly matches with that given by the  
formula  $|g_m R_C|$  in magnitude.

For  $V_D = 10 \text{ mV}$  which is  $< V_T$ , the gain is  $\rightarrow -197.7$   
very close to the theoretical value  $|g_m R_C| \rightarrow +200$ .

Q4

$Q_3, Q_4$  have emitters connected to DC ( $V_{ce}$ ) and bases connected to DC ( $V_b$ ). These are functioning like current source active loads.

(a) The ac equivalent circuit is:

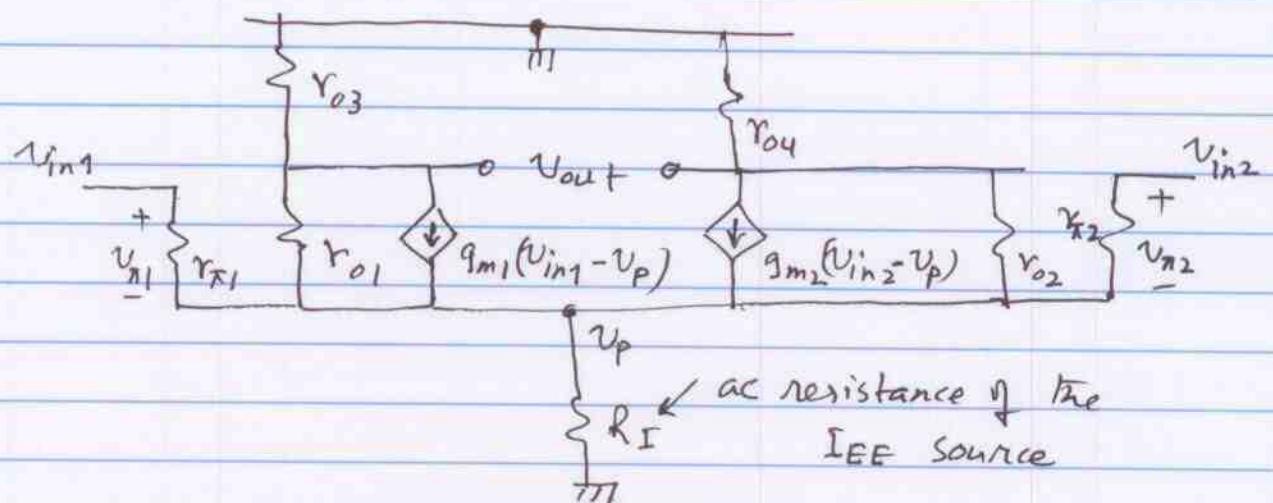


(b) When  $v_{in1}, v_{in2}$  are balanced differential signals,  $v_p = 0$  (see lecture note derivation)

Each half of the circuit behaves as a CE-BJT amplifier.

$$\text{Then } v_{o1} = -g_{m1}(v_{in1}) \cdot r_{o1} r_{o3}$$
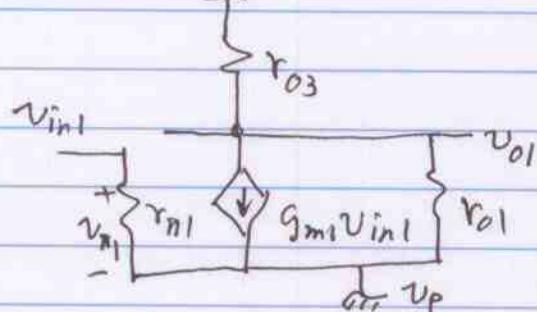
$$\text{Similarly, } v_{o2} = -g_{m2}(v_{in2}) r_{o2} r_{o4}$$



Assuming the BJTs are matched by pairs ( $\beta_p$ ,  $\beta_n$ ,  $\alpha_1 = \alpha_2$ )

$$V_{out} = V_{o1} - V_{o2}$$

$$= -g_{mn} \cdot r_{on} r_{op} v_{in1} + g_{mn} r_{on} r_{op} v_{in2}$$

Q4 (Contd.)

$$\text{Note: } r_{o1} = r_{o2} = r_{on}$$

$$r_{o3} = r_{o4} = r_{op}$$

$$g_{m1} = g_{m2} = g_{mn}$$

$$V_{out} = V_{o1} - V_{o2}$$

$$= -g_{mn} r_{on} \parallel r_{op} (V_{in1} - V_{in2})$$

$$S_o \frac{V_{out}}{V_{in1} - V_{in2}} = -g_{mn} \cdot r_{on} \parallel r_{op}$$

In the above

$$r_{o1} = r_{o2} = r_{on}; \quad r_{o3} = r_{o4} = r_{op},$$

$$g_{m1} = g_{m2} = g_{mn}$$

From the given data:  $I_{c1} = I_{c2} = I_{EE}/2 = 1mA$

$$r_{op} = \frac{V_{Aop}}{I_c} = \frac{50V}{1mA} = 50k\Omega$$

$$r_{on} = r_{o3} = \frac{V_{Aon}}{I_c} = \frac{25V}{1mA} = 25k\Omega$$

$$g_{mn} = \frac{1mA}{25mV} = 0.04 \text{ mho}$$

$$\text{Voltage gain} = -0.04 \times 25k\Omega \parallel 50k\Omega = -666.67 \text{ V/V}$$