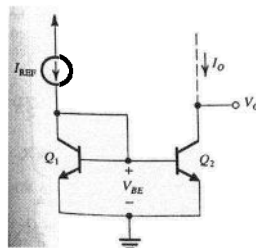


Course	Number	Section
Electronics II	ELEC 312	W
Examination pages	Date	Time
Final Examination	April 27, 2005	3 hours
Instructor(s)		# of
Dr. R. Raut		3
Materials allowed:	<input checked="" type="checkbox"/> No	<input type="checkbox"/> Yes (Please specify)
Calculators allowed:	<input type="checkbox"/> No	<input checked="" type="checkbox"/> Yes
Students are allowed to use silent, non-programmable electronic calculators without text display.		
Special Instructions:		
Show all steps clearly in neat and legible handwriting (preferably in ink). Students are required to return question paper together with exam booklet(s).		


Q.1: Consider the basic BJT current mirror shown below. The transistor Q_2 has m -times the area of Q_1 .



(a) What will be the current transfer ratio obtained?

(b) If the minimum β is specified to be 80, what is the largest current transfer ratio possible while keeping the error due to finite β limited to 5%?

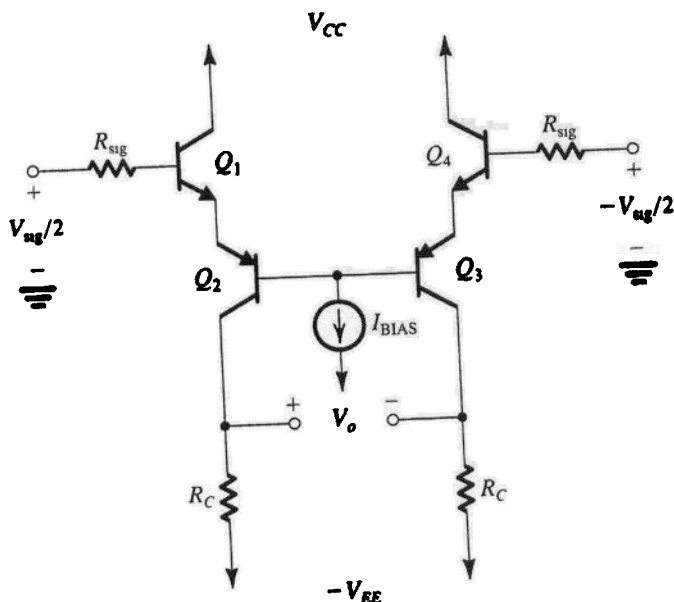Q.2: For the circuit shown below, let I_C for each transistor be $100 \mu\text{A}$. The BJTs have $\beta=200$, $f_T=600 \text{ MHz}$, and $C_{\mu}=0.2 \text{ pF}$. Further $R_{sig}=R_C = 50 \text{ k}\Omega$.




Find the low frequency gain, the high frequency poles and an estimate for f_H . You can neglect r_o and r_x for the transistors.

Q.3: A series-series feedback amplifier employs a transconductance amplifier having $G_m=100 \text{ mA/V}$, input resistance of $10 \text{ k}\Omega$, and an output resistance of $100 \text{ k}\Omega$. The feedback network has $\beta=0.1 \text{ V/mA}$, an input resistance (with port 1-open-circuited) of 100Ω , and an input resistance (with port 2 open-circuited) of $10 \text{ k}\Omega$. The amplifier operates with a signal source having a resistance of $10 \text{ k}\Omega$ and with a load resistance of $10 \text{ k}\Omega$. Find A_f and R_{in} for the system.

Q.4: In a MOS amplifier, you are given the following: $R_S=100 \text{ ohms}$, $C_{gs}=0.1 \text{ pF}$, $C_{gd}=20 \text{ fF}$, $g_m =50 \mu \text{ mho}$, $I_{DC}=50 \mu\text{A}$, $V_A=20 \text{ V}$, and $R_L= 5 \text{ k ohms}$. The MOS amplifier is configured to operate as CS amplifier. Find the dominant high-frequency pole of the amplifier using nodal analysis.

Q.5: A dc amplifier has an open-loop gain of 1000 and two poles, a dominant pole at 1 kHz and a high frequency pole whose location can be controlled. It is required to connect this amplifier in a negative-feedback loop that provides a dc closed-loop gain of 100 and a maximally flat response. Find the required value of β and the frequency at which the second pole can be placed.


Q.6: The figure below shows a MOSFET class AB output stage. All transistors have $|V_{t1}|=1\text{ V}$ and $k_1=k_2=nk_3=nk_4$, where $k=\mu C_{ox}(W/L)$ is the MOSFET transconductance parameter. Also $k_3=2\text{mA/V}^2$.

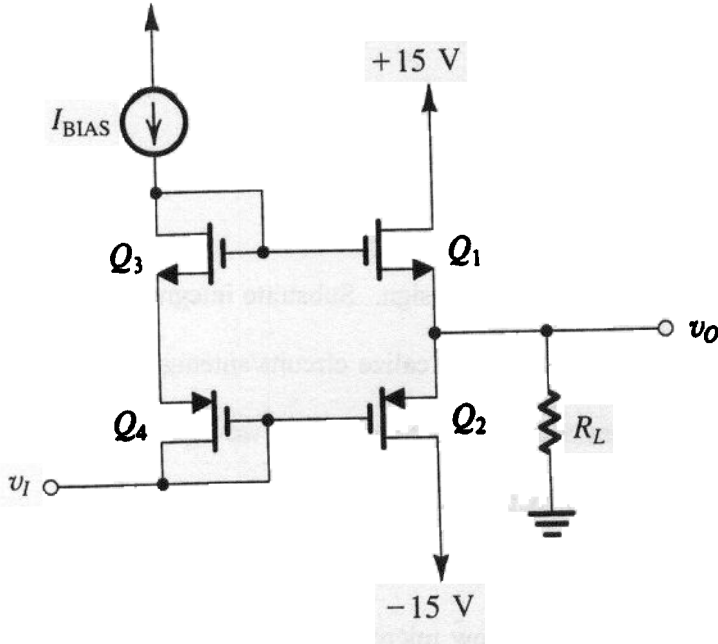

For $I_{BIAS} = 100\ \mu\text{A}$ and $R_L=1\ \text{k}\Omega$, find the value of n that results in a small-signal gain of 0.99 for output voltages around zero. Find the corresponding value of I_Q .

Bonus Question (6 marks)

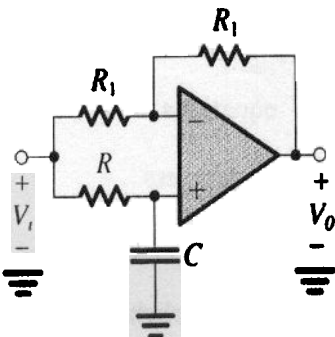For the network shown below find an expression for $T(s)$, the voltage transfer function. In this network R can be adjusted to obtain various phase shifts.



If the signal frequency is $10^4\ \text{rad/sec.}$, and if $C=10\ \text{nF}$, what values of R will produce a phase shift of -60° and -150° respectively?