

Q. 1

$$A(s) = A_m \frac{(1 - s/\omega_p)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$$= 10^2 \frac{1 - s/10^9}{(1 + s/10^6)(1 + s/10^9)}$$

$$|A(s)| = 10^2 \frac{1}{\sqrt{1 + \omega^2/10^{12}}}.$$

$$\begin{aligned} \underline{A(s)} &= -\tan^{-1} \frac{\omega}{10^9} - \tan^{-1} \frac{\omega}{10^6} - \tan^{-1} \frac{\omega}{10^9} \\ &= -\tan^{-1} \frac{\omega}{10^6} - 2 \tan^{-1} \frac{\omega}{10^9} = -\phi \end{aligned}$$

For gain margin, we need to find $\underline{|A(s)|} = -180^\circ$

$$\text{Say } \omega = 10^6, \text{ Then } \phi \Rightarrow 45^\circ + 2 \tan^{-1} \frac{10^6}{10^9} < 180^\circ$$

$$\text{Say } \omega = 10^9; \text{ Then } \phi \Rightarrow +\tan^{-1} \frac{10^3}{10} + 90^\circ \approx 180^\circ$$

$$\text{At } \omega = 10^9, |A(s)| = 10^2 \frac{1}{\sqrt{1 + \frac{10^{18}}{10^{12}}}} \approx 10^2 \cdot \frac{1}{\sqrt{10^6}} = \frac{1}{10}$$

$$|A(s)\beta| = 0.1, \text{ since } \beta = 1 \text{ given}$$

$$\text{Gain margin} = 0 - 20 \log |A(s)\beta| = 20 \text{ dB}$$

For phase margin, we need to set $|A(s)\beta| = 1$ first

$$\text{i.e. } 10^2 \frac{1}{\sqrt{1 + \omega^2/10^{12}}} = 1 \quad \Rightarrow 1 + \frac{\omega^2}{10^{12}} = 10^4 \quad \boxed{10^4} \quad \boxed{10^6}$$

$$\left. \begin{array}{l} \omega_p = 10^3 \\ A_m = 10^6 \\ \beta = 1 \\ GM = 0 \text{ dB} \end{array} \right\}$$

Q1:

$$\frac{\omega^2}{10^{12}} \approx \left(10^9\right)^{10^6}, \quad \omega = 10^{16} \quad \omega = 10^8 \text{ rad/sec}$$

Then $\phi = \tan^{-1} \frac{10^8}{10^6} + 2 \tan^{-1} \frac{10^8}{10^9} = 180^\circ$

Phase margin $180^\circ - |\phi| = 180 - 100.8 = 2 \rightarrow 0^\circ$

for a phase margin of 60° , $\phi = 120^\circ$

i.e. $\tan^{-1} \frac{\omega}{10^6} + 2 \tan^{-1} \frac{\omega}{10^9} \Rightarrow 120^\circ$, what is ω ?

say $\omega = 10^6$, $\phi = 1 + 2 \tan^{-1}(0.001) \approx 1.002$

$\omega = 10^8$; $\phi = \tan^{-1} 10^2 + 2 \tan^{-1}(1) \Rightarrow 100.85^\circ$

$\omega = 2 \times 10^8$; $\phi = \tan^{-1}(200) + 2 \tan^{-1}(2) \Rightarrow 112.3^\circ$

$\omega = 4 \times 10^8$; $\phi = \tan^{-1}(400) + 2 \tan^{-1}(4) \Rightarrow 133.45^\circ$

$\omega = 3 \times 10^8$; $\phi = \tan^{-1}(300) + 2 \tan^{-1}(3) \Rightarrow 123.2^\circ$


$\omega = 2.8 \times 10^8$; $\phi = \tan^{-1}(280) + 2 \tan^{-1}(0.28) \Rightarrow 121.07^\circ$

So we take $\omega = 2.8 \times 10^8$


Then $|A\beta| = 10^2 \frac{1}{\sqrt{1 + \frac{10^{16} \times 2.8}{10^{12}}}} \cdot \beta = 1$

$\beta = \frac{\sqrt{1 + 2.8^2 \times 10^9}}{(10^2)^{10^3}} \approx 2.8$ (a bit unrealistic)

Q2:

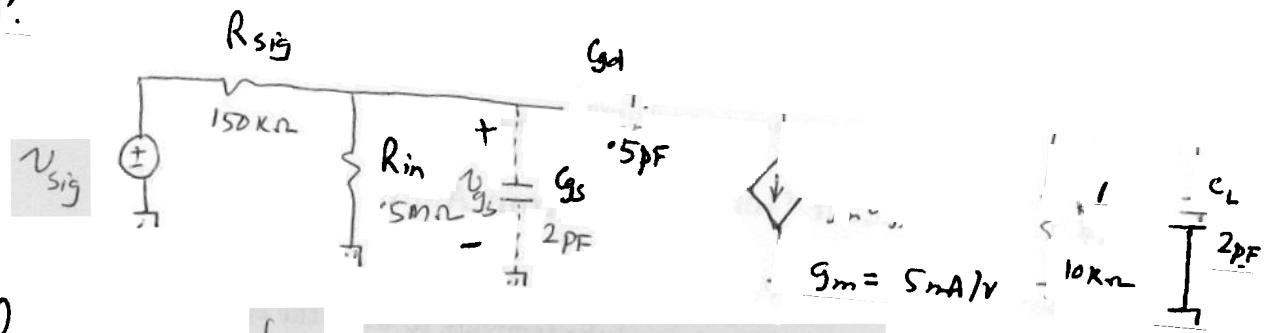

Reorganize for Nodal matrix formulation.

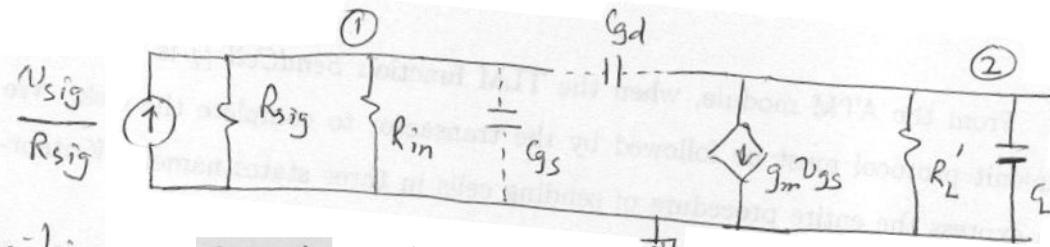

Writing $\frac{v}{R} = \frac{1}{g}$ for all cases

$$\begin{bmatrix} g_{sig} + g_{in} + s(g_d + g_s) & -s(g_d) \\ g_m - s(g_d) & s(g_d + g_L' + sC_L) \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{sig} v_{sig} \\ 0 \end{bmatrix}$$

$$V_2 = \frac{1}{\Delta} \begin{vmatrix} g_{sig} + g_{in} + s(g_d + g_s) & g_{sig} v_{sig} \\ g_m - s(g_d) & 0 \end{vmatrix} = -\frac{(g_m - s(g_d)) g_{sig} v_{sig}}{\Delta}$$

Where $\Delta = \begin{vmatrix} g_{sig} + g_{in} + s(g_d + g_s) & -s(g_d) \\ g_m - s(g_d) & g_L' + s(g_d + g_s) \end{vmatrix}$

Q2
contd

Thus

$$\Delta = [g_{sig} + g_{in} + (g_d + g_s)] [g_L' + s(c_L + g_d)] + s g_d (g_m - s g_d)$$

$$= (g_{sig} + g_{in}) g_L' + s^2 (g_d + g_s)(c_L + g_d) + s [(c_L + g_d)(g_{sig} + g_{in}) + g_L' (g_d + g_s)] + s g_m g_d - s^2 g_d^2$$

$$= (g_{sig} + g_{in}) g_L' + s [(c_L + g_d)(g_{sig} + g_{in}) + g_L' (g_d + g_s) + g_m g_d] + s^2 (g_d c_L + g_s c_L)$$

(b) The gain-bandwidth is $= |g_{av} (\text{at DC})| \times 3\text{dB BW}$

For gain at DC, we put $s \rightarrow j\omega = 0$ Then

$$A(0) = \frac{V_{out}}{V_{sig}} \text{ at } \omega = 0 = \frac{-g_m g_{sig}}{(g_{sig} + g_{in}) g_L'} \\ \Rightarrow -\frac{(g_m - s g_d) g_{sig}}{\Delta} \text{ at } s = 0$$

$$A(0) = -\frac{5 \times 10^{-3} \times \frac{1}{150 \times 10^3}}{\frac{1}{150 \times 10^3} + \frac{1}{500 \times 10^3}}$$

note: $g_{sig} = \frac{1}{R_{sig}}$
 $g_{in} = \frac{1}{R_{in}}$

$$|A(0)| = \frac{1}{\frac{1}{150 \times 10^3} + \frac{1}{500 \times 10^3}} = 577.73 \text{ v/v}$$

For 3dB BW, we shall take $\omega_{-3\text{dB}} \approx \omega_{Dom}$

where ω_{Dom} = dominant high frequency pole

$$= \frac{g_L' (g_{sig} + g_{in})}{(c_L + g_d)(g_{sig} + g_{in}) + g_d (g_d + g_s) + g_m g_d}$$

$$\begin{aligned}
 \text{Q2} \\
 \omega_{\text{Dom}} &= \frac{\frac{1}{10^4} \cdot \left[\frac{1}{150 \times 10^3} + \frac{1}{520 \times 10^3} \right]}{\left[(2 \times 10^{-12} + 5 \times 10^{-12}) \left(\frac{1}{150 \times 10^3} + \frac{1}{520 \times 10^3} \right) \right.} \\
 &\quad \left. + \frac{1}{10^4} (5 \times 10^{-12} + 2 \times 10^{-12}) + 5 \times 10^{-3} \times 5 \times 10^{-12} \right] \\
 &= \frac{8.67 \times 10^{-10}}{2.17 \times 10^{-17} + 2.5 \times 10^{-16} + 2.5 \times 10^{-15}} \text{ rad/sec} \\
 &= 312804.42 \text{ rad/sec} \rightarrow 49784.37 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 S_0 \quad (1) \quad \text{gain-bandwidth} &= 577.73 \times 49784.37 \text{ Hz} \\
 &= 28761923.53 \rightarrow 28.76 \text{ MHz} \\
 &\quad (\text{approx})
 \end{aligned}$$

Q3:

In class A operation i_{E1} will always remain non zero ie.

$$i_{E1} = i_L + I > 0$$

With signal swings at the input, i_{E1} goes down when i_L is < 0 ie. v_I and v_o are negative going.

According to P_L and R_L values, we have

$$\frac{1}{2} i_L^2 R_L = P_L = 0.5 \text{ watts}$$

$$\textcircled{2} \quad i_L^2 = \frac{1}{100} \cdot 0.1 \text{ A}^2, \quad i_L = 0.1 \text{ Amp}$$

Thus, i_L swings between $+0.1 \text{ Amp}$ and -0.1 Amp .
① To keep $i_{E1} > 0$, I must be $> 0.1 \text{ Amp}$. Let $I = 0.1 \text{ Amp}$
 $v_o = i_L R_L = \pm 0.1 \times 100 = \pm 10 \text{ V}$.

② $v_{o\min} = -10 \text{ V}$. To keep Q_2 in active region, we must have


$$v_{o\min} - v_{cc} > v_{CE(\text{sat})} \text{ of } Q_2$$

$$-10 - v_{cc} > 0.2 - (-10) \rightarrow 10.2 \text{ V}$$

$$\therefore v_{cc} \leq -10.2 \text{ V}, \text{ let } v_{cc} = -12 \text{ V}$$

② Similarly, let $v_{cc} = +12 \text{ V}$.

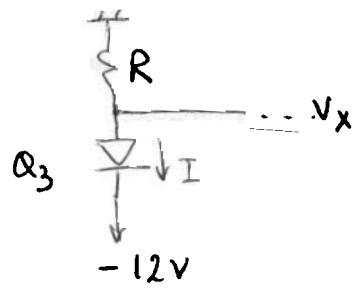Based on -12 V for $-v_{cc}$, we can design the current mirror as follows



$$v_X = -12 \text{ V} + 0.7 \text{ V} = -11.3 \text{ V.} \quad \textcircled{2}$$


The current mirror carries $I = 0.1 \text{ A}$

Then IR drop = 11.3 V

$$R = \frac{11.3}{0.1} = 113 \Omega$$

\textcircled{1}

Q4

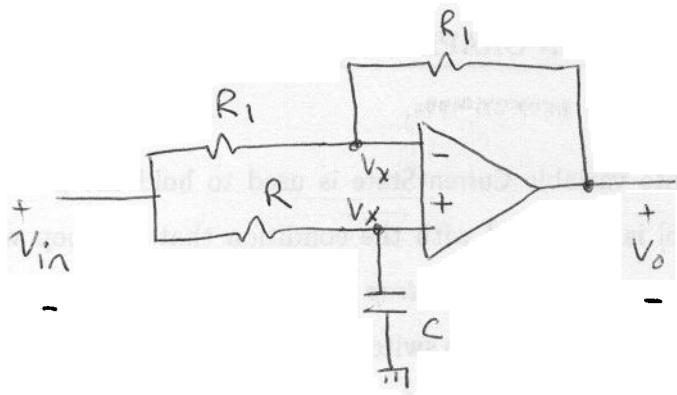

Ideal op-amp has a virtual short between + and - input terminals. Let V_x be the voltage at these terminals. Then the following KCL apply

$$\textcircled{2} \quad \frac{V_x - V_{in}}{R} + V_x sC = 0 \quad \frac{V_x - V_{in}}{R_1} + \frac{V_x - V_o}{R_1} = 0$$

Thus, $V_x = \frac{V_{in} + V_o}{2}$ and

$$\frac{V_{in} + V_o - V_{in}}{2R} + sC \cdot \left(\frac{V_{in} + V_o}{2} \right) = 0 ; \quad \frac{V_o - V_{in}}{R} + sC V_{in} + sC V_o = 0$$

$$\frac{V_o}{R} + sC V_o + sC V_{in} - \frac{V_{in}}{R} = 0 ; \quad V_{in} \left(\frac{1}{R} - sC \right) = V_o \left(\frac{1}{R} + sC \right)$$

$$\textcircled{4} \quad V_{in} \frac{\frac{1-sRC}{R}}{R} = V_o \frac{\frac{1+sRC}{R}}{R} \quad \frac{V_o}{V_{in}} = \frac{1-sRC}{1+sRC} = T(s)$$

$$\textcircled{2} \quad T(s) = -\tan^{-1} \omega RC - \tan^{-1} \omega RC = -2 \tan^{-1} \omega RC = \phi$$

$$\text{For } \phi = -30^\circ, \quad \tan^{-1} \omega RC = 15^\circ$$


Then $\omega RC = \tan 15^\circ = 0.2679$, Using values of ω and C as given

$$\textcircled{1} \quad R = \frac{0.2679}{2\pi \times 10^3 \times 10^{-8}} = 4264.5 \Omega \times 2\pi \rightarrow 26k$$

$$\text{For } \phi = -90^\circ, \quad \tan^{-1} \omega RC = 45^\circ, \quad \omega RC = \tan 45^\circ = 1$$

$$\textcircled{1} \quad R = \frac{1}{2\pi \times 10^3 \times 10^{-8}} = 15915.49 \Omega \times 2\pi \rightarrow 100k$$

Q5. A TIA has an equivalent circuit

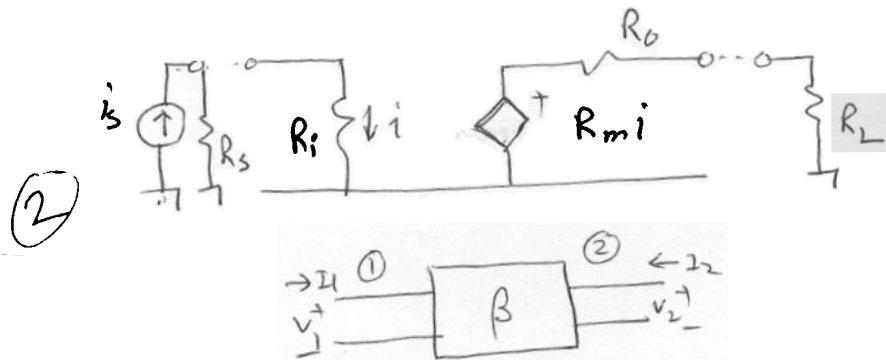

$$R_m = \frac{100V}{mA} = 100 \times 10^3$$

$$R_i = 1k\Omega$$

$$R_o = 1k\Omega$$

TIA is a CCVS configuration so it has shunt-in, series-out β -network will have a

(2) shunt-in, shunt-out configuration modeled in terms of Y-parameters So it is to be true for I_{in}

β -network

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$



It is given that

$$\left. \frac{V_2}{I_2} \right|_{V_1=0} = 10k\Omega = \frac{1}{Y_{22}} = R_{22}$$

and $\left. \frac{V_1}{I_1} \right|_{V_2=0} = R_{11} = \frac{1}{Y_{11}} = 10k\Omega$

(2) Feedback factor is the Y_{12} value $= \left. \frac{I_1}{V_2} \right|_{V_1=0} = 0.1 \frac{mA}{V}$
i.e. $\beta = 0.1 \times 10^{-3}$ mho


The loaded amplifier is

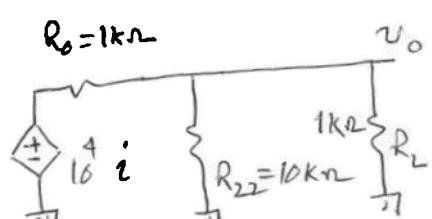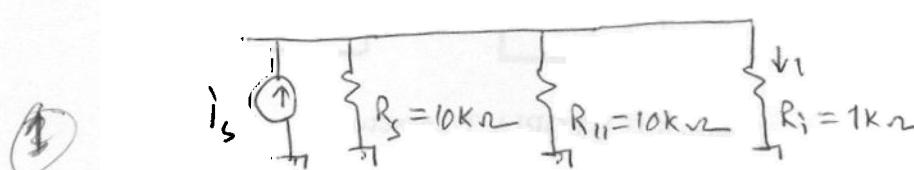

We need to find $A = \frac{v_o}{i_s} = \frac{V_o}{V_A} \rightarrow \text{ohm}$

(Q5)

At the input side we can draw

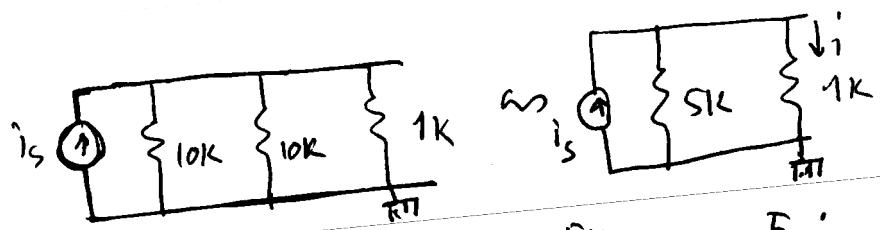

$$\frac{100}{11} \approx 9.09$$

so that $i = i_s + \frac{5k}{6k} = \frac{5}{6} i_s$

At the output

$$v_o = (10^9 i) \cdot \frac{\frac{11}{11} R_L}{R_o + \frac{11}{11} R_L} \quad \text{by series division of voltage.}$$

$$= 10^9 \cdot \frac{5}{6} \cdot i_s \cdot \frac{11}{11 + 10} K = 10^9 \cdot \frac{5}{6} \cdot \frac{0.909}{1.909} i_s$$

~~$4145.73 \times 3968.05 \frac{V}{A}$~~


(2) $\therefore A = v_o / i_s = 10^9 \cdot \frac{5}{6} \times \frac{0.909}{1.909} =$

Then by the feedback formula

$$(1) A_f = \frac{A}{1 + A\beta} = \frac{4145.73}{1 + 4145.73 \times 1} = 9.975 \frac{V/A}{ohm}$$

$$= \frac{3968}{1 + 3968 \times 1} = 9.97$$

Q6:

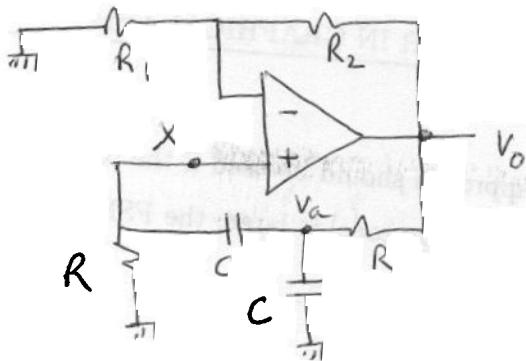

For ideal op-amp, with reference to node X ,

$$V_0 = \left(1 + \frac{R_2}{R_1}\right) V_x = KV_x \text{ (say)}$$

In the lower path between V_x and V_a via V_a node, we have the KCLs

① V_a node $(V_a - V_x)SC + V_a SC + \frac{V_a - V_0}{R} = 0$

$$V_a \left(SC + SC + \frac{1}{R}\right) - V_x SC - \frac{V_0}{R} = 0 \quad \dots \textcircled{1}$$

② V_x node $\frac{V_x}{R} + (V_x - V_a)SC = 0 ; \text{ or } V_a SC = V_x \left(SC + \frac{1}{R}\right)$

So $V_a = V_x \left(1 + \frac{1}{SRC}\right)$ sub in ①

$$V_x \left(1 + \frac{1}{SRC}\right) \left(\frac{1}{R} + 2SC\right) - V_x SC - \frac{V_0}{R} = 0$$

$$V_x \left[\frac{1+SRC}{SRC} \frac{1+2SRC}{R} - SC \right] = \frac{V_0}{R} = \frac{KV_x}{R}$$

⑥ So $\frac{(1+SRC)(1+2SRC)}{SRC} - SCR = \frac{K}{R}$

$$1 + 3SRC + 2S^2R^2C^2 - S^2C^2R^2 = KSRC$$

Equating Re- and Im- parts of the equation in complex variable $s = j\omega$, we shall get

Q6:

$$K = 3 \quad \text{and} \quad 1 + \frac{R_2}{R_1} = 3 \quad \text{is a condition for oscillation}$$

(2)

$$1 - s^2 C^2 R^2 + 2s^2 C^2 R^2 = 0$$

$$\therefore 1 + \omega^2 C^2 R^2 - 2\omega^2 C^2 R^2 = 0 \quad \text{or, } \omega^2 C^2 R^2 = 1$$

$$\omega = \frac{1}{CR} \quad \text{is the frequency of oscillation}$$

$$\text{Let } \omega_0 = \frac{1}{CR}$$

$$\text{we require } \omega_0 = 2\pi \times 10^9 \text{ with } C = 10 \mu F = 10^{-5}$$

$$\text{Then } R = \frac{1}{C\omega} = \frac{1}{10^{-5} \times 2\pi \times 10^9} = \frac{10}{2\pi} = 1.59 \Omega$$

(2)

$$\text{For } K=3, \text{ we can choose } R_2 = 2K\Omega, R_1 = 1K\Omega$$

$$\text{making } K = 1 + \frac{R_2}{R_1} = 3$$

Design values

$$\left. \begin{aligned} R &= 1.59 \Omega \\ R_1 &= 1K \\ R_2 &= 2K \\ C &= 10 \mu F \end{aligned} \right\}$$