

Topic/Chapter	Problem#	Answer/Note
DA,CM,multi-stage amp		7.49 100 micro A, Vo,min=0.2V,Vo,nom=0.7V, 5 micro A 7.57 0.2 mA, 10% 8.21 Ad=gm*RD/(1+gm*Rs/2), continue (Ch.2) 8.24 ID(Q1,Q2)=50 micro A, find other ID values Vov7=0.3, Vov6=-0.3 etc. W/L=2*ID/(mu*Cox*Vov^2) etc. 8.49 RC=6.19 k ohms, RE=235 ohms 8.59 50, 50.5*1E3 ohms 8.61 diff pair:alpha*Rc/(2*re); cascade: same
Freq. resp. of amp.		9.18 routine analysis 9.57 Cl=200.2pF, fH=795kHz, fu=(1000/2*pi)*(1/Cl*Rsig) (Ch.3) 9.61 fH=652kHz, AM=-80; tau gs=16.4%, tau gd=67.2% etc 9.75 gain=16, fp1=398MHz, fp2=3.79MHz, fH=3.79MHz (app)
D9.81		Vov=0.2V, ID=0.2mA,fH=56.7MHz, fT=284.2MHz, AM=-99 fH=2.92MHz, fT remains about the same 9.94 work with half circuit, assume ro=infinity A(low freq)=-66.22, fH=452kHz, GBW=30MHz 9.96 Ad=50, fp1=15.9MHz, fp2=1.6GHz, fz=3.2GHz 9.112 (a)-(d) as follows (a) A(DC)=10,000 (b) Cin1=525fF (c) fp1=30.3MHz (d) Cin2=530fF
Negative feedback		10.16 fL'=1Hz, fH'=1MHz 10.31 AF=9.9, Rif=202, Rof=19.8 (Ch.4) 10.43 Af=9.4 m mho, Rin=474.2 k ohms, Rout=1.76 Mega ohms 10.53 Af=-9.87 k ohms, Rin=11.08 ohms, Rout=1.085 ohms 10.83 w=1.1E5 rad/sec, beta>=0.0244 10.89 fc=1MHz, phase margin=90 deg 10.92 fc=3.16E5, beta=49E-6, AcL=16.9E3
Output stage		11.9 dead zone +-7 mV, slope (gain)=0.99, without feedback dead zone +-700 mV, slope (gain) =1 11.11 PL(max)=0.5W; Ps+=Ps-=0.318W; efficiency=78.5% for half output: PL=1/8W; Ps(tot)=0.318W, eff=39.3% 11.15 IQ=6.25mA; VBB=1.26V E11.9 see ref book #1, p.935 D11.19 n=relative size:1.25/0.1=12.5 D11.25 RL/(RL+1/(2*gm)), gm=24.5 mA/V;n=12.25; IQ=1.225mA
Oscillator		17.10 frequency shift 15%; new freq. of osc.=1.15/(RC)

(Ch.6)

$$17.13 \quad L(s) = sCR/(1+3sCR+(sCR)^2); \quad R2/R1 \geq 2; \quad w(freq) = 1/(CR)$$

$$17.21 \text{ (b)} \quad gm + (1/R) + s(C1+C2) + (s^2 * C2 * L) / R + s^3 * C1 * C2 * L = 0$$

$$w(freq) = \sqrt{(C1+C2)/C1C2L}; \quad gm * R = C2/C1$$