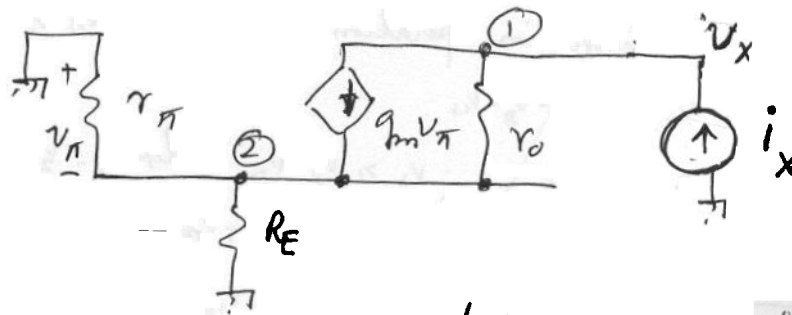


# Ch 1 / ELEC 312 lecture note pack

Q1:



For nodal analysis use a dummy  $i$ -source

The NAM:  $\det g \rightarrow \frac{1}{r}$  for all

$$\begin{bmatrix} g_0 & -g_0 \\ -g_0 & g_E + g_\pi + g_0 \end{bmatrix} \begin{bmatrix} v_{(1)} \\ v_{(2)} \end{bmatrix} = \begin{bmatrix} i_x - g_m v_\pi \\ g_m v_\pi \end{bmatrix}$$

But  $v_\pi = 0 - v_{(2)} = -v_{(2)}$

$$\begin{bmatrix} g_0 & -g_0 \\ -g_0 & g_E + g_\pi + g_0 \end{bmatrix} \begin{bmatrix} v_{(1)} \\ v_{(2)} \end{bmatrix} = \begin{bmatrix} i_x - g_m(-v_{(2)}) \\ g_m(-v_{(2)}) \end{bmatrix}$$

Move ' $g_m v_{(2)}$ ' term from RHS to LHS  $v_{(2)}$  goes to column (2)

$$\begin{bmatrix} g_0 & -g_m - g_0 \\ -g_0 & g_E + g_\pi + g_0 + g_m \end{bmatrix} \begin{bmatrix} v_{(1)} \\ v_{(2)} \end{bmatrix} = \begin{bmatrix} i_x \\ 0 \end{bmatrix}$$

Solve for  $v_x \rightarrow v_{(1)}$ :

$$v_{(1)} = \frac{\begin{vmatrix} i_x & -g_m - g_0 \\ 0 & g_E + g_\pi + g_0 + g_m \end{vmatrix}}{\begin{vmatrix} g_0 & -g_m - g_0 \\ -g_0 & g_E + g_\pi + g_0 + g_m \end{vmatrix}}$$


Then find  $v_{(1)} / i_x \rightarrow R_{out}$

Q2

For the BJT with  $V_{be} = V_B + V_{EE}$  a dc value the ac equivalent circuit becomes

So the ac equivalent to

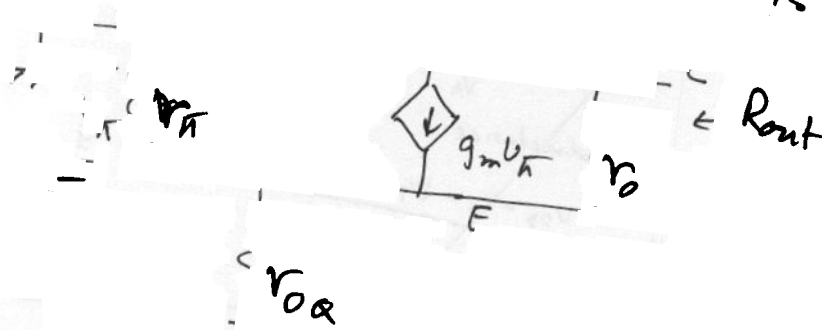$g_m V_{\pi} \rightarrow 0$ , open circuit current source is.




Proceed on with  $R_E \rightarrow r_{oa}$

Q4



ac equivalent

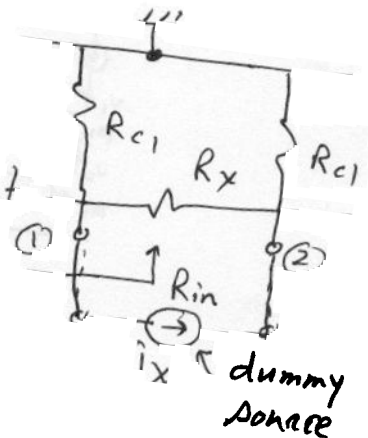


For the ac equivalent circuit

$$\begin{bmatrix} g_{c1} + g_x & -g_x \\ -g_x & g_{c1} + g_x \end{bmatrix} \begin{bmatrix} v_{(1)} \\ v_{(2)} \end{bmatrix} = \begin{bmatrix} -i_x \\ i_x \end{bmatrix}$$

Solve for  $v_{(1)}, v_{(2)}$ . Then  $R_{in} = \frac{v_{(1)} - v_{(2)}}{i_x}$

is the nodal admittance matrix (NAM)

Q5

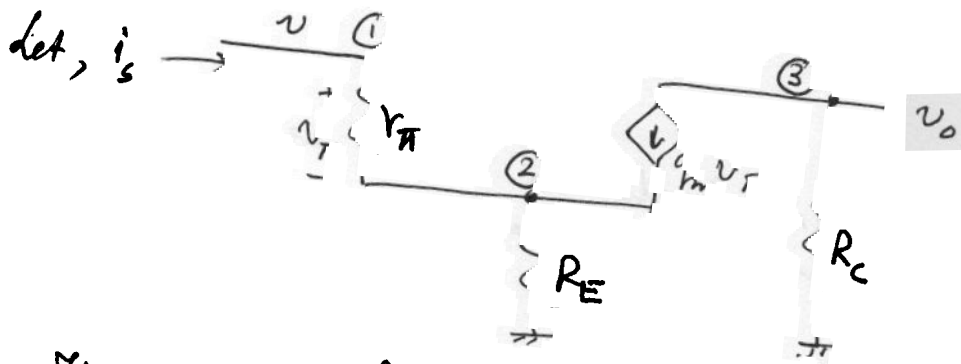

The NAM is formed as below

$$\begin{matrix}
 \textcircled{1} & & \textcircled{2} & & \textcircled{3} \\
 \begin{bmatrix} g_{\pi} & & 0 \\ -g_{\pi} & & 0 \\ 0 & & 0 \end{bmatrix} & & \begin{bmatrix} -g_{\pi} & & 0 \\ g_{\pi} + g_E & & 0 \\ 0 & & 0 \end{bmatrix} & & \begin{bmatrix} 0 \\ 0 \\ g_c \end{bmatrix}
 \end{matrix}
 \begin{bmatrix} v_{(1)} \\ v_{(2)} \\ v_{(3)} \end{bmatrix} = \begin{bmatrix} i_s \\ g_m v_{\pi} \\ -g_m v_{\pi} \end{bmatrix}$$

But  $v_{\pi} = v_{(1)} - v_{(2)}$

$$\begin{bmatrix} g_{\pi} & & 0 \\ -g_{\pi} & & 0 \\ 0 & & 0 \end{bmatrix}
 \begin{bmatrix} -g_{\pi} & & 0 \\ g_{\pi} + g_E & & 0 \\ 0 & & 0 \end{bmatrix}
 \begin{bmatrix} v_{(1)} \\ v_{(2)} \\ v_{(3)} \end{bmatrix} = \begin{bmatrix} i_s \\ g_m [v_{(1)} - v_{(2)}] \\ -g_m [v_{(1)} - v_{(2)}] \end{bmatrix}$$

$$\begin{bmatrix} g_{\pi} & & 0 \\ -g_m - g_{\pi} & & 0 \\ g_m & & 0 \end{bmatrix}
 \begin{bmatrix} -g_{\pi} & & 0 \\ g_m + g_{\pi} + g_E & & 0 \\ -g_m & & 0 \end{bmatrix}
 \begin{bmatrix} v_{(1)} \\ v_{(2)} \\ v_{(3)} \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \\ 0 \end{bmatrix}$$

$$\frac{v_0}{v_i}$$

is same as

$$\frac{v_{(3)}}{v_{(1)}}$$

Q5 (contd.)

$$V_{(3)} = \frac{1}{\Delta} \begin{vmatrix} g_{\pi} & -g_{\pi} & i_s \\ -g_m g_{\pi} & g_m + g_{\pi} + g_E & 0 \\ g_m & -g_m & g_c \end{vmatrix}$$

$\Delta$  = determinant of the NAM

$$V_{(1)} = \frac{1}{\Delta} \begin{vmatrix} i_s & -g_{\pi} & 0 \\ 0 & g_m + g_{\pi} + g_E & 0 \\ 0 & -g_m & g_c \end{vmatrix}$$

You can find  $V_{(3)} = -g_m g_E i_s$

$$V_{(1)} = g_c (g_m + g_{\pi} + g_E) i_s$$

Then  $\frac{V_{(3)}}{V_{(1)}} = -\frac{R_c}{R_c + R_E + R_E \frac{r_e}{r_{\pi}}}$ , using  $\frac{1}{g_m} \approx r_e$

Q9:

$$Y_{11} = G + jX$$

$$G = \text{Re}(Y_{11})$$

$$X = \text{Im}(Y_{11})$$

$G = 10^{-11}$  in all results so  $R = \frac{1}{10^{-11}} = 10^{11} \Omega$

$X = 6.06 \times 10^{-6} \text{ @ } f = 100$

$60.6 \times 10^{-6} \text{ @ } f = 1000$

X increases by 10 as f increases by 10. Means a capacitive reactance.


So  $X = f \cdot C$  (like  $y = mx$  graph)

$C = X/f = \frac{6.06 \times 10^{-6}}{100}$  so on


Q 10

$$T(s) = \frac{10}{s+20}, \quad |T(s)| = \frac{10}{\sqrt{\omega^2 + 20^2}}$$

$T(s)$  has a pole at  $\omega = 20$  rad/sec  
 at  $\omega = 0$ ,  $|T(s)| = 0.5$

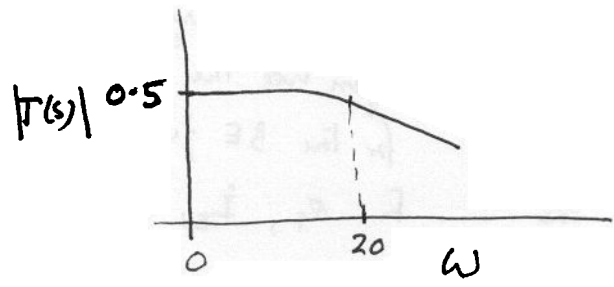

Bode plot is  $20 \log_{10} |T(s)|$

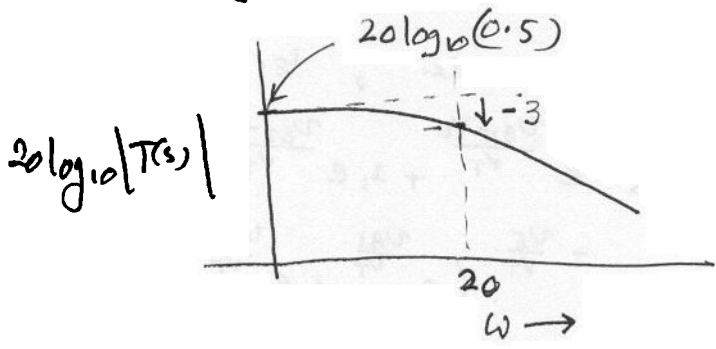


Q 11:

$$T(s) = \frac{200s}{(s+10)(s+300)}$$

Has a zero at  $\omega = 0$   
 poles at  $\omega = 10, 300$

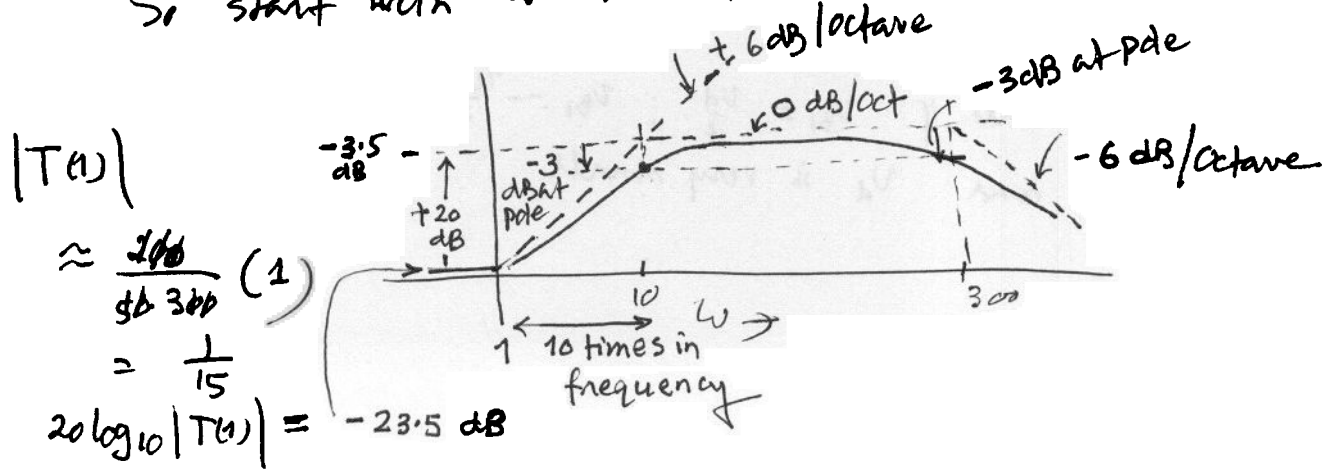As  $\log(0) \rightarrow -\infty$ , it cannot be shown  
 So start with  $\omega = 1$  rad/sec



$$\begin{aligned} |T(\omega)| &\approx \frac{200}{\omega} \quad (\omega = 1) \\ &= \frac{1}{15} \\ 20 \log_{10} |T(\omega)| &= -23.5 \text{ dB} \end{aligned}$$