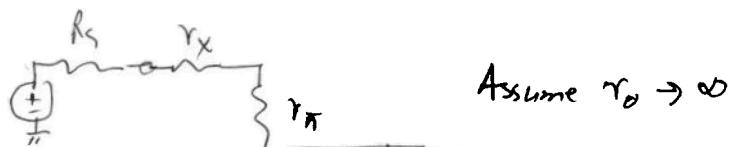


ELEC 312, Ch 3, Lecture note pack

3.8.1

(a) very simple series RC circuit-

(b)




Assume $r_o \rightarrow \infty$

\rightarrow reflected in $(\beta+1)z$

$$\text{where } z = \frac{\frac{1}{sC_E} \cdot R_E}{R_E + \frac{1}{sC_E}} = \frac{R_E}{1 + sC_E R_E}$$

So the equivalent circuit is

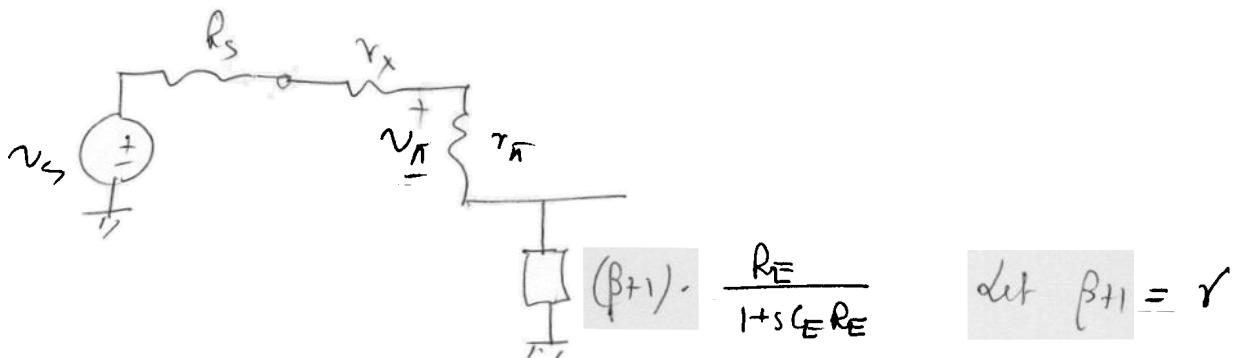


$$\begin{aligned} \text{Then } V_\pi &= \frac{r_\pi}{R_s + r_x + r_\pi + r} V_s \\ &= V_s \frac{r_\pi (1 + sC_E R_E)}{(1 + sC_E R_E)(R_s + r_x + r_\pi) + r R_E} \end{aligned}$$

V_π has a zero at $\omega = 1/C_E R_E$ because of the term $1 + sC_E R_E$ in the numerator

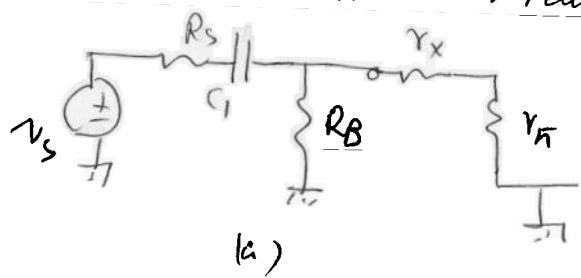
3.8.2

Use short circuit time-constant method. The three sub-circuits to consider are:



time constant
 $C_1 R_{TH1}$.


3.8.2

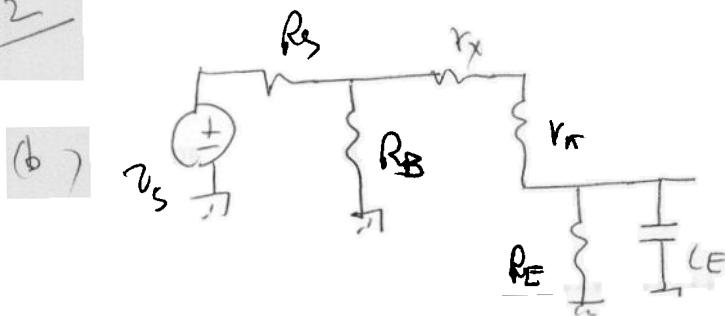

time constant

$$\tau_E = R_{TH2}$$

(c)

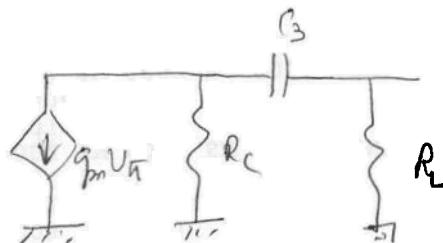

time constant

$$C_3 R_{TH3}$$

$$C_1 = 1 \mu F; C_2 = C_E = 25 \mu F; C_3 = 10 \mu F$$

3.8.3

(a) $R_{TH}|_{C_{TH}} = r_\pi'' (r_x + R_B'' R_s) \rightarrow R_s$

$$R_{TH}|_{C_M} = R_s' + (1 + g_m R_s') \cdot R_L' \quad R_L' = R_L'' R_C \quad r_o \rightarrow \infty \text{ assumed.}$$

OR $R_L' = R_L'' R_C'' r_o$ if r_o is known.

Here $R_s = 100 \Omega, R_B = 1 k\Omega$

$$r_x = 50 \Omega; r_\pi = \frac{\beta}{g_m} = \frac{2k}{g_m} = \frac{99 \times 25mV}{1mA} = 2475 \Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{50V}{1mA} = 50k\Omega$$


So calculate now

(b) $\omega_H \approx \frac{1}{r_\pi + r_o}$


where $\tau_\pi = R_{TH}|_{C_\pi} \times C_\pi$

$$\tau_o = R_{TH}|_{C_M} \times C_M$$

(c) Take the schematic

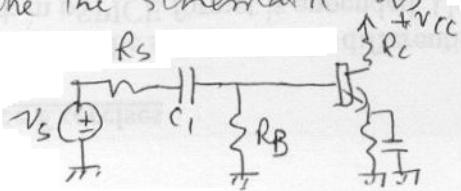

The equivalent circuit is:

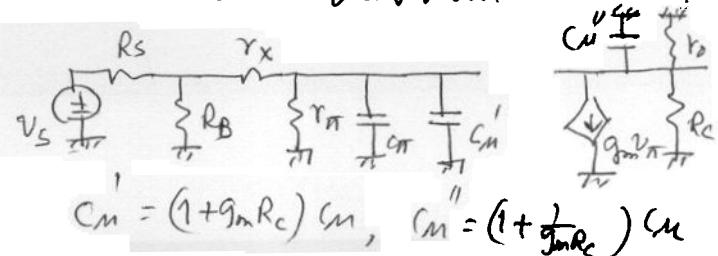

3.8.3 (contd.) (d) pole freq. due to $C_{\pi} + C_{\mu}' \rightarrow \frac{1}{(C_{\pi} + C_{\mu}') \cdot R_X}$

$$R_X = r_{\pi}'' (r_X + R_S'' R_B)$$

pole freq. due to $C_{\mu}'' \rightarrow \frac{1}{C_{\mu}'' (r_0'' R_C)}$

(e) $\omega_H \approx \frac{1}{\tau_1 + \tau_2}, \tau_1 = (C_{\pi} + C_{\mu}') R_X$
 $\tau_2 = C_{\mu}'' (r_0'' R_C)$

(f) The full transfer function is (P14) of ch 3 notes

$$T(s) = - \frac{(g_m - sC_m) g_s'}{s^2 C_{\pi} C_{\mu} + s[(g_{\pi} + g_s') C_m + (g_o + g_L)(C_{\pi} + C_{\mu}) + g_m C_m] + (g_s' + g_{\pi})(g_o + g_L)}$$

$$= - \frac{N(s)}{D(s)}$$

Solve for $D(s) = 0$ The roots are the pole frequencies
 (with positive signs)

(g) Dominant pole $\omega_{DP} = \frac{(g_s' + g_{\pi})(g_o + g_L)}{(g_{\pi} + g_s')(C_m + (g_o + g_L)(C_{\pi} + C_{\mu}) + g_m C_m)}$

(h) Results in (f) and (g)

(i) Simple mark

3.8.4 - routine procedure as in 3.8.3 above Use relevant expressions (formula?)

3.8'5

3.8.5 Expanding the matrix equation with $v_{(2)} = 0$

$$[g_{o1} + g_{m1} + s(g_{s1} + g_{s2} + g_{d2})] v_{(1)} = i_1$$

$$[g_{m2} - s g_{d2}] v_{(1)} = i_2$$

$$S_o = \frac{i_2}{i_1} = \frac{g_{m2} - s g_{d2}}{g_{o1} + g_{m1} + s(g_{s1} + g_{s2} + g_{d2})}$$

It has a zero at $\omega = g_{m2}/g_{d2}$ on RHS of s -plane
 and a pole at $\omega = \frac{g_{o1} + g_{m1}}{g_{s1} + g_{s2} + g_{d2}}$ on LHS of s -plane

3.8.6

Remembering that the transition frequency


$$\omega_T = \frac{g_m}{C_{\mu} + C_{\pi}}, \text{ for thisBJT}$$

$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu}, \text{ where } g_m \approx \frac{I_E}{V_T} = \frac{5mA}{25mV} = 0.2 \text{ A}$$


$$\omega_T = 2\pi f_T = 2\pi \times 600 \times 10^6$$

$$C_{\pi} = \frac{2}{2\pi \times 600 \times 10^6} - 5 \times 10^{-12} = 52.55 \text{ pF}$$

Now the ac equivalent circuit is:

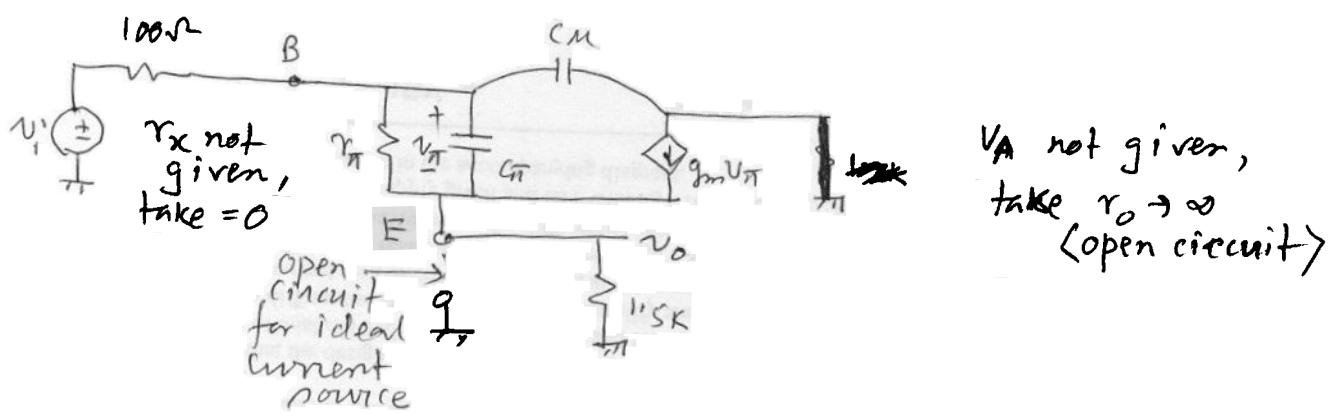

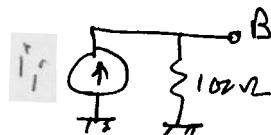V_i in series with 100Ω can be transformed to




$$\text{with } i_1 = \frac{V_i}{100}$$

3.86

(contd.)

Then the AC equivalent circuit is:

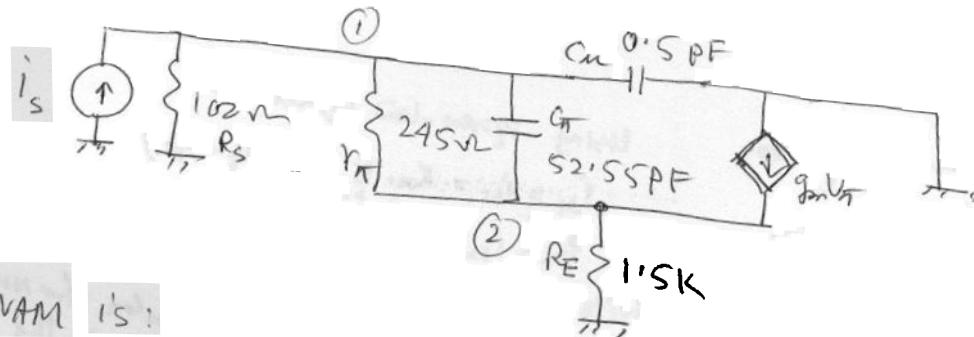

The NAM is:

$$\begin{bmatrix} g_s + g_n + s(c_n + c_m) & -sC_{\pi} - g_{\pi} \\ -g_{\pi} - sC_{\pi} & g_{\pi} + g_E + s(c_{\pi}) \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_s \\ g_m v_{\pi} \end{bmatrix}$$

$$\begin{bmatrix} g_s + g_n + s(c_n + c_m) & -g_{\pi} - sC_{\pi} \\ -g_m - g_{\pi} - sC_{\pi} & sC_{\pi} + g_m + g_{\pi} + g_E \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$

But $v_{\pi} = v_1 - v_2$

$$v_2 = \frac{1}{\Delta} \begin{vmatrix} g_s + g_n + s(c_n + c_m) & i_s \\ -g_m - g_{\pi} - sC_{\pi} & 0 \end{vmatrix}$$

For ω_H determination

$$\Delta = \begin{vmatrix} g_s + g_n + s(c_n + c_m) & -s_{\pi} - sC_{\pi} \\ -g_m - g_{\pi} - sC_{\pi} & \dots \end{vmatrix}$$

$$\text{So } \Delta = [g_s + g_n + s(c_n + c_m)] [g_m + g_{\pi} + g_E + sC_{\pi}] - (g_{\pi} + sC_{\pi})(g_m + g_{\pi} + sC_{\pi})$$

$$= 0.002 + 0.6629 \times 10^{-12} s + 0.2627 \times 10^{-22} s^2$$

The dominant pole

$$\omega_H \approx \frac{0.002}{6629 \times 10^{-12}} = 0.3017 \times 10^{10} \text{ rad/sec}$$

3.8.6
(Contd.)

For mid-band gain, we take the NAM as
(assume $s \rightarrow 0$ now)

$$\begin{bmatrix} g_s + g_\pi & -g_\pi \\ -g_m - g_\pi & g_m + g_\pi + g_E \end{bmatrix} \begin{bmatrix} v_{(1)} \\ v_{(2)} \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$


$$\Delta = \begin{vmatrix} g_s + g_\pi & -g_\pi \\ -g_m - g_\pi & g_m + g_\pi + g_E \end{vmatrix} = 0.002$$

$$v_{(2)} = \frac{1}{\Delta} \begin{vmatrix} g_s + g_\pi & i_s \\ -g_m - g_\pi & 0 \end{vmatrix} = \frac{1}{\Delta} i_s (g_m + g_\pi) \\ = \frac{1}{\Delta} g_s \cdot v_s (g_m + g_\pi)$$

$$\text{So } A_m = \frac{v_{(2)}}{v_s} = \frac{v_o}{v_s} = \frac{1}{\Delta} g_s (g_m + g_\pi) = 0.995$$

$$\text{finally, } A(s) = 0.995 \frac{-3017 \times 10^{10}}{s + 3017 \times 10^{10}}$$

3.8.7

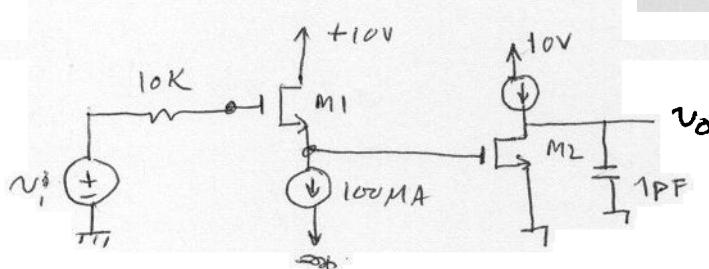

$$I_{DC} = 50 (V_{GS} - V_{TH})^2 \text{ mA} \\ = 100 \text{ mA for M1}$$

$$(V_{GS} - V_{TH})^2 = 2$$

$$V_{GS} = V_{TH} \pm 1.414 \rightarrow 2.414 \text{ (acceptable)}$$

$$g_m = \frac{\partial I_{DC}}{\partial V_{GS}} = 100 (V_{GS} - V_{TH}) = 100 \times 1.414 \quad \uparrow (V_{GS} - V_{TH}) = \sqrt{2}$$

Now one can construct the ac equivalent circuit

$$r_o \text{ of } M1 + M2 = \frac{V_A}{I_{DC}} = \frac{20}{0.1 \text{ mA}} = 200 \text{ k}\Omega$$