

ELEC 312 , Ch 4 , Problems

Q1:  $A_o = 10^4, \omega_H = 100 \times 2\pi \quad T(s) = \frac{A_o \omega_H}{s + \omega_H}$

With neg feedback  $A_o \rightarrow A_f = \frac{A_o}{1 + A_o \beta} = 50$

$$1 + A_o \beta = \frac{A_o}{50} = \frac{10^4}{50} = 10 \times 2 \quad ; \quad \beta \approx \frac{200}{10^4} = 2 \times 10^{-2}$$

(a)  $T(s) = A(s) = \frac{A_o \omega_H}{s + \omega_H}$


(b) now  $f_H |_{FB.} = (1 + A_o \beta)$  times  $f_H$  without feedback.

So  $\omega_{Hf} = (1 + A_o \beta) \omega_H = 2\pi \times 2\pi \times 100 \text{ rad/sec}$

(c) Feedback factor at lf  $1 + A_o \beta = 200$

Q2

Using the hints

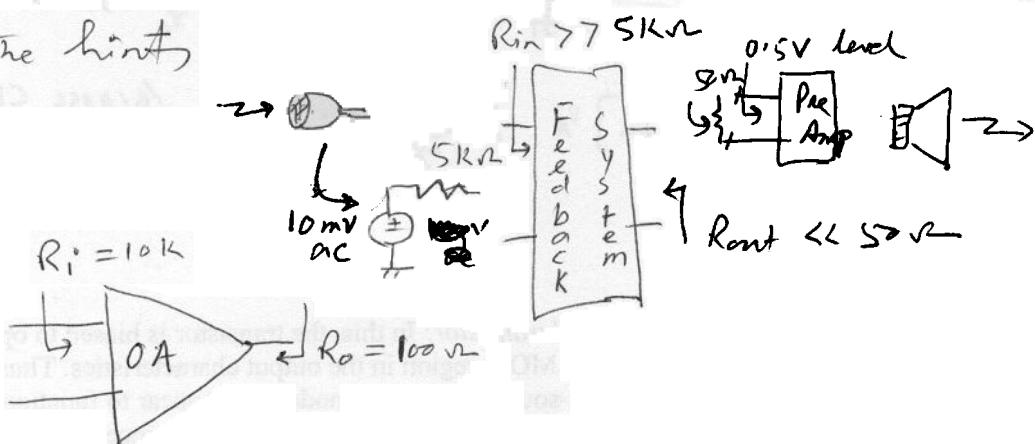

We need to achieve  $R_{if} \gg 5k$  and even  $\gg 10k$

$$R_{of} \ll 50 \text{ k} \text{ i.e. } \ll 100 \text{ ohms}$$

So a series in (to make  $R_{in} \uparrow$ ) and shunt out (to make  $R_{o} \downarrow$ ) feedback will be needed.

Also under feedback the voltage gain  $\frac{0.5V}{10mV} = 50 = A_f$

The OA gain (open loop)  $= 10^4$

$$\frac{10^4}{1 + 10^4 \beta} = 50 \quad 10^4 = 50 + 10^4 \cdot 50 \cdot \beta$$

$$\beta = \frac{10^4 - 50}{50 \times 10^4} = 0.0199$$

Q2

Further

for feedback factor


p2/13

For series -in network will be like

$$1 + A\beta = \frac{10^4}{50} = 200$$

Shunt out feedback for

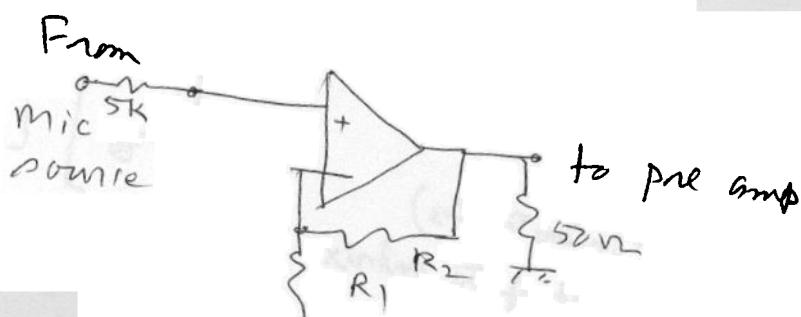and the overall feedback system will be like



We need to design  $R_1, R_2$

Check  $A_f = 4.7 - 4.8$  in the lecture note-pack

$$h_{11} = R_1'' R_2 ; \quad R_{in} = 5k + 10k + h_{11} \quad \beta = \frac{R_1}{R_1 + R_2} = 0.199$$

$$R_{inf} = R_{in} (1 + A\beta) = 200 (15k + h_{11})$$

$$R_{out} = R_o'' R_2'' R_{22} , \quad R_{22} = \frac{1}{h_{22}} \approx h_{22}$$

$$R_{out/f} = \frac{R_{out}}{1 + A\beta} = \frac{R_o'' R_2'' R_{22}}{200} \quad \frac{1}{R_1 + R_2}$$

Since  $A_f = 50$  is required,  $\beta = 0.2$  is required

Let  $R_1 = 1k$ , then  $\frac{1k}{R_2 + R_1} \approx 0.2$

$$1000 - 20 \quad k_2 \times 0.2 \quad ; \quad R_2 = \frac{1k}{0.2} = 5k$$

$$\text{Then } h_{11} = 1k'' 49k \approx 1k \quad ; \quad R_{in} = 16k$$

$$R_{inf} = \frac{16k \times 200}{3200k} = 3.2m\Omega \text{ is } > 10k$$

so this is satisfactory

R<sub>2</sub>  
contd.

$$h_{22} \rightarrow R_{22} = R_1 + R_2 = 50\text{K}$$

$$R_{\text{out}} = \frac{50\text{K}}{100\text{K}} \parallel 50\text{K} \parallel 50\text{K} \approx 33.33\Omega$$


$$R_{\text{out}} \text{ if } = \frac{33.33\Omega}{200} = \frac{0.17\Omega \ll 50\Omega}{\text{part is factory}}$$

So a design soln is  $R_1 = 1\text{K}$        $R_2 = 99\text{K}$




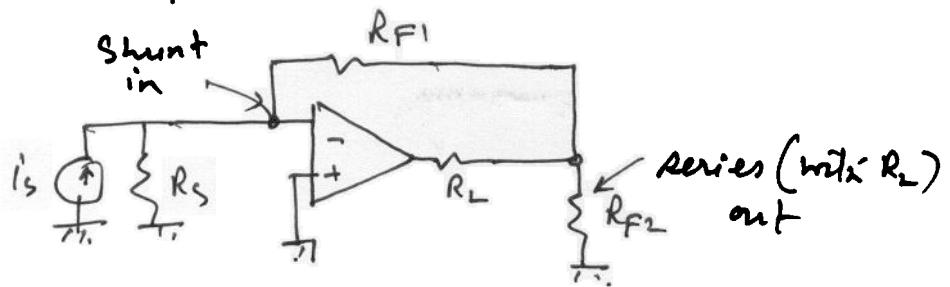Q3

A preferred feedback schematic will be (p 4.18 of p4/13  
lecture note pack)



The feedback network is

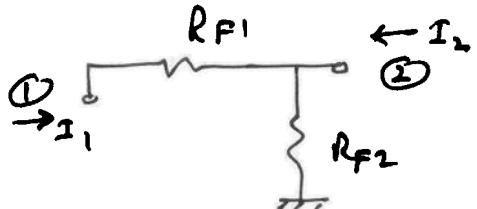

for shunt-in series out connection g-parameters need to be calculated

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} = \frac{1}{R_{F1} + R_{F2}}$$



$$R_{11} \rightarrow R_{F1} + R_{F2}$$

$$g_{12} \rightarrow \beta = \frac{I_1}{I_2} \Big|_{V_1=0} = \frac{-R_{F2}}{R_{F1} + R_{F2}}$$

$g_{21} \approx 0$  for one direction feedback only

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} = R_{F1}^{\prime\prime} R_{F2}$$





The loaded A - circuit is now

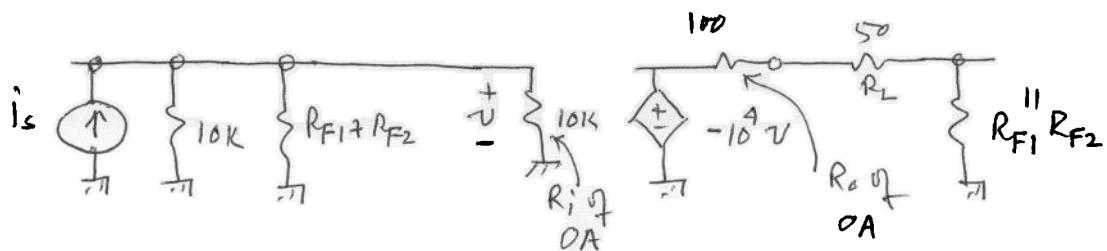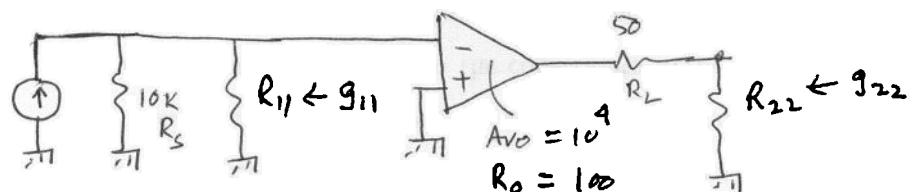

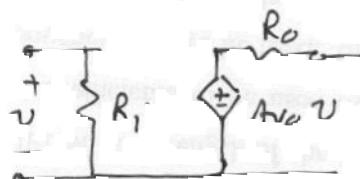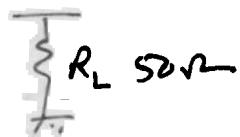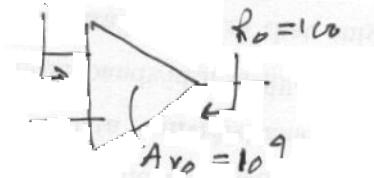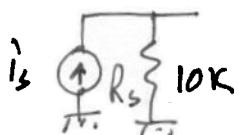Q3

$$\text{Closed loop } A_{if} = 10 \rightarrow \frac{A_{io}}{1 + \beta A_{io}}$$

$A_{io} \rightarrow$  open loop current gain (i.e. without feedback)  
 $R_i = 10\text{k}$



OA equiv cat.

To receive as much of  $i_s$  as possible at the input, the feedback system  $R_{in}$  should be  $\ll R_s \rightarrow 10\text{k}$ .

But OP-AMP  $R_{in}$  is  $= 10\text{k} \rightarrow$  This has to be lowered

So 'shunt' connection at input is required

The output is a current signal across  $50\text{mV}$ .

The output of the feedback system should have a resistance  $> R_L \rightarrow 50\text{mV}$

But OA has  $R_o = 100\text{mV}$ , this is to be increased

Hence a 'series' connection at the output is

-1

Q3

We yet do not know about  $R_{F1}$ ,  $R_{F2}$  we could get a clue about them via  $\beta$  ie

$$A_{if} = 10 = \frac{A_{io}}{1 + \beta A_{io}}$$

So we need to find  $A_{io}$  ie  $i_o / i_s$ ,  $i_o$  output current through  $R_L = 50 \Omega$

$$v = i_s \times z, z = 10k \parallel 50k \parallel (R_{F1} + R_{F2}) = 5k \parallel (R_{F1} + R_{F2})$$

$$v = i_s \cdot \frac{(R_{F1} + R_{F2}) 5k}{5k + R_{F1} + R_{F2}}$$

$$i_o = -10^9 v / (100 + 50 + R_{F1} \parallel R_{F2})$$

$$= -10^9 \cdot \frac{1}{150 + \frac{R_{F1} R_{F2}}{R_{F1} + R_{F2}}} v$$

$$= -10^9 \cdot \frac{R_{F1} + R_{F2}}{150(R_{F1} + R_{F2}) + R_{F1} R_{F2}} \cdot \frac{(R_{F1} + R_{F2}) 5k}{5k + R_{F1} + R_{F2}} i_s$$

$$\text{Let } X = R_{F1} + R_{F2}, Y = R_{F1} \cdot R_{F2} = R_{F1}(X - R_{F1}) = R_{F1}X - R_{F1}^2$$

$$\frac{i_o}{i_s} = A_{io} = - \frac{10^9 \cdot X}{150X + Y} \cdot \frac{X \cdot 5000}{5000 + X}$$

$$A_{io}\beta = - \frac{10^9 X}{150 + Y} \cdot \frac{5000}{5000 + X} X \cdot \frac{-R_{F2}}{X}$$

$$= \frac{10^9 \cdot 5000 \cdot R_{F2}}{(150 + Y)(5000 + X)} \quad \beta = g_{12} = -\frac{R_{F2}}{R_{F1} + R_{F2}}$$

$$A_{if} = \frac{A_{io}}{1 + A_{io}\beta} = \frac{10^9 X^2 \cdot 5000}{(150 + Y)(5000 + X)} \cdot \frac{(150 + Y)(5000 + X)}{[(150 + Y)(5000 + X) + 10^9 R_{F2} 5000 X]}$$

Q3

$$A_{if} = 10 = \frac{10^4 x^2 5000}{(150+y)(5000+x) + 10^4 R_{F2} 5000 x}$$

We have two unknowns  $x, y$  (i.e.,  $R_{F1}, R_{F2}$ ), but one equation. So we shall use trial method. Let  $x = 10^4 K \leftarrow R_{F1} + R_{F2}$  (such choice has limitation viz.,  $g_{21}$  must be  $\rightarrow 0$ )

Then

~~10~~

$$\cancel{10^4} \times \cancel{5000} \times \cancel{10^4} \times \cancel{10^4}$$

$$10 = \frac{10^4 \cdot 5000 \cdot (10^4)^2}{(150+y)(5000+10,000) + 10^4 \cdot R_{F2} \cdot 5000 \cdot 10,000}$$

$$(150+y)(15000) + 5 \cdot 10^{11} \cdot R_{F2} = \frac{10^3 \cdot 5000 \cdot (10^4)^2}{10^4} = 10^{14} \cdot 5$$

$$\text{Now } y = R_{F1} \cdot 10^4 - R_{F1}^2$$

$$R_{F2} = 10^4 - R_{F1}$$

Subst. for  $y$  &  $R_{F2}$  in terms of  $R_{F1}$

$$R_{F1} = -0.33 \times 10^8, 9000, 27$$

Sdn#1 → Acceptable is  $R_{F1} = 9000$  (say), then  $R_{F2} = 1000$

Had we taken  $x = 30K$  (say)  $\rightarrow 30,000$

$$\text{Then } A_{if} = 10 = \frac{10^4 \cdot x^2 5000}{(150+y)(5000+x) + 10^4 \cdot R_{F2} \cdot 5000 \cdot x}$$

$$(150+y)(5000+x) + 5 \cdot 10^7 \cdot R_{F2} x = x^2 \cdot 5 \cdot 10^6$$

$$\text{Now using } y = R_{F1} \cdot x - R_{F1}^2$$

$$R_{F2} = x - R_{F1}, \quad x = 30 \times 10^4$$

Sdn#2 →  $R_{F1} = -0.428 \times 10^8, 27001.9$ , Accept  $R_{F1} \approx 27000$   
Then  $R_{F2} = 3000$

Q5

$R_F$  is the feedback element  
For shunt-shunt feedback, we need  $\gamma$ -parameters  
for  $R_F$



$$I_1 = \gamma_{11}V_1 + \gamma_{12}V_2$$

$$I_2 = \gamma_{21}V_1 + \gamma_{22}V_2$$

$$\gamma_{11} \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{R_F} \rightarrow R_{11} = R_F \text{ in shunt with input}$$


$$= -\frac{1}{R_F} \rightarrow \beta \text{ factor}$$

$$\gamma_{12} \frac{I_1}{V_1} \Big|_{V_2=0}$$

$\gamma_{21}$  is to be ignored, as  $L$  is small

$$\gamma_{22} = \frac{1}{R_F} \Rightarrow R_{22} = R_F$$

So, A-circuit is:

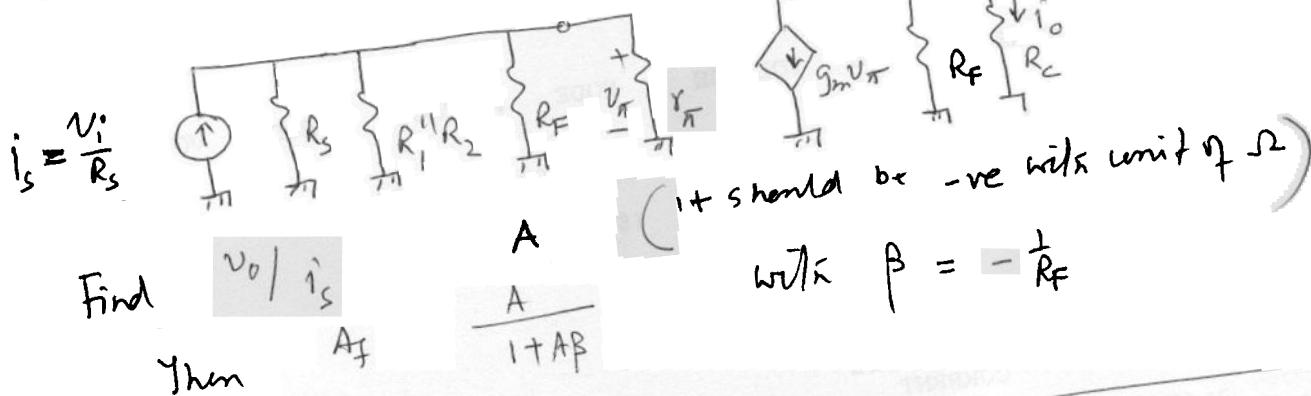

Q6

P

i)  $\beta = \dots$  is given

We can find ' $f$ ' such that ( $f = f_x$ , say)

$|T(f)| = |A\beta| = 1$  and then  
find if  $\boxed{T(f)}$  at this  $f_x = -180^\circ$  or not

If yes, the system is unstable at  $f_x$

If no, the system is stable at  $f_x$

Alternatively, we can find  $f = f_y$  where

$$\boxed{T(f)} \rightarrow \left| \frac{100}{(1+j \frac{f}{105})^3} \right| = -180^\circ \quad (\text{zero phase margin case})$$

Then investigate  $\left| \frac{100\beta}{(1+j \frac{f}{105})^3} \right|$  at  $f = f_y$ .

let's try with  $f_y$

$$T'(f) = \frac{100}{(1+j \frac{f}{105})^3} \rightarrow \boxed{T'(f)} = -3 \tan^{-1} \frac{f}{105} = -180^\circ$$

(remember: for  $\frac{1}{A+jB}$ , L is  $-\tan^{-1} \frac{B}{A}$ )  
for  $A+jB$ , L is  $+\tan^{-1} \frac{B}{A}$ ) review complex variable algebra !!.

So,  $\tan^{-1} \frac{f_y}{105} = 60^\circ$ ,  $\tan 60^\circ = \frac{f_y}{105}$ ;  $f_y = 1.732 \times 10^5$  Hz.

Then for  $\beta = 0.2$   $\boxed{T(f)} \text{ @ } f = f_y ?$

Q6.

$$|T(f)| = \frac{100 \times 0.2}{\left[1 + \frac{f^2}{10^{10}}\right]^{\frac{3}{2}}}$$

$$\left(\text{recall } \cancel{\left|1 + j \frac{f}{f_a}\right|} = \left[1 + \frac{f^2}{f_a^2}\right]^{\frac{1}{2}}\right)$$

$$= \frac{20}{\left[1 + \frac{1.732 \times 10^{10}}{10^{10}}\right]^{\frac{3}{2}}} = \frac{20}{\left[1 + 1.732^2\right]^{\frac{3}{2}}}$$

$$= \frac{20}{7.999} = 2.5$$

$\therefore |T(f)| > 1 \rightarrow \text{When } T(f) = -180^\circ$   
 Case of potential instability at  $f = 1.732 \times 10^5$

Investigate at  $f = f_x$  with  $\beta = 0.2$

$$\frac{100 \times 0.2}{\left[1 + \frac{f^2}{10^{10}}\right]^{\frac{3}{2}}} = 1 \quad (\text{zero gain margin case})$$

$$20 = \left(1 + \frac{f^2}{10^{10}}\right)^{\frac{3}{2}} = \left(1 + \frac{f^2}{10^{10}}\right)^{1.5}$$

$$1 + \frac{f^2}{10^{10}} = (20)^{\frac{2}{3}} = 7.368$$

$$\frac{f^2}{10^{10}} = 6.368, \quad f = f_x = 252.35 \times 10^3 \approx 2.523 \times 10^5 \text{ Hz}$$

Q6 Now  $|T(f)| \text{ at } f = f_x$  P11/13

i.e.  $|T'(f)| \text{ at } f = f_x$

$$\begin{aligned} |T'(f)| &= -3 \tan^{-1} \frac{f_x}{10^5} = -3 \tan^{-1}(2.523) \\ &= -3 \times (1.193 \text{ radian}) \\ &= -3 \times 68.37^\circ \approx -205^\circ \text{ which is} \\ &> 180^\circ \text{ in value} \end{aligned}$$

So the system will be unstable around  $f_y = 2.523 \times 10^5 \text{ Hz}$

So for  $\beta = 0.2$ , the system has potential instability.

Repeat for  $\beta = 0.2$

Start with zero phase margin Case i.e.  $|T'(f)| = -180^\circ$

We already know  $f_y = 1.732 \times 10^5 \text{ Hz}$

$$\begin{aligned} \text{Then for } \beta = 0.2, \quad |T(f)| &= \frac{100 \times 0.2}{\left[1 + \frac{f_y^2}{10^{10}}\right]^{\frac{3}{2}}} \\ &= \frac{2}{\left[1 + 1.732^2\right]^{\frac{3}{2}}} = \frac{2}{7.999} \approx 0.25 \end{aligned}$$

So  $|T(f)| < 1$

System will be stable around  $f = f_y = 1.732 \times 10^5 \text{ Hz}$

Gain margin?  $\rightarrow 0 - 20 \log_{10}(0.25) = 0 - (-12)$

$$0 - 20 \log_{10} |T(f)|$$

$$= 12 \text{ dB}$$

(Continue

yourself)

a positive gain margin  $\leftarrow$  stable

Q7:

$$T(f) = \frac{100\beta}{(1+j\frac{f}{10^3})(1+j\frac{f}{5 \times 10^9})(1+j\frac{f}{10^6})}$$

For phase margin of  $45^\circ$ , we should get

$$\boxed{T(f)} = -135^\circ \text{ if } 45^\circ \text{ below } 180^\circ \text{ (with a delay)}$$

$$\phi_M = 180^\circ - |\theta|, |\theta| = 135^\circ$$

For causal system

$\theta$  is negative

$$\boxed{T(f)} = \boxed{T'(f)} \text{ where } T'(f) = \frac{100}{D(f)}$$

$$\boxed{T'(f)} = -\tan^{-1} \frac{f}{10^3} - \tan^{-1} \frac{f}{5 \times 10^9} - \tan^{-1} \frac{f}{10^6}$$

This is non-linear we need to use iterations  
We start with the second pole i.e.  $f \approx 5 \times 10^9$

$$\text{Then } \theta_1 = -\tan^{-1} \frac{5 \times 10^9}{10^3} = -\tan^{-1}(50) = -1.5507 \text{ rad}$$

$$= -88.85^\circ$$

$$\theta_2 = -\tan^{-1} \frac{5 \times 10^9}{5 \times 10^9} = -\tan^{-1}(1) = -45^\circ$$

$$\theta_3 = -\tan^{-1} \left( \frac{5 \times 10^9}{10^6} \right) = -\tan^{-1}(0.5) \rightarrow -2.86^\circ$$

$$\text{So } \theta = -88.85 - 45 - 2.86 = 136.7^\circ$$

This is slightly  $> 135^\circ$ . So we can run another trial with  $f < 5 \times 10^9$ , say  $4.8 \times 10^9$

Find ' $\theta$ ' again if  $\theta \approx 135^\circ$  at this

choice of  $f$ , let  $f = f_x$

Now evaluate  $|T(f)| = 1$   $\textcircled{a} f=f_x$  then solve for  $\beta$ .

Q8 Solve in line of solutions to  
Problem #6 & #7

Q9: Hint is sufficient