

For Graduate Students

Q.1 :

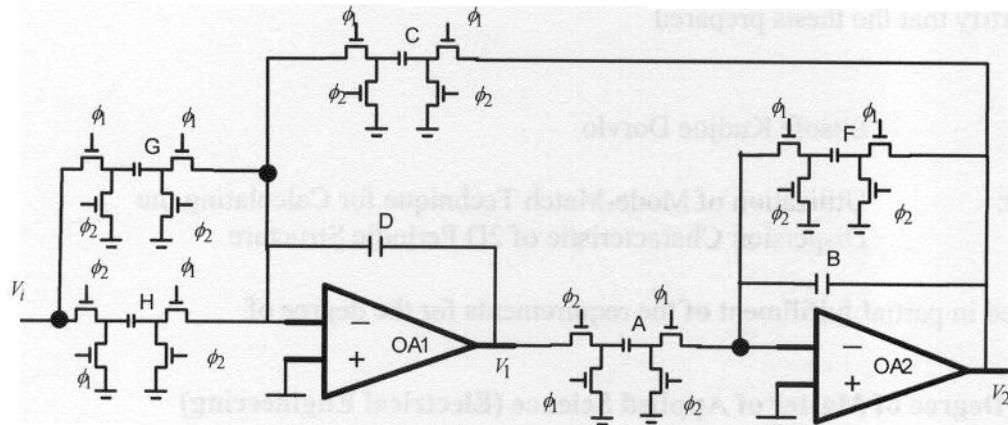


Figure 1:

The figure above shows a second order switched capacitor filter using parasitic insensitive switched capacitor integrators. Find an expression for the Z-domain transfer function $\frac{V_2^{(1)}}{V_i^{(1)}}$. You can assume that the sample-and-hold property holds for the signals V_i , and V_1 i.e., $V_i^{(2)} = z^{-\frac{1}{2}}V_i^{(1)}$ etc.,.

Q.2: The schematic below represents a normalized low-pass CHEB filter of order 3 with equal terminating resistances.

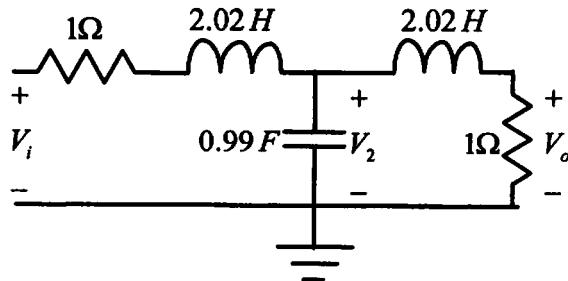


Figure 2(a):

Produce an active RC design for the above ladder filter with 100Ω terminations, and a pass-band edge frequency of 1000 radians. Use *operational simulation* technique, according to the leap-frog interconnection as shown below (Fig.2(b)).

MT2, April '09, Grd

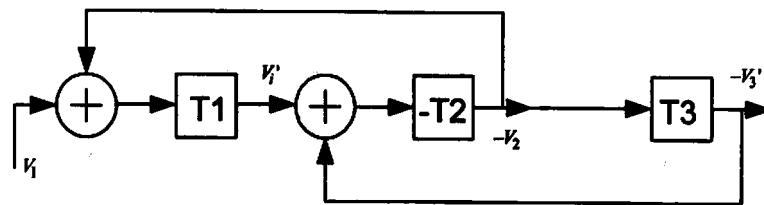


Figure 2(b):

In the above T_1 , T_3 are the voltage transfer functions (VTF) associated with the series R,L segments and $-T_2$ is the VTF associated with the shunt capacitance segment of the ladder filter.

Show your schematic and the designed element values clearly.

Q.3: Design, using OP-AMP or OTA, a second order notch filter which corresponds to a frequency normalized transfer function $T_N(s) = \frac{s^2 + 1}{s^2 + 1.5s + 1}$. The stop-band frequencies of the notch filter are: $\Omega_l = 1000 \text{ rad/sec}$, and $\Omega_h = 4000 \text{ rad/sec}$ respectively. Note that the pole frequency of the filter is same as the (geometric) center frequency .

Show the components of your designed circuit, and the schematic clearly.

For Undergraduate students

Q.1:

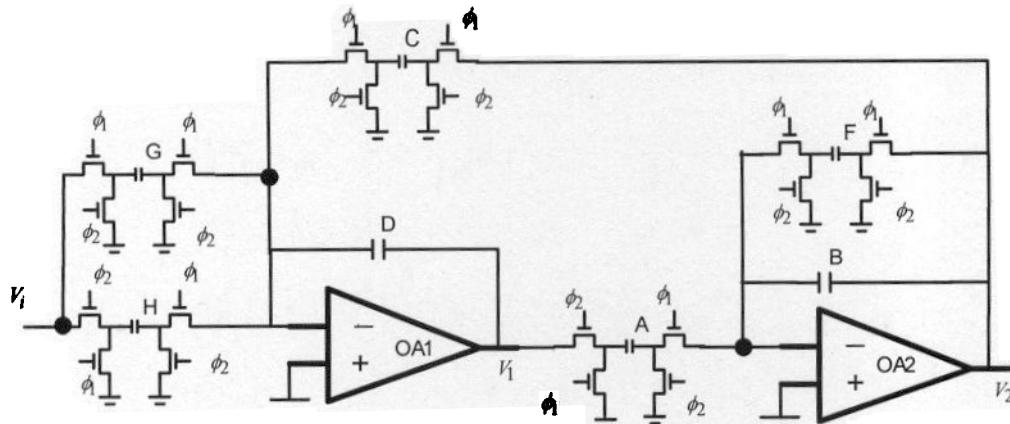


Figure 1:

The figure above shows a second order switched capacitor filter using parasitic insensitive switched capacitors. Find an expression for the Z-domain transfer function $\frac{V_2^{(1)}}{V_i^{(1)}}$. You can assume that the sample-and-hold property holds for the signals V_i , and V_1 i.e., $V_i^{(2)} = z^{-\frac{1}{2}}V_i^{(1)}$ etc.,.

Q.2: The schematic below represents a normalized low-pass CHEB filter of order 3 with equal terminating resistances.

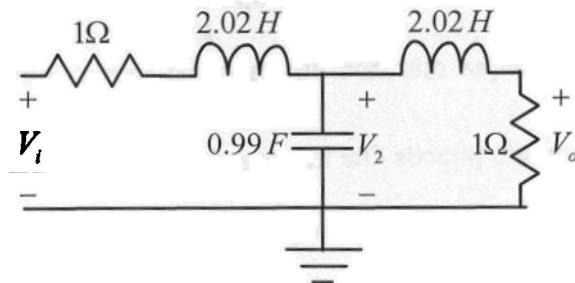


Figure 2:

Produce an active RC design for the above ladder filter with 100Ω terminations, and a pass-band edge frequency of 1000 radians. Use FDNR (frequency dependent negative resistance) technique.

Show the components of your designed circuit, and the schematic clearly.

MT2, April '09, U6

Q.3: Design , using OP-AMP or OTA, a second order band-stop filter which corresponds to a frequency normalized transfer function $T_N(s) = \frac{s^2 + 1}{s^2 + 1.5s + 1}$. The stop-band frequencies of the filter are:

$\Omega_L = 1000$ rad/sec , and $\Omega_H = 4000$ rad/sec respectively. Note that the pole frequency of the filter is same as the (geometric) center frequency .

Show the components of your designed circuit, and the schematic clearly.

~~Q1~~
Q1:

By inspection - $\frac{MT2, April 1999 UG & G}{ELEC 441) 6081}$ - } soln

at receiver input at phase 1 So

p1/11

$$V_1^{(1)} = - \frac{1}{D} \cdot V_i^{(1)} G \cdot \frac{1}{1-z^{-1}} + \frac{1}{D} \cdot V_i^{(2)} H \cdot \frac{\bar{z}^{1/2}}{1-z^{-1}} - \frac{1}{D} \cdot V_2^{(1)} C \cdot \frac{1}{1-z^{-1}}$$

$$= - \frac{G}{D} \frac{1}{1-z^{-1}} V_i^{(1)} + \frac{H}{D} \cdot \frac{\bar{z}^{1/2}}{1-z^{-1}} V_i^{(2)} - \frac{C}{D} \frac{1}{1-z^{-1}} V_2^{(1)}$$

Using $V_i^{(2)} = \bar{z}^{-1/2} V_i^{(1)}$

$$V_1^{(1)} = - \frac{G}{D} \frac{1}{1-z^{-1}} V_i^{(1)} + \frac{H}{D} \frac{\bar{z}^{-1}}{1-z^{-1}} V_i^{(1)} - \frac{C}{D} \frac{1}{1-z^{-1}} V_2^{(1)}$$

For OA 2 , similarly,

$$V_2^{(1)} = - \frac{F}{B} \frac{1}{1-z^{-1}} V_2^{(1)} + \frac{A}{B} \frac{\bar{z}^{-1}}{1-z^{-1}} V_1^{(2)}$$

Using $V_1^{(2)} = \bar{z}^{-1/2} V_1^{(1)}$

$$V_2^{(1)} = - \frac{F}{B} \frac{1}{1-z^{-1}} V_2^{(1)} + \frac{A}{B} \cdot \frac{\bar{z}^{-1}}{1-z^{-1}} V_1^{(1)}$$

Changing sides

$$V_2^{(1)} \left[1 + \frac{F}{B} \frac{1}{1-z^{-1}} \right] = \frac{A}{B} \cdot \frac{\bar{z}^{-1}}{1-z^{-1}} V_1^{(1)}$$

$$V_2^{(1)} \left[1 + \frac{F}{B} \frac{1}{1-z^{-1}} \right] = \frac{A}{B} \frac{\bar{z}^{-1}}{1-z^{-1}} \left[\left(-\frac{G}{D} + \frac{H}{D} z^{-1} \right) \frac{1}{1-z^{-1}} V_i^{(1)} - \frac{C}{D} \frac{1}{(1-z^{-1})} V_2^{(1)} \right]$$

$$\text{or } V_2^{(1)} \left[1 + \frac{F}{B} \frac{1}{1-z^{-1}} + \frac{AC}{BD} \cdot \frac{\bar{z}^{-1}}{(1-z^{-1})^2} \right] = \frac{A}{B} \cdot \frac{\bar{z}^{-1}}{(1-z^{-1})^2} \left(-\frac{G}{D} + \frac{H}{D} z^{-1} \right) V_i^{(1)}$$

$$V_2^{(1)} \frac{\left[BD(1-z^{-1})^2 + ED(1-z^{-1}) + ACz^{-1} \right]}{BD(1-z^{-1})^2} = \frac{A}{B} \frac{1}{(1-z^{-1})^2} \cdot \left(-\frac{G}{D} \bar{z}^{-1} + \frac{H}{D} \bar{z}^{-2} \right) V_i^{(1)}$$


$$Q_1: V_2^{(1)} = [B_D \left(1-z^{-1}\right)^2 + E_D \left(1-z^{-1}\right) + A(z^{-1})] \\ = A_D \left[-\frac{1}{3}z^{-1} + \frac{1}{6}z^{-2} \right] V_1^{(1)}$$

$$\frac{V_2^{(1)}}{V_1^{(1)}} = \frac{AH\bar{z}^{-2} - GA\bar{z}^{-1}}{BD(\bar{z}^{-1})^2 + ED(\bar{z}^{-1}) + AC\bar{z}^{-1}}.$$


Q.2:

The frequency denormalized filter is.

p 3/4

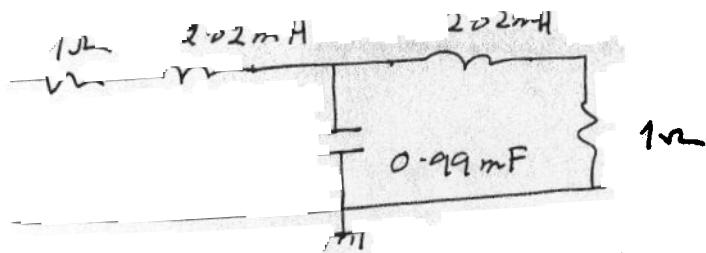

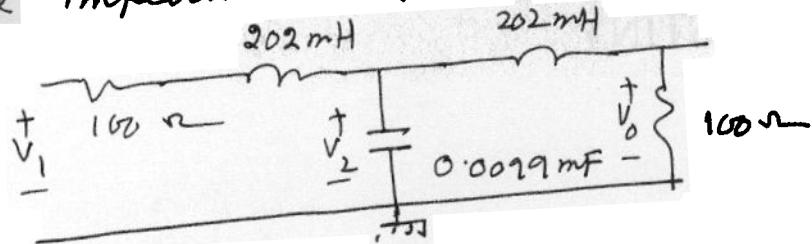The impedance & frequency denormalized filter is



For operational simulation:



$$Y_1 \rightarrow \frac{100}{202 \times 10^{-3}} \rightarrow \frac{1}{100 + s \times 202 \times 10^{-3}} = \frac{1}{202 \times 10^{-3}} \cdot \frac{1}{s + \frac{100}{202 \times 10^{-3}}}$$

$$T_1 = R Y_1 = \frac{R / 202 \times 10^{-3}}{s + \frac{100}{202 \times 10^{-3}}}$$

$$-Z_2 = -\frac{1}{s \times 0.0099 \text{ mF}} = -\frac{1}{s \times 9.9 \times 10^{-7}} = -\frac{1}{s \times 9.9 \times 10^{-6}}$$


$$-T_2 = -\frac{Z_2}{R} = -\frac{1}{s \times R \times 9.9 \times 10^{-6}}$$
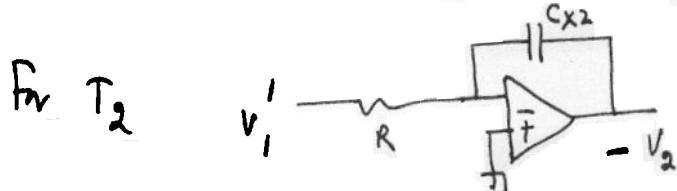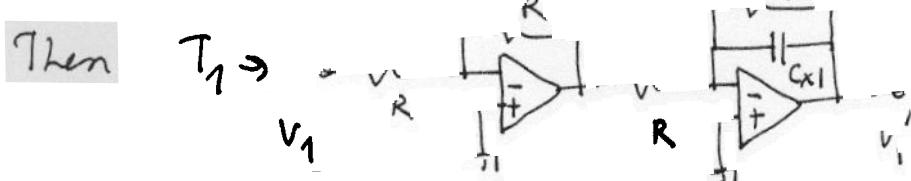
$$Y_3 \rightarrow \frac{1}{202 \times 10^{-3}} \rightarrow T_3 = \frac{R / 202 \times 10^{-3}}{s + \frac{100}{202 \times 10^{-3}}}$$



Q302
Contd:

For T_3

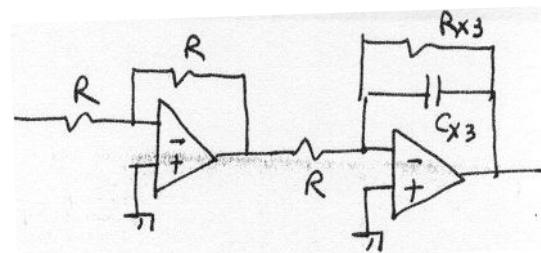


P 4 / 11
11

Let $R = 1 \text{ k}\Omega$

The design equations are: $R_x = \frac{R^2}{R_s} \quad \text{and} \quad C_x = \frac{L}{R^2}$

Thus for T_1 we have

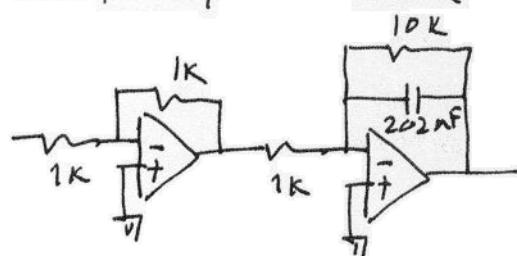


$$R_x = \frac{10^6}{100} = 10^4 = 10\text{K}$$

$$C_x = \frac{L}{R^2} = \frac{202\text{mH}}{10^6} = 202 \cancel{\text{nH}} \text{ nF}$$

So also for T_3


For $T_2 \Rightarrow$

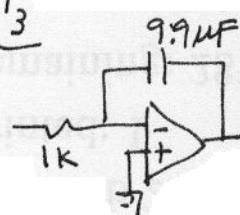

$$\frac{1}{RC_{x2}} \rightarrow \frac{1}{RC}$$

$$C_{x2} = C = 9.9\mu\text{F}$$

The interconnection is:

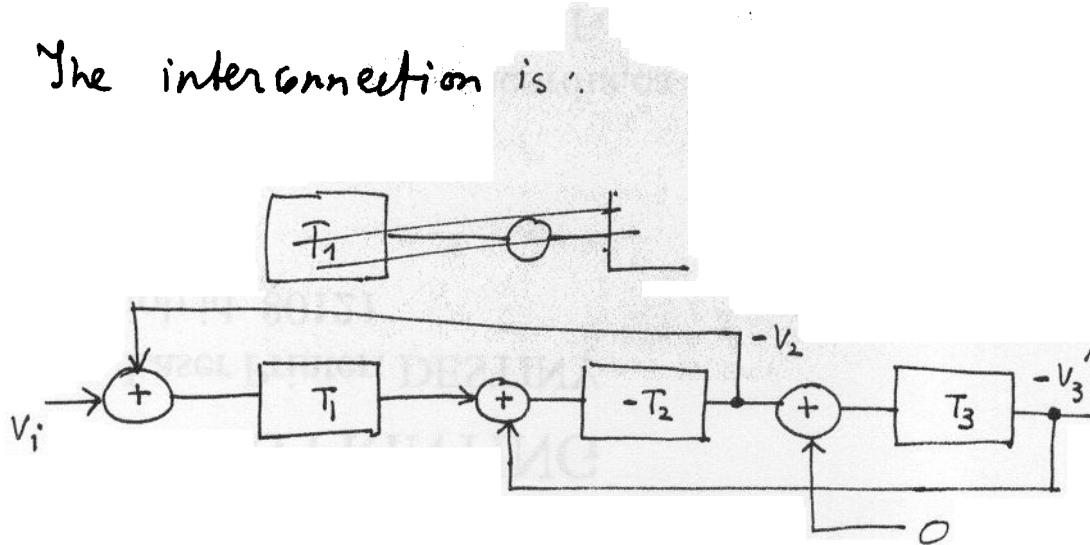


Q2 (A4.) VG class only

The Frequency denormalized

and impedance scaled L to L_s , R ladder
filter is

ELEC 441, MT.
W0809

PSI
11

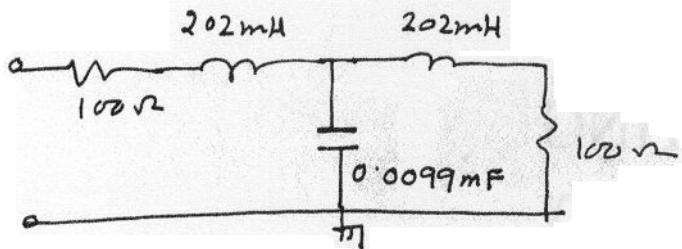


For FIDNR technique we consider an impedance scaling by $\frac{1}{R_s}$ so

$$R \rightarrow \frac{R}{R_s} = \frac{1}{s(\frac{R}{R_s})} = \frac{1}{s\bar{C}} ; \bar{C} = \frac{R}{R_s}$$


$$L \rightarrow sL / R_s = \frac{L}{R_s} = \bar{R} ; \bar{R} = \frac{L}{R_s}$$

$$C \rightarrow \frac{1}{sC} \cdot \frac{1}{R_s} = \frac{1}{s^2} \frac{1}{kC} = -\frac{1}{\omega^2 D} , D = kC$$

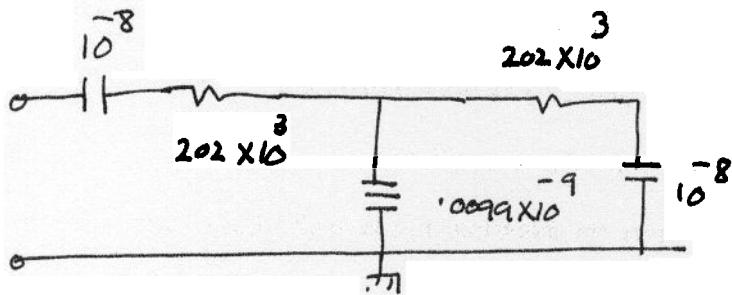The new filter will then look like let $k = 10^{-6}$



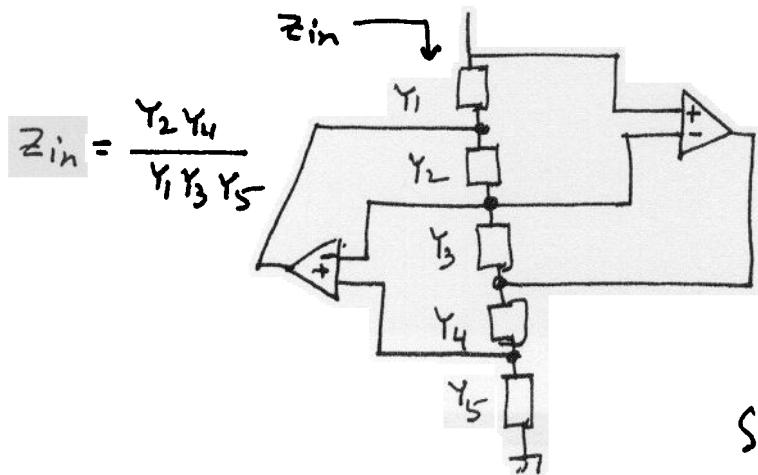For the super capacitor D, we use the GIC circuit



$$Z_{in} = \frac{Y_2 Y_4}{Y_1 Y_3 Y_5}$$

~~With $Y_2, Y_4, Y_5 \rightarrow \frac{1}{sC_x}$ each

$\therefore Y_1, Y_3 = \frac{1}{sL_x}$ each

$Z_{in} = \frac{1}{s^2 C_x^2} \frac{1}{sL_x} = \frac{1}{\omega^2} \frac{1}{C_x} G_x$

$\therefore D = kC = \frac{C_x}{G_x}$~~

Q2 (alt)
↙ Vh class only

But here $D = \frac{0.0099 \times 10^{-1}}{G_x^3} = \cancel{\frac{1}{G_x^3}}$

Let $G_x \rightarrow \frac{1}{R_x} = 10^{-2}$ i.e. $R_x = 100 \Omega$

Then $\frac{1}{G_x} = \frac{0.0099 \times 10^{-1}}{10^{-6}} = 0.0099 \times 10^{-15}$

p6 / 11
11

But here $D = \frac{0.0099 \times 10^{-1}}{G_x^3} = \cancel{\frac{G_x}{G_x^3}} \frac{G_x}{G_x}$

$G_x = G_x \times 99 \times 10^{-13}$

If $G_x = 10^{-2}$, i.e. $R_2, R_3, R_4 = 100 \Omega$ each

$G_x = 99 \times 10^{-15} = 99 f = 0.099 pF$

Q2: With $Y_2, Y_1, Y_3 = G_x$, $Y_4, Y_5 \rightarrow \propto G_x$ each


$Z_{in} = \frac{G_x}{s^2 C_x^2} = -\frac{1}{\omega^2 G_x^2} G_x = -\frac{1}{\omega D}$, so $D = \frac{C_x^2}{G_x}$

But here, $D = \frac{0.0099 \times 10^{-1}}{G_x^3} = \frac{G_x^2}{G_x}$

Let $G_x = 10^{-2}$ i.e. $R_2 = R_4 = R_3 = 100 \Omega$

So $G_x^2 = 0.0099 \times 10^{-11} = 99 \times 10^{-15}$
 $G_x = \sqrt{99 \times 10^{-15}} = 0.315 \times 10^{-6}$

So design for D is

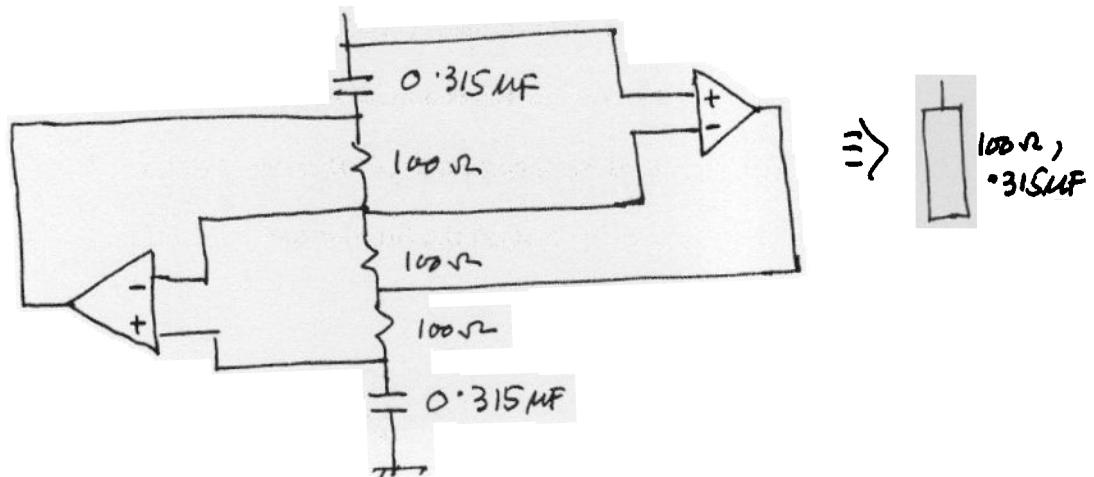


Q2
Alt.

UG class only

The overall complete system will include buffers at input and output, together with resistive paths through the filter structure. Thus:

P7/1
11

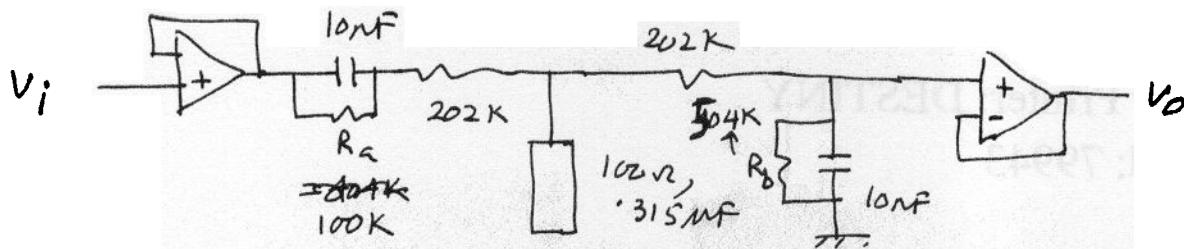

DC gain of the designed network is:

$$\frac{R_b}{R_b + R_a + 404K} = \text{DC gain of original ladder filter}$$

$$= 0.5$$

$$R_b = 0.5 R_a + \frac{202K}{0.5 R_b}, \quad \text{If } R_a = R_b = R \Rightarrow 0.5R = 202K$$

$$R = 404K \quad R_b = R_a + 404K; \quad \text{let } R_a = 100K, \quad \text{then } R_b = 504K$$

This completes the system design.

$$\left\langle \frac{504K}{100K + 404K + 504K} \right\rangle \rightarrow 0.5 \text{ DC gain}$$

Q3:
Q4:

$$T_N(s) = \frac{s^2 + 1}{s^2 + 1.5s + 1}$$

p8 |||

One can frequency denormalize by $\omega_0 = \sqrt{\mu_1 \mu_2} = 2000$ rad/sec
or, one can design the filter for

$$T_N = \frac{s^2 + 1}{s^2 + 1.5s + 1} \text{ and}$$

then use frequency denormalization.

After frequency denormalization, one gets

$$T(s) = \frac{\frac{s^2}{\omega_n^2} + 1}{\frac{s^2}{\omega_n^2} + 1.5 \frac{s}{\omega_n} + 1} = \frac{s^2 + \omega_n^2}{s^2 + 1.5 s \omega_n + \omega_n^2}$$

Example designing state variable technique } Possible Design #1


Tow-Thomas biquad

For $T_N(s)$, we see $T_N(s)|_{s \rightarrow \infty} = 1$; $\omega_n^2 = \omega_p^2 = 1$

So $C_1 = C$; $R_1 = \text{open}$ (does not exist)

$R_2 = R \cdot \left(\frac{\omega_p}{\omega_n}\right)^2 / \alpha = R$ $\because \omega_p = \omega_n$ here. e hf. gain = 1

The circuit is:

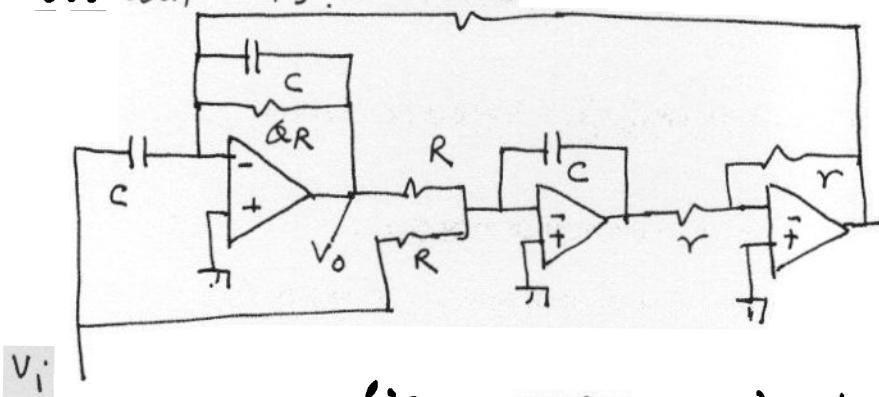


$$\frac{\omega_p}{\alpha} = \text{coeff. of } s \text{ in denom} \\ = 1.5, \text{ while } \omega_p^2 = 1$$

$$\alpha = \frac{\omega_p}{1.5} = \frac{1}{1.5} = 0.67$$

Q3:
(Q1 contd.)

Thus the circuit is:

p9
11

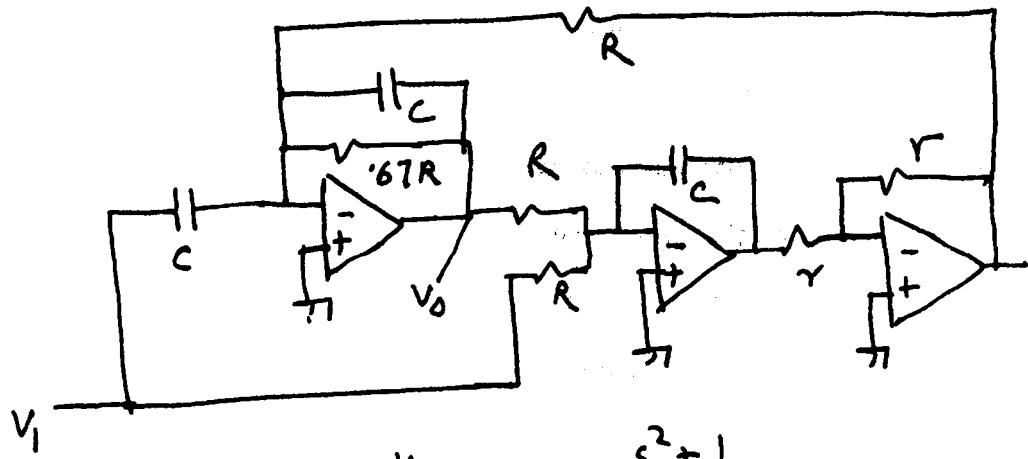

$$T_N(s) = \frac{V_0}{V_1} = \frac{s^2 + 1}{s^2 + 1 \cdot s + 1}$$

For normalized filter we take $R = 1$, $r = 1$, $C = 1$

For frequency denormalized filter, $\therefore \omega_p = 2000 \text{ rad/sec}$

we can take $R = \frac{1}{\sqrt{2000}}$ & $C = \frac{1}{\sqrt{2000}}$, so

that $\frac{1}{RC}$ becomes 2000. ~~we can keep~~

$$\text{Thus } R = 2.236 \times 10^{-2}; C = 2.236 \times 10^{-2}$$


For practical $R = 1 \text{ k}$, we use impedance

scaling by $\frac{1000}{2.236 \times 10^{-2}} = 44721.36$

$$\text{Then } R = 1 \text{ k}, C = \frac{2.236 \times 10^{-2}}{44721.36} = 0.499 \mu\text{F}$$

Let $r = 1 \text{ k}$ also. So final design is:
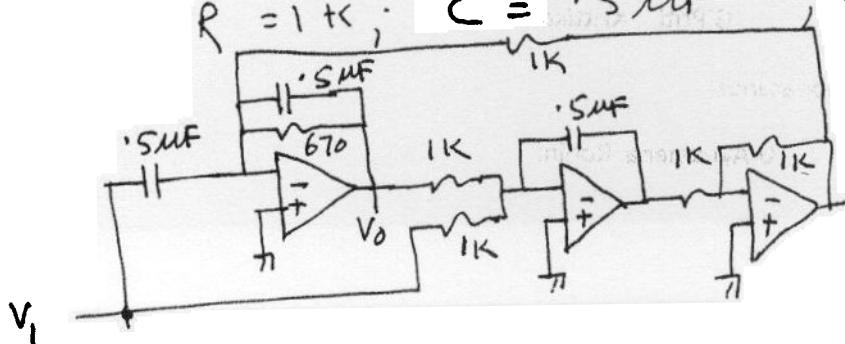
$$R = 1 \text{ k}; C = 0.5 \mu\text{F}, r = 1 \text{ k}$$



Q3:

(Contd.) Using Fleischer-Tor circuit

Possible Design #2

P10
11

$$\frac{V_o}{V_i} = - \frac{\left(\frac{R_8}{R_8}\right)s^2 + \frac{1}{R_1 C_1} \left[\frac{R_8}{R_8} - \frac{R_1 R_8}{R_4 R_7} \right] s + \frac{R_8}{\frac{R_3 R_5}{R_2} C_1 C_2 R_7}}{s^2 + \frac{1}{R_1 C_1} s + \frac{R_8}{\frac{R_2 R_3}{R_4 R_7} C_1 C_2 R_7}}$$

To match with

$$|T_N| = \frac{s^2 + 1}{s^2 + 1.5s + 1}$$

We shall make $\frac{R_8}{R_8} = 1$; $\frac{R_8}{R_3 R_5 R_7 C_1 C_2} = 1$

$$\frac{R_8}{R_8} = \frac{R_1 R_8}{R_4 R_7}, \quad \frac{1}{C_1 R_1} = 1.5, \quad \frac{R_8}{R_2 R_3 C_1 C_2 R_7} = 1$$

Let $R_8 = 1 = R_8 = R_3 = R_5 = R_7 = C_1 = C_2 = R_2$


Then

$$\frac{1}{C_1 R_1} \rightarrow \frac{1}{R_1} = 1.5; \quad R_1 = 0.67$$

$$\frac{1}{R_2} = 1, \quad R_2 = 1$$

$$\frac{R_1 R_8}{R_4 R_7} = \frac{0.67 \cdot 1}{R_4 \cdot 1} = \frac{R_8}{R_8} = 1 \quad \text{So } R_4 = 0.67 = R_1$$

Thus, the normalized design circuit is:

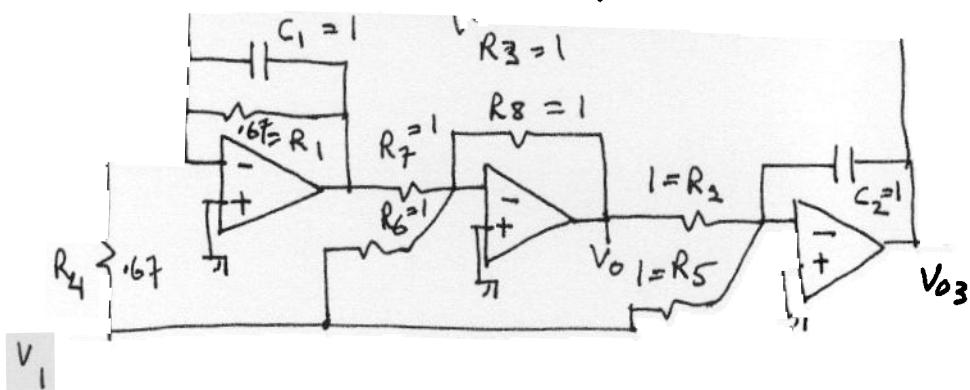

For frequency denormalized filter, since

$$\frac{R_8}{R_3 R_5 R_7 C_{1/2}} = \omega_0^2 = \frac{R_8}{R_2 R_3 C_{1/2} R_7}$$

Q3:

P11
11

$$\text{we can make } C_1 = C_2 = \frac{1}{\omega_0} = \frac{1}{2000}$$

Second int design is:


$$C_1 = 0.0005 \text{ F}, \text{ all others as before}$$

If now we want $R_8 = R_8 = R_3 = R_5 = R_7 = 1 \text{ k}\Omega$
we do impedance scaling Then

$$C_1 = 0.0005 / 1000 = 5 \times 10^{-7} = 0.5 \mu\text{F}$$

$$R_1 = R_4 = 670 \Omega, \text{ other resistances} = 1 \text{ k}\Omega$$

Final circuit is

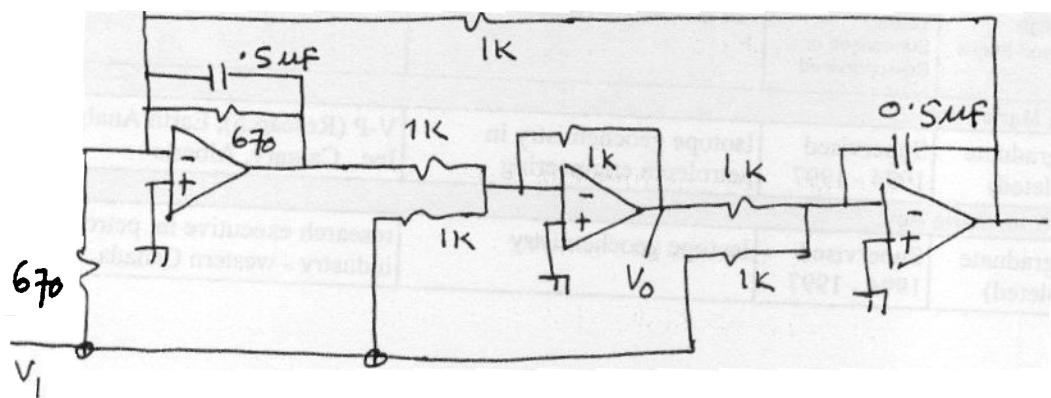

X —