

with notes

Mid-Term Examination Analog/IC Filter Design (ELEC 441/6081)


Electrical and Computer Engineering Department
Concordia University

February 28, 2007

Instructor: Dr. R. Raut

Time: 75 minutes

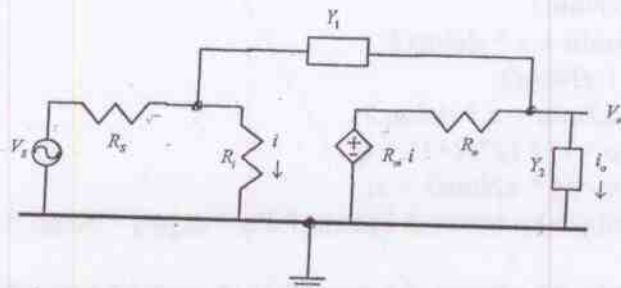
Q.1: In the figure below all voltage and currents are *small ac* signals. The elements Y_1, Y_2 can be chosen to produce different signal processing functions pertaining to electronic filters.



- (a) What will be your choice for Y_1, Y_2 so that the function V_o/V_s is a second order transfer function in $s = j\omega$? Prove your point by an analytical expression for V_o/V_s .
- (b) If in the ideal case of $R_1 \rightarrow 0, R_o \rightarrow 0$, and $R_m Y_1 \gg 1$, show that V_o/V_s becomes an inverting integrator function with $Y_1 = sC_1$
- (c) With the same conditions as in (b) above and further that $Y_2 = sC_2$, and $Y_1 = 1/R_1$, show that i_o/V_s represents a differentiator function.

Q.2: You are required to design a BPF with the pass-band extending from $\omega = 10^5$ rad/sec to $\omega = 4 \times 10^5$ rad/sec. The filter has *equal ripple* characteristic in the pass-band with peak-to-peak value not exceeding 1 dB. At $\omega = 15.263 \times 10^5$ rad/sec, the response must be at least 60 dB down relative to the pass-band.

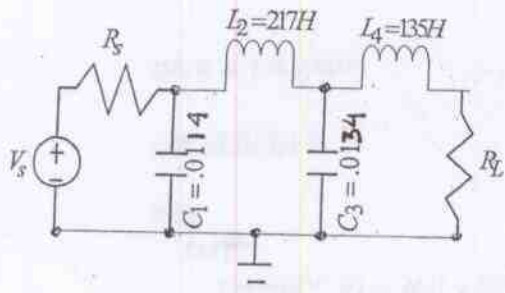
- (a) Synthesize the normalized low-pass filter function associated with the intended band-pass filter.
- (b) The figure below shows an L,C realization of the low-pass filter function in (a). Based on this, design the band-pass filter as specified in Q.2 above.



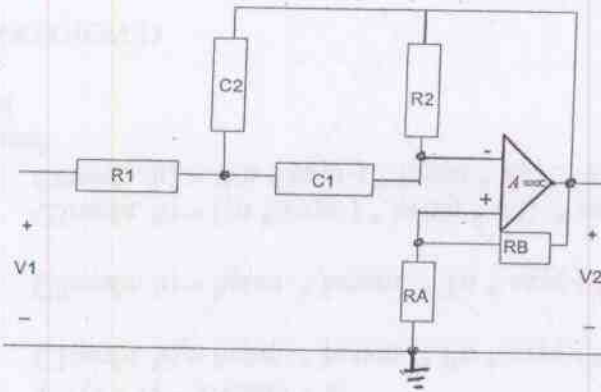Q.3: Consider the band-pass filter network of figure below. It combines both positive and negative feed-back around an ideal OA. The voltage transfer function is given by:

$$\frac{V_2}{V_1} = \frac{-s(K+1)/(R_1 C_2)}{s^2 + s[1/(R_2 C_2) + 1/(R_2 C_1) - K/(R_1 C_2)] + 1/(R_1 R_2 C_1 C_2)}, \text{ with } K = R_A/R_B.$$

Assume $K=1$. Design the element values to meet the specifications: $f_p=10$ kHz, $Q_p=10$ and $C=0.1$ μ F each.



Filter Function Tables

A.1: Coefficients of denominator polynomial, in the form $s^n + a_1s^{n-1} + a_2s^{n-2} + \dots + a_{n-2}s^2 + a_{n-1}s + 1$, for Butterworth filter function of order n , with pass-band from 0 to 1 rad/sec⁺.

n	a_1	a_2	a_3	a_4	a_5	a_6
2	1.4142					
3	2.0000	2.0000				
4	2.6131	3.4142	2.6131			
5	3.2361	5.2361	5.2361	3.2361		
6	3.8637	7.4641	9.1416	7.4641	3.8637	
7	4.4940	10.0978	14.5918	14.5918	10.0978	4.4940

A.2: Coefficients of denominator polynomial, in the form $s^n + a_1s^{n-1} + a_2s^{n-2} + \dots + a_{n-2}s^2 + a_{n-1}s + a_n$, for Chebyshev filter function of order n , with pass-band from 0 to 1 rad/sec⁺.


Pass-band ripple A_p	n	a_1	a_2	a_3	a_4	a_5	a_6
0.5 dB $\epsilon=0.3493$	1	2.863					
	2	1.425	1.516				
	3	1.253	1.535	0.716			
	4	1.197	1.717	1.025	0.379		
	5	1.1725	1.9374	1.3096	0.7525	0.1789	
	6	1.1592	2.1718	1.5898	1.1719	0.4324	0.0948
1.0 dB $\epsilon=0.5089$	1	1.965					
	2	1.098	1.103				
	3	0.988	1.238	0.491			
	4	0.953	1.454	0.743	0.276		
	5	0.9368	1.6888	0.9744	0.5805	0.1228	
	6	0.9282	1.9308	1.2021	0.9393	0.3071	0.0689
2.0 dB $\epsilon=0.7648$	1	1.308					
	2	0.804	0.637				
	3	0.738	1.022	0.327			
	4	0.716	1.256	0.517	0.206		
	5	0.7065	1.4995	0.6935	0.4593	0.0817	
	6	0.7012	1.7459	0.8670	0.7715	0.2103	0.0514

A.3: Coefficients of denominator polynomial, in the form $s^n + a_1s^{n-1} + a_2s^{n-2} + \dots + a_{n-2}s^2 + a_{n-1}s + a_n$, for Bessel-Thomson filter function of order n ⁺.


n	a_1	a_2	a_3	a_4	a_5	a_6
1	1					
2	3	3				
3	6	15	15			
4	10	45	105	105		
5	15	105	420	945	945	
6	21	210	1260	4725	10395	10395

⁺ R. Schaumann et al, "Design of Analog Filters- Passive, Active RC, and Switched Capacitor", Prentice-Hall Inc., © 1990

Q1:

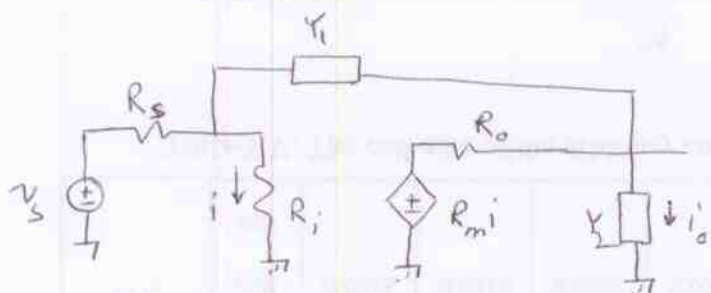

(a) For nodal analysis we re-draw

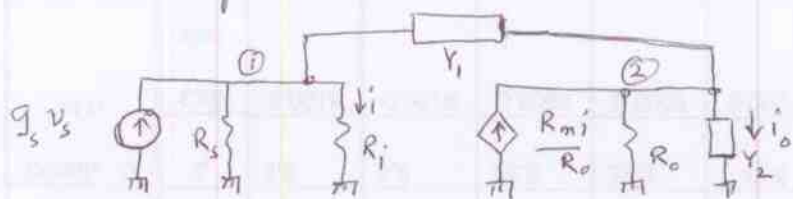

$$\begin{pmatrix} g_s + g_i + Y_1 & -Y_1 \\ -Y_1 & Y_1 + g_o + Y_2 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} g_s v_s \\ \frac{R_m}{R_o} i \end{pmatrix}$$

But $i = V_1 g_i$
 $\frac{R_m}{R_o} i = \frac{R_m}{R_o} g_i V_1$

$$\begin{pmatrix} g_s + g_i + Y_1 & -Y_1 \\ -Y_1 - \frac{R_m}{R_o} g_i & Y_1 + g_o + Y_2 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} g_s v_s \\ 0 \end{pmatrix}$$

$$\Delta = (g_s + g_i + Y_1)(Y_1 + g_o + Y_2) - Y_1 \left(Y_1 + \frac{R_m}{R_o} g_i \right)$$

$$V_0 = V_2 = \frac{1}{\Delta} \begin{vmatrix} g_s + g_i + Y_1 & g_s v_s \\ -Y_1 - \frac{R_m}{R_o} g_i & 0 \end{vmatrix} = \frac{g_s v_s \left(Y_1 + \frac{R_m}{R_o} g_i \right)}{\Delta}$$

$$\text{So } \frac{V_0}{V_s} = \frac{g_s \left(Y_1 + \frac{R_m}{R_o} g_i \right)}{(g_s + g_i + Y_1)(Y_1 + g_o + Y_2) - Y_1 \left(Y_1 + \frac{R_m}{R_o} g_i \right)}$$

This will be a second order transfer function, ie $s^2 + bs + c$ if both Y_1 and Y_2 are capacitive admittances. We shall have

$$\begin{aligned} D(s) &= g_s Y_1 + g_s g_o + g_s Y_2 + g_i Y_1 + g_i g_o + g_i Y_2 + Y_1 g_o + Y_1 Y_2 - Y_1 g_i \frac{R_m}{R_o} \\ &= s^2 c_1 c_2 + s (c_1 g_s + c_2 g_s + c_1 g_i + c_2 g_i + c_1 g_o - c_1 g_i \frac{R_m}{R_o}) + g_s g_o + g_i g_o \end{aligned}$$

Q1(b) $R_i \rightarrow 0, R_o \rightarrow 0$ implies $G_i, G_o \rightarrow \infty$, note $G_o = \frac{1}{R_o}$; $G_i = \frac{1}{R_i}$

$$\frac{V_o}{V_s} = \frac{G_i G_o g_s \left(\frac{Y_1}{G_i G_o} + R_m \right)}{G_i G_o \left(\frac{G_s}{G_i} + 1 + \frac{Y_1}{G_i} \right) \left(\frac{Y_1}{G_o} + \frac{Y_2}{G_o} + 1 \right) - G_i G_o Y_1 \left(\frac{Y_1}{G_i G_o} + R_m \right)}$$

The ratio $\rightarrow \frac{g_s R_m}{1 - Y_1 R_m}$ as $G_i, G_o \rightarrow \infty$

If $Y_1 R_m \gg 1$, then this becomes $\approx -\frac{g_s}{Y_1} = -\frac{g_m}{s C_1}$ an inverting integrator

(c) With same assumptions and noting

$$i_o = Y_2 V_o$$

$$\frac{i_o}{V_s} = Y_2 \frac{V_o}{V_s} = -\frac{g_s Y_2}{Y_1} = -g_s R_1 C_2 = -s g_s R_1 C_2 \text{ inverting differentiator.}$$

Q2: $B = \omega_2 p_2 - \omega_1 p_1 = 3 \times 10^5 \rightarrow \omega_c$ in the associated LPF.
equal ripple \rightarrow CHEB approximation

Considering the LP \rightarrow BP frequency transformation

$$\bar{s} = \frac{\omega_0}{B} \left(\frac{s}{\omega_0} + \frac{\omega_0}{s} \right) \text{ leads to } (s \rightarrow j\omega)$$

$$\bar{\omega} = \frac{\omega_0}{B} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

Set $\omega_0 = \sqrt{\omega_{p2} \omega_{p1}}$, $\omega = 15.263 \times 10^5$ in the stop-band

$$\bar{\omega} = \frac{2 \times 10^5}{3 \times 10^5} \left(\frac{15.263 \times 10^5}{2 \times 10^5} - \frac{2}{15.263} \right) = 5.003$$

$\bar{\omega}$ is the normalized stop-band frequency in the associated LPF.

Q2(a): Using $A_p = 1 \text{ dB}$, $A_a = 60 \text{ dB}$ and the above ratio $\omega_a/\omega_c = 5$, we can calculate the order of the associated LPF with CHEB response.

$$\text{Thus } D = \frac{10^{.1A_a} - 1}{10^{.1A_p} - 1} = \frac{10^6 - 1}{10^1 - 1} = 3862112.232$$

$$\sqrt{D} =$$


$$n \approx \frac{\cosh^{-1} \sqrt{D}}{\cosh^{-1}(\omega_a/\omega_c)} = 3.61 \text{ . We take } n = 4$$

Using Tables


$$H_n(s) = \frac{1/2^3 \times .50885}{s^4 + .9528s^3 + 1.4539s^2 + .7426s + .27563}$$

note, for $A_p = 1 \text{ dB}$, $E = \sqrt{10^{.1} - 1} = .50885$.

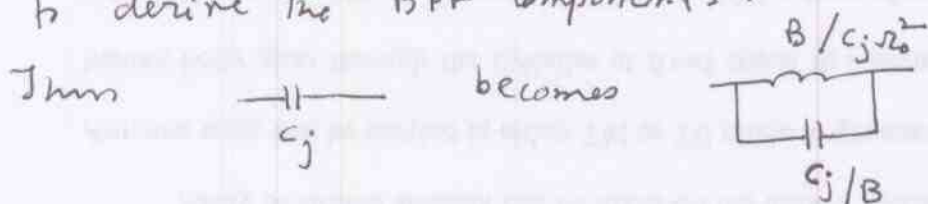2(b) We have to use component transformation formula to derive the BPF components.



The BPF network will be:

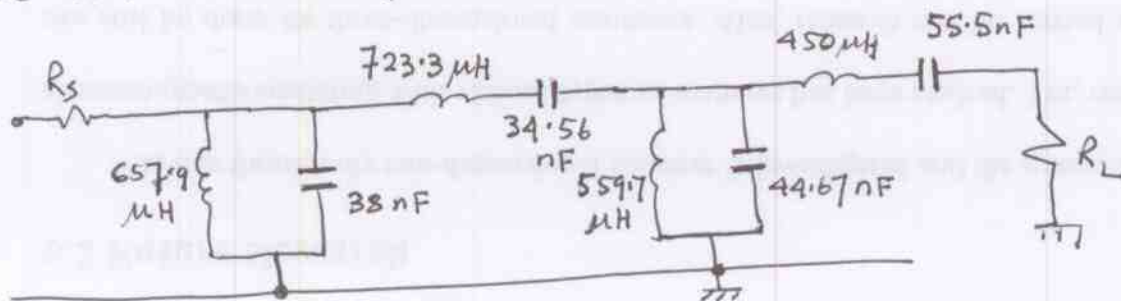

We used $\omega_0 = 2 \times 10^5$, $B = 3 \times 10^5$

Q3:

Compare with the standard BPF expression

$$T(s) = \frac{-H_0 \left(\frac{\omega_p}{\omega_p} \right) s}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

We see:

$$H_0 \frac{\omega_p}{Q_p} = (k+1)/R_1 C_2 = 2/R_1 C_2 \quad \because k=1 \text{ given}$$

$$\frac{\omega_p}{Q_p} = \frac{1}{R_2 C_2} + \frac{1}{R_2 C_1} - \frac{1}{R_1 C_2}$$

$$\omega_p = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

Further given $C_1 = C_2 = 0.1 \mu\text{F}$ each.

$$\text{Thus } \omega_p = \frac{1}{C} \frac{1}{\sqrt{R_1 R_2}}$$

$$\frac{\omega_p}{Q_p} = \frac{1}{C} \left(\frac{1}{R_2} + \frac{1}{R_2} - \frac{1}{R_1} \right) = \frac{1}{C} \left(\frac{2}{R_2} - \frac{1}{R_1} \right)$$

Given specs. $\omega_p = 2\pi \times 10^4$; $Q_p = 10$.

$$\text{So } \frac{1}{C} \frac{1}{\sqrt{R_1 R_2}} = 2\pi \times 10^4 \quad ; \quad \frac{1}{\sqrt{R_1 R_2}} = 2\pi \times 10^4 \times 10^{-7} = 2\pi \times 10^{-3} \dots (1)$$

$$\frac{\omega_p}{Q_p} = \frac{2\pi \times 10^4}{10} = 2\pi \times 10^3 = \frac{1}{C} \left(\frac{2}{R_2} - \frac{1}{R_1} \right)$$

$$\frac{2}{R_2} - \frac{1}{R_1} = 2\pi \times 10^3 \times 10^{-7} = 2\pi \times 10^{-4} \dots (2)$$

$$\text{And } \frac{2}{R_1 C_2} = \frac{2}{R_1} \cdot 10^7 = H_0 \cdot \frac{2\pi \times 10^4}{10} = H_0 \cdot 2\pi \times 10^3$$

$$\frac{1}{R_1} = H_0 \cdot \frac{2\pi \times 10^3}{2 \times 10^7} = H_0 \cdot \pi \times 10^{-4} \dots (3)$$

Q3 (contd.)

Eqs. (1) and (2) are more important in the present case since these relate to ω_p and Q_p .

$$\text{Let } R_2 = m^2 R_1$$

$$\text{Then } \frac{1}{\sqrt{R_1 \cdot m^2 R_1}} = 2\pi \times 10^{-3} \quad \text{or } m R_1 = \frac{10^3}{2\pi} \dots (4)$$

$$\text{and } \frac{2}{m^2 R_1} - \frac{1}{R_1} = 2\pi \times 10^{-4} \quad ; \quad \frac{1}{R_1} \left(\frac{2}{m^2} - 1 \right) = 2\pi \times 10^{-4} \dots (5)$$

Multiply (4) and (5)

$$\frac{2}{m} - m = \frac{10^3}{2\pi} \times 2\pi \times 10^{-4} = 10^{-1}$$

$$2 - m^2 = 0.1m \quad ; \quad m^2 + 0.1m - 2 = 0.$$

$$m = \frac{-0.1 \pm \sqrt{0.01 + 8}}{2} = \frac{-0.1 \pm 2.8302}{2}$$

$$= 1.365 \text{ or } -2.9302$$

Acceptable value of m is 1.365 (a +ve number)

$$\text{So } R_2 = 1.365^2 R_1 = 1.86323 R_1$$

$$\text{Using (4)} \quad R_1 = \frac{10^3}{2\pi \times 1.365} \approx 116.6 \, \Omega \quad C_1 = C_2 = 0.1 \, \mu\text{F}$$

$$\text{Then } R_2 = 217.25 \, \Omega$$

DESIGN

$$\text{The filter will have } H_0 = \frac{10^4}{\pi R_1} \quad \text{from eqn (4)}$$

$$= 27.299 \approx 27.3$$

Since $K = \frac{R_A}{R_B} = 1$, we can choose $R_A = R_B = 100 \, \Omega$