

Analog/IC Filter Design (ELEC 441/6081) Mid-Term Test#1 (Winter 2011-2012)

Electrical and Computer Engineering Department
Concordia University
February 27, 2012

NOTE to UG students: Answer ONLY THREE questions. If you answer *more than three* questions, the last answer will be discarded (i.e., NOT marked).

Student id# _____

Time: 60 minutes

Q.1: Figure 1 shows a filter circuit with a voltage amplifier (VCVS) of gain K . Derive the expression for the voltage transfer function (VTF) $V_2(s)/V_1(s)$.

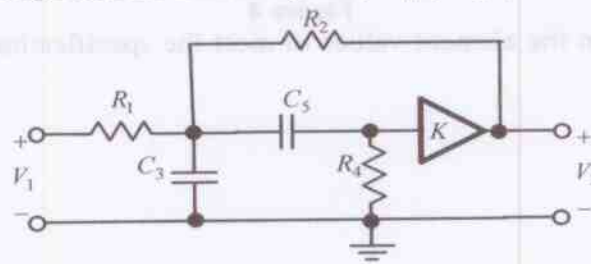


Figure 1

Q.2: Determine the transfer function of a *maximally flat* low-pass filter with a loss of 1dB at the pass-band edge frequency $f_c = 10$ kHz, and an attenuation of at least 25 dB at $f_a = 40$ kHz.

Q.3: You are required to design a BPF with the pass-band extending from $\omega = 10^5$ rad/sec to $\omega = 4 \times 10^5$ rad/sec. The filter has *equal ripple* characteristic in the pass-band with peak-to-peak value not exceeding 1 dB. At $\omega = 15.263 \times 10^5$ rad/sec, the response must be at least 60 dB down relative to the pass-band.

- (a) Synthesize the *normalized low-pass filter function* associated with the intended band-pass filter.
- (b) Show the L, C ladder realization of the *normalized low-pass filter* terminated in a 1 ohm resistance and fed from an *ideal voltage source*.

Q.4: Consider the band-pass filter network of figure 4. It combines both positive and negative feed-back around an ideal OA. The voltage transfer function is given by:

$$\frac{V_2}{V_1} = \frac{-s(K+1)/(R_1 C_2)}{s^2 + s[1/(R_2 C_2) + 1/(R_2 C_1) - K/(R_1 C_2)] + 1/(R_1 R_2 C_1 C_2)}, \text{ with } K = R_A / R_B.$$

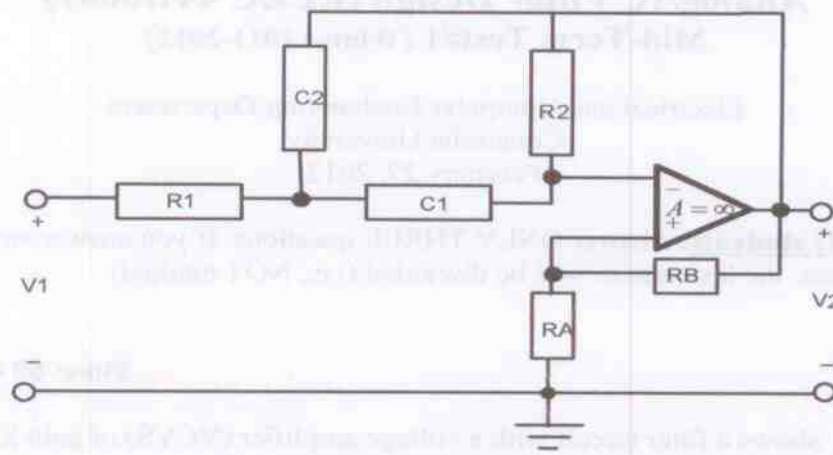


Figure 4

Assuming $K=1$, design the element values to meet the specifications: $f_p=10$ kHz, $Q_p=5$ and $C=0.1 \mu\text{F}$ each.



Filter Function Tables

(next page)

Filter Function Tables

A.1: Coefficients of denominator polynomial, in the form $s^n + a_1s^{n-1} + a_2s^{n-2} + \dots + a_{n-2}s^2 + a_{n-1}s + 1$, for Butterworth filter function of order n , with pass-band from 0 to 1 rad/sec⁺.

| n | a_1 | a_2 | a_3 | a_4 | a_5 | a_6 |
|-----|--------|---------|---------|---------|---------|--------|
| 2 | 1.4142 | | | | | |
| 3 | 2.0000 | 2.0000 | | | | |
| 4 | 2.6131 | 3.4142 | 2.6131 | | | |
| 5 | 3.2361 | 5.2361 | 5.2361 | 3.2361 | | |
| 6 | 3.8637 | 7.4641 | 9.1416 | 7.4641 | 3.8637 | |
| 7 | 4.4940 | 10.0978 | 14.5918 | 14.5918 | 10.0978 | 4.4940 |

A.2: Coefficients of denominator polynomial, in the form $s^n + a_1s^{n-1} + a_2s^{n-2} + \dots + a_{n-2}s^2 + a_{n-1}s + a_n$, for Chebyshev filter function of order n , with pass-band from 0 to 1 rad/sec⁺.

| Pass-band ripple A_p | n | a_1 | a_2 | a_3 | a_4 | a_5 | a_6 |
|-----------------------------|-----|--------|--------|--------|--------|--------|--------|
| 0.5 dB $\epsilon=0.3493$ | 1 | 2.863 | | | | | |
| | 2 | 1.425 | 1.516 | | | | |
| | 3 | 1.253 | 1.535 | 0.716 | | | |
| | 4 | 1.197 | 1.717 | 1.025 | 0.379 | | |
| | 5 | 1.1725 | 1.9374 | 1.3096 | 0.7525 | 0.1789 | |
| | 6 | 1.1592 | 2.1718 | 1.5898 | 1.1719 | 0.4324 | 0.0948 |
| 1.0 dB $\epsilon=0.5089$ | 1 | 1.965 | | | | | |
| | 2 | 1.098 | 1.103 | | | | |
| | 3 | 0.988 | 1.238 | 0.491 | | | |
| | 4 | 0.953 | 1.454 | 0.743 | 0.276 | | |
| | 5 | 0.9368 | 1.6888 | 0.9744 | 0.5805 | 0.1228 | |
| | 6 | 0.9282 | 1.9308 | 1.2021 | 0.9393 | 0.3071 | 0.0689 |
| 2.0 dB $\epsilon=0.7648$ | 1 | 1.308 | | | | | |
| | 2 | 0.804 | 0.637 | | | | |
| | 3 | 0.738 | 1.022 | 0.327 | | | |
| | 4 | 0.716 | 1.256 | 0.517 | 0.206 | | |
| | 5 | 0.7065 | 1.4995 | 0.6935 | 0.4593 | 0.0817 | |
| | 6 | 0.7012 | 1.7459 | 0.8670 | 0.7715 | 0.2103 | 0.0514 |

⁺ R. Schaumann et al, "Design of Analog Filters- Passive, Active RC, and Switched Capacitor", Prentice-Hall Inc., © 1990