


# Ch. 5 (Hints & Solns)

S.1

(a)  $H(s) = H_0 \frac{s^2}{s^2 + 0.1s + 1}$

$C_1 = C_3 = 1F$   
 $R_2 = R_4$

Use the configuration (Fig 5.5)

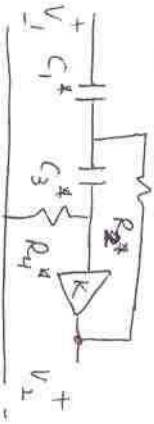

From Table 5.4

$\omega_p^2 = 1 = \frac{1}{R_2 R_4 C_1 C_3}$

$\frac{1}{\omega_p} = 0.1 = \frac{\sqrt{R_2 C_1}}{\sqrt{R_4 C_3}} + (1-K) \sqrt{\frac{R_4 C_3}{R_2 C_1}}$

Using  $R_2 = R_4 = R$  ;  $\omega_p^2 = 1 = \frac{1}{R^2 C_1}$

or  $R = 1 \Omega$

Then  $\frac{1}{\omega_p} = 0.1 = 1 + 1 + 1 - K = 3 - K$  ;  $K = 3 - 0.1 = 2.99$

Then,  $H(s) = 2.99 \frac{s^2}{s^2 + 0.1s + 1}$

with  $C_1 = C_3 = 1F$


$R_2 = R_4 = 1 \Omega$

$K = 2.99$

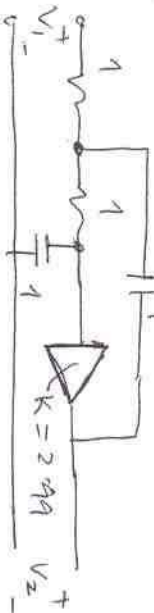(b) On using OR: RC transformation

$H(s) \rightarrow H^*(s) = \frac{(\frac{\omega_p^2}{s})^2}{(\omega_p^2/s)^2 + 0.1 \frac{\omega_p^2}{s} + 1} = \frac{1}{1 + 0.1s + s^2}$

which is a LPF with  $\omega_p = 1$ ,  $1/\omega_p = 0.1$  the transformed filter is



(5.2)

$\omega_p = 2\pi \times 1000$  MF  
 $\omega_p = 10$   
 $H_0 = 4$

$G_s = \sigma_s = 0.1$  ;  $r = C$   
 see Remark of Fig. 5 and Table 4.2

$$H_0 = \frac{k/R_1}{\dots}$$

$$\frac{1}{\omega_p} = \frac{[ (1-k) (R_1/R_2) + 1 ] \sqrt{\frac{R_4 G_s}{R_1 G_s}} + \sqrt{\frac{R_1 G_s}{R_4 G_s}} + \sqrt{\frac{R_1 G_s}{R_4 G_s}}}{\sqrt{1 + R_1/R_2}}$$

$$\omega_p = \frac{\sqrt{1 + R_1/R_2}}{C \sqrt{R_1/R_2}} \quad \text{where } C = 0.1 \text{ MF}$$

Let  $R_1/R_2 = m$  ;  $R_1/R_4 = n$ . Then

$$H_0 = \frac{k/R_1}{\frac{1/R_1 + \frac{m}{R_1} + \frac{2n}{R_1} - \frac{km}{R_1}}{k}} = \frac{k}{1 + m + 2n - km} = 4$$

5.2 contd

$$\frac{1}{\sigma_p} = \frac{\sqrt{1+m}}{[(1-k)m+1]\left[\sqrt{\frac{1}{n}} + \sqrt{n} + \sqrt{n}\right]} = 0.1$$

$$\sigma_p = \frac{\sqrt{1+m}}{2} = 2\pi \times 1000$$

$$\text{dof } k = 2; H_0 = 4 = \frac{1+m+2n-2m}{2} = \frac{1+2n-m}{2}$$

$$2 + 4n - 2m = 1 \Rightarrow 4n - 2m = -1 \Rightarrow m = 2n + 5$$

$$\text{Plug into } 1/\sigma_p = 0.1 = \frac{\sqrt{1+m}}{(1-m)\left(\frac{1}{n} + 2\sqrt{n}\right)} = \frac{\sqrt{1+m}}{(8-2n)\left(\frac{1}{n} + 2\sqrt{n}\right)}$$

$$0.1 \sqrt{1.5+2n} = \frac{\sqrt{n}}{.5-2n} + 2\sqrt{n} = \frac{\sqrt{n}}{.5-2n+2n}$$

$$\text{or } 0.1 \sqrt{1.5n+2n^2} = 0.5 \Rightarrow 2n^2 + 1.5n - 25 = 0$$

$$n = \frac{1}{2} \left[ -1.5 \pm \sqrt{2.25 + 200} \right] = \frac{1}{2} [-1.5 \pm 14.23] \Rightarrow 3.1826 = n$$

$$\text{Then } m = 2n + 5 = 6.865 = m \quad (\text{the positive value})$$

$$\text{Plug into } \sigma_p = \frac{\sqrt{1+6.865}}{2.8045} = \frac{C \cdot R_y \cdot \sqrt{3.1826}}{1.78398} = \frac{C \cdot R_y}{1} = 2\pi \times 1000$$

Put  $C = 0.01$  MPa, get  $R_y$

$$R_y = \frac{2.8045}{1} \cdot 10^8 \cdot \frac{1.78398}{2\pi \times 1000} = 25.0199 \text{ k}$$

$$\text{Then } R_1 = n R_y = 79.6283 \text{ k}$$

$$R_2 = \frac{R_1}{m} = 11.599 \text{ k}$$

Then,  $k = 2, R_1 = 79.628 \text{ k}, R_2 = 11.599 \text{ k}, R_3 = 35.02 \text{ k}$   
 $C_3 = C_5 = 0.01$  MPa is the design. (TRY  $k = 3, 4$ .)

S.3

(a)

SK, BP filter with

$$H(\omega) = \frac{600s}{s^2 + 600s + 3 \times 10^8}$$

$$\omega_p^2 = 3 \times 10^8$$

$$\text{So } \omega_p = 10^4 \sqrt{3} = 1.732 \times 10^4$$

$$\omega_p / \omega_c = 600 \quad ; \quad \omega_c = \frac{600}{\omega_p} = 1.732 \times 10^4 / 600 = 28.9$$

The design equations are (see Table 5.4)

↓ connection required



Let  $w_{pR} = \alpha$  then  
 Note  $3 \times 10^8 \times (R) \rightarrow$  is unitless number

$$H_0 = 1 = \frac{n+1+1+(1-k)mn}{nR} = \frac{2 + \frac{3 \times 10^8 CR^2}{m+1} + (1-k)m(m+1)}{\frac{3 \times 10^8 CR^2}{m+1} + k}$$

Also  $H_0 = \frac{k/Rc}{\frac{1}{Rc} + \frac{1}{nRc} + \frac{1}{(1-k)m/R}}$

$$\sqrt{\frac{3 \times 10^8 R^2 C^2}{1+m}} = 28.9 \left\{ 2 + n + m(1-k) \right\}$$

$$\sqrt{n(1+m)} = 28.9 \left[ 2 + \left\{ 1 + m(1-k) \right\} n \right]$$

$$= \frac{\sqrt{n(1+m)}}{[1+m(1-k)]n+2} = \frac{1}{28.9} = c \cdot \frac{R_1}{m}$$

$R_2 C = R_1 C$

$$\frac{1}{\Delta p} = \frac{1}{28.9} = \frac{\sqrt{1+m}}{[1+m(1-k)]\left[\sqrt{n} + \frac{1}{n} + \frac{1}{m}\right]}$$

Then  $w_p^2 = 3 \times 10^8 = \frac{1+m}{nR_1^2 C^2} \Rightarrow n = \frac{3 \times 10^8 (R_1 C)^2}{(1+m)}$

Let  $R_1 = R$ ,  $R_2 = m$ ,  $R_3 = n$ , Let  $R_1 = R$ ,  $C_3 = C = c$ ,  $R_3 = n$

$$H_0 = \frac{k/R_1 C_3}{\frac{1}{R_1 C_3} + \frac{1}{n R_1 C_3} + \frac{1}{(1-k)/R_2 C_3}}$$

$$\frac{1}{\Delta p} = \frac{1}{28.9} = \frac{1+R_1/R_2}{\frac{R_1 R_2 C_3}{1+R_1/R_2} + \sqrt{\frac{R_1 C_3}{R_2 C_3}} + \sqrt{\frac{R_1 C_3}{R_3 C_3}}}$$

5.13 cond.

$$1 = \frac{(m+1)k}{2 + \frac{m+1}{\alpha^2} + (1-k)m(m+1)}$$

$$1 = \frac{(m+1)k}{2\alpha^2 + (m+1) + (1-k)(m+1)m} \leftarrow \text{from H}_0$$

$$\frac{\alpha}{1+m} = 28.9 \left[ 2 + \{1+m(1-k)\} \frac{1+m}{\alpha^2} \right] \leftarrow \text{from } \frac{1}{\alpha^2}$$

$$\alpha(1+m) = 28.9 \left[ 2\alpha^2 + (1+m) \{1+m-mk\} \right]$$

$$\alpha(1+m) = 28.9 \left[ 2\alpha^2 + (1+m)^2 - m(1+m)k \right]$$

From the expression, we can solve for  $k$  in terms of  $m$  &  $\alpha$

$$\text{Thus } k = \frac{1+2m+m^2+2\alpha^2}{1+2m+m^2} = 1 + \frac{2\alpha^2}{1+2m+m^2}$$

$$1-k = - \frac{2\alpha^2}{1+2m+m^2} = 1+m(1-k) = 1+m \frac{1+2m+m^2-2\alpha^2}{1+2m+m^2} = 1 - \frac{2m\alpha^2}{1+2m+m^2}$$

Thus from  $\frac{1}{\alpha^2}$  expression

$$\frac{\alpha}{1+m} = 28.9 \left[ 2 + \left\{ 1 - \frac{2m\alpha^2}{1+2m+m^2} \right\} \frac{1+m}{\alpha^2} \right]$$

$$(1+m)\alpha = 28.9 \left[ 2\alpha^2 + (1+m) \left( 1 - \frac{2m\alpha^2}{1+2m+m^2} \right) \right]$$

We can solve the above eqn and obtain  $m$  in a function of  $\alpha = N_p CR$ . Thus, for  $\alpha = 33$ ,  $m = 122.9$ ,  $k = 1.148$ ,  $n = 0.1138$

5.3  
Contd

$$\alpha = 33, \omega_p CR = 1.732 \times 10^4 CR$$

$$\text{but } C = R = \sqrt{\frac{33}{1.732 \times 10^4}} \approx 0.04365$$

Then  $C_3 = C_5 = 0.04365$

$$R_1 = R = 0.04365, R_2 = \frac{R_1}{m} = \frac{0.04365}{122.9} = 0.000355$$

$$R_4 = nR_1 = 0.1138 \times 0.04365 = 0.004966$$

If we take  $R_2$  to  $100 \Omega$  (scale factor 281557.8465)

$$R_2 = 100 \Omega, R_1 = 12290 \Omega, R_4 = 1398.3 \Omega$$

$$C_3 = C_5 = C = 0.04365 / 281557.8465 = 0.155 \mu F$$


$$K = 1.142$$

Verified:  $\omega_p^2 = 0.2999 \times 10^9$ ;  $H_0 = 1.013$ ,  $\omega_p = 29.284$



5.4

Average for nodal analysis:

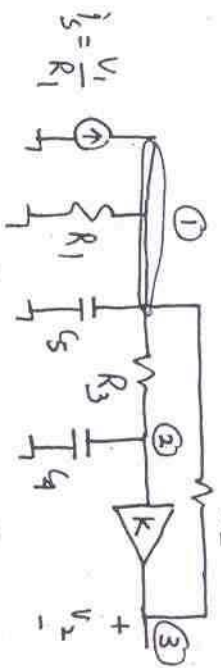

$$\begin{bmatrix} G_1 + G_3 + G_2 + sC & -G_3 & -G_2 \\ -G_3 & G_3 + sG_4 & 0 \\ -G_2 & 0 & G_2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \\ 0 \end{bmatrix}$$

All  $G_i = \frac{1}{R_i}$   
 $i = 1, 2, \dots$

$\therefore V_3 = V_2 = K V_1$  eliminate node ③ by subst. for node ②  
 $f(V_2) = Y_2 + K Y_3$ , then discard row ③

$$\begin{bmatrix} G_1 + G_2 + G_3 + sC & -G_3 - K G_2 \\ -G_3 & G_3 + sG_4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$

$$\text{Then } V_2 = \frac{1}{\Delta} \cdot \begin{vmatrix} G_1 + G_2 + G_3 + sC & i_s \\ -G_3 & 0 \end{vmatrix} = \frac{G_3 i_s}{\Delta} = \frac{G_3 V_1 G_1}{\Delta}$$

$$\frac{V_2}{V_1} = \frac{G_3 G_1}{\Delta} ; \frac{V_2}{V_1} = \frac{K Y_2}{Y_1} = \frac{K \cdot G_1 G_3}{\Delta} = \frac{N(s)}{D(s)}$$

Since  $N(s)$  has no power of 's', it must be a K.P.F. function.



5.8

A second order BT filter has a transfer function

$$T(s) = \frac{H}{s^2 + a_1s + a_0}$$

The denominator is

$$D(s) = s^2 + a_1s + a_0 \rightarrow a_0 - \omega^2 + j\omega a_1$$

$$\sqrt{D(j\omega)} = \sqrt{a_0 - \omega^2} = \sqrt{a_0 - \omega^2} = \sqrt{a_0 - \omega^2}$$

$$\alpha = \frac{a_1\omega}{a_0 - \omega^2}$$

Delay is  $\frac{\partial}{\partial \omega} [D(j\omega)]$ , i.e.,  $-\frac{\partial}{\partial \omega} [T(j\omega)]$

5.5

In 5.4

$$D(s) = \Delta = (s^2 + a_2s + a_1)(s^2 + a_3s + a_4) - (a_3 + s a_4)(a_2 + s a_1)$$

$$= (s^2 + a_2s + a_1)(s^2 + a_3s + a_4) + s a_4(a_2 + a_3) + s a_3 a_1 + s^2 a_4 a_1$$

$$- a_3^2 - k a_2 a_3$$

$$= (a_1 + a_2)(a_3 - k a_2 a_3) + s(a_3 a_1 + a_4 a_2 + a_4 a_3) + s^2 a_4 a_1$$

$$= a_4 s \left[ s^2 + s \left( \frac{a_3}{a_4} + \frac{a_2}{a_2} + \frac{a_1}{a_1} \right) + \frac{a_3}{a_4} + \frac{a_2}{a_2} + \frac{a_1}{a_1} \right] + \frac{a_4 a_3}{1 + k}$$

If  $a_1 = a_2 = a_3 = 10F$ ,  $a_4 = 10F$ ,  $k = 10F$

denominator  $\rightarrow s^2 + s \left( 0.1 + \frac{3}{10} \right) + \frac{1 + k}{10}$

So  $\frac{3}{10} = 0.1$  with make the s-coeff = 0.2.

$$s = 3/10 = 30F$$

$$\frac{2-k}{10s} \rightarrow 1 \text{ (res)} \cdot 2-k = 10 \times 30 \times 1 = 300$$

$$k = 2 - 300 = -298$$

So  $s = 30F$ ,  $k = -298$  are the solutions

$$D(\omega) = \frac{a_1}{a_0} \frac{1 - \omega^2/a_0}{\omega} - \frac{1}{3} \cdot \frac{a_3}{a_3} \cdot \frac{\omega^3}{\omega^3} (1 - \omega^2/a_0)^3 + \dots$$

$$= f_1(\omega) + f_3(\omega) + \dots$$

Now  $\frac{\partial}{\partial \omega} [f_1(\omega)] = \frac{a_1}{a_0} \cdot \frac{(1 - \omega^2/a_0) + 2\omega^2}{\omega^2} \rightarrow \frac{a_1}{a_0}$  at DC i.e.  $\omega = 0$

$$\frac{\partial}{\partial \omega} [f_3(\omega)] = -\frac{1}{3} \cdot \frac{a_3}{a_3} \cdot \frac{3\omega^2 (1 - \omega^2/a_0)^2 + \dots}{\omega^3} \rightarrow 0$$
 at DC i.e.  $\omega = 0$

If we set  $t_0 = \text{delay at DC} = \frac{a_1}{a_0}$ , then  $a_1 = a_0 t_0$

Further, using the Binomial expansion  $(1+x)^n \approx 1+nx$  to the terms  $(1 - \omega^2/a_0)^{-1}$  and  $(1 - \omega^2/a_0)^3$  in  $D(\omega)$ , we can write

$$D(\omega) = \frac{a_1}{a_0} \omega (1 + \frac{\omega^2}{a_0} + \dots) - \frac{1}{3} \cdot \frac{a_3}{a_3} \omega^3 (1 + \frac{3\omega^2}{a_0} + \dots)$$

$$= \frac{a_1}{a_0} \omega + \left[ \frac{a_1^2}{a_0^2} - \frac{1}{3} \cdot \frac{a_3}{a_3} \right] \omega^3 + \dots$$

For linear phase  $D(\omega) \approx a_0 t_0$ , so

$$\frac{a_1}{a_0} - \frac{1}{3} \cdot \frac{a_3}{a_3} = 0$$

Using  $a_1 = a_0 t_0$ , gives

$$a_0 = 3/t_0^2$$

If  $t_0 = 1 \text{ ms}$ ,  $a_0 = \frac{10^6}{3} = 3 \times 10^6$

$$a_1 = a_0 t_0 = 3 \times 10^6$$

Then  $T(s) = \frac{H}{s^2 + 3 \times 10^6 s + 3 \times 10^6}$

DC gain = 1.  $H \rightarrow 3 \times 10^6$

This is a low-pass filter with  $\omega_p/\omega_0 = 3 \times 10^6$

5.6  
contd.

Use the schematic of Fig. 4 for LPF using SK architecture. For equal C, equal R design

$$\omega_p = \frac{1}{RC}$$

$$\frac{1}{\omega_p} = 2 + (1-K) = 3-K$$

Let  $C = 1 \text{ F}$  to start, then  $\omega_p = \sqrt{3 \times 10^6} = \frac{1}{RC}$ ;  $R \rightarrow$   
 $577.4 \times 10^{-6}$   
ohm

$$\frac{\omega_p}{\omega_p} = \frac{3 \times 10^3}{3 \times 10^6} ; \frac{1}{\omega_p} = \frac{3 \times 10^3}{\sqrt{3 \times 10^6}} = 1.732 = 3-K, K \rightarrow 1.27$$

$C = 1 \text{ F}$ ,  $R = 577.4 \mu\Omega$ ,  $K = 1.27$  are initial design values

If  $C \rightarrow 0.1 \mu\text{F}$ , scale R by  $10^7$  i.e.  $R = 5774 \Omega$

Then (see Fig. 4)  $C_2 = C_1 = 0.1 \mu\text{F}$

$$R_1 = R_3 = 5774 \Omega$$

$$K = 1.27$$

} are a possible design set

5.4

According to Table 4.3, let  $G_1 = H, G_2 = G = 1$

$$G_2 = 2\omega_p \omega_p - H, \quad G_5 = \omega_p / 2\omega_p \rightarrow \frac{2\pi \times 10^6}{2 \times 10} = 3.1416 \times 10^5$$

H is yet unknown.

The BP-gain (ie.  $s=j\omega_p$ ) is:  $\frac{Hs}{\omega_p s} = \frac{H\omega_p}{\omega_p} = 1$  (assume)

Then  $H = \frac{\omega_p}{\omega_p} = 6.28319 \times 10^3 = G_1$  (by initial choice)  $G_1 = 6.28319 \times 10^3$

$$G_2 = 2 \times 2\pi \times 10^6 \times 10 - 6.28319 \times 10^3 = 1.25035 \times 10^6$$

hope:  $D(s) = s^2 + \frac{\omega_p}{\omega_p} s + \omega_p^2 \rightarrow \frac{\omega_p}{\omega_p} s$  at  $s = j\omega_p$

Thus, initial design solution is:

$$G_1 = 6.28319 \times 10^3 \text{ mho}, \quad G_2 = 1.25035 \times 10^6 \text{ mho}$$

$$G_5 = 3.1416 \times 10^5 \text{ mho}; \quad C_3 = G_4 = 1 \text{ F}$$

5.7 (contd.)

But by given spec.  $G = C = 1 \mu F$  ie.  $\Delta$  scale factor of  $10^9$ . Then

$$\left. \begin{aligned}
 R_1 &= \frac{1}{G_1} \rightarrow \frac{1}{1} \times 10^9 = 159.15 \text{ k}\Omega \\
 R_2 &= \frac{1}{G_2} \rightarrow \frac{1}{\frac{1}{2}} \times 10^9 = 797.78 \Omega \\
 R_5 &= \frac{1}{G_5} \rightarrow \frac{1}{\frac{1}{5}} \times 10^9 = 318.309 \text{ k}\Omega
 \end{aligned} \right\} \begin{array}{l} \text{A design for} \\ \text{BPF according to} \\ \text{schematic in} \\ \text{Table 4.3.} \end{array}$$

5.8

The nodal analysis and method of constraints. Assuming  $K = \frac{R_A}{R_B}$ , the voltage transfer function will be:

$$\frac{V_2(s)}{V_1(s)} = \frac{-s(K+1)/R_1 R_2}{s^2 + s [1/R_2 G_2 + 1/R_2 G_1 - K/R_1 G_2] + 1/R_1 R_2 G_1 G_2}$$

Comparing with standard form of beyond BPF transfer function ie.

$$\frac{H_0 (w_p/q_p) s}{s^2 + (w_p/q_p) s + w_p^2}, \text{ we get}$$

$$w_p = \frac{1}{\sqrt{R_1 R_2 G_1 G_2}}$$

$$\frac{1}{q_p} = \sqrt{\frac{R_1}{R_2}} \cdot \left( \sqrt{\frac{G_2}{G_1}} + \sqrt{\frac{G_1}{G_2}} - K \cdot \frac{R_1}{R_2} \cdot \sqrt{\frac{G_1}{G_2}} \right)$$

$$|H_0| = \frac{(K+1)/R_1 G_1}{1/R_2 G_2 + 1/R_2 G_1 - K/R_1 G_1}$$

Simplified design: let  $G_1 = G_2 = C \rightarrow 0.1 \mu F$  suggested.

$$\frac{R_1}{R_2} = m \quad ; \quad R_1 = m R_2 \quad ; \quad \text{let } R_2 = R$$

$$\text{Then } w_p = \frac{1}{C \cdot R \sqrt{m}}$$

contd.  $\frac{1}{\sigma_p} = \sqrt{m} \left( 1 + 1 - k \cdot \frac{1}{m} \right) \Rightarrow \frac{1}{\sigma_p} = 2 - \frac{k}{m}$

Separating:  $\frac{1}{m \sigma_p^2} = 4 + \frac{m^2}{k^2} - 2 \cdot 2 \cdot \frac{m}{k} = 4 + \frac{m^2}{k^2} - \frac{4m}{k}$

ie.  $\frac{m}{\sigma_p^2} = 4m^2 + k^2 - 4km$ ;  $4m^2 - m \left( 4k + \frac{1}{\sigma_p^2} \right) + k^2 = 0$   
 Giving  $m = \frac{8}{\left( 4k + \frac{1}{\sigma_p^2} \right) \pm \sqrt{\left( 4k + \frac{1}{\sigma_p^2} \right)^2 - 16k^2}}$

OR  $m = \frac{1}{8} \cdot \left[ \left( 4k + \frac{1}{\sigma_p^2} \right) \pm \sqrt{\frac{1}{\sigma_p^4} + \frac{8k}{\sigma_p^2}} \right]$

Assume  $k=1$ , then  $m = \frac{1}{8} \left[ \left( 4 + \frac{1}{\sigma_p^2} \right) \pm \sqrt{\frac{1}{\sigma_p^4} + \frac{8}{\sigma_p^2}} \right]$

$= \frac{1}{8} (4.01 \pm .283)$   
 $\rightarrow .5366$  OR  $0.4659$

Assume  $k=2$ , then  $m = \frac{1}{8} \left[ \left( 8 + \frac{1}{\sigma_p^2} \right) \pm \sqrt{\frac{1}{\sigma_p^4} + \frac{16}{\sigma_p^2}} \right]$

$= \frac{1}{8} [8.01 \pm .4]$

$\rightarrow 1.051$  OR  $0.951$

Consider:  $m = .5366$ ; Then  $\omega_p = \frac{1}{\sigma_p} = \frac{1}{\sqrt{m \sigma_p^2}}$  gives  $R = \frac{1}{\sigma_p}$

ie.  $R = \frac{1}{\sqrt{.5366 \times 10^{-7} \times 2\pi \times 10^4}} = 217.27 \Omega$

$R_1 = m R_2 = 116.58 \Omega$   
 $R_2 = 217.27 \Omega$   
 Admittance spread =  $\frac{217.27}{116.58} \rightarrow 1.86$  ie. less than 100

Consider  $m = .4659$   
 $R = \frac{1}{\sqrt{.4659 \times 10^{-7} \times 2\pi \times 10^4}} = 233.17 \Omega = R_2$   
 $R_1 = m R_2 = 108.63 \Omega$   
 $R_2 = 233.17 \Omega$   
 Admittance spread =  $\frac{233.17}{108.63} = 2.14$  ie. less than 100

$R_1, R_2$  remaining five choice with  $R_1 = R_2$ , since  $k=1$   
 One can take  $R_1 = R_2 = 100 \Omega$  each.



5.9

See figure 9(b), for a LRF.

$$\frac{V_o}{V_i} = - \left[ \frac{1 + R_2/R_1}{R_1 R_2 C_1 C_2} \right] \cdot \frac{1}{R_1 R_2 C_1 C_2} D(s)$$

$$\text{with } D(s) = \frac{s^2 + \frac{R_1 C_1}{R_2 C_2} s + \frac{R_1 R_2 C_1 C_2}{R_1 R_2 C_1 C_2}}{1 + R_2/R_1 + \frac{R_1 C_1}{R_2 C_2} s + \frac{R_1 R_2 C_1 C_2}{R_1 R_2 C_1 C_2}}$$

$$\omega_{LP} = \sqrt{\frac{R_2/R_1}{R_1 R_2 C_1 C_2}} \quad ; \quad \frac{1}{Q} = \frac{1 + R_2/R_1}{R_5 R_2 C_2} \cdot \sqrt{\frac{R_5 R_2 C_2}{R_6 R_1 C_1}}$$

Let  $C_1 = C_2 = 1 \text{ F}$ ;  $R_1 = R_2 = 1 \Omega$

Then  $\omega_{LP} = 1$  radian with  $R_5 = R_6$

$$\frac{1}{Q} = \frac{2}{1 + R_2/R_1} = \frac{2}{2} = 1 \quad ; \quad \frac{20}{1} = \frac{20}{1} \quad ; \quad \text{So } 1 + \frac{R_4}{R_3} = 40 \quad ; \quad \frac{R_4}{R_3} = 39$$

One can take  $R_3 = 100 \Omega$ ,  $R_4 = 3900 \Omega$ .  
 i.e.  $R_3 = 39 R_4$ .

$$\text{Gain at DC} \rightarrow \frac{1 + R_2/R_1}{1 + R_3/R_4} = \frac{2}{1 + \frac{1}{39}} = \frac{78}{40} = 1.95$$

So a possible design is:  $C_1 = C_2 = 1 \text{ F}$ ;  $R_1 = R_2 = 1 \Omega$  (suggested)

$$R_5 = R_6 = 100 \Omega \text{ each}$$

$$R_3 = 100 \Omega, R_4 = 3900 \Omega$$

$$\text{Gain at DC} = 1.95$$

5.10

See figure 10 and Table 4-9. For a positive gain

BPF:  $C_1 \rightarrow 0$ ;  $R_1 \rightarrow \text{open}$ ,  $R_2 \rightarrow \text{open}$

$$R_3 = \frac{R_2}{R_1} = \frac{15 \cdot r}{5} = 3r$$

$C = 1 \text{ F}$  suggested;  $\omega_{LP} = 1$  rad/sec given

$$R = 1/\omega_{LP} = 1 \Omega$$

then  $R_3 = 3 \Omega$

So a design set is:  $C = 1 \text{ F}$ ;  $R = 1 \Omega$ ;  $r = 1 \Omega$   
 $R_3 = 3 \Omega$ ;  $R_4 = 15 \Omega$   
 $R_5 = 3 \Omega$ ;  $R_6 = 15 \Omega$



5.11

see figure 11  
 let:  $b_1 = 0, b_0 = 0$

$b_2 = 5 = 2$

see eqns. (9), (10)

$$\omega_p = \sqrt{\frac{R_s}{R_2 R_3 C_1 C_2 R_7}}$$

= 1 rad/sec

Op = 8 =  $\omega_p \cdot R_1 C_1$

$b_1 = 0$  leads to  $\frac{R_s}{R_2} - \frac{R_1 R_7}{R_3} = 0$

$b_0 = 0$  leads to  $\frac{R_s}{R_2 R_3 R_7 C_1 C_2} = 0$

$b_2 = 2$  leads to  $\frac{R_s}{R_2} = 2$

let  $R_5 \rightarrow$  open circuit i.e.  $\infty$  then will make  $b_0 \rightarrow 0$

Then  $\frac{R_s}{R_2} = 2 = \frac{R_1}{R_3} \cdot \frac{R_7}{R_2}$

let  $\frac{R_1}{R_3} = 2, \frac{R_7}{R_2} = 1$ , then will make  $b_1 = 0$

Now  $\omega_p = \sqrt{\frac{R_s}{R_2 R_3 C_1 C_2 R_7}} = \sqrt{\frac{1}{R_2 R_3 C_1 C_2}}$

let  $R_2 = R_3 = 1 \Omega, C_1 = C_2 = 1F$ , then  $\omega_p = 1$  rad/sec

But Op = 8 =  $\omega_p R_1 C_1$ , then  $R_1 = \frac{8}{\omega_p C_1} = 8 \Omega$

$\therefore \frac{R_1}{R_3} = 2$  has been assumed,  $R_1 = 8 \Omega$  makes  $R_3 = 4 \Omega$

So a possible design set is:

- $R_5 \rightarrow$  open
- $R_8 = R_7 = 100 \Omega$  (any)
- $R_1 = 8 \Omega$
- $R_4 = 4 \Omega$
- $C_1 = C_2 = 1F$
- $R_2 = R_3 = 1 \Omega$  (any)
- $R_6 = \frac{R_s}{2} = 50 \Omega$

See figure 11, for Band reject filter

$$V_0 = -b_2 \cdot \frac{s^2 + a_1s + a_0}{s^2 + b_0/b_2}$$

with  $b_1 = 0$

and  $b_0/b_2 = a_0 = \omega_p^2$  ( $\because$  we can not be specified, we take  $\omega_2 = \omega_p$ )

DC gain ( $\omega$  at  $s=0$ )  $\frac{b_0}{a_0} = 1$

Gain at infinity  $= b_2 = 1$

Then  $\frac{R_5}{R_6} = 1 \rightarrow b_2 = 1$

$$\frac{R_5}{R_6} - \frac{R_1 R_8}{R_4 R_7} = 0 \rightarrow b_1 = 0$$

$$\frac{R_5}{R_6} = \frac{R_1 R_8 R_2 R_7}{R_3 R_4 R_5 R_7} = \omega_p^2 = 1 = a_0 = b_0 = \frac{R_3 R_5 R_7^2}{R_4 R_6 R_2 R_7}$$

$$\omega_p = \omega_p \cdot R_1 C_1 = 1 \omega$$

Let  $\frac{R_1}{R_4} = \frac{R_5}{R_6} = 1$  each. This makes  $b_1 = 0$ .  $\therefore \frac{R_5}{R_6} = 1$


$$1 = \frac{R_5}{R_6} \cdot \frac{1}{R_1 R_3} \cdot \frac{1}{C_1^2} = \frac{R_7}{R_2 R_3} \cdot \frac{1}{C_1^2}$$

$$\text{Let } C_1 = C_2 = 1; R_2 = R_3 = R_5 = 1$$

Then  $1 \omega = R_1 \cdot 1 \cdot \omega_p$ , makes  $R_1 = 1 \omega$

Hence, a possible design set is:

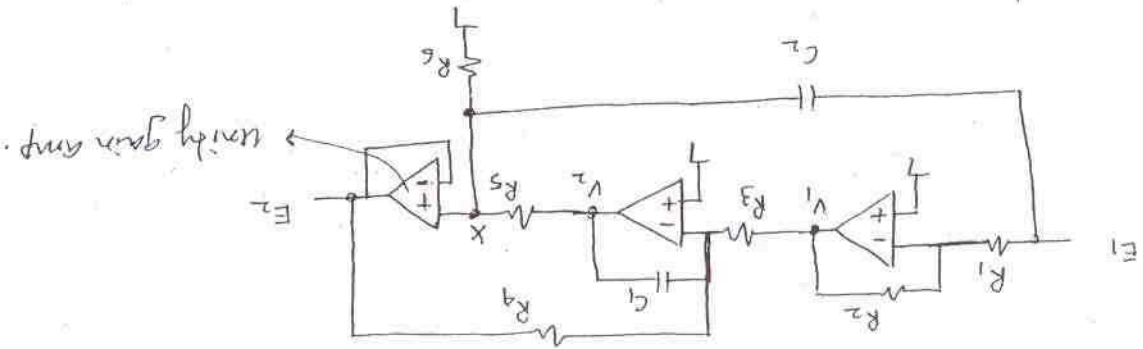- $R_2 = R_3 = R_5 = 1 \omega$
- $R_1 = 12 \omega$
- $R_4 = 12 \omega$
- $R_7 = R_8 = 1 \omega$
- $C_1 = C_2 = 1 F$
- $R_6 = 1 \omega$



working by each op-amp:

$$V_1 = -\frac{R_2}{R_1} E_1 \quad ; \quad V_2 = -\frac{1}{R_3} V_1 - \frac{1}{R_4} E_2$$

$$V_2 - E_2 + (E_1 - E_2) \frac{R_6}{R_5} = \frac{R_6}{R_5} \rightarrow \text{KCL at node X}$$

re-arranging:

$$-\frac{R_1}{R_2} V_1 = E_1 \quad \text{--- (1)}$$

$$\frac{V_1}{R_5} + V_2 + \frac{E_2}{R_4} = 0 \quad \text{--- (2)}$$

$$\frac{V_2}{R_5} - E_2 \left( \frac{1}{R_5} + \frac{R_6}{R_5} \right) = -E_1 \frac{R_6}{R_5} \quad \text{--- (3)}$$

from (1) & (2)  $V_2 + \frac{E_2}{R_4} = -\frac{1}{R_5} \cdot \frac{-R_2}{R_1} E_1 = \frac{R_2}{R_1} \frac{1}{R_5} E_1$  --- (4)

from (3) & (4)

$$\left. \begin{aligned} \frac{V_2}{R_5} - \left( \frac{1}{R_5} + \frac{R_6}{R_5} \right) E_2 &= -s q R_4 E_1 \\ \frac{V_2}{R_5} + \frac{E_2}{R_4} &= \frac{R_2}{R_1} \frac{1}{R_5} E_1 \end{aligned} \right\}$$

By Kramer's rule:

$$E_2 = \frac{1}{\Delta} \cdot \begin{vmatrix} 1 & 1 \\ \frac{1}{R_5} & \frac{R_2}{R_1} \frac{1}{R_5} \end{vmatrix} = \frac{-s q R_4 E_1}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 1 & 1 \\ \frac{1}{R_5} & -\left( \frac{1}{R_5} + \frac{R_6}{R_5} + s q R_4 \right) \end{vmatrix}$$

5.14

$$s^2 + \frac{a}{s} + 1 = (s+1)^2 - k\alpha s \quad \text{can be simplified to:}$$

$$\frac{1}{a} = 2 - k\alpha \quad \text{Since } 1/a = a', \text{ obviously,}$$

$$\frac{1}{a} = -\frac{1}{s} \quad \text{where } \frac{1}{a} = 2 - k\alpha = \frac{1}{s} \text{ (say)}$$

Considering 'k' as the only variable, since 'a' is independent of k

$$dy = -\alpha dx \quad ; \quad \frac{dy}{y} = -\alpha$$

$$\frac{dy/y}{dx/k} = \frac{1}{k} \cdot (-\alpha) = \frac{1}{k} \cdot \alpha = \frac{1}{2-k\alpha}$$

$$\int \frac{1}{2-k\alpha} = \int \frac{1}{k} \cdot \alpha = \frac{1}{k} \cdot \frac{1}{2-k\alpha}$$

The solution is:

$$\frac{E_2/E_1}{V_s/V_0} = \frac{s^2 (g_2 g_1 + g_5 g_1 g_3) (g_2 (g_4 g_5 + s(g_4 + g_5) + s^2 c_1 c_2))}{g_2 c_1 c_2 [s^2 + \frac{g_1 g_3 g_5}{g_2 c_1 c_2}] + g_1 g_3 g_5 / g_2 c_1 c_2} \left[ s^2 + \frac{g_2 c_1 c_2}{c_1 c_2} s + \frac{g_4 g_5}{c_1 c_2} \right]$$

$$T(s) = \frac{s^2 + \frac{g_4 g_5}{c_1 c_2} s + \frac{g_1 g_3 g_5}{g_2 c_1 c_2}}{s^2 + \omega_z^2} \quad \text{where}$$

with  $g_1 = g_2 = 1F$ , the design equations are:

$$\omega_z = \sqrt{\frac{g_1 \cdot g_3 g_5}{g_2}} = \sqrt{g_1 g_3 g_5} \quad ; \quad \omega_p = \sqrt{g_4 g_5} \quad ; \quad \frac{1}{T} = (g_5 + g_6) / \sqrt{g_4 g_5}$$

5.13

5.15

check problem 5.8

$$\frac{1}{a} = \sqrt{\frac{R_1}{R_2}} \cdot \left[ \sqrt{\frac{c_1}{c_2}} + \sqrt{\frac{c_1}{c_2}} - k \cdot \frac{R_1}{R_2} \cdot \sqrt{\frac{c_1}{c_2}} \right]$$

$$a \sim a \cdot c_1^{\frac{1}{2}} c_2^{-\frac{1}{2}} + a \cdot c_2^{\frac{1}{2}} c_1^{-\frac{1}{2}} - b \cdot c_1^{\frac{1}{2}} c_2^{-\frac{1}{2}}$$

$$a = \sqrt{\frac{R_1}{R_2}} \cdot k \cdot \frac{R_1}{R_2}$$

but  $y = \frac{1}{a} = a \cdot c_1^{\frac{1}{2}} c_2^{-\frac{1}{2}} + a \cdot c_2^{\frac{1}{2}} c_1^{-\frac{1}{2}} - b \cdot c_1^{\frac{1}{2}} c_2^{-\frac{1}{2}}$

then  $s_y^R = -s_y^C$  etc.

for  $s_y^C$ , consider  $\frac{\partial y}{\partial c_1} \rightarrow a \cdot \frac{1}{2} \cdot c_1^{-\frac{1}{2}} \cdot c_2^{-\frac{1}{2}} - a \cdot \frac{1}{2} \cdot c_1^{\frac{1}{2}} \cdot c_2^{-\frac{3}{2}}$   
 $- b \cdot c_2^{-\frac{1}{2}} \cdot c_1^{-\frac{1}{2}}$

$$\frac{\partial y}{\partial c_1} = \frac{1}{2} \cdot \left[ \frac{\sqrt{c_1/c_2}}{a} - a \cdot \frac{c_1/c_2}{\sqrt{c_1/c_2}} - b \cdot \frac{1}{\sqrt{c_1/c_2}} \right]$$

$$\frac{c_1}{a} \cdot \frac{\partial y}{\partial c_1} = \frac{1}{2} \cdot \frac{1}{a} \cdot \left[ a \cdot \sqrt{\frac{c_1}{c_2}} - a \sqrt{\frac{c_1}{c_2}} - b \sqrt{\frac{c_1}{c_2}} \right] = \frac{1}{2} \cdot \frac{1}{a} \cdot \left[ -b \sqrt{\frac{c_1}{c_2}} \right]$$

$$y = \frac{1}{a} = a \cdot \sqrt{\frac{c_1}{c_2}} + a \cdot \sqrt{\frac{c_2}{c_1}} - b \cdot \sqrt{\frac{c_1}{c_2}}$$

So  $s_y^C = \frac{\partial y / \partial c_1}{y} = \frac{1}{2} \cdot \left[ 1 - a \sqrt{\frac{c_1}{c_2}} \right]$

$$s_y^R = \frac{1}{2} \cdot \left[ a \sqrt{\frac{c_2}{c_1}} - 1 \right] \text{ and so on ...}$$

5.16

LEFT AS AN EXERCISE

For equal R, equal C design:

$$\frac{V_2(s)}{V_1(s)} = \frac{H}{s^2 + 5.714s + 1}$$

$$C_P = \frac{1}{RC} = 1 \quad \frac{\partial P}{\partial P} = \frac{1}{P} = 0.5714 = 3 - k$$

So  $k = 3 - 5.714 = 2.43$

We can let  $R = 1$ ,  $C = 1$  and  $k = 2.43$  in the design. With  $k = 1.43$ , for the LDF, we shall have values.



The transfer function with ideal OA is:

$$H_{HP} = \frac{K \cdot g_1 g_3 / g_2 g_4}{s^2 + s \left( 3 \frac{g_2}{g_1} - K \frac{g_2}{g_1} \right) + \frac{g_2 g_4}{g_1 g_3}}$$

$\therefore g_1 = g_3 = g = 1$   
 $g_2 = g_4 = 1$  have  
 been assumed.

If OA has a transfer function  $A(s) \sim \frac{s}{\omega_T}$ , the gain  $K$  becomes (see p.66)

$$K(s) \sim K_T = \frac{1 + \frac{A}{K}}{1 + \frac{Ks}{\omega_T}} = \frac{1 + \left(\frac{\omega_T}{K}\right)s}{K}$$

Then

$$H_{HP} \rightarrow \overline{H_{HP}} = \frac{K / (1 + \frac{\omega_T}{K}s)}{s^2 + s \left( 3 - \frac{K}{1 + \frac{\omega_T}{K}s} \right) + 1}$$

$$\det \beta = \frac{\omega_T}{K}$$

$$\overline{H_{HP}} = \frac{s^2 + s \left( 3 - \frac{K}{1 + \beta s} \right) + 1}{K (1 + \beta s)}$$

$$= \frac{s^2 (1 + \beta s) + s (3 (1 + \beta s) - K) + (1 + \beta s)}{K}$$

$$= \frac{\beta s^3 + s^2 + 3s (1 + \beta s) - Ks + 1 + \beta s}{K}$$

$$= \frac{\beta s^3 + (1 + 3\beta) s^2 + s (3 - K + \beta) + 1}{K}$$

is the new

network function that will be realized.

The new  $\omega_p$  will be dictated by the Re-part of  $D(s) \rightarrow 0$

$$\text{i.e. } (1 + 3\beta) \cdot \left( -\frac{\omega_p^2}{2} \right) + 1 = 0 \quad \text{or } \omega_p = \sqrt{\frac{1}{1 + 3\beta}} = \sqrt{\frac{1}{1 + 3 \frac{\omega_T}{K}}}$$

Retaining the symbols for R, C

$$D(s) = s^2 + \frac{c}{g} \cdot s \cdot (3-k) + \frac{c^2}{g^2} \text{ with ideal op.}$$

$$\overline{D(s)} \Rightarrow s^2 + \frac{c}{g} \cdot s \cdot (3 - \frac{k}{1+ps}) + \frac{c^2}{g^2}$$

$$\rightarrow ps^3 + s^2 + 3\frac{c}{g} \cdot s + 3\frac{c}{g} \cdot ps^2 - k\frac{c}{g} \cdot s + \frac{c}{g} + \frac{c^2}{g^2} ps$$

$$\rightarrow ps^3 + s^2 (1+3p\frac{c}{g}) + s(3\frac{c}{g} - k\frac{c}{g} + \frac{c}{g} \cdot p) + \frac{c^2}{g^2}$$

Then  $\omega_p^2 = \frac{g^2/c^2}{1+3p\frac{c}{g}} = \omega_p^2 \therefore \frac{g^2}{c^2} = \frac{g^2}{c^2} \sqrt{1+3p\frac{c}{g}} = \frac{\sqrt{1+3p\frac{c}{g}}}{g/c}$

for new  $\omega_p$ , consider the imaginary part of  $\overline{D(s)}$ .

$$-j\frac{\beta\omega}{3} \frac{1+3p\frac{c}{g}}{1+3p\frac{c}{g}} + j\omega \frac{3\frac{c}{g} - k\frac{c}{g} + \beta\frac{c^2}{g^2}}{1+3p\frac{c}{g}} \leftarrow j\omega \frac{c}{g}$$

$$\text{ie. } -\frac{\beta\omega}{3} \frac{1+3p\frac{c}{g}}{1+3p\frac{c}{g}} + \frac{3\frac{c}{g} - k\frac{c}{g} + \beta\frac{c^2}{g^2}}{1+3p\frac{c}{g}} = \frac{c}{g}$$

$\therefore \frac{c}{g} = \omega_p$  in ideal case.

$$\frac{1}{\omega_p} = -\frac{\beta\omega_p}{3} \frac{1+3p\frac{c}{g}}{1+3p\frac{c}{g}} + \frac{3p - k + \beta\frac{c}{g}}{1+3p\frac{c}{g}} + \frac{3p - k + \frac{c}{g}}{1+3p\frac{c}{g}}$$



5.17 (b)

Nothing that  $\omega_p = \frac{c}{a}$  in the ideal case

$$\omega_p = \frac{\sqrt{1+3\omega_p K}}{\omega_p} \quad \therefore \beta = \frac{K}{\omega_p} \text{ by substitution}$$

$$\frac{1}{\omega_p} = \frac{3-K+K\frac{\omega_p}{\omega_p}}{\sqrt{1+3K\frac{\omega_p}{\omega_p}}} \cdot \frac{1+3\frac{\omega_p}{\omega_p}}{K\frac{\omega_p}{\omega_p}}$$

For equal R, equal C case  
 $K = 2.43$  found out.

So evaluate  $\omega_p$ ,  $\omega_{cp}$  for  $\frac{\omega_p}{\omega_{cp}} = 7.5$  i.e.  $\frac{\omega_p}{\omega_{cp}} = 7.5$

Note, the flat gain remains unchanged to the value K


(5.17) (c) For convenience of presentation, we shall use  $\omega_p = 10$  rad/sec.  $R = 10K$ ,  $C = 0.1\mu F$ , so that  $\omega_p = \frac{10 \cdot 10^{-6}}{0.1} = 10$  rad/sec.

Then average a non-ideal op with a gain function

$$A(s) = \frac{\omega_T}{s} \text{ thus } \omega_T = 7.5 \times 10^3 \text{ rad/sec. Thus:}$$

$$V_{o1} = + \frac{sL}{R} \text{, with } \frac{L}{R} = \omega_T$$
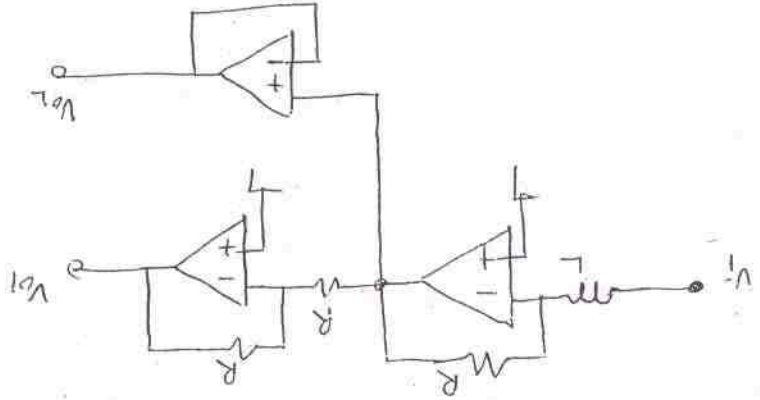
$$V_{o2} = - \frac{sL}{R} \text{, with } \frac{L}{R} = \omega_T$$



For a differential mode of operation, the system will be:

non-ideal op with


$$A(s) = \frac{s}{\omega_T}$$

$$\omega_T = \frac{R}{L}$$

$$R = 750 \Omega$$

$$L = 0.1 H$$
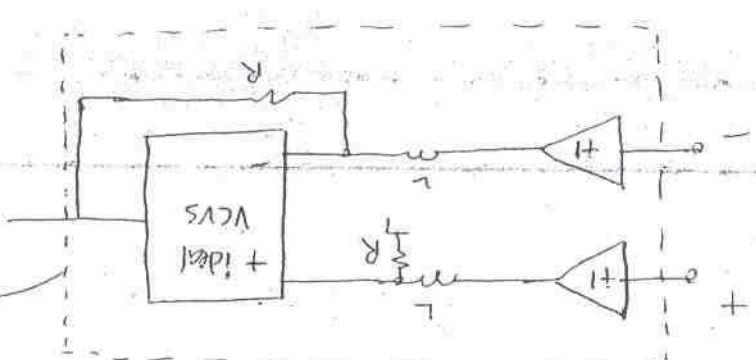
$$\text{for } \omega_T = 7.5 \times 10^3$$



5.18 (a)

Given  $T(s) = \frac{s^2 + 5.714s + 1}{s}$

with equal R, equal C assumption, the network function

$$T(s) = \frac{SK/RC}{s^2 + s \left[ \frac{4}{RC} - \frac{1}{RC} \right] + \frac{1}{RC}}$$

derived from

$$T_N(s) = \frac{SK/R_1C_1}{s^2 + s \left[ \frac{1}{R_1C_1} + \frac{1}{R_2C_2} - \frac{K}{R_2C_2} \right] + \left( \frac{1}{R_1C_1} \right) \left( \frac{1}{R_2} + \frac{1}{R_1} \right)}$$

Then

$$\omega_p^2 = \frac{2}{RC^2} ; \omega_p = \frac{\sqrt{2}}{RC}$$

$$\omega_p = \frac{1}{RC} (4-K) ; \frac{1}{RC} = \frac{1}{RC} (4-K) \cdot \frac{\sqrt{2}}{\sqrt{2}} = \frac{4-K}{\sqrt{2}}$$

Given  $\omega_p = 1 \rightarrow \frac{\sqrt{2}}{RC} = 1$  ; we can let  $R = 1 - \Omega$

Given  $Q = \frac{1}{1.5714} \approx 1.75 \rightarrow \frac{\sqrt{2}}{4-K} ; K = 3.192$

$H_0 =$

$$\frac{K/RC}{\frac{1}{RC} (4-K)}$$

$$= \frac{K}{4-K} \rightarrow 3.95$$

Initial design values

$$R = 1\Omega, C = \sqrt{2}F, K = 3.192$$

(b) Now with  $A(s) = \frac{s}{1+s}$ ,  $K(s) = \frac{1 + \frac{1}{K}s}{K}$  as before

Then

$$D(s) = s^2 + \frac{1}{RC} s \left( 4 - \frac{1}{K} \right) + \frac{R^2 C^2}{2}$$

$$= \frac{R^2 C^2 (1 + \beta s)}{R^2 C^2 \beta^3 s^3 + (R^2 C^2 + 4RC\beta) s^2 + (4RC - KRC + 2\beta) s + 2}$$

S.K.RC

$$T(s) = \frac{3\beta R^2 C^2 + s^2 (R^2 C^2 + 4RC\beta) + s(4RC - KRC + 2\beta) + 2}{S.K.RC}$$

Then the new  $\omega_p$  and  $H_0$  will be

(b) Control  
5.18

$$\frac{1}{\omega_p} = \frac{\beta \omega_p}{1 + \frac{\beta}{\omega_p}} + \frac{\omega_p}{4 - K + 2\beta \omega_p / \sqrt{2}}$$

$$\frac{1}{\omega_p} = \frac{\beta \omega_p}{1 + \frac{\beta}{\omega_p}} + \frac{\omega_p}{4 - K + 2\beta \omega_p / \sqrt{2}}$$

$$\frac{1}{\omega_p} = \frac{\sqrt{2} \omega_p}{4 - K + \sqrt{2} K \frac{\omega_p}{\omega_p}} - \frac{1 + 2\sqrt{2} K \frac{\omega_p}{\omega_p}}{K \frac{\omega_p}{\omega_p}}$$

At  $\omega = \omega_p$  near

$$\bar{T}(s) = \frac{SKRC}{s^3 \beta RC^2 + s(4RC - KRC + 2\beta)} = \frac{KRC}{4RC - KRC + 2\beta + s^3 \beta RC^2}$$

If we let  $s \rightarrow j\omega_p$

$$\bar{T}(s) \Big|_{s=j\omega_p} = \frac{KRC}{4RC - KRC + 2\beta - \omega_p^2 \beta RC^2}$$

$$= \frac{4 - K + 2\frac{\beta}{RC} - \omega_p^2 \beta \cdot RC}{K}$$

$$= \frac{4 - K + 2 \cdot \frac{\omega_p}{\omega_t} \cdot \frac{K}{\omega_t} + \omega_p^2 \cdot \frac{K}{\omega_t} \cdot \frac{\sqrt{2}}{\omega_p}}{K}$$

$$= \frac{4 - K + \sqrt{2} K \frac{\omega_p}{\omega_t} - \sqrt{2} K \cdot \frac{\omega_p \cdot \omega_t}{\omega_p^2}}{K}$$

With  $\omega_p/\omega_t = \sqrt{2}$ , and nominal  $\omega_p = 1$

$$\omega_p = 0.6736 \text{ rad/sec}$$

$$\frac{1}{\omega_p} = 0.5415 \rightarrow \omega_p = 1.846 ; H_0 = 2.808$$

5.19


LEFT AS AN EXERCISE

X

$f_0 = 159.33 \rightarrow \text{Hz} \rightarrow 1000 \cdot \frac{1}{2\pi \cdot 1000} \text{ rad/sec}$   
 $\omega = 159.33 / 90.7302$   
 $\rightarrow 1.756$   
 $H_0 = 3.95$   
 $f_0 = 111.354 \text{ Hz}$   
 $\omega = 61.012 \text{ Hz}$   
 $\rightarrow 1.826$   
 $H_0 = 2.833$

$Q = 1.826$   
 $\omega_p = 7.5 \text{ rad/sec}$   
 $A(s) = \frac{0.49}{s}$

Simulation with ideal op.

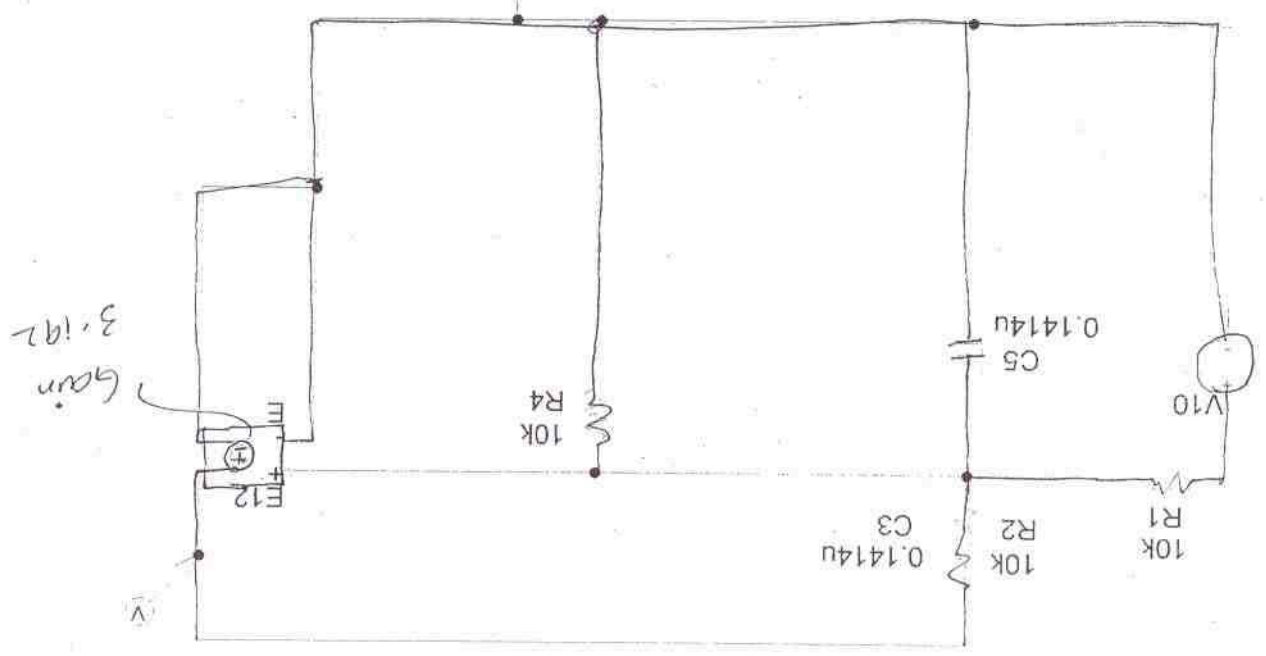

5.18

5.20


Peak-to-peak ripple implies a CHEB magnitude approximation. Using the data  $A_p = 1dB$ ,  $A_n = 50dB$ ,  $f_c = 10kHz$ ,  $f_a = 60kHz$ , we find

$N_{CHEB} = 3$   
 $\epsilon = 0.5088$

Then  $H(s) = \frac{1}{1 + \frac{1}{D(s)}} = \frac{0.9914}{(s + 0.994)(s^2 + 0.9905s + 0.994)}$

$$= \frac{0.994}{s^2 + 0.9905s + 0.994} \cdot \frac{s + 0.994}{s + 0.994}$$

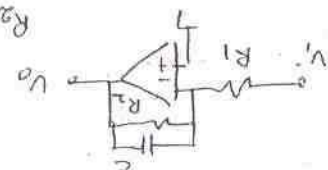Consider a 1st order and 2nd order RC networks.




for the first order network consider  $\frac{V_o}{V_i} = \frac{R_1}{R_2 + \frac{R_1}{sC}} = \frac{R_1 s C}{R_2 + R_1 + s R_1 C}$

$$= \frac{R_1}{R_2 + R_1} \cdot \frac{s R_1 C + 1}{s + 1/R_1 C}$$

$$\frac{V_o}{V_i} = R_1 = R_2 = R, \quad \frac{1}{R_1 C} = 1/0.994 = 2.024 \mu s^{-1}$$


but  $C = 1F, R = 1/0.994 = 2.024 \mu s^{-1}$ , making  $1/RC = 0.994$

Then

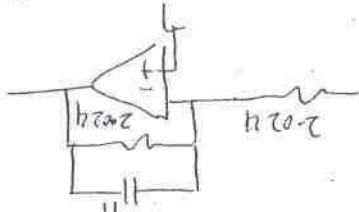

will produce  $\frac{s + 0.994}{0.994}$  transfer function

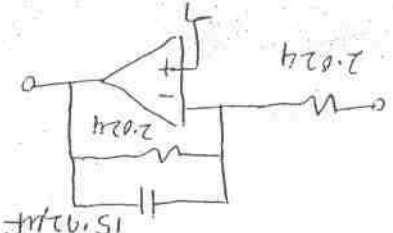Then use for  $\omega_c = 1 \text{ rad/sec}$ . But given  $f_c = 10 \text{ kHz}$ ,  $\omega_c = 2\pi \times 10^4$ . So frequency  $\omega_c$  is required. Make  $C = 1/2\pi \times 10^4 = 15.92 \mu F$ .



will be one part of the demand filter.



Consider

$$\frac{s^2 + .490s + .994}{.994}$$

Then is LPF of DC gain = 1,  $wp = \sqrt{.994}$  and

$$\frac{1}{wp} = .990, \quad \frac{1}{wp} = .990 = .991476, \quad \omega_p = .993$$

Consider a SK design (see p. 53-54)

Then  $det K = 1$

$$wp = \frac{1}{\sqrt{R_1 R_3 G_4}} = \sqrt{\frac{R_1 G_4}{R_3 G_2}} + \sqrt{\frac{R_1 G_4}{R_3 G_2}}$$

Take  $n = \frac{R_1}{R_3}$ ;  $m = G_4/G_2$ , then solve for a good 'm'

from  $m < 1/40^2$  i.e.  $m < .061$ , let  $m = .04$

Then  $n = \left( \frac{1}{2mG_p^2} - 1 \right) \pm \frac{1}{2mG_p^2} \cdot \sqrt{1 - 4mG_p^2}$ , gives

$$n = 2.0333 \pm 1.7704 = 3.8037 \text{ OR } 0.2629$$

Take  $n = 3.8037$

Then  $R_3 = 3.8037 R_1$ ;  $G_4 = .04 G_2$  and

$$wp = \frac{1}{\sqrt{3.8037 \times .04 \times G_2 R_1}} = \frac{1}{\sqrt{.994}} = 0.996995$$

Let  $G_2 = 1F$ , let  $R_1 = 1$

Then  $G_4 = .04F$ ,  $R_3 = 3.8037$

confirm:  $wp = \frac{1}{\sqrt{2.5714 \times 9.7809 \times 1 \times .04}} = .997 \approx .996995$

$$\frac{1}{wp} = \sqrt{\frac{R_3 G_4}{R_1 G_2}} + \sqrt{\frac{R_1 G_4}{R_3 G_2}} = \sqrt{3.8037 \times .04} + \sqrt{\frac{1}{3.8037} \times .04}$$

$$= 0.4926 \approx .4914$$

Then  $R_1 = 2.5714 \Omega$ ,  $R_3 = 9.7809 \Omega$ ,  $C_2 = 1F$ ,  $C_4 = .04F$  is a possible design for  $wp = 1 \text{ rad/sec}$ , was frequency

5.20


Let's make  $C \rightarrow C / (2\pi \times 10^4)$ , so

$$R_1 = 2.5714 \Omega, R_3 = 9.7809 \Omega$$

$$C_2 = 15.92 \mu F; C_4 = 0.637 \mu F \text{ will realize}$$

$$\omega_c \rightarrow 2\pi \times 10^4 \text{ rad/sec}$$

The overall filter is a cascade:

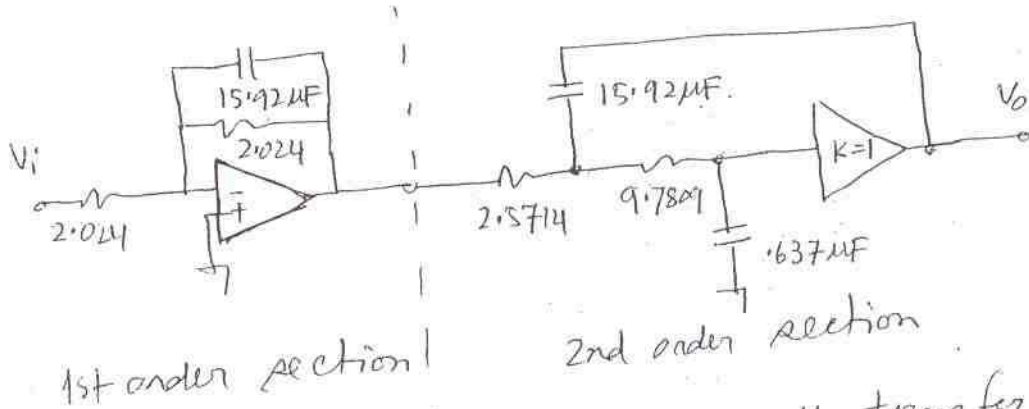

There is a sign inversion in the overall transfer function. For magn. approx, this is immaterial.

5.21

Find  $n_{\text{CHEB}} = 3$  with  $\epsilon = 0.7648$

$$H_N(s) = \frac{1}{2 \cdot \epsilon} \cdot \frac{1}{D(s)} = \frac{0.327}{(s + 0.402)(s^2 + 0.369s + 0.886)}$$

$$= \frac{0.402}{s + 0.402} \cdot \frac{0.886}{s^2 + 0.369s + 0.886}$$

This is the associated normalized L.F. transfer function

For the normalized HPF,  $s \rightarrow \frac{1}{s}$


$$H_N|_{\text{HP}} = \frac{0.402 s}{1 + 0.402s} \cdot \frac{0.886 s^2}{1 + 0.369s + 0.886s^2}$$

$$= \frac{s}{s + 2.4876} \cdot \frac{s^2}{s^2 + 0.4165s + 1.1287}$$




5.21  
Control -

For the first order HP section consider

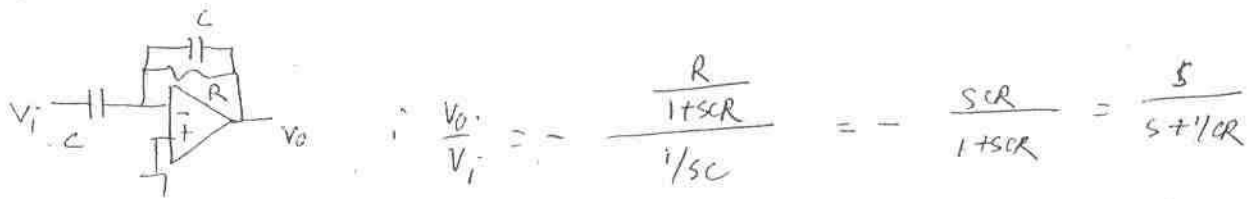

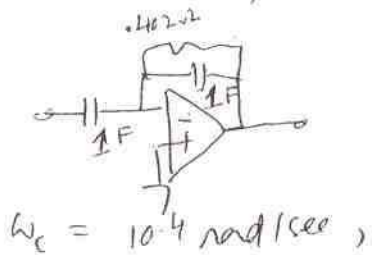
Let  $C = 1F$ ,  $R = 1/2.4876$ ,  $= 0.402 \Omega$



is the network. On denormalization for


the scale factor is  $10^4$

So make  $C = 10^{-4} F = 100 \mu F$

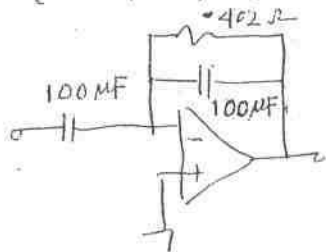

For the second order HP section, consider, the following

with  $k=1$

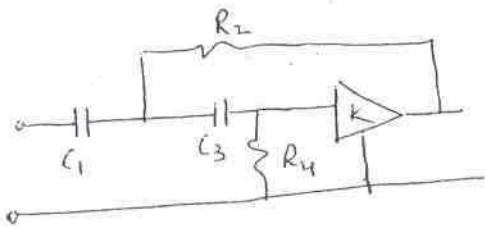

Then  $\omega_p = \sqrt{1.1287}$   
 $= \frac{1}{\sqrt{C_1 C_3 R_2 R_4}}$

$\frac{1}{\omega_p} = \sqrt{\frac{R_2}{R_4} \frac{C_1}{C_3}} + \sqrt{\frac{R_2}{R_4} \frac{C_3}{C_1}} = \frac{0.4165}{\omega_p} = 0.392$

Following method similar

to (4.21), let  $1/m = \frac{R_4}{R_2}$ ,  $1/n = \frac{C_3}{C_1}$ . Solve for  $m < \frac{1}{4R_p^2}$

$m < \frac{1}{4} \cdot 0.153664 \rightarrow 0.038$ . Let  $m = 0.01$

Then  $n = \left( \frac{1}{2mR_p^2} - 1 \right) \pm \frac{1}{2mR_p^2} \sqrt{1 - 4mR_p^2}$ , with  $m = 0.02$

$n = 5.5014$  or  $0.1818$ . Let  $n = 0.1818$

Then  $\omega_p = \sqrt{1.1287} = 1.0624 = \frac{1}{\sqrt{nC_3^2 m R_4^2}} = \frac{1}{\sqrt{nm}} \frac{1}{R_4 C_3}$


Let  $C = 1F$  then  $R_4 = 15.61 \Omega$

5.21

$$C_1 = n C_3 = .1818 \text{ F}$$

$$R_2 = m R_4 = .02 \times 15.61 = .3122 \Omega$$


Thus

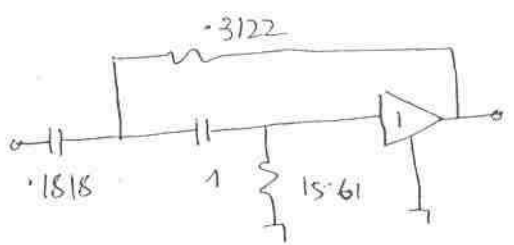

is the normalized network  
i.e. for  $\omega_c = 1$  rad/sec


For  $\omega_c = 10^4$  rad/sec, scale by  $10^4$

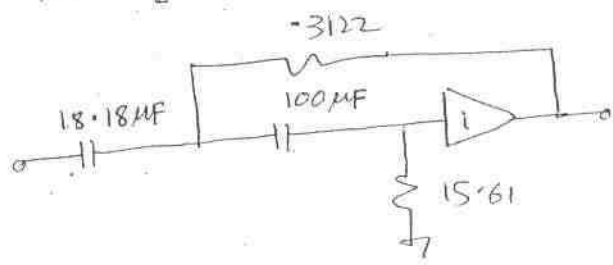So make  $C_3 = 1 \text{ F} \rightarrow 100 \mu\text{F}$   
 $C_1 = C_3 \times .1818 = 18.18 \mu\text{F}$



is the frequency denormalized network

Complete network

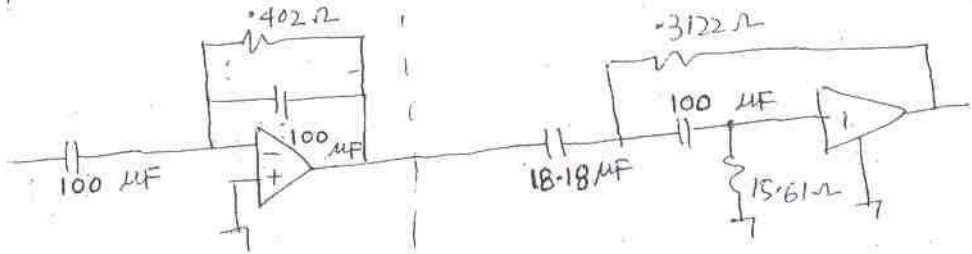

1st order

2nd order


← overall 3rd order filter →

5.21


Alternative design using RC:CR transformation

First realize the HN/LP obtained i.e.
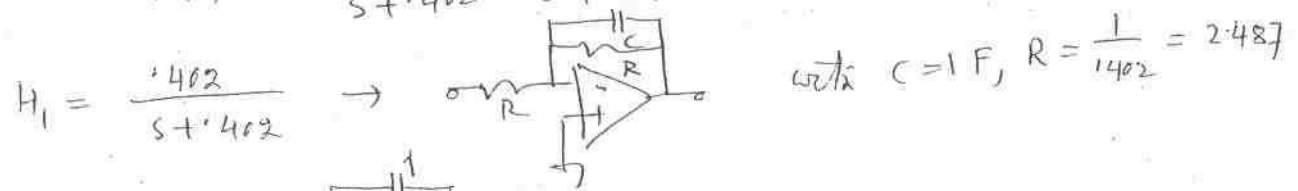
$$H_{in}(s) = \frac{.402}{s + .402} \cdot \frac{.886}{s^2 + .369s + .886} = H_1 H_2$$



So

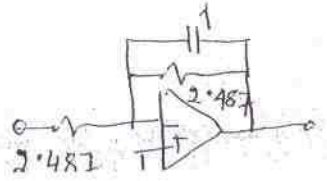

is the normalized  $H_1$  network

5.21

All design

$$H_2 = \frac{.886}{s^2 + .369s + .886}$$

$$\omega_p = \sqrt{.886} = .9413$$

$$\frac{\omega_p}{Q_p} = .369; \quad \frac{1}{Q_p} = .342, \quad Q_p = 2.551$$

Using  $K=1$  and  $m = \frac{C_4}{C_2}$ ;  $n = \frac{R_3}{R_1}$ , we get as before


$$m < \frac{1}{4Q_p^2} \rightarrow .038. \quad \text{Let } m = .02, \quad \text{then } n = 5.5014 \text{ or } 0.1818.$$

Let  $n = 0.1818$ , let  $C_2 = 1F$ ,  $R_1$  is then  $= 17.62 \Omega$


$$\text{Then } \omega_p = .9413 = \frac{1}{\sqrt{m} R_1 C_2}$$

$$\text{Then } R_3 = n R_1 = 3.203 \Omega; \quad C_4 = m C_2 = .02 F$$

So the normalized  $H_2$  is:

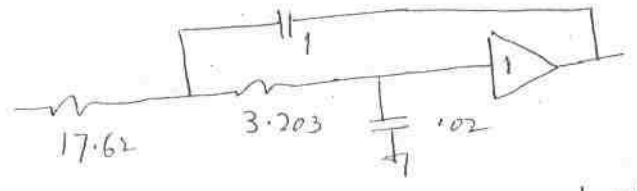

Overall normalized 3rd order network is:

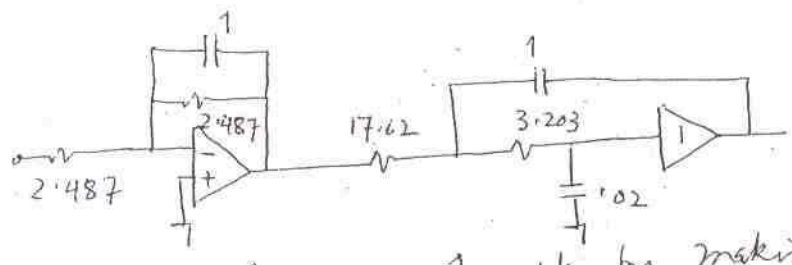

LPF for  $\omega_c \rightarrow 1 \text{ rad/sec}$ .


Denormalize for  $\omega_c = 10^4 \text{ rad/s}$  by making

$$C \rightarrow C/10^4 \quad (R \rightarrow R/10^4 \text{ will be also O.K.})$$

First convert the LP to HP using RC:CR transformation i.e.

$$R_{HP} \rightarrow \frac{1}{C_{LP}}; \quad C_{HP} \rightarrow \frac{1}{R_{LP}}$$

So

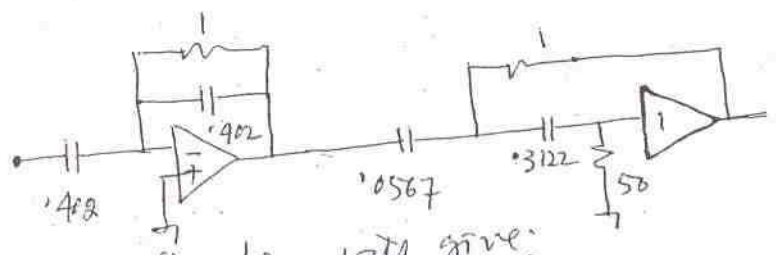

This is normalized HP with  $\omega_c = 1 \text{ rad/sec}$ .

denormalization will give:



5.22

$\omega_{p1} = 1000$ ,  $\omega_{p2} = 4000$ ,  $B = 3000$ ,  $\omega_0 = \sqrt{\omega_{p1} \omega_{p2}} = 2000$   
 $\omega_s = 12 \times 10^3$  rad from center of band.

Using  $A = \frac{\omega_0}{B} \left( \frac{s}{\omega_0} + \frac{\omega_0}{s} \right) \rightarrow \omega = \frac{\omega_0}{B} \left( \frac{\Omega}{\omega_0} - \frac{\omega_0}{\Omega} \right)$

$\Delta \rightarrow$  normalized frequency  $j\omega$   
 $\Omega \rightarrow$  BP domain frequency  $j\Omega$

Let  $\Omega = 12 \times 10^3$ ,  $\omega = \frac{2000}{3000} \left( \frac{12000}{2000} - \frac{2000}{12000} \right) = 3.89$

Thus  $\omega_c/\omega_0 = \omega_s = 3.89$ , using this to find the order of the nominal low-pass CHEB filter with  $A_p = 0.5$  dB, we get  $n_{CHEB} \geq 2.55$ . Take  $n_{CHEB} = 3$

For  $A_p = 0.5$  dB,  $\epsilon = 0.3493$

(Alt. If we associate  $B \rightarrow \omega_c = 3000$ ,  $\omega_a \rightarrow 12000$ ,  $\omega_s = 4$ ,  $n_{CHEB} \geq 2.52$ . Take  $n_{CHEB} = 3$ )

So the nominal normalized LPF has

$$H_N = \frac{1}{2 \cdot \epsilon} \cdot \frac{1}{D(s)} = \frac{1}{4 \times 0.3493} \cdot \frac{1}{(s+0.626)(s^2+0.626s+1.142)}$$

$$= \frac{0.626}{s+0.626} \cdot \frac{1.142}{s^2+0.626s+1.142}$$

On applying the  $s \leftrightarrow \frac{\omega_0}{B} \left( \frac{s}{\omega_0} + \frac{\omega_0}{s} \right)$  transformation and following up the derivations to split a 4th order function into cascade of two second order functions, we get the designable BP transfer function as (frequency denormalized):


$$H(s) = \frac{1878 \cdot s}{s^2 + 1878s + 4 \times 10^6} \cdot \frac{3.2059 \times 10^3}{s^2 + 361.5718s + 9.5375 \times 10^5}$$

$$\frac{3.2059 \times 10^3}{s^2 + 1.5164 \times 10^3 s + 1.6776 \times 10^7}$$

which represents a cascade of 3 second order BPF.

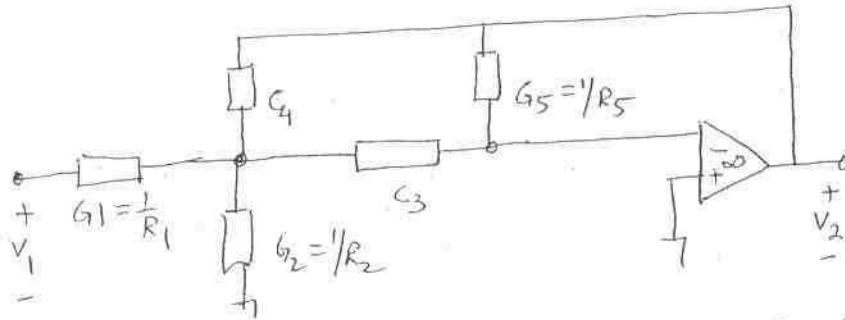5.22

Each BPF can be designed using the I<sub>G</sub>-LAB architecture (see Table 4.3)



With the design equations:  $G_3 = G_4 = 1$   
 $G_1 = H, G_2 = 2\omega_p Q_p - H$   
 $G_5 = \frac{1}{2} \frac{\omega_p}{Q_p}$

For  $\frac{1878 \Delta}{s^2 + 1878 \Delta + 4 \times 10^6}$ ;  $H = 1878$   
 $\omega_p = 2000$   
 $\frac{\omega_p}{Q_p} = 1878, Q_p = 1.065$

These give  $G_1 = 1878, G_2 = 2382, G_5 = 939, G_3 = G_4 = 1$


If  $G_3 = G_4 = 0.1 \mu F$  is made, scale the resistances by  $10^7$ .  
 Then  $G_3 = G_4 = 0.1 \mu F$ ;  $R_1 = \frac{10^7}{G_1} = 5.325 K, R_2 = \frac{10^7}{G_2} = 4.198 K,$   
 $R_5 = \frac{10^7}{G_5} = 10.65 K.$

Proceeding similarly, we get the following results:

$H(s)$	$G_1 = G_2 = 0.1 \mu F$	$R_1$	$R_2$	$R_5$
$\frac{1878 \Delta}{s^2 + 1878 \Delta + 4 \times 10^6}$	$0.1 \mu F$ each	$5.325 K$	$4.198 K$	$10.65 K$
$\frac{3.2059 \times 10^3 \Delta}{s^2 + 361.5718 \Delta + 9.5375 \times 10^5}$	$0.1 \mu F$ each	$3.12 K$	$4.83 K$	$55.31 K$
$\frac{3.2059 \times 10^3 \Delta}{s^2 + 1.5164 \times 10^3 \Delta + 1.6776 \times 10^7}$	$0.1 \mu F$ each	$3.12 K$	$528.54$	$13.19 K$



5.23

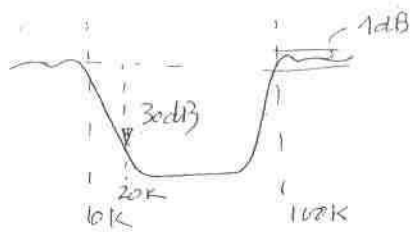

$$\Omega_c = \sqrt{10k \cdot 100k} = 3162 k \times 2\pi$$

$$B = 100k - 10k = 90k \times 2\pi$$

$s \rightarrow \frac{Bs}{s^2 + \Omega_c^2}$  is the LP  $\rightarrow$  BS transformation.

$$\omega_n = \frac{B}{\Omega_c} \cdot \frac{1}{\frac{\sqrt{b}}{\omega} - \frac{\omega}{\sqrt{a}}}$$

For  $\omega = 20k \times 2\pi$   
 $\omega_n \approx 3$

For  $A_p = 1$  dB,  $\epsilon = .5088$ ,  $n_{\text{CHEB}} = 3$ .

$$H_N(s) = \frac{.491}{(s + .494)(s^2 + .495s + .994)}$$

$$= \frac{.494}{s + .494} \cdot \frac{.994}{s^2 + .495s + .994}$$

$$\rightarrow \frac{A}{s+A} \cdot \frac{b}{s^2 + as + b}$$

$s \rightarrow \frac{Bs}{s^2 + \Omega_c^2}$  transformation gives

$$\frac{A}{s+A} \rightarrow \frac{s^2 + \Omega_c^2}{s^2 + \frac{A}{B}s + \Omega_c^2}$$

$$\frac{b}{s^2 + as + b} \rightarrow \frac{(s^2 + \Omega_c^2)^2}{s^4 + \frac{aB}{b}s^3 + \frac{B^2 + 2b\Omega_c^2}{b}s^2 + \frac{aB\Omega_c^2}{b}s + \Omega_c^4}$$

With  $A = .494$ ,  $a = .49$ ,  $b = .994$  we shall have  $\left( \begin{matrix} B = 2\pi \times 90 \times 10^3 \\ \Omega_c = 2\pi \times 3162 \times 10^3 \end{matrix} \right)^3$

$$\frac{.494}{s + .494} \rightarrow \frac{s^2 + (2\pi \times 3162 \times 10^3)^2}{s^2 + 1.1447 \times 10^6 s + (2\pi \times 3162 \times 10^3)^2} \Rightarrow T_1$$

$$\frac{.994}{s^2 + .495s + .994} \rightarrow \frac{s^2 + (2\pi \times 3162 \times 10^3)^2}{s^2 + 2.561 \times 10^9 s + 3.9931 \times 10^9} \cdot \frac{s^2 + (2\pi \times 3162 \times 10^3)^2}{s^2 + 2.5315 \times 10^5 s + 3.9017 \times 10^{11}} \Rightarrow T_3$$

So we have a cascade of  $T_1, T_2, T_3$ , three second order band reject filters.

contd. 5.23

For  $T_1$ , consider Fleischer - Towl Universal biquad  
(section 4.6.4)

$$\frac{V_o}{V_i} = - \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0}$$

For notch filter as in  $T_1$   
 $b_1 = 0, b_0/b_2 = a_0$

Then  $\frac{R_8}{R_6} - \frac{R_1 R_8}{R_4 R_7} = 0$  ;  $b_2 = 1, \frac{b_0}{b_2} = a_0$ , gives  $\frac{R_8}{R_6} = 1$  ... (A)

$$\frac{b_0}{b_2} = \frac{R_6}{R_3 R_5 R_7} \cdot \frac{1}{C_1 C_2} ; a_0 = \frac{R_8}{R_2 R_3 R_7 C_1 C_2} ; \frac{b_0}{b_2} = a_0 \text{ gives}$$

$$\frac{R_8}{R_2} = \frac{R_1}{R_5} ; R_2 = R_5 \dots (B)$$

$$b_1 = 0 \quad \frac{R_8}{R_6} - \frac{R_1}{R_4} \cdot \frac{R_8}{R_7} = 0 ; \frac{R_1}{R_4} \cdot \frac{R_8}{R_7} = 1 \quad \because \frac{R_8}{R_6} = 1 \text{ by (A)}$$

$$R_8 = R_7, R_1 = R_4 \dots (C)$$

$$a_0 = \omega_p^2 = \frac{R_8}{R_7 \cdot R_2 R_3 C_1 C_2} \rightarrow \frac{1}{R_2 R_3 C_1 C_2} = \frac{1}{(RC)^2}$$

$$\text{if } R_2 = R_3 = R, C_1 = C_2 = C \dots (D)$$

$$a_1 = \frac{1}{RC} = \frac{\omega_p}{Q} \dots (E)$$

Let  $C = 1F$ ; Then  $R = R_2 = R_3 = \frac{1}{\omega_p^2} = \frac{1}{2\pi \times 31.62 \times 10^3}$

$$R = 5.033 \times 10^{-6} = R_2 = R_3 \dots (1)$$

$$C_1 = C_2 = 1F \dots (2)$$

$$R_1 = \frac{C_p}{\omega_p C} = \frac{1}{C a_1} = 8.736 \times 10^{-6} \dots (3)$$

Let us make  $C = 0.1 \mu F$ , a practical value

Then  $R = R_2 = R_3 = 10^7 \times 5.033 \times 10^{-6} = 50.33 \Omega$

$$R_1 = R_4 = 8.736 \Omega$$

$$R_5 = R_2 = 50.33 \Omega$$

$$R_6 = R_8 = R_7 = 10 \Omega \text{ (free choice)}$$

one possible design



5.23  
Contd.

For a notch such as  $T_2, T_3$

$$b_2 = 1, \quad b_1 = 0, \quad b_0 = \omega_z^2, \quad a_1 = \frac{\omega_p}{\omega_z}, \quad a_0 = \omega_p^2$$

$$\frac{R_8}{R_6} = 1, \quad R_8 = R_6 \quad \dots \textcircled{A}$$

$$\frac{R_8}{R_6} - \frac{R_4 R_8}{R_4 R_7} = 0, \quad \frac{R_4}{R_4} \cdot \frac{R_8}{R_7} = 1 \quad \dots \textcircled{B}$$

$$\frac{R_8}{R_3 R_5 R_7} \cdot \frac{1}{C_1 C_2} = \omega_z^2, \quad \text{let } R_8 = R_7, R_3 = R_5, C_1 = C_2 = C, \text{ then}$$

$$\frac{1}{R'} \cdot \frac{1}{C} = \omega_z^2 \quad \text{where } R' = R_3 = R_5 \text{ with } R_8 = R_7 \quad \dots \textcircled{C}$$

$$\frac{1}{R_1 C_1} = a_1 \quad \text{or } R_1 = \frac{1}{a_1 C} \quad \dots \textcircled{D}$$

$$\frac{R_8}{R_2 R_3 R_7} \cdot \frac{1}{C_1 C_2} \rightarrow \frac{1}{R_2 R'} \cdot \frac{1}{C^2} = \omega_p^2 = a_0 \quad \dots \textcircled{E}$$

Let  $C = 1F$ ; From  $\textcircled{C}$ ,  $R' = \frac{1}{\omega_z^2} = \frac{1}{2\pi \times 3162 \times 10^3} = 5.033 \times 10^{-6} \quad \dots \textcircled{1}$

From  $\textcircled{E}$   $\frac{1}{R_2 R' C^2} = \omega_p^2$ ;  $\frac{1}{R_2} = \omega_p^2 \cdot R'$  if  $C=1$  assumed

$$\text{So } R_2 = \frac{1}{R' \omega_p^2} = \frac{1}{(5.033 \times 10^{-6}) \cdot 3.9931 \times 10^9} = 4.976 \times 10^{-5} \quad \dots \textcircled{2}$$

$$\text{From } \textcircled{D} \rightarrow R_1 = \frac{1}{a_1 C} = \frac{1}{a_1} = \frac{1}{2.561 \times 10^4} = 3.905 \times 10^{-5} \quad \dots \textcircled{3}$$

So  $R_1 = 3.905 \times 10^{-5}$ ,  $R_2 = 4.976 \times 10^{-5}$ ,  $R_3 = R_5 = R' = 5.033 \times 10^{-6}$

Let  $R_4 = R_1 = 3.905 \times 10^{-5}$ ;  $R_6 = R_8 = R_7 = 10 \Omega$  (say)

Scale  $C = 0.1 \mu F$ . Then

$$\left. \begin{aligned} R_4 = R_1 = 390.5 \Omega, \quad R_2 = 497.6 \Omega, \quad R_3 = R_5 = 50.33 \Omega \\ R_6 = R_7 = R_8 = 10 \Omega \quad C_1 = C_2 = C = 0.1 \mu F \end{aligned} \right\} \text{Possible design for } T_2$$

5.23  
Contd.

For  $T_3$  we can follow same approach. But now

$$a_1 = \frac{\omega_z}{\omega_p} = 2.5315 \times 10^5 \text{ and } a_0 = \omega_p^2 = 3.9017 \times 10^{11}$$

$$\text{Hence } R_1 = \frac{1}{2.5315 \times 10^5} = 3.95 \times 10^{-6}$$

$$R_2 = \frac{1}{(5.033 \times 10^6) \cdot 3.9017 \times 10^{11}} = 5.092 \times 10^{-7}$$

} For  $C=1F$

Using  $C = 0.1 \mu F$ , we get

$$R_1 = R_4 = 39.5 \Omega ; R_2 = 5.092 \Omega ; R_3 = R_5 = 50.33 \Omega$$

$$R_6 = R_7 = R_8 = 10 \Omega \quad C_1 = C_2 = C = 0.1 \mu F$$

} possible design for  $T_3$

5.24

Use Tow-Thomas structure (see Table 4.4).

Let  $C = 0.1 \mu F$ , flat gain = 10 (say).


$$\text{Then } R = \frac{1}{\omega_{pc}} = \frac{10^7}{50 \times 10^3} = 200 \Omega$$

$$R_1 \rightarrow \text{open}, R_2 = R/10 = 20 ; R_3 = R/10 = \frac{10 \cdot r}{100} = 100 \Omega$$

if  $r = 100 \Omega$

$$C_1 = C(10) = 1 \mu F$$


So the network is:

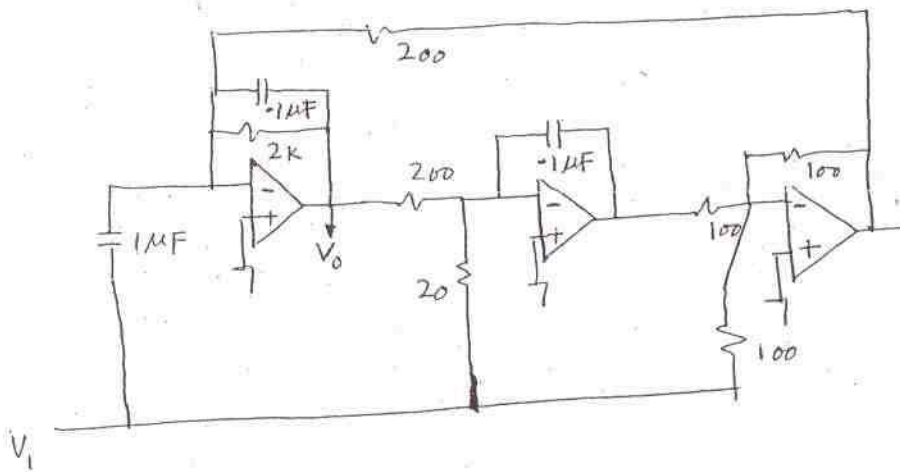

OA-s are assumed ideal.

5.25

Take clue from

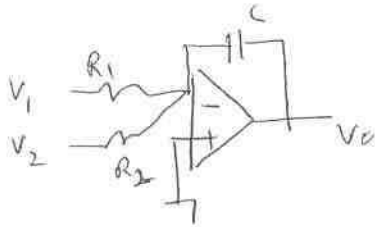

$$V_0 = - \frac{1}{R_f} \frac{1}{s} \cdot V_1 - \frac{1}{R_2} \frac{1}{s} V_2$$

$\frac{1}{R_1 C}$ ,  $\frac{1}{R_2 C}$  etc. will emulate the


branch gains  $a, b, \dots$  and so on.

Each summing junction has two inputs.

So each summing integ. will have two inputs.

$$a = \frac{1}{R_1 C_1} ; e = \frac{1}{R_2 C_1}$$
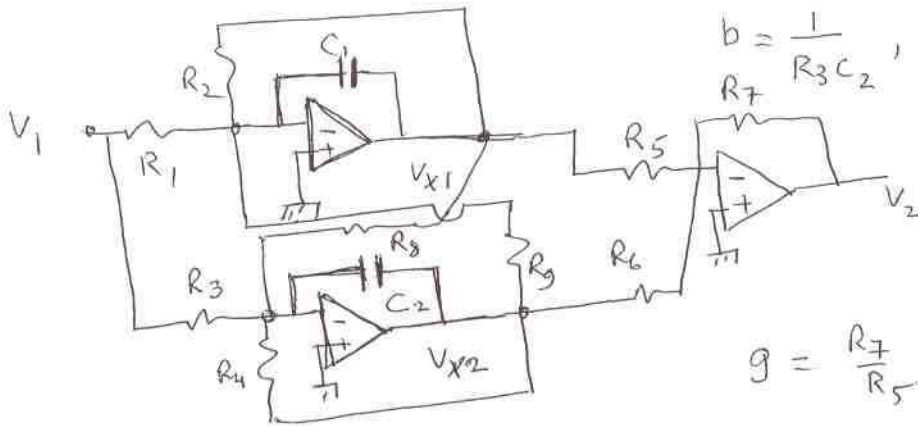
$$b = \frac{1}{R_3 C_2} ; f = \frac{1}{R_4 C_2}$$



$$g = \frac{R_7}{R_5} ; h = \frac{R_7}{R_6}$$

$$d = \frac{1}{R_8 C_2} ; c = \frac{1}{R_9 C_1}$$

$$V_{x1} = - \frac{a}{s} V_1 - \frac{e}{s} V_{x1} - \frac{c}{s} V_{x2} \quad \text{or} \quad V_{x1} \left(1 + \frac{e}{s}\right) = - \frac{a}{s} V_1 - \frac{c}{s} V_{x2}$$

$$V_{x2} = - \frac{b}{s} V_1 - \frac{f}{s} V_{x2} - \frac{d}{s} V_{x1} \quad \text{or} \quad V_{x2} \left(1 + \frac{f}{s}\right) = - \frac{b}{s} V_1 - \frac{d}{s} V_{x1}$$

$$V_2 = -g V_{x1} - h V_{x2}$$

Arrange

in a  
matrix  
form

$$\begin{bmatrix} 1 + \frac{e}{s} & \frac{c}{s} \\ \frac{d}{s} & 1 + \frac{f}{s} \end{bmatrix} \begin{bmatrix} V_{x1} \\ V_{x2} \end{bmatrix} = \begin{bmatrix} -\frac{a}{s} \\ -\frac{b}{s} \end{bmatrix} \begin{bmatrix} V_1 \end{bmatrix}$$

$$V_{x1} = \frac{V_1}{\Delta} \begin{vmatrix} -\frac{a}{s} & \frac{c}{s} \\ -\frac{b}{s} & 1 + \frac{f}{s} \end{vmatrix} ; V_{x2} = \frac{V_1}{\Delta} \begin{vmatrix} 1 + \frac{e}{s} & -\frac{a}{s} \\ \frac{d}{s} & -\frac{b}{s} \end{vmatrix}$$

$$\Delta = \begin{vmatrix} 1 + \frac{e}{s} & \frac{c}{s} \\ \frac{d}{s} & 1 + \frac{f}{s} \end{vmatrix}$$

< continue >

5.26

$H_N(s)$ , CHEB order 2 is  $\frac{1}{2^1 \epsilon} \cdot \frac{1}{s^2 + 0.804s + 0.637}$   
& 2dB ripple

where  $\epsilon = 10^{0.1A_p} - 1 = 0.7648$

So  $H(s) = H_x \frac{1}{s^2 + 0.804s + 0.637}$  where  $H_x = 2 \times 0.637 = 1.274$

a) By multiple feedback structure

Identify  $\omega_p^2 = 0.637$  ;  $\omega_p = 0.798$

$\omega_p / Q_p = 0.804$  ;  $Q_p = \frac{\omega_p}{0.804} = 0.993$

Follow the guidelines in Table 5.5, remembering


$H_0 = \frac{R_2}{R_1} = 1.274$ .

b) By state variable structure

Use Tow-Thomas universal biquad structure, Table 5.6

---

5.27

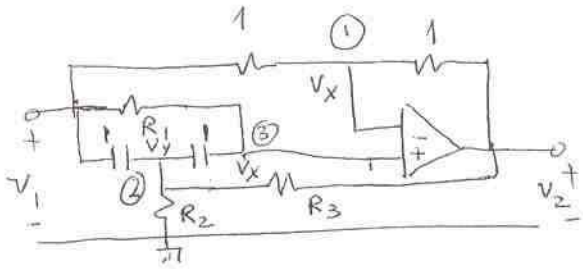

KCL @ ①  $V_1 - V_x = V_x - V_2$

So  $V_x = \frac{V_1 + V_2}{2}$

KCL @ ②

$(V_y - V_1)G_1 + (V_y - V_2)G_3 + (V_y - V_x)G_2 = 0$

Solving for  $V_y$  ;  $V_y = \frac{1}{2} \cdot \frac{3V_1 G_1 + 2V_2 G_3 + V_2 G_2}{2G_1 + G_3 + G_2}$

KCL @ ③  $(V_x - V_1)G_1 + (V_x - V_y)G_2 = 0$

Subst. for  $V_x, V_y$  ;  $V_2 = V_1 \frac{G_1^2 + (2G_1 - G_3 - G_2)G_1 + G_1 G_3 + G_1 G_2}{G_1^2 + (2G_1 - G_3 + G_2)G_1 + G_1 G_3 + G_1 G_2}$

So  $\frac{V_2}{V_1} = \frac{V_2}{V_1} = \frac{G_1^2 + (2G_1 - G_3 - G_2)G_1 + G_1 G_3 + G_1 G_2}{G_1^2 + (2G_1 - G_3 + G_2)G_1 + G_1 G_3 + G_1 G_2}$


To obtain a design  $\frac{V_2}{V_1} = \frac{s^2 - 5s + 10}{s^2 + 5s + 10}$

Let  $\begin{cases} 2G_1 - G_2 - G_3 = -5 \\ G_1 G_3 + G_1 G_2 = 10 \end{cases}$  Solving   
 $G_2 = 2G_1 - G_3 + 5$   
 $G_3 = 2G_1$


$G_1 = -\frac{5}{4} \pm \frac{1}{4}\sqrt{105} \rightarrow -\frac{5}{4} + \frac{1}{4}\sqrt{105}$  is acceptable.

So  $G_1 = -\frac{5}{4} + \frac{1}{4}\sqrt{105} = 1.312$  ;  $G_2 = 5$  ;  $G_3 = 2.624$

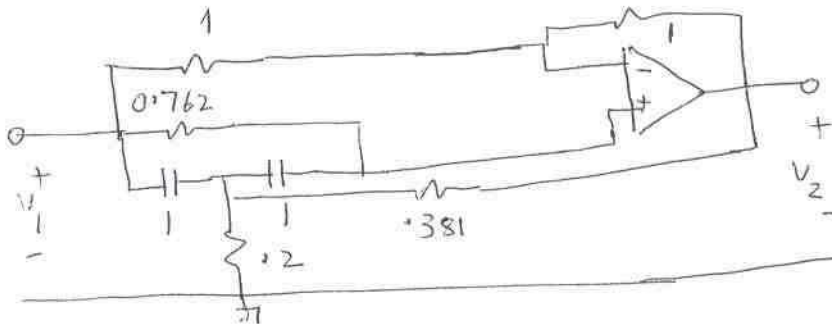$R_1 = 0.762$  ;  $R_2 = 0.2$  ;  $R_3 = 0.381$



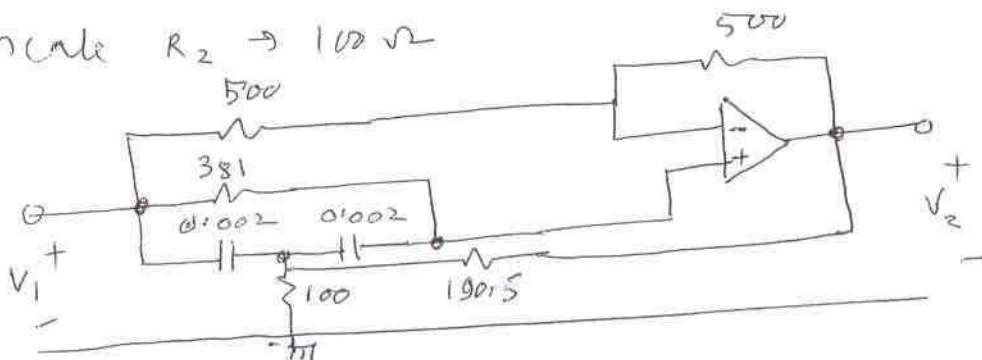If we scale  $R_2 \rightarrow 100 \Omega$



Alternate design



5.28

$$\left. \begin{aligned} V_{o1} &= -V_i \frac{1}{sC_1 R} - V_{o1} \frac{1}{sC_1 R_1} - V_{o2} \frac{1}{sC_1 R_2} \\ V_{o1} \left(1 + \frac{1}{sC_1 R_1}\right) &= -\frac{V_i}{sC_1 R} - \frac{V_{o2}}{sC_1 R_2} \end{aligned} \right\} \text{around OA \# 1.}$$

$$V_{o1} g + V_{o2} \left(\frac{-Y_2}{Y_1}\right) \cdot sC_2 = 0 \quad \text{around OA \# 2, \# 3.}$$

$$V_{o2} = \frac{Y_1}{Y_2} \frac{1}{sC_2} g V_{o1}$$

Putting back:  $V_{o1} \left(1 + \frac{1}{sC_1 R_1}\right) = -\frac{V_i}{sC_1 R} - \frac{1}{sC_1 R_2} \left(\frac{Y_1}{Y_2} \frac{1}{sC_2} g\right) V_{o1}$

$$\text{or } V_{o1} \left[1 + \frac{1}{sC_1 R_1} + \frac{Y_1}{Y_2} \cdot \frac{1}{s^2 C_1 C_2 R_2 R_1}\right] = -\frac{V_i}{sC_1 R}$$

$$V_{o1} \left[ \frac{s^2 C_1 C_2 R_2 R_1 Y_2 R_1 + s C_2 R_2 Y_2 + Y_1}{s^2 C_1 C_2 R_2 R_1 Y_2} \right] = -\frac{V_i}{sC_1 R}$$


$$\frac{V_{o1}}{V_i} = - \frac{s^2 C_1 C_2 R_2 R_1 Y_2}{s C_1 R} \cdot \frac{1}{Y_1 + s C_2 R_2 Y_2 + s^2 C_1 C_2 R_2 R_1 Y_2}$$

$$= - \frac{s C_2 R_2 R_1 Y_2 / R}{C_1 C_2 R_2 R_1 Y_2 \left[ s^2 + s \frac{C_2 R_2 Y_2}{C_1 C_2 R_2 R_1 Y_2} + \frac{Y_1}{C_1 C_2 R_2 R_1 Y_2} \right]}$$

$$\frac{V_{o1}}{V_i} = - \frac{s / RC_1}{s^2 + s / C_1 R_1 + Y_1 / (C_1 C_2 R_2 R_1 Y_2)} \quad \text{a BPF function}$$

5.29

For finite gain A of the OA consider

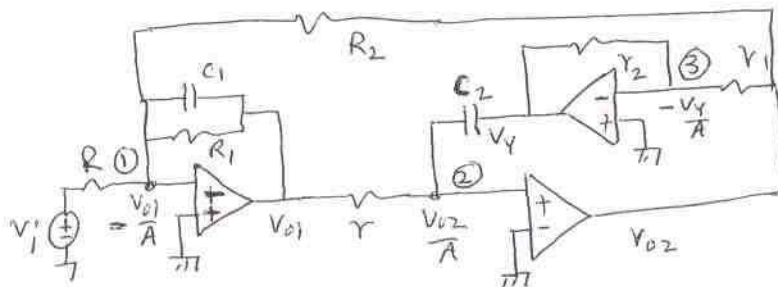



5.29 (cont.)

KCL (a) (1)

$$\left( v_i + \frac{v_{o1}}{A} \right) g + (g_1 + sC_1) \left( v_{o1} + \frac{v_{o1}}{A} \right) + g_2 \left( v_{o2} + \frac{v_{o1}}{A} \right) = 0$$

KCL (a) (2)

$$\left( v_{o1} - \frac{v_{o2}}{A} \right) g + \left( v_y - \frac{v_{o2}}{A} \right) sC_2 = 0$$

KCL (a) (3)

$$\left( v_{o2} + \frac{v_y}{A} \right) g_1 + \left( v_y + \frac{v_y}{A} \right) g_2 = 0$$

From KCL (3),  $v_y = - \frac{g_1}{g_2 \left( 1 + \frac{1}{A} \right) + \frac{g_1}{A}} v_{o2}$

Subst. in KCL (2) we get

$$v_{o1} = v_{o2} \left[ \frac{1}{A} + \frac{sC_2/g}{A} + \frac{sC_2 g_1/g}{g_2 \left( 1 + \frac{1}{A} \right) + \frac{g_1}{A}} \right]$$

Subst. in KCL (1)


$$g v_i + \frac{v_{o1}}{A} g + v_{o1} \left( 1 + \frac{1}{A} \right) (g_1 + sC_1) + v_{o2} g_2 + v_{o1} \frac{g_2}{A} = 0$$

$$g v_i = - \left[ g_2 + \left( \frac{1}{A} \left( 1 + \frac{sC_2}{g} \right) + \frac{sC_2 g_1/g}{g_2 \left( 1 + \frac{1}{A} \right) + \frac{g_1}{A}} \right) \left( \frac{g + g_2}{A} + (g_1 + sC_1) \left( 1 + \frac{1}{A} \right) \right) \right] v_{o2}$$

So

$$\begin{aligned} \frac{v_{o2}}{v_i} &= - \frac{g}{g_2 + \left( \frac{1}{A} \frac{g + sC_2}{g} + \frac{sC_2 g_1}{g \left( g_2 \left( 1 + \frac{1}{A} \right) + \frac{g_1}{A} \right)} \right) \cdot \left( \frac{g + g_2}{A} + (g_1 + sC_1) \left( 1 + \frac{1}{A} \right) \right)} \\ &= - \frac{g g}{g_2 g + \left( \frac{g + sC_2}{A} + \frac{sC_2 g_1}{g_2 + \frac{g_1 + g_2}{A}} \right) \left( \frac{g + g_2}{A} + (g_1 + sC_1) \left( 1 + \frac{1}{A} \right) \right)} \\ &= - \frac{1/R_T}{\frac{1}{R_2 R} + \left( \frac{1}{R} + \frac{1}{R_2} + \left( 1 + \frac{1}{A} \right) \left( \frac{1}{R_1} + sC_1 \right) \right) \left( \frac{sC_2 / R_1}{\frac{1}{R_2} + \frac{1/R_1 + 1/R_2}{A}} + \frac{1/R + sC_2}{A} \right)} \end{aligned}$$

5.30

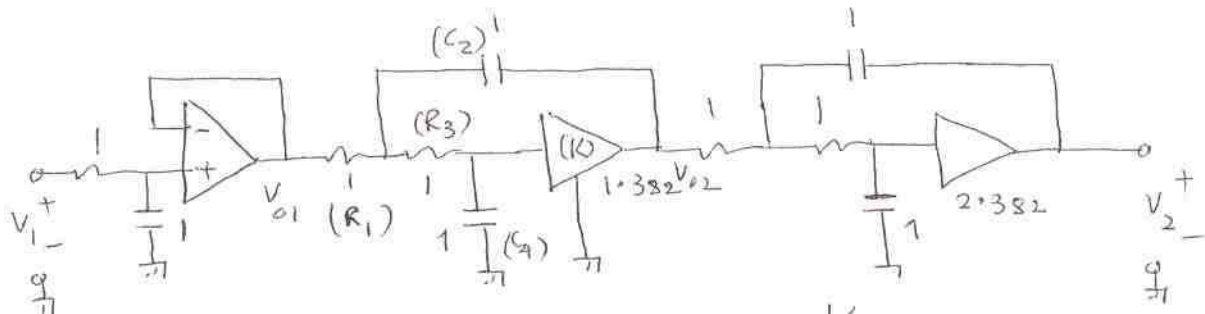

The first order network has  $V_{o1} = \frac{1/s}{1+1/s} V_1 = \frac{1}{s+1}$

The second network has  $\frac{V_{o2}}{V_{o1}} = \frac{K(G_1 G_3 / C_2 G_4)}{s^2 + s \left\{ \frac{G_1}{C_2} + \frac{G_3}{C_2} + (1-K) \frac{G_3}{G_4} \right\} + \frac{G_1 G_3}{C_2 G_4}}$

$G_1 = G_3 = C_2 = G_4 = 1$


$$\frac{V_{o2}}{V_{o1}} = \frac{1.382}{s^2 + s(1+1+(1-1.382)) + 1} = \frac{1.382}{s^2 + 1.618s + 1}$$

Similarly for  $\frac{V_2}{V_{o2}}$

So overall TF is:  $\frac{1}{s+1} \cdot \frac{1.382}{s^2 + 1.618s + 1} \cdot \frac{2.382}{1 + 1.618s + 1}$

We need to adjust  $H_1 H_2 H_3 = 1.382 \times 2.382$

5.31

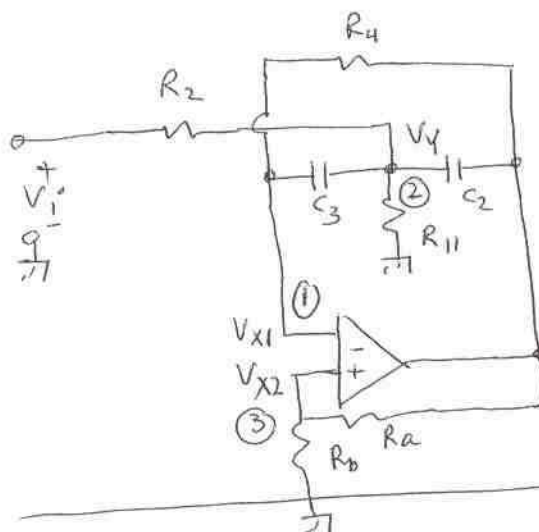

KCL (1)  $(V_{x1} - V_y) s C_3 + (V_{x1} - V_0) G_4 = 0$

KCL (2)  $-(V_1 - V_y) G_2 + (V_y - V_{x1}) s C_3 + V_y G_{11} + (V_y - V_0) s C_2 = 0$

KCL (3)  $V_{x2} G_b + (V_{x2} - V_0) G_a = 0$

Using  $G_i = \frac{1}{R_i}$  here

From KCL (1)  $V_{x1} = \frac{V_y s C_3 + V_0 G_4}{s C_3 + G_4}$

From KCL (3)  $V_{x2} = \frac{V_0 G_a}{G_a + G_b}$

For ideal OA,  $V_{x1} = V_{x2}$  giving

$$V_y = V_0 \frac{-G_b G_b + s G_a C_3}{(G_a + G_b) s C_3}$$

5.32 (cont.) : If  $A = \frac{w_t}{s}$ , we will get


$$\frac{V_o}{V_i} = \frac{N(s)}{D(s)}$$

$$\text{w/r } N(s) = -G_2 (G_a + G_b) w_t C_3 s$$

$$\begin{aligned}
 D(s) = & (C_2 C_3 G_a + C_2 C_3 G_b) s^3 + (C_2 G_4 G_b + C_2 G_4 G_a + G_{11} C_3 G_a + G_4 C_3 G_b + G_4 C_3 G_a + G_2 C_3 G_b \\
 & + G_2 C_3 G_a + C_2 C_3 G_b w_t + G_{11} C_3 G_b) s^2 \\
 & + (G_2 G_4 G_b + G_2 G_4 G_a + C_2 G_4 G_b w_t + C_3 G_4 G_b w_t + G_{11} G_4 G_a + G_{11} G_4 G_b \\
 & - G_2 C_3 G_a w_t - G_{11} C_3 G_a w_t) s + G_2 G_4 G_b w_t + G_{11} G_4 G_b w_t
 \end{aligned}$$

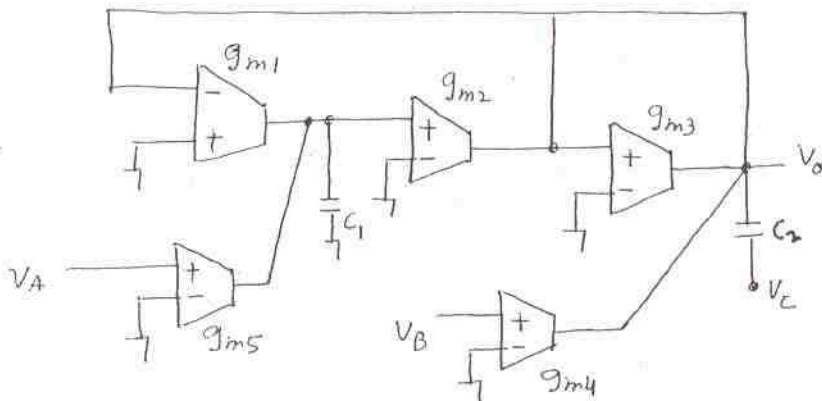5.33


Consider the general biquad structure (Fig. 1)



$$V_o = \frac{g_{m2}g_{m5}V_A - s g_{m4}C_1 V_B + s^2 C_1 C_2 V_C}{s^2 C_1 C_2 + s g_{m3}C_1 + g_{m1}g_{m2}}$$

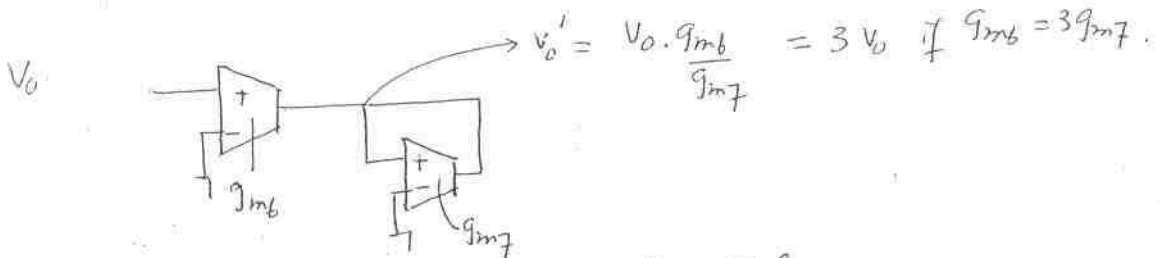a) HP,  $V_A = V_B = 0$        $\omega_p = \sqrt{\frac{g_{m4}g_{m2}}{C_1 C_2}}$  ;  $\alpha_p = \frac{C_2}{g_{m3}} \omega_p$

Flat gain at  $\omega = \infty$  1. To get a gain of 3 we need a voltage amplifier using OTA. Thus



Let  $C = 0.01 \mu F = C_1 = C_2$  ;  $g_{m1} = g_{m2} = g_m$ .

Then  $2000 = \frac{g_m}{C}$  ;  $g_m = 2000 \times 10^{-8} = 20 \mu V$

$\alpha_p = 5 = \frac{10^{-8}}{g_{m3}} \cdot 2000$  ;  $g_{m3} = \frac{2000}{5} \cdot 10^{-8} = 400 \times 10^{-8} = 4 \mu V$

Let  $g_{m7} = 4 \mu V$ , then  $g_{mb} = 12 \mu V$  for a flat gain  $H=3$ .

Total  $g_m = g_{m4} + g_{m2} + g_{m3} + g_{mb} + g_{m7} = (20 + 20 + 4 + 4 + 12) = 60 \mu V$

For the BJT-based OTA,  $g_m |_{out} = \frac{I_{DC} |_{out}}{V_T} \Rightarrow 60 \times 10^{-6}$  total

$\sum I_{DC} |_{out} = 60 \times 10^{-6} \times 25 \times 10^{-3}$   $\because V_T = 25 mV$  at room temp.

$= 1500 \times 10^{-6} mA$        $P = 3000 \times 10^{-6} \times 10 mW$

$\therefore I_{DC} = 3000 \times 10^{-6} mA$        $\therefore P = 30 \mu W$

5.33 (b) contd.

Let  $C_1 = C_2 = 0.1 \mu F$ ;  $g_{m1} = g_{m2} = g_m$

$5000 = \frac{g_m}{C}$ ;  $g_m = 10^8 \times 5000 = 5 \cdot 10^{-5} = 50 \mu S$

$g_{m1} = g_{m2} = 50 \mu S$ ;  $Q_p = \frac{10^8}{g_{m3}} \cdot 5000$ ;  $g_{m3} = \frac{10^8 \times 5000}{19} = 500 \times 10^8 = 50 \mu S$

Gain of  $10^4$   $H = \frac{g_{m4}}{g_{m3}}$ ; so  $g_{m4} = 50 \mu S$

$\sum g_m = 100 + 5 + 50 = 155 \mu S \leftarrow g_{m1} + g_{m2} + g_{m3} + g_{m4}$

$\sum I_{out}|_{DC} = 10^6 \times 155 \times 25 \text{ mA}$ ;  $\sum I_{BIAS} = 2 \sum I_{out}|_{DC} = 50 \times 155 \times 10^{-6} \text{ mA}$

$P_{DC} = \sum I_{BIAS} \times 10V = 50 \times 155 \times 10^{-6} \times 10 \text{ mW} = 77.5 \mu W$

(c) APF;  $g_{m1} = g_{m2} = g_m = C \times \omega_p = 10^{-8} \times 300 = 3 \mu S$

$Q_p = \frac{C}{g_{m3}} \omega_p$ ;  $g_{m3} = \frac{C \omega_p}{Q_p} = \frac{10^{-8} \times 300}{3} = 10^{-6} = 1 \mu S$

$H=1$  will require  $g_{m5} = g_{m1}$ ;  $g_{m4} = g_{m3}$

So  $\sum g_m = 3 + 3 + 1 + 3 + 1 = 11 \mu S$

$\sum I_{DC}|_{out} = 25 \times 10^{-3} \times 11 \times 10^{-6}$ ;  $\sum I_{BIAS} = 2 \times \sum I_{DC}|_{out} = 50 \times 10^{-3} \times 11 \times 10^{-6}$

$P_{DC} = 10 \times 50 \times 10^{-3} \times 11 \times 10^{-6} \text{ W} = 10 \times 50 \times 11 \times 10^{-9} \mu W = 5.5 \mu W$

(d) LPN:

$\frac{s^2 C_1 C_2 + g_{m2} g_{m5}}{s^2 C_1 C_2 + s g_{m3} C_1 + g_{m1} g_{m2}}$

with  $V_B = 0$ ,  $V_A = V_C$



5.33

Contd.

(d)

$$\frac{g_{m1} g_{m2}}{C_1 C_2} = \omega_p^2 \quad ; \quad \text{let } C_1 = C_2 = C = 10^{-8}$$

$$g_{m1} g_{m2} = 10^{-6} \times 2000 \times 2000 \quad \dots \textcircled{1}$$

$$\omega_p = 5; \quad g_{m3} = \frac{C \omega_p}{g_p} = \frac{10^{-8} \times 2000}{5} = 400 \times 10^{-8} = 4 \mu\text{V}$$

$$H=1 \quad \text{means (Low-pass notch)} \rightarrow g_{m5} = g_{m1}$$

$$\omega_z = \sqrt{\frac{g_{m2} g_{m5}}{C^2}} = 3000 \quad ; \quad \sqrt{g_{m2} g_{m5}} = 3000 C = \sqrt{g_{m2} g_{m1}}$$

$$\text{But } \sqrt{g_{m1} g_{m2}} \text{ is also } = \omega_p C = 2000 C$$

So  $C_1 = C_2$  is not a good assumption OR  $g_{m5} = g_{m1}$  is not a good design.

Let  $g_{m5} \neq g_{m1}$ , then  $H=1$  will be arranged later.


$$\text{Then } \left. \begin{aligned} \sqrt{g_{m2} g_{m5}} &= 3000 C \\ \sqrt{g_{m2} g_{m1}} &= 2000 C \end{aligned} \right\} \sqrt{\frac{g_{m5}}{g_{m1}}} = \frac{3}{2} \quad ; \quad g_{m5} = \frac{9}{4} g_{m1}$$

$$g_{m5} = 2.25 g_{m1}$$

$$\text{Make } g_{m1} = g_{m2} = g_m = \omega_p C = 2000 \times 10^{-8} = 20 \mu\text{V}$$

$$\text{So } g_{m1} = g_{m2} = 20 \mu\text{V}; \quad g_{m3} = 4 \mu\text{V}; \quad g_{m5} = 20 \times 2.25 = 45 \mu\text{V}$$

To make  $H=1$ , we need

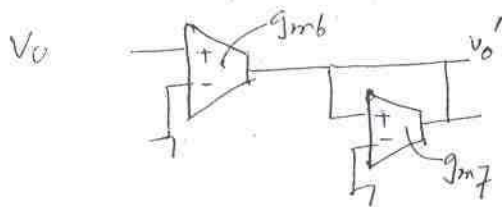

$$v_o' = \frac{g_{m6}}{g_{m7}} v_o = \frac{4}{9} v_o$$

$$\text{i.e. } g_{m6} = \frac{4}{9} g_{m7}$$

$$\text{or } g_{m7} = 2.25 g_{m6}$$

$$\text{Let } g_{m6} = 4 \mu\text{V}; \quad g_{m7} = 9 \mu\text{V}$$

$$\text{Then } \sum g_m = 20 + 20 + 4 + 45 + 4 + 9 = 102 \mu\text{V}$$

$$\sum I_{DC|OUT} \rightarrow 102 \times 10^{-6} \times 25 \text{ mA}$$

$$\sum I_{BIAS} = 102 \times 10^{-6} \times 25 \times 2 \text{ mA}$$

$$P_D = 10 \times 102 \times 10^{-6} \times 25 \times 2 \text{ mW} = 51 \times 10^{-3} \text{ mW} = 51 \mu\text{W}$$

5.33


(e)

left as an exercise

5.34

Work with ac equivalent circuits.

(a)

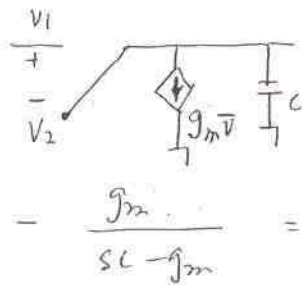

$$\frac{V_2}{V_1} =$$

$$= -\frac{g_m}{sC - g_m}$$

x


$$\bar{V} = V_1 - V_2$$

$$V_2 = -g_m \bar{V} \cdot \frac{1}{sC} = -g_m (V_1 - V_2) \frac{1}{sC}$$

$$V_2 \left(1 - \frac{g_m}{sC}\right) = -g_m \frac{V_1}{sC} \quad \text{OR} \quad \frac{sC - g_m}{sC} V_2 = -\frac{g_m V_1}{sC}$$

$$\frac{g_m}{g_m - sC} = -\frac{g_m / C}{s - g_m / C}$$

(b)

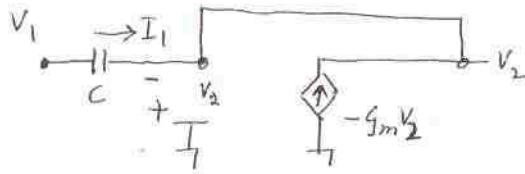


$$\frac{V_2}{V_1} = \frac{sC}{sC + g_m} = \frac{s}{s + g_m / C}$$

KCL gives

$$-sC(V_1 - V_2) + g_m V_2 = 0$$

$$(g_m + sC)V_2 + sC V_1 = 0$$

(c)

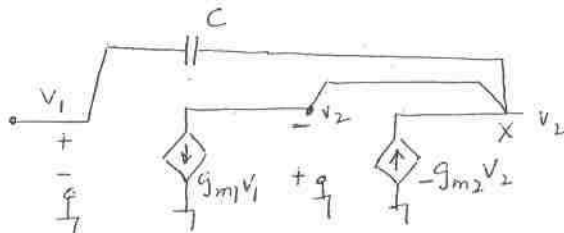

$$\frac{V_2}{V_1} = -\frac{g_{m1} - sC}{g_{m2} + sC}$$


KCL at x

$$-sC(V_1 - V_2) + g_{m1}V_1 + g_{m2}V_2 = 0$$

$$(g_{m1} - sC)V_1 + (g_{m2} + sC)V_2 = 0$$

$$\frac{g_{m1}/C - s}{g_{m2}/C + s} = -\frac{s - g_{m1}/C}{s + g_{m2}/C}$$

5.35

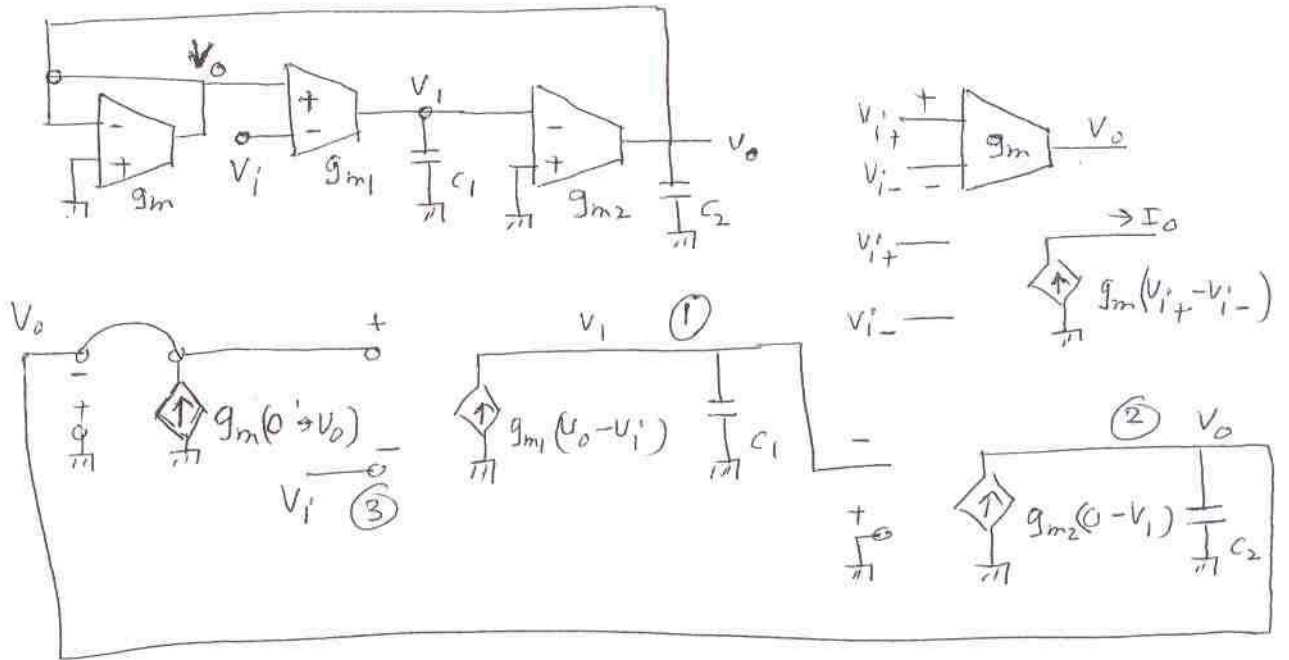


At ①  $V_1 = \frac{1}{sC_1} \cdot g_{m1} (V_o - V_i)$

At ②  $V_o = [g_{m2}(-V_1) + g_m(-V_o)] / sC_2$   
 $= (-g_{m2}V_1 - g_m V_o) / sC_2$

Subst. for  $V_1$   $V_o = V_i \frac{g_{m1} g_{m2}}{s^2 C_1 C_2 + s g_m C_1 + g_{m1} g_{m2}}$

which is a L.P.F

5.36

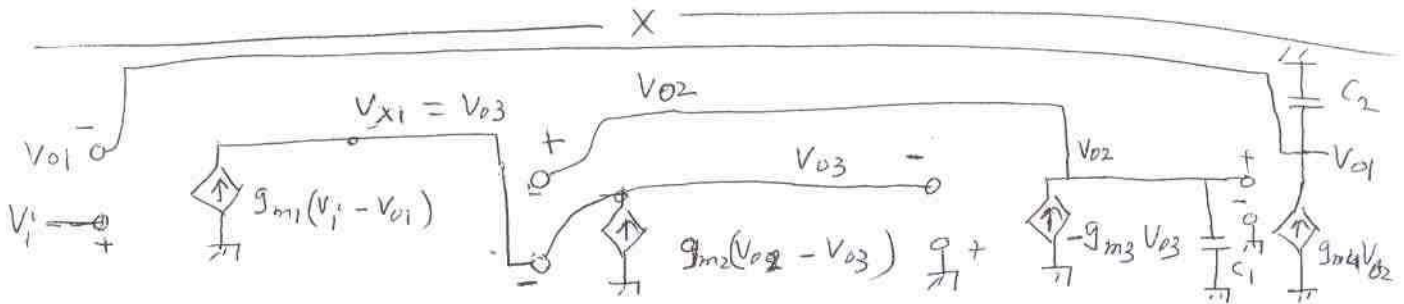

KCL #1  $g_{m1} (V_i - V_{o1}) + g_{m2} (V_{o2} - V_{o3}) = 0$

$V_{o2} = -g_{m3} V_{o3} / sC_1$  ;  $V_{o1} = g_{m4} V_{o2} / sC_2$

Subst. in KCL #1,  $V_{o1}$ ,  $V_{o2}$ , to derive


$\frac{V_{o3}}{V_i} = \frac{g_{m1} g_1 C_2 s^2}{-g_{m1} g_{m4} g_{m3} + g_{m2} g_{m3} C_2 s + g_{m2} C_1 C_2 s^2} \rightarrow$  a HAF (sign of  $g_{m1}$  or  $g_{m4}$  need be reversed!)

Then  $\frac{V_{o2}}{V_i} = \frac{g_{m1} g_1 C_2 s}{D(s)}$  ;  $\frac{V_{o1}}{V_i} = \frac{g_{m1} g_1 C_2}{D(s)}$

$D(s) = -g_{m1} g_{m4} g_{m3} + (g_{m2} g_{m3} C_2) s + (g_{m2} C_1 C_2) s^2$   
 Note: sign of  $g_{m1}$  or  $g_{m4}$  need be reversed!!

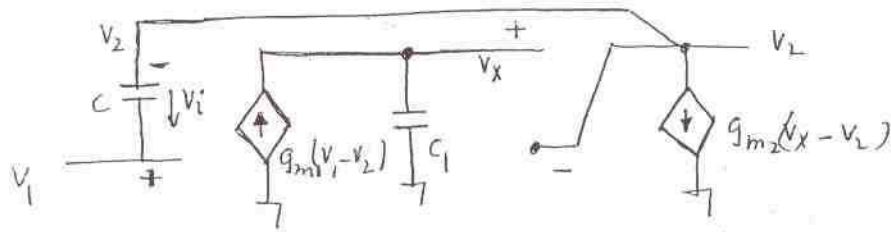5.37

Ideal OTA case ( $C_i, C_o \rightarrow 0, R_o \rightarrow \infty$ )



$$-sC_2(V_1 - V_2) + g_{m2}(V_x - V_2) = 0 \quad ; \quad V_x = g_{m1}(V_1 - V_2) \frac{1}{sC_1}$$

$$g_{m2} \cdot g_{m1} \cdot \frac{1}{sC_1} (V_1 - V_2) = sC_2(V_1 - V_2) + g_{m2}V_2$$

$$\left( -\frac{g_{m1}g_{m2}}{sC_1} + sC_2 - g_{m2} \right) V_2 = \left( sC_2 - \frac{g_{m1}g_{m2}}{sC_1} \right) V_1$$

537  
Contd.

non ideal OTA, low frequency

$$\Delta = sC_2 \left[ G_{o2} - g_{m2} + s(C_2 + C_{o2}) \right] \left[ G_{o1} + s(C_1 + C_{o1}) \right] - g_{m1} g_{m2}$$

$$+ sC_2 \left[ -sC_2 (G_{o1} + s(C_1 + C_{o1})) \right]$$

$$- g_{m1} \left[ -sC_2 \cdot g_{m2} \right]$$

$$V_2 = \frac{1}{\Delta} \cdot \begin{vmatrix} sC_2 & I_1 & 0 \\ -sC_2 & 0 & g_{m2} \\ -g_{m1} & 0 & sC_1 + sC_1 + G_{o1} \end{vmatrix} ; V_1 = \frac{1}{\Delta} \cdot \begin{vmatrix} I_1 & -sC_2 & 0 \\ 0 & G_{o2} + sC_2 & g_{m2} \\ 0 & sC_2 - g_{m2} & sC_1 + sC_1 + G_{o1} \end{vmatrix}$$

$$\frac{V_2}{V_1} = \frac{A_1}{A_2}$$

$$A_1 = sC_2 \cdot 0 + sC_2 \cdot I_1 \cdot (sC_1 + sC_1 + G_{o1}) - g_{m1} \cdot I_1 \cdot g_{m2}$$

$$= I_1 \left[ -g_{m1} g_{m2} + sC_2 G_{o1} + s^2 (C_2 C_1 + C_2 C_1) \right]$$

$$A_2 = I_1 \cdot \left[ (G_{o2} + sC_2 + sC_2 - g_{m2}) (sC_1 + sC_1 + G_{o1}) - g_{m1} g_{m2} \right]$$

$$= I_1 \cdot \left[ s^2 (C_1 C_2 + C_2 C_1 + C_2 C_1 + C_2 C_1) + s (G_{o2} C_1 + G_{o1} C_2 + C_2 G_{o1} - C_1 g_{m2} - C_1 g_{m2}) + G_{o1} G_{o2} - g_{m2} G_{o1} - g_{m1} g_{m2} \right]$$


$$\text{Thus } \frac{V_2}{V_1} = \frac{s^2 (C_2 C_1 + C_2 C_1) + s C_2 G_{o1} - g_{m1} g_{m2}}{s^2 (C_1 C_2 + C_2 C_1 + C_2 C_1 + C_2 C_1) + s (G_{o2} C_1 + G_{o1} C_2 + C_2 G_{o1} - C_1 g_{m2} - C_1 g_{m2}) + G_{o1} G_{o2} - g_{m2} G_{o1} - g_{m1} g_{m2}}$$

which is of the form:  $\frac{A_1 s^2 + B_1 s + C_1}{A_2 s^2 + B_2 s + C_2}$

It is no longer a notch filter function, since  $B_1 \neq 0$



5.38

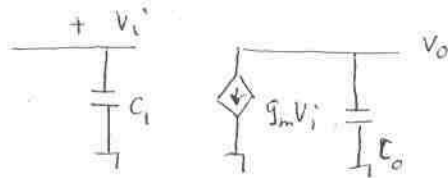

$$V_o = -\frac{g_m V_i}{s C_o} = -\frac{g_m}{s C_o} V_i$$

Unity gain @  $\omega C_o = g_m$ ,  $\omega = \frac{g_m}{C_o}$

$$\omega = \frac{250 \times 10^6}{0.99 \times 10^{-12}} \rightarrow 1315.789 \times 10^6 \rightarrow 209.414 \text{ MHz}$$

For  $f_u \rightarrow 9 \text{ MHz}$ , let  $C_L$  be the load cap.

Then  $\omega = 2\pi \times 9 \times 10^6 = \frac{g_m}{C + C_L}$ ;  $C + C_L = \frac{250 \times 10^6}{2\pi \times 9 \times 10^6} = \frac{250}{18\pi} \text{ pF}$

(a)  $C_L = \frac{250}{18\pi} - 0.119 \text{ pF} = 4.23 \text{ pF}$

(b) For DC gain of 7 dB? DC gain is  $= -g_m R_L$  for a load  $R_L$

So  $|-g_m R_L| > 7 \text{ dB} \rightarrow 10^{3.5} R_L > \frac{10^{3.5}}{250 \times 10^6} \rightarrow 12649110.64 \rightarrow 12.65 \text{ M}\Omega$


So  $R_o > 12.65 \text{ M}\Omega$

Simulation ?  $\rightarrow$  Left as an exercise.

5.39




(b)  $R_{sim}$  (floating)

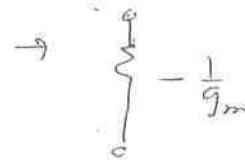

We need to arrange

for a grounded inductor

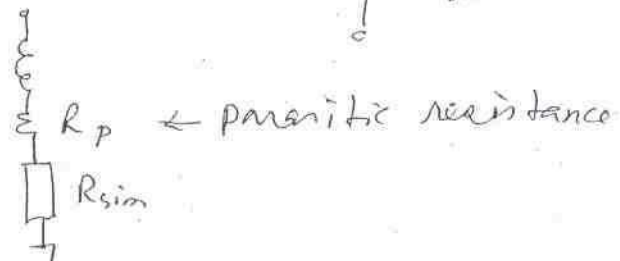


So to make  $R_{tot} = 0$

$$R_p + R_{sim} = 0$$

$$-R_{sim} = R_p = \frac{1}{g_m}; \quad g_m = \frac{1}{R_p} = \frac{1}{250}$$

Required  $g_m \rightarrow 4 \text{ milli mho}$

5.40

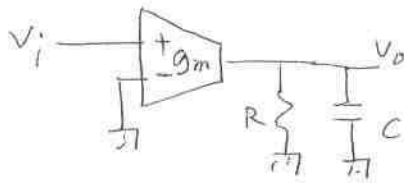

$$V_o = g_m V_i \cdot \frac{\frac{1}{sC} R}{R + \frac{1}{sC}}$$
$$= g_m V_i \frac{R}{1 + sCR} = \frac{g_m R}{CR} \cdot \frac{1}{s + 1/CR} V_i$$

So  $T_1(s) = \frac{g_m}{C} \cdot \frac{1}{s + 1/CR}$  ; DC gain =  $g_m R = 70 \text{ dB}$   
 $\Rightarrow 3162.28$

So  $R = \frac{3162.28}{250 \times 10^6} = 12649110.6 \Omega \approx 12.65 \text{ M}\Omega$

For unity gain frequency  $|j\omega| \gg 1/CR$ , so

$$T_1(s) \approx \frac{g_m}{C} \frac{1}{s} \quad ; \quad |T_1(s)| = 1 = \frac{g_m}{|j\omega C \omega|} ; \quad \omega_u = \frac{g_m}{C} = 2\pi \times 10^7$$

So  $C = \frac{g_m}{2\pi \times 10^7} = \frac{250 \times 10^{-13}}{2\pi} = 3.978 \text{ pF}$

$R = 12.65 \text{ M}\Omega ; C = 3.978 \text{ pF}$

---



5.41

(a) MEM approximation, 3rd order: For  $\omega_c = 1 \text{ rad/sec}$ ,  $A_p = 3 \text{ dB}$   
 1st - BUT filter



$$H_N(s) = \frac{K}{s^3 + 2s^2 + 2s + 1} = \frac{K_1}{(s+1)} \cdot \frac{K_2}{(s^2 + s + 1)}$$

$K_1 K_2 = \text{dc gain} = 30$

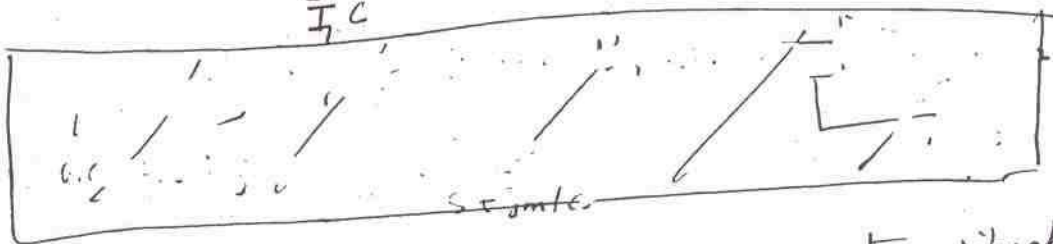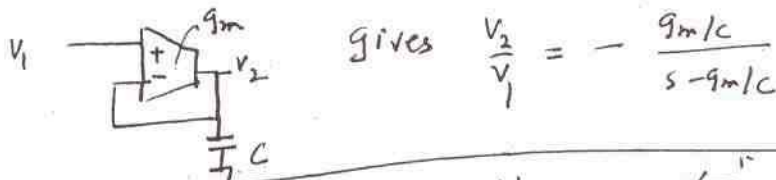The first order section can be obtained by a network similar to those shown in problem 4.27. Thus



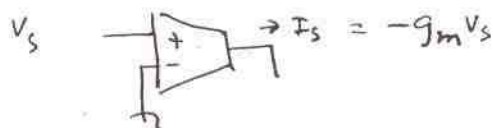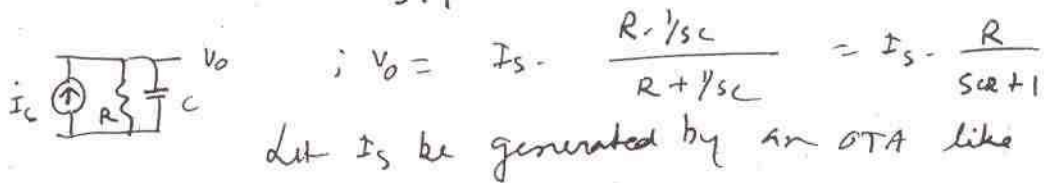
To obtain a T.F.  $\sim \frac{K_1}{s+1}$ , consider the situation



and the 'R' be generated by another OTA like:



Then  $V_1$  will be equivalent to

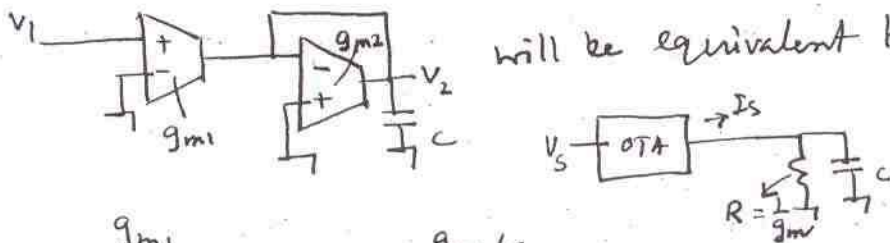

$$\frac{V_2}{V_1} = -\frac{g_{m1}}{g_{m2} + sC} \rightarrow -\frac{g_{m1}/c}{g_{m2}/c + s}$$


5.41  
Contd. (a)

Let  $g_{m1}/C = K_1$   
 $g_{m2}/C = 1$

by assuming  $C = 1$ ,  $g_{m2} = 1$   
 $g_{m1} = K_1$

Then we get


$$\frac{V_2}{V_1} = -\frac{K_1}{s+1}$$

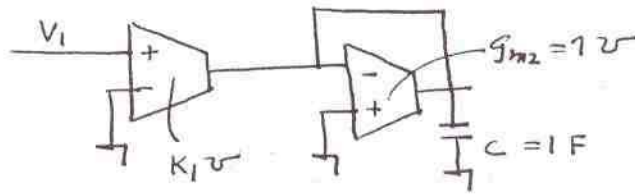

FIRST ORDER NETWORK

For the second order network with a TF.

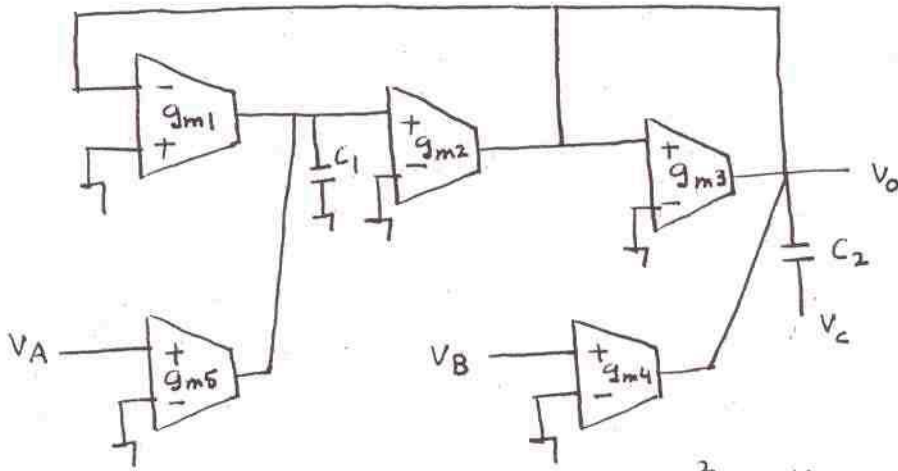$\sim \frac{K_2}{s^2 + s + 1}$ , we can take the universal form of L.P.F., i.e. (see Fig. 21)



SECOND ORDER NETWORK

$$V_0 = \frac{g_{m2}g_{m5} V_A + s g_{m4} C_1 V_B + s^2 C_1 C_2 V_C}{s^2 C_1 C_2 + s g_{m3} C_1 + g_{m1} g_{m2}}$$

With  $V_B, V_C \rightarrow 0$  i.e.  $g_{m4}$  -OTA absent  $\frac{V_0}{V_A}$  will have the form of a L.P.F.

$$\frac{g_{m2} g_{m5} / C_1 C_2}{s^2 + s \frac{g_{m3}}{C_2} + \frac{g_{m1} g_{m2}}{C_1 C_2}}$$

Let  $g_{m1} = g_{m2} = 1 \text{ } \Omega$   
 $C_1 = C_2 = 1 \text{ F}$ , and  $g_{m5} = K_2 \text{ } \Omega$   
 $g_{m3} = 1 \text{ } \Omega$

That will produce

$$\frac{V_0}{V_A} = \frac{K_2}{s^2 + s + 1}$$

Assume  $K_1 = K_2 = \sqrt{30}$   
 $= 5.48$

5.41 (B)

$n_{CHEB} = 3$

$\epsilon = 0.2674$

Roots of  $D(s)$  are:

k	$\sigma_k$	$\omega_k$
0	0.3646	1.0719
1	0.7293	$\sim 0$
2	-0.3646	-1.0719
3	-0.3646	-1.0719
4	-0.7293	$\sim 0$
5	-0.3646	1.0719

For realizable filter, take  $\sigma_k$  with negative values

$$D(s) = (s + 0.7293)(s + 0.3646 + j1.0719)(s + 0.3646 - j1.0719)$$



$$= (s + 0.7293)([s + 0.3646]^2 + 1.0719^2)$$

$$= (s + 0.7293)(s^2 + 0.7292s + 1.2819)$$

$H_N(s) = \frac{1}{\frac{3-1}{2}\epsilon} \cdot \frac{1}{s}$

$$H_N(s) = \frac{0.9349}{(s + 0.7293)(s^2 + 0.7292s + 1.2819)}$$
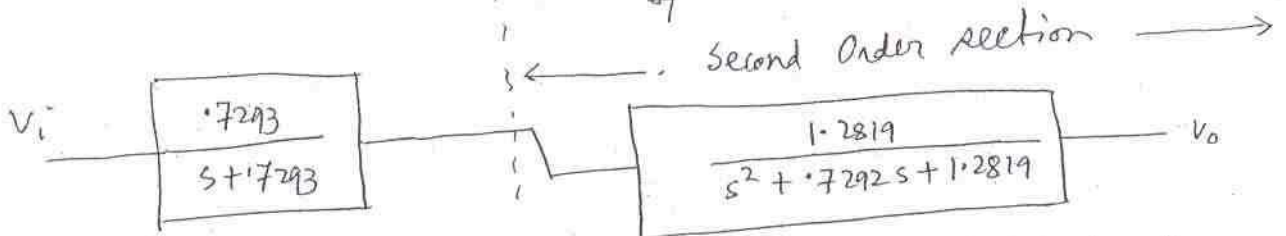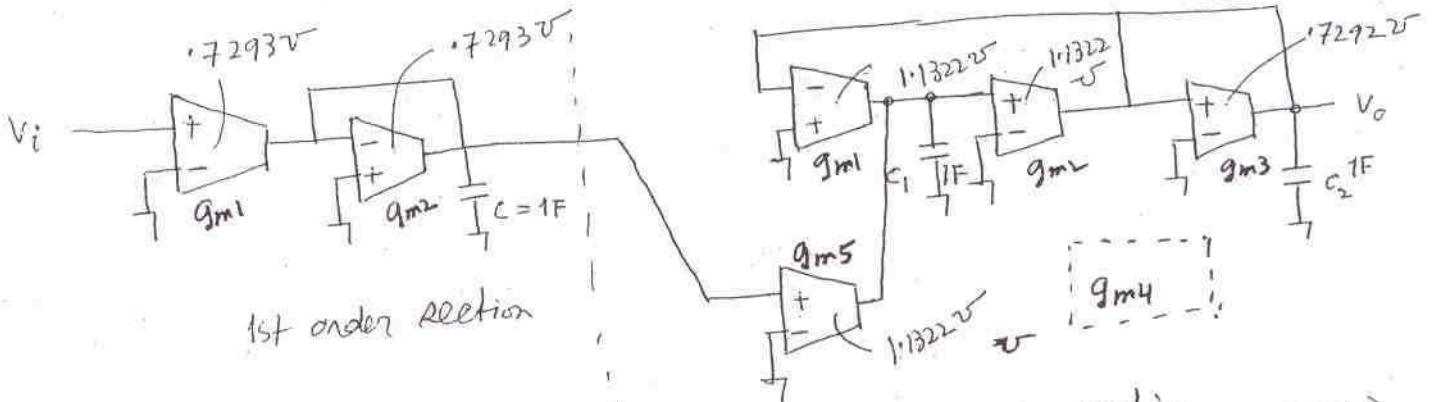
$$= \frac{0.7293}{s + 0.7293} \cdot \frac{1.2819}{s^2 + 0.7292s + 1.2819}$$



The above represents the design of the normalized 3rd order CHEB LPF.

To frequency denormalize, use the scaling of  $10^7 \times 2\pi$   
 Make all  $C = 10^{-7} F = 0.1 \mu F / 2\pi = 0.016 \mu F$



5.41  
 (C)

For  $A_p = 1$  dB,  $\epsilon = 0.5089$ , For  $n = 7$ , the normalized LPF transfer function is:

$$H_N(s) = \frac{1}{2^6 \epsilon} \cdot \frac{1}{(s + 2.054)(s^2 + 0.914s + 0.9927)(s^2 + 2.562s + 6.535)(s^2 + 3.702s + 2.304)}$$

$$= \frac{0.2054}{s + 2.054} \cdot \frac{0.9927}{s^2 + 0.914s + 0.9927} \cdot \frac{6.535}{s^2 + 2.562s + 6.535} \cdot \frac{2.304}{s^2 + 3.702s + 2.304}$$


The denormalized HPF transfer function will be  $(s \rightarrow \omega_p/s)$ ,  $\omega_p = 2\pi \times 15 \times 10^6$

$$H(s) \Big|_{HP} = \frac{s}{s + 458.84495 \times 10^6} \cdot \frac{s^2}{s^2 + 8.6776 \times 10^6 s + 8.94796 \times 10^{15}}$$

$$\frac{s^2}{s^2 + 36.94917 \times 10^6 s + 13.59242 \times 10^{15}} \cdot \frac{s^2}{s^2 + 151.43458 \times 10^6 s + 38.55314 \times 10^{15}}$$

Compare the second order coefficients with the network (figure 21 of notes on ch 4):
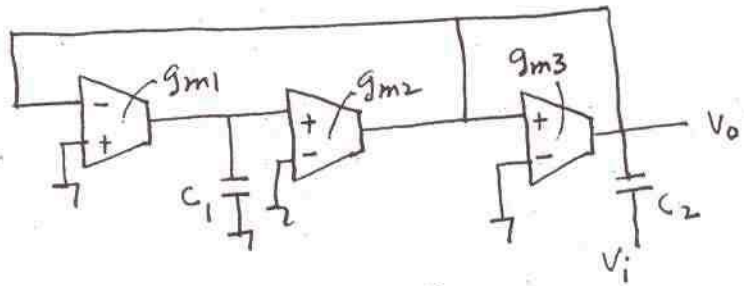
$$\frac{V_o}{V_i} = \frac{s^2}{s^2 + \frac{g_{m3}}{C_2} s + \frac{g_{m1} g_{m2}}{C_1 C_2}} \quad \text{with } V_A = 0, V_B = 0, V_C = V_i$$



Let  $C_1 = C_2 = 1$  nF each.



Then  $8.6776 \times 10^6 \rightarrow \frac{g_{m3}}{C_2}$  gives  $g_{m3} = 8.6776 \text{ mS}$

$8.94796 \times 10^{15} \rightarrow \frac{g_{m1} g_{m2}}{C_1 C_2}$  gives  $g_{m1} g_{m2} = 8.94796 \times 10^{-3}$

i.e.  $g_{m1} = g_{m2}$  (assume) =  $94.594 \text{ mS}$


5.41

C = 1nF in each section

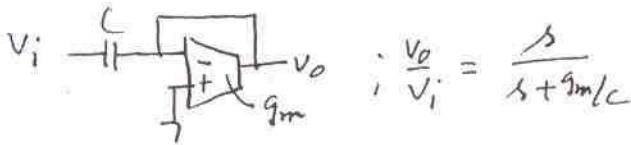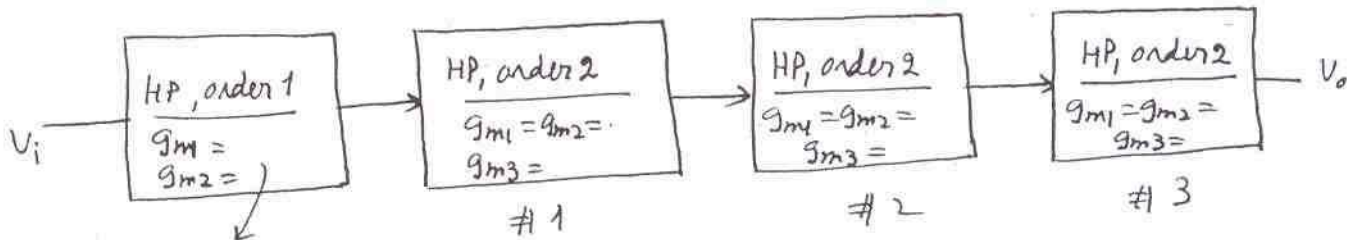

Section	gm1	gm2	gm3	gm4	gm5
First order HP	458.85 mS	-	-	-	-
HP Second order #1	94.594 mS	94.594 mS	8.6776 mS	-	-
HP Second order #2	116.59 mS	116.59 mS	36.9492 mS	-	-
HP Second order #3	196.35 mS	196.35 mS	151.4346 mS	-	-

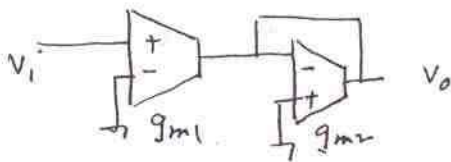An additional gain stage can be added to make up the required flat gain. Thus a network




will provide a voltage gain (or attenuation) of  $\left| \frac{gm_1}{gm_2} \right|$ .

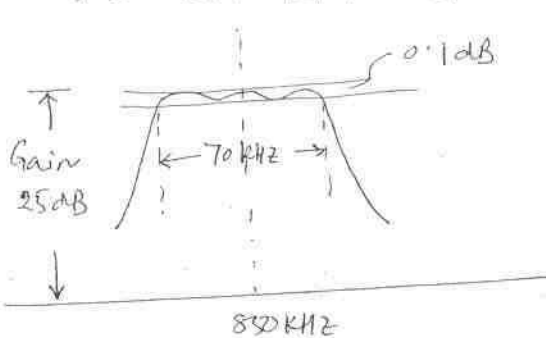5.91

Fifth order BPF implies an associated normalized LPF of order 5. (BPF is an even function characteristic, it can never be 5, 7, 9... order!)

So we have to start-off from a 5th order LPF transfer function.



$$\begin{aligned}\omega_c \omega_{cr} &= 2\pi \times 850 \times 10^3 \\ \omega_c &= 35 \times 10^3 \times 2\pi \\ B &= 70 \times 2\pi \times 10^3 \\ \omega_0 &= 2\pi \times 850 \times 10^3\end{aligned}$$

$$H_N(s) = \frac{1}{2^4 \cdot \epsilon} \cdot \frac{1}{D(s)}$$

where  $\epsilon = 0.1526$  and

roots of  $D(s) = 0$  are as:

only the ones with neg. real roots are shown in the table on left.

k	$\sigma_k$	$\omega_k$
0	-	-
1	-	-
2	-	-
3	-	-
4	-	-
5	-0.1665	-1.0804
6	-0.4359	-0.6677
7	-0.5389	0
8	-0.4359	0.6677
9	-0.1665	1.0804

$$\begin{aligned}D(s) &= (s + 0.5389) \\ &\quad \left[ (s + 0.1665)^2 + 1.0804^2 \right] \\ &\quad \left[ (s + 0.4359)^2 + 0.6677^2 \right] \\ &= (s + 0.5389)(s^2 + 0.3336s + 1.19499) \\ &\quad (s^2 + 0.8718s + 0.6358321)\end{aligned}$$

Then

$$H_N(s) \Big|_{LP} = \frac{0.5389}{s + 0.5389} \cdot \frac{1.19499}{s^2 + 0.3336s + 1.19499} \cdot \frac{0.63583}{s^2 + 0.8718s + 0.63583}$$

$T_1$                        $T_2$                        $T_3$

On using the algorithm and MATLAB program pertaining to LP  $\leftrightarrow$  BP transformation we shall have

$T_1 \rightarrow$  a second order TF.

$T_2 \rightarrow$  two second order TF in cascade

$T_3 \rightarrow$  two second order TF in cascade

5.4 / Thurs

$$T_1 \rightarrow \frac{2.3702 \times 10^5 \cdot s}{s^2 + 2.3702 \times 10^5 s + 2.8523 \times 10^{13}} = T_{1B}$$


$$T_2 \rightarrow \frac{4.808 \times 10^5 s}{s^2 + 6.9176 \times 10^4 s + 2.6096 \times 10^{13}} \cdot \frac{4.808 \times 10^5 s}{s^2 + 7.6485 \times 10^4 s + 3.1176 \times 10^{13}}$$

$T_{21}$        $Q_p = 73.0022$        $T_{22}$

$$T_3 \rightarrow \frac{3.5071 \times 10^5 s}{s^2 + 1.8645 \times 10^5 s + 2.6997 \times 10^{13}} \cdot \frac{3.5071 \times 10^5 s}{s^2 + 1.9699 \times 10^5 s + 3.0136 \times 10^{13}}$$

$T_{31}$        $Q_p = 27.8675$        $T_{32}$

For each second order, use the network:

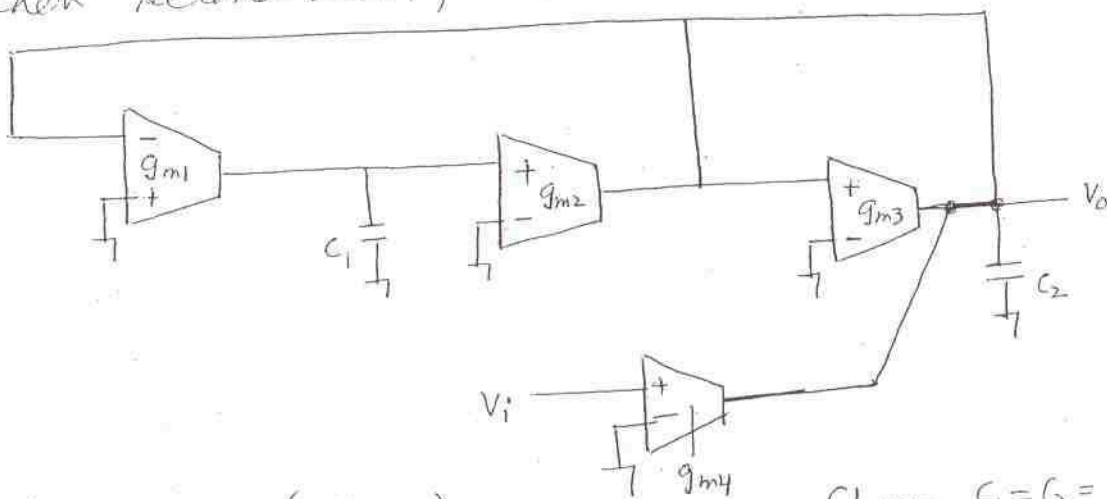

$$\frac{V_0}{V_i} = - \frac{(g_{m4}/C_2) s}{s^2 + \frac{g_{m3}}{C_2} s + \frac{g_{m1}g_{m2}}{C_1 C_2}}$$

Choose  $C_1 = C_2 = 1 \text{ nF}$  (say)

Then  $g_{m3} = 10^9 \times \left(\frac{\omega_p}{Q_p}\right)$

Let  $g_{m4} = g_{m2}$

$$\text{Then } g_{m4} = g_{m2} = \omega_p \times 10^9$$

Further  $\frac{g_{m4} s}{C_2} \rightarrow$  HoS in the numerator.

$$\text{So } g_{m4} = H_0 \times 10^9$$

Design the FIVE BPF sections and put in cascade using a VCVS as interface between adjacent signal sections.




5.41  
e

Since 'k' is not specified, assume  $k = 16.9$ .  
Then the three sections to cascade is:

$$\frac{16.9}{s + 16.9} \cdot \frac{s^2 + 29.2^2}{s^2 + 19.4s + 20.01^2} \cdot \frac{s^2 + 43.2^2}{s^2 + 4.72s + 22.52^2} \quad \Delta \text{ in Mrad/sec.}$$

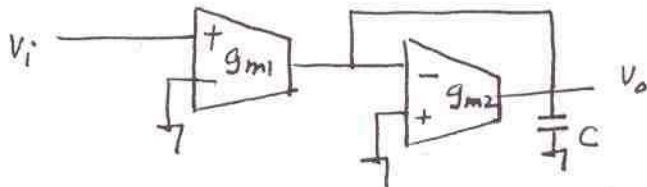For the first order LP section, use the network:




With  $C = 1F$

$$g_{m2} = 16.9 \text{ v} \leftarrow \frac{g_{m2}}{C}$$

$$g_{m1} = 16.9 \text{ v} \leftarrow \frac{g_{m1}}{C}$$

For the second order notch section use:

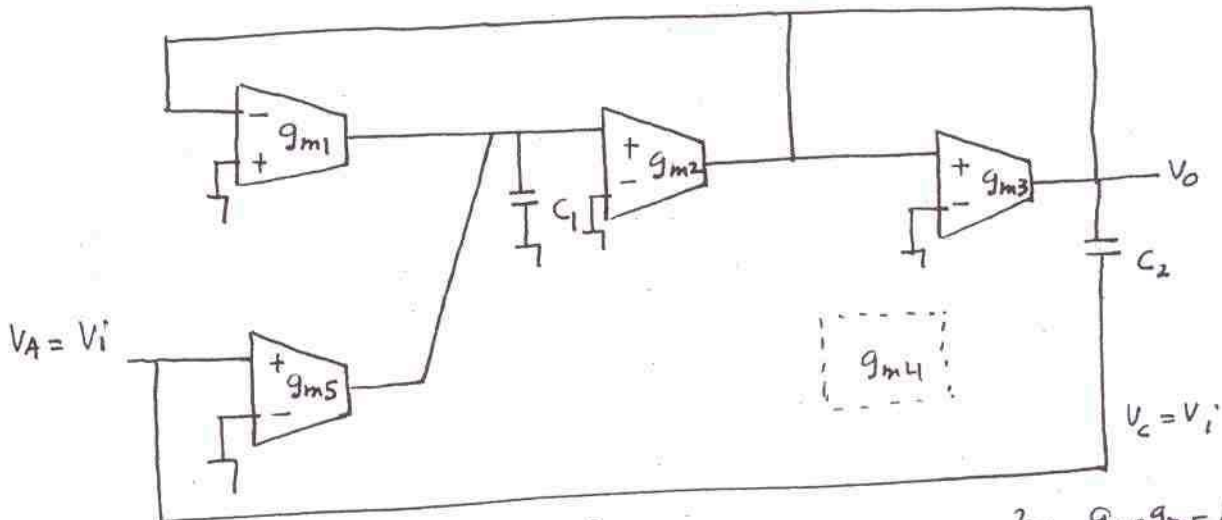

$$\frac{V_o}{V_i} = \frac{g_{m2}g_{m5} + s^2 C_1 C_2}{s^2 C_1 C_2 + g_{m3} C_1 s + g_{m1}g_{m2}} = \frac{s^2 + g_{m2}g_{m5}/C_1 C_2}{s^2 + s \frac{g_{m3}}{C_2} + \frac{g_{m1}g_{m2}}{C_1 C_2}}$$

Let  $C_1 = C_2 = C = 1F$ ;  $g_{m1} = g_{m2} = g_m$ ;  $g_{m5} = \frac{\omega_z^2 \cdot C^2}{g_{m2}} \rightarrow \frac{\omega_z^2}{g_{m2}}$

$g_m = \omega_p C$ ;  $g_{m3} = \left(\frac{\omega_p}{\omega_z}\right) C \rightarrow \frac{\omega_p}{\omega_z}$  ( $\because C = 1$  assumed)

$\rightarrow \omega_p$

network	$g_{m1}$	$g_{m2}$	$g_{m3}$	$g_{m4}$	$g_{m5}$
LP	16.9 v	16.9 v	-	-	-
Notch #1	20.1 v	20.1 v	19.4 v	-	42.42 v
Notch #2	22.52 v	22.52 v	4.72 v	-	82.87 v

Follow methods  
as in  
previous  
problems




5.42

$$H(s) = H_1(s) H_2(s) H_3(s)$$

$$= \frac{K}{s+16.9} \cdot \frac{s^2 + 29.2}{s^2 + 19.4s + 201.2} \cdot \frac{s^2 + 43.2}{s^2 + 4.72s + 22.52}$$

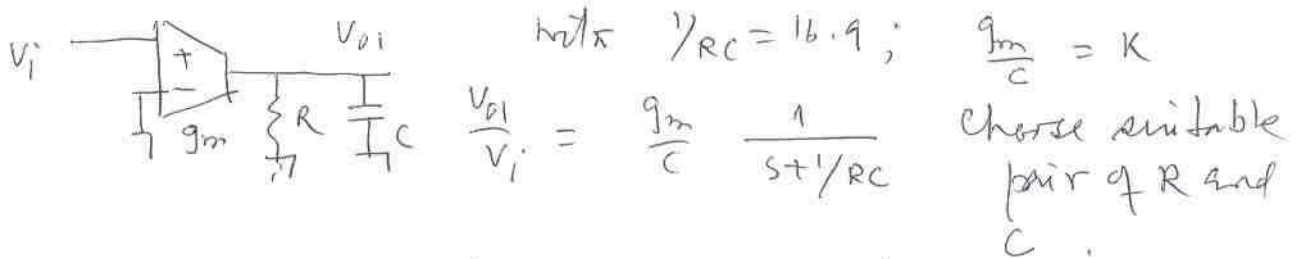For the first order section we can use (as in P5.40)



For the second order sections we can use the universal structure as in Fig 5.19 (a). Then

$$V_o = \frac{1}{D(s)} \cdot \left[ s^2 V_c + (g_{m3}/C_2) s V_B + \frac{g_{m2} g_{m5}}{C_1 C_2} V_A \right]$$

with  $D(s) = s^2 + (g_{m3}/C_2) s + g_{m1} g_{m2} / C_1 C_2$

Let  $V_B = 0$  and  $V_A = V_c$ .

Then  $H_2(s) = \frac{1}{D(s)} \left[ \frac{s^2 + g_{m2} g_{m5} / C_1 C_2}{s^2 + (g_{m3}/C_2) s + g_{m1} g_{m2} / C_1 C_2} \right] = \frac{V_o}{V_c}$

Thus

$H_2$	$H_3$
$\frac{g_{m2} g_{m5}}{C_1 C_2} = 29.2$	$\frac{g_{m2} g_{m5}}{C_1 C_2} = 43.2$
$\frac{g_{m3}}{C_2} = 19.4$	$\frac{g_{m3}}{C_2} = 4.72$
$\frac{g_{m1} g_{m2}}{C_1 C_2} = 201.2$	$\frac{g_{m1} g_{m2}}{C_1 C_2} = 22.52$

Choose  $g_{m1}, g_{m2}, \dots, g_{m5}, C_1, C_2$  suitably.

\* note: While simulating the filter, insert a unit gain voltage buffer circuit as an interstage between two OTA-stages. This is to ensure that each OTA-block receives the input signal from a voltage source.