

Winter 08-09

1/9 ✓

Q1:  $0.707 \text{ nH} \rightarrow 707 \text{ nH}$  involves a scaling by 1000.

So impedance scaling by 1000 has been done.

This takes  $C = 1 \text{ F} \rightarrow \frac{1}{1000} = 1 \text{ mF}$  ~~so scaling voltage~~

But final  $C$  is  $0.1 \text{ mF} = 10^{-7} \text{ F}$

So ' $C$ ' has been further scaled by  $10^7 / 10^{-3} = 10^4$

Scaling on ' $C$ ' alone implies frequency scaling.

Frequency scaling ' $s$ ' by ' $a$ '  $\rightarrow s/a$

makes  $s_{\text{new}} = a \cdot s_{\text{old}}$

This scales  $C$  as  $C_{\text{new}} = C_{\text{old}} / a \rightarrow C_{\text{old}} / 10^4$

Thus  $s_{\text{new}} = 10^4 \cdot s_{\text{old}}$

Hence  $T_1(s) \rightarrow T_1'(s)$  <sup>remains</sup> same due to impedance scaling

$T_1'(s) \rightarrow T_1''(s) \Big| s \rightarrow s/a$  due to frequency scaling

$$T_1(s) \Big|_{\text{new}} = \frac{s^2}{s^2 + \sqrt{2}s + 1} \Big|_{s \rightarrow s/10^4} = \frac{\frac{s^2}{10^8}}{\frac{s^2}{10^8} + \sqrt{2} \frac{s}{10^4} + 1}$$

$\downarrow$   $T_2(s) = \frac{2 \times 10^8}{s^2 + \sqrt{2} 10^4 s + 10^8}$

$$T_2(s) = \frac{2 \times 10^8}{s^2 + \sqrt{2} 10^4 s + 10^8}$$

Q2:

$$\omega_{a_1} = 4300 \text{ rad/sec}, \omega_{a_2} = 6000 \text{ rad/sec}$$

$$\omega_{p_1} = 3500 \text{ rad/sec}, \omega_{p_2} = 7000 \text{ rad/sec}$$

$$\text{Band-stop filter, so } \omega_s = \frac{\omega_{p_2} - \omega_{p_1}}{\omega_{a_2} - \omega_{a_1}} = \frac{3500}{1700}$$

$$\omega_s = 2.059$$

Pass-band has ripple  $\rightarrow$  CHEB feature.

$$\text{So we calculate } D = \frac{10^{-1} \times 40}{10^{-1} \times 5} = 81946.6$$

$$10^{-1} \times 5 - 1 \approx 81947$$

$$\sqrt{D} = 286.26$$

$$\text{Then } \frac{\cosh^{-1} \sqrt{D}}{\cosh^{-1} \omega_s} = 4.702 \rightarrow \text{order of assoc. normalized LP filter}$$

Take  $n = 5$  for the normalized LPF.

We consult table to get

$$H_N(s) = \frac{1}{2^{5-1}} \cdot \frac{1}{D(s)}$$

$$\text{where } \epsilon = \sqrt[10]{10^{-1}} = 0.3493$$

$$H_N(s) = \frac{0.1789}{s^5 + 1.1725s^4 + 1.9374s^3 + 1.3096s^2 + 0.7525s + 0.1789}$$

To synthesize the frequency denormalized BSF, we need to use the frequency transformation

$$s \rightarrow \frac{\beta}{\omega_0} \cdot \left[ \frac{1}{\frac{s}{\omega_0} + \frac{\omega_0}{s}} \right]$$

$$\text{where } \beta = \omega_{a_2} - \omega_{a_1} = 1700 \text{ rad/sec}$$

$$\omega_0^2 = \omega_{a_1} \omega_{a_2} = 4300 \times 6000 \text{ rad}^2/\text{sec}^2$$


$$\omega_0 = 5079.37 \text{ rad/sec.}$$

Q. 3.

Given  $H(s) = T_N(s) = \frac{19825}{s^2 + 1.098s + 1.103}$
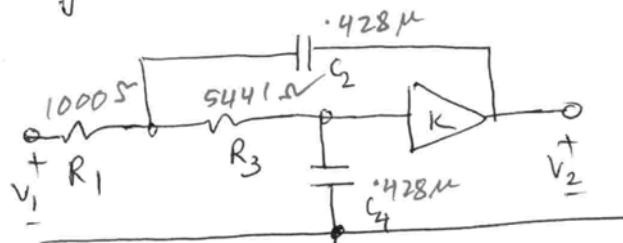
### Finite Gain SAB (FGSAB - S&K) design

The given TF. is a LPF. So we consider the circuit



The network TF. is:

$$\frac{K / R_1 R_3 C_2 C_4}{s^2 + s \left( \frac{1}{R_3 C_4} + \frac{1}{R_1 C_2} + \frac{1}{R_3 C_2} - K / R_3 C_4 \right) + \frac{1}{R_1 R_3 C_2 C_4}}$$

The above TF. has a DC gain of  $K = 5$ .  
We set  $K = 5$  as required in Q.4.  
Then by comparing with the theoretical function

$$T_{LP}(s) = \frac{K \omega_p^2}{s^2 + \frac{\omega_p}{\alpha_p} s + \omega_p^2}$$

$$\text{we can see } \frac{1}{R_1 R_3 C_2 C_4} = \omega_p^2 = 1.103$$

$$\frac{1}{R_3 C_4} + \frac{1}{R_1 C_2} + \frac{1}{R_3 C_2} - 5 / G R_3 = \frac{\omega_p}{\alpha_p} = 1.098$$

$$\text{let } C_2 = C_4 = C = 1 \text{ F}$$

$$\text{Then } \frac{1}{R_1 R_3} = 1.103 ; \quad \frac{1}{R_1} - \frac{3}{R_3} = 1.098$$

Q3:

$$R_3 - 3R_1 = 1.098 \quad R_1 R_3 = \frac{1.098}{1.103} = 0.995$$

4/9

$$R_3 = 3R_1 + 0.995$$

Subst. back in  $\frac{1}{R_1 R_3} = 1.103$

$$R_1 \cdot (3R_1 + 0.995) = \frac{1}{1.103} = 0.9066$$

$$3R_1^2 + 0.995R_1 - 0.9066 = 0$$

$$R_1 = \frac{-0.995 \pm \sqrt{0.995^2 + 4 \times 0.9066 \times 3}}{2 \times 3}$$

acceptable  $\Rightarrow$   
positive value

$$\frac{-0.995 + 3.445}{6} = 0.408$$

$$3 \times 0.408 + 0.995 = 2.22$$

$$\text{Then } R_3 = \frac{3 \times 0.408 + 0.995}{2.22} = 3.215$$

First int design values

$$C_3 = C_4 = C = 1F$$

satisfies

$$R_1 = 0.408 \Omega$$

$$R_3 = 3.215 \Omega$$

$$\frac{\omega_p}{\omega_n} = 1.098$$

$$\omega_n^2 = 1.103$$

Actual  $\omega_p = 1000 \text{ rad/sec}$ .

So we need to scale frequency by  $\frac{1000}{\sqrt{1.103}} = 952.165$

This will alter  $C \rightarrow \frac{1}{952.165} \approx 1.05 \text{ mF}$ .

Second int design:  $R_1 = 408 \Omega \quad C_2 = C_3 = 1.05 \text{ mF}$

$$R_3 = 2.22 \Omega$$

To make  $R_1 \rightarrow 1000 \Omega$ , impedance scale by 2450.98

Then


Q3 Then, the final design values come

59

$$R_1 = 1000 \Omega ; R_3 = 5441.18 \Omega$$


$$C_2 = C_4 = C = \frac{1.05 \text{ mF}}{2450.98} = 0.428 \text{ mF}$$

$K = 5$  is obtained using an OA as:

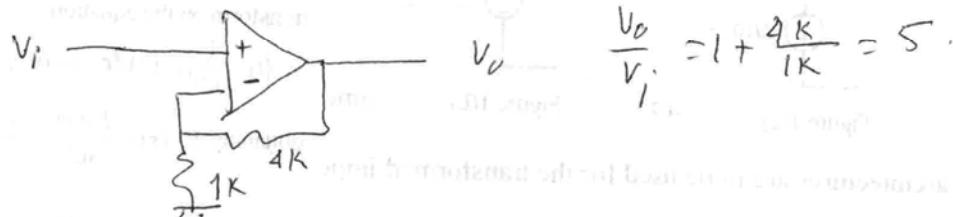

Q3: IG - SAB design  $\rightarrow$  IG  $\rightarrow$  Infinite gain

Now consider the circuit (LPF)

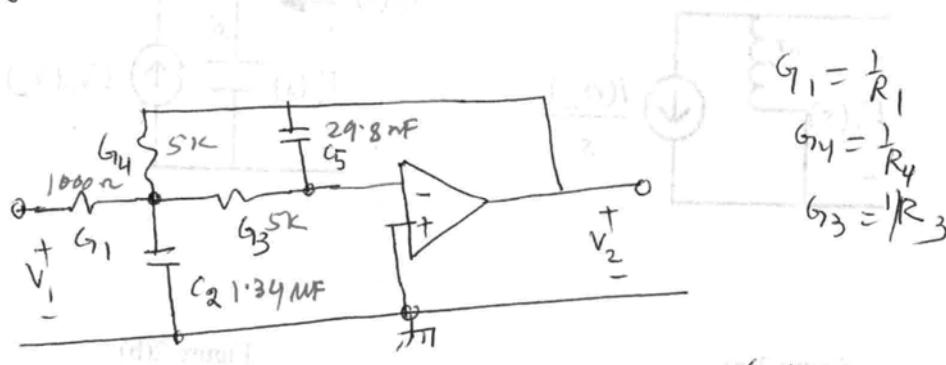

The network TF. is:

$$H(s) = \frac{-G_1 G_3}{s^2 C_2 C_5 + s C_2 C_5 (G_1 + G_3 + G_4) + G_3 G_4}$$

The associated theoretical TF. is:

$$H(s) = \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q} s + \omega_p^2}$$

We re-write the network TF. as:

$$H(s) = \frac{-G_1 G_3 / C_2 C_5}{s^2 + \left( \frac{G_1}{C_2} + \frac{G_3}{C_2} + \frac{G_4}{C_2} \right) s + \frac{G_3 G_4}{C_2 C_5}}$$

## ~~Q3.~~ (1G-SAB design contd.)

Comparing with theoretical TF.

$$\frac{G_1 G_3}{G_2 G_5} = H$$

$$\frac{G_1}{C_2} + \frac{G_3}{C_2} + \frac{G_4}{C_2} = \frac{\omega_p}{\alpha_p}$$

$$\frac{G_3 G_4}{G_2 C_5} = \omega_p^2$$

$$\text{DC gain } \frac{G_1 G_3}{G_3 G_4} = \frac{G_1}{G_4} = \frac{H}{\omega_p^2} = 5 \text{ required}$$

$$\therefore G_1 = 5 G_4 \quad \text{and} \quad H = 5 \omega_p^2$$

Suggested design eqns are:

$$G_1 = \frac{H}{\omega_p} ; \quad C_2 = \frac{\alpha_p}{\omega_p^2} (2\omega_p^2 + H) ; \quad G_3 = \omega_p$$

$$G_4 = G_3 ; \quad C_5 = \frac{\omega_p}{\alpha_p (2\omega_p^2 + H)} = \frac{1}{C_2}$$

In the given TF.

$$\omega_p^2 = 1.103 ; \quad \text{So } H = 5 \times 1.103 = 5.515$$

$$\omega_p = \sqrt{1.103} = 1.05$$

$$G_1 = \frac{5 \omega_p^2}{\omega_p} = 5 \omega_p = 5 \times 1.05 = 5.25 \text{ V}$$

$$G_3 = 1.05 \text{ V} = G_4 ; \quad C_2 = \frac{\alpha_p}{\omega_p} \left( \omega_p + \frac{H}{\omega_p} \right)$$

$$C_2 = \frac{1}{1.098} \left( 1.05 \times 2 + \frac{5.515}{1.05} \right) \quad \because \frac{\omega_p}{\alpha_p} = 1.098 \text{ in the given TF. (coeff. of } F \text{ is term in D(s))}.$$

$$= 6.696 F$$

$$C_5 = 1/C_2 = 0.149 F$$

First cut design values are:

$$G_1 = 5.25 \text{ V} \rightarrow 0.1905 \Omega$$

$$G_3 = G_4 = 1.05 \text{ V} \rightarrow 0.9524 \Omega$$

$$C_2 = \frac{0.07425}{6.696 F} = 0.007425 \text{ F}$$

$$C_5 = \frac{0.07425 \times 0.007425}{0.149} \text{ verified} \left\{ \begin{array}{l} \omega_p^2 = 1.103 \\ \frac{\omega_p}{\omega_p} = 1.098 \end{array} \right.$$

$R_1$  is lowest valued resistance

To make it  $1000 \Omega$ , impedance scale by  $\frac{1000}{0.1905}$

$$= 5249.34$$

$$\text{So, } R_1 = 0.1905 \Omega \rightarrow 1000 \Omega$$

$$R_3 = R_4 = 0.9524 \Omega \rightarrow 4999.47 \approx 5000 \Omega$$

$$C_2 = \frac{6.696 F}{5249.34} = 1.2756 \text{ mF}^{-5}$$

$$C_5 = \frac{0.149}{5249.34} = 2.8384 \times 10^{-5} \text{ mF}^{-5}$$

$$C_5 = \frac{0.149}{5249.34} = 2.8384 \text{ mF}^{-5}$$

The above is for  $\omega_p = 1.05 \text{ rad/sec}$

To achieve  $\omega_p = 1000 \text{ rad/sec}$ , we

frequency scale by  $\frac{1000}{1.05} = 952.38$

This changes only the capacitors

So, final design

$$R_1 = 1000 \Omega$$


$$R_3 = R_4 = 5000 \Omega$$

$$C_2 = \frac{1.2756 \times 10^{-3}}{952.38} = 1.34 \text{ mF}$$


$$C_5 = \frac{2.8384 \text{ mF}}{952.38} = 0.0029.8 \text{ mF}$$

Q.4:

819

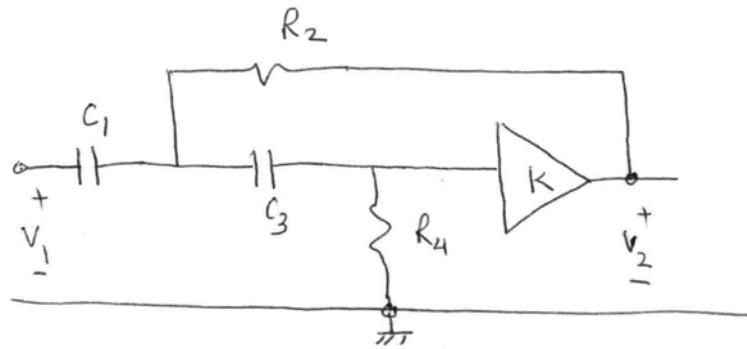

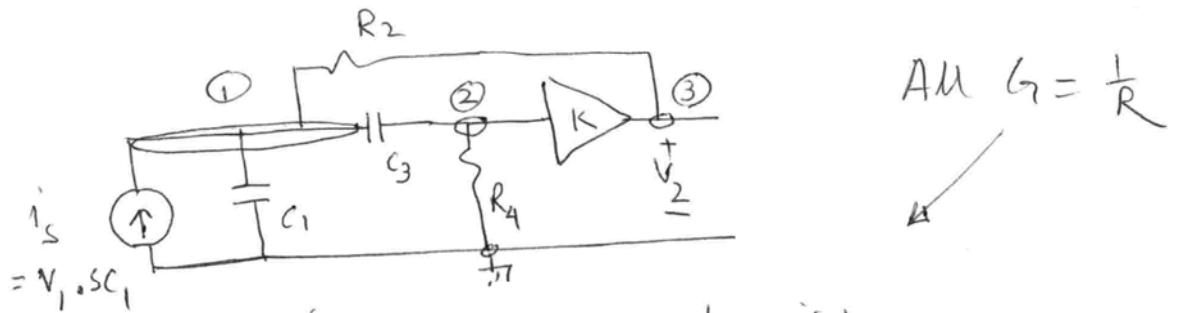For nodal matrix analysis, we re-configure the above circuit as:



The NAM for the 3-node system is:

$$\begin{pmatrix} \textcircled{1} & \textcircled{2} & \textcircled{3} \\ \begin{pmatrix} \alpha C_1 + \alpha C_3 + G_2 & -\alpha C_3 & -G_2 \\ -\alpha C_3 & G_4 + \alpha C_3 & 0 \\ -G_2 & 0 & G_2 \end{pmatrix} & \begin{pmatrix} v_{(1)} \\ v_{(2)} \\ v_{(3)} \end{pmatrix} = \begin{pmatrix} i_s \\ 0 \\ 0 \end{pmatrix} \end{pmatrix}$$

Applying the constraint  $v_{(3)} = K v_{(2)}$ , we write

$$v_{(3)} = v_{(2)} + K v_{(2)}$$

$$\begin{pmatrix} \alpha C_1 + \alpha C_3 + G_2 & -\alpha C_3 - KG_2 & 0 \\ -\alpha C_3 & G_4 + \alpha C_3 & KG_2 \\ -G_2 & 0 & 0 \end{pmatrix} \begin{pmatrix} v_{(1)} \\ v_{(2)} \\ v_{(3)} \end{pmatrix} = \begin{pmatrix} i_s \\ 0 \\ 0 \end{pmatrix}$$

Then, we discard row ③ corresponding to node ③

Q4

9/9

i.e., the output node of a voltage amplifier

So,

we will consider the circuit diagram given below. Note that we want to find the short-circuit current  $i_s$  at the output node.

$$\begin{pmatrix} \beta C_1 + \beta C_3 + G_2 & -\beta C_3 - K G_2 \\ -\beta C_3 & G_4 + \beta C_3 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} i_s \\ 0 \end{pmatrix}$$

Det of the matrix is

$$(\beta C_1 + \beta C_3 + G_2)(G_4 + \beta C_3) - \beta C_3(\beta C_3 + K G_2) = \Delta.$$

Simplifying:  $\Delta = \beta^2 C_1 C_3 + \beta(C_1 G_4 + C_3 G_4 + C_3 G_2 - K C_3 G_2) + G_2 G_4$

By applying Kramer's method:

$$V_2 = \frac{1}{\Delta} \cdot \begin{vmatrix} \beta C_1 + \beta C_3 + G_2 & i_s \\ -\beta C_3 & 0 \end{vmatrix}$$

$$= \frac{\beta C_3 i_s}{\Delta}$$

$$\text{So } V_2 = \frac{\beta C_3}{\Delta}, \quad V_1 \propto C_1 \quad \therefore i_s = V_1 \beta C_1$$

$$\frac{V_2}{V_1} = \frac{\beta^2 C_1 C_3}{\Delta}$$

$$\text{But } V_2 = K V_2 \quad ; \quad \text{So}$$

$$\frac{V_2}{V_1} = K \frac{\beta^2 C_1 C_3}{\Delta} = \frac{\beta^2 K C_1 C_3}{\beta^2 C_1 C_3 + \beta(C_1 G_4 + C_3 G_4 + C_3 G_2 - K C_3 G_2) + G_2 G_4}$$

$$\text{Proved} = \frac{K \beta^2}{\beta^2 + \beta \left( \frac{1}{C_3 R_4} + \frac{1}{C_1 R_4} + \frac{1}{G_2 R_2} - K \frac{1}{C_1 R_2} \right) + \frac{1}{R_2 R_4 C_1 C_3}}$$