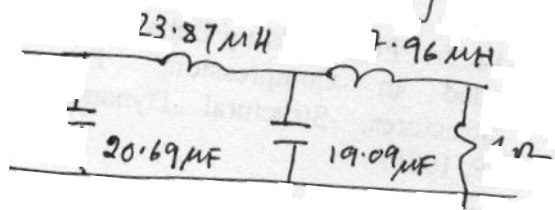


Q1:

(a)

Using frequency scaling by  $\omega = 2\pi \times 10^9$  rad/s




$$1.3 \text{ F} \rightarrow \frac{1.3}{2\pi \times 10^9} \text{ F}$$

$$1.5 \text{ H} \rightarrow \frac{1.5}{2\pi \times 10^9} \text{ H}$$

R  $\rightarrow$  does not change

Using impedance scaling by 75

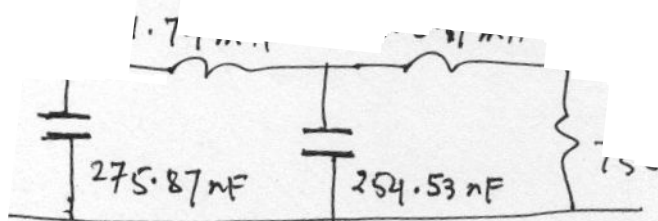$C \rightarrow C/75$ ,  $L \rightarrow L \times 75$ ;  $R \rightarrow R \times 75$



is the Final Circuit

(b)

For hpf we apply component transformation

Thus  $L_i \rightarrow C_i$  ;  $C_i = \frac{1}{L_i \omega_{ch}}$  ;  $\omega_{ch} = 2\pi \times 400$  rad/s

$C_j \rightarrow L_j$  ;  $L_j = \frac{1}{C_j \omega_{ch}}$

Thus:

$1.3 \text{ F} \rightarrow$  inductance  $L_j = \frac{1}{1.3 \times 2\pi \times 400} = 0.306 \text{ mH}$

$1.2 \text{ F} \rightarrow 0.331 \text{ mH}$


$1.5 \text{ H} \rightarrow C_i = \frac{1}{1.5 \times 2\pi \times 400} = 265.26 \text{ nF}$

$0.5 \text{ H} \rightarrow = 795.77 \text{ nF}$

Q1 (b)


First cut

2/6

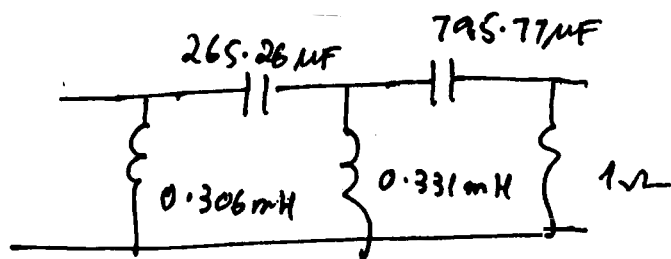


For  $100 \Omega$  termination, use impedance scaling

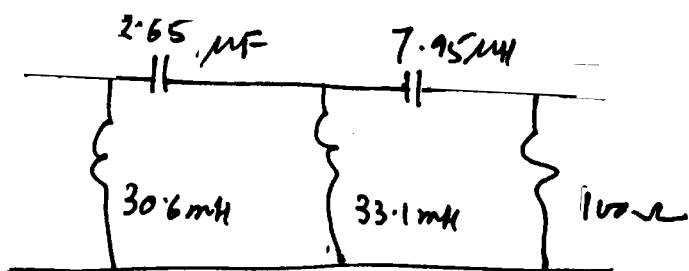$L \rightarrow 100 \times L$ ,  $C \rightarrow C/100$ ,  $R \rightarrow R \times 100$  -



Final answer

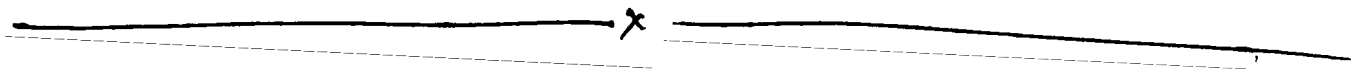

Q2:

At the passband edge,  $\omega_n = 1$   $A_p = 1$  dB

$$\epsilon = \sqrt{10^{0.1A_p} - 1} = \sqrt{0.2589} = 0.5088$$

$$a) \quad |H_N(j\omega_n)|^2 = \frac{1}{1 + 0.2588^2 \omega_n^{2m}} = \frac{1}{1 + 0.2589 \omega_n^{2m}}$$

At  $f = 10$  kHz,  $\omega_n = \frac{10}{1} = 10$

$$|H_N(j\omega_n)|^2 = \frac{1}{1 + 0.2589 \times 10^{10}} \quad m = \text{order} = 5$$

$$\approx \frac{10^{-10}}{0.2589}$$

$$P_r \text{ dB} \rightarrow 10 \log_{10} | |^2 = -100 \text{ dB} - 10 \log_{10}(0.2589) = -100 + 5.87 = -94.13$$

Attenuation =  $\frac{94.13}{1} \text{ dB}$  Ans

(b) Now  $10 \log_{10} |H_N(j\omega_n)|^2 = -40$  at  $\omega_n = 40 = \frac{40 \text{ kHz}}{1 \text{ kHz}}$

$$10 \log_{10} \left[ \frac{1}{1 + 0.2589 \times (40)^{2m}} \right] = -40$$

$$-10 \log_{10} [1 + 0.2589 \times (40)^{2m}] = -40 \quad \log_{10} 1 = 0$$

$$10^4 = 1 + 0.2589 \times (40)^{2m}; \quad 0.2589 \times (40)^{2m} \approx 10^4$$

$$(40)^{2m} = \frac{10^4}{0.2589} = 38.6249 \times 10^3$$

$$2m \log_{10}(40) = \log_{10}(38.6249 \times 10^3) = 4.5869$$

$$m = \frac{4.5869}{2 \times 1.6020} = 1.43 \rightarrow 2 \text{ order} \quad \underline{\underline{\text{Ans}}}$$

Q.3

Passband ripple implies a CHEB approximation

$A_p = 0$  dB leads to  $\epsilon = 0.3493$

$$D = \frac{10^{0.1A_p} - 1}{10^{0.1A_s} - 1} = \frac{10^{0.1 \times 3.5} - 1}{10^{0.1 \times 1} - 1} = 25908.2$$

4/6

$$\frac{\omega_s}{\omega_c} = \frac{15}{7.8} = \omega_s = 1.923$$

$$\sqrt{D} = 160.96$$

$$\cosh^{-1}(160.96) = 5.77 ; \cosh^{-1}(1.923) = 1.271$$

Order of filter  $> \frac{\cosh^{-1} \sqrt{D}}{\cosh^{-1}(\omega_s)} = 4.539 \rightarrow 5$

The normalized LDF transfer function is

$$H_N(s) = \frac{1}{s^5 + 1.1725s^4 + 1.9374s^3 + 1.3096s^2 + 0.7525s + 0.1789}$$


For 1<sup>st</sup> order HPF with  $\omega_{CH} = 15 \times 10^3 \times 2\pi$ , 1<sup>st</sup> order frequency de-normalized transfer function will be:

$$H(s) = \frac{0.1789}{\left[ \left( \frac{2\pi \times 15 \times 10^3}{s} \right)^5 + 1.1725 \left( \frac{2\pi \times 15 \times 10^3}{s} \right)^4 + 1.9374 \left( \frac{2\pi \times 15 \times 10^3}{s} \right)^3 + 1.3096 \left( \frac{2\pi \times 15 \times 10^3}{s} \right)^2 + 0.7525 \left( \frac{2\pi \times 15 \times 10^3}{s} \right) + 0.1789 \right]}$$

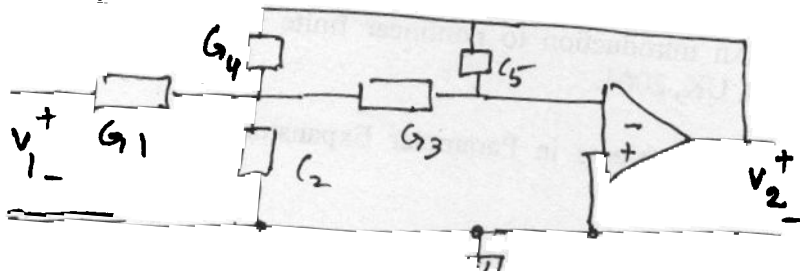
Q4

5/6

The given circuit is a LPF using infinite gain voltage amplifier. It can be compared with



Thus,

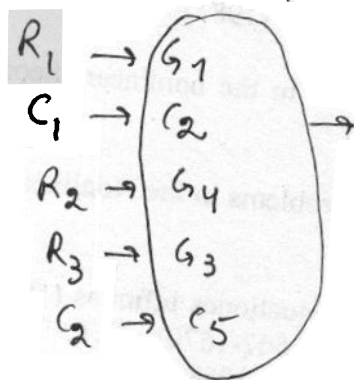

Design guidelines for these are given in Table 4.3

$$\frac{E_2}{E_1} = \frac{G \omega_0^2}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$$

can be compared with

$$\frac{V_2}{V_1} = \frac{H}{s^2 + \left(\frac{\omega_p}{Q_p}\right)s + \omega_p^2}$$

So

$$H = G \omega_0^2 \quad \omega_0 \equiv \omega_p, \quad Q \equiv Q_p$$

From given data  $H = 5 \omega_0^2 = 5$ ,  $\omega_0^2 = 1$  given  $= b_0$

$$b_1 = \frac{\omega_0}{Q} = \frac{\omega_p}{Q_p} = 1.2 = \frac{1}{Q_p}$$

$$So \quad Q_p = \frac{1}{1.2} = 0.833$$

Let's use the design guidelines

Q4)

Contd.

$$G_1 = \frac{H}{\omega_p} = \frac{5}{1} = 5$$

$$\text{So } R_1 = \frac{1}{5} = 0.2 \Omega$$

$$G_2 = \frac{Q_p (2\omega_p^2 + H)}{\omega_p^2} = \frac{0.833 (2 + 5)}{1} = 5.831 \text{ F}$$

Thus  $C_1 = 5.831 \text{ F}$  in the given circuit

$$G_3 = \omega_p = 1$$

So  $R_3 = G_3 = 1 \Omega$  in the given circuit

$$G_4 = G_3 = 1,$$

$R_2 = 1 \Omega$  in the given circuit

$$C_5 = \frac{\omega_p^2}{Q_p (2\omega_p^2 + H)} = \frac{1}{5.831} = 0.1715 \text{ F}$$

$C_5 \rightarrow C_2 = 0.1277 \text{ F}$  in the given circuit

Hence:

$$R_1 = 0.2 \Omega$$

$$R_2 = 1 \Omega$$

$$R_3 = 1 \Omega$$

$$C_1 = 5.831 \text{ F}$$

$$C_2 = 0.1715$$

needed  
design  
values

Proof:

$$\frac{1}{R_2 R_3 C_1 C_2} = \frac{1}{1 \cdot 1 \cdot 5.831 \times 0.1715} \approx 1 = b_0 = \omega_0^2$$

$$\frac{1}{C_1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{1}{5.831} (5 + 1 + 1) \approx 1.2 = b_1$$

$$\frac{1}{R_1 R_3 C_1 C_2} = \frac{1}{0.2 \cdot 1 \cdot 1} = 5 = G b_0$$