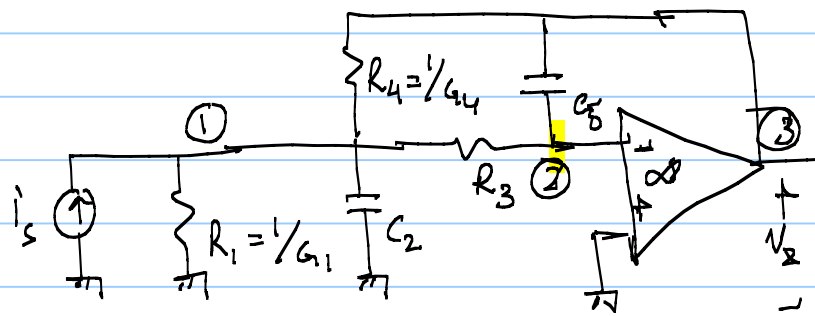


ELEC 441/6081 MT test #1, Feb 2013, Sol/hint

Note Title

2/13/2013

Q1: Using source transformation the circuit becomes



with $i_s = v_i G_1$

The nodal admittance matrix is:

$$\begin{bmatrix}
 \textcircled{1} & & \\
 G_1 + G_4 + G_3 + sC_2 & -G_3 & -G_4 \\
 -G_3 & G_3 + sC_5 & -sC_5 \\
 -G_4 & -sC_5 & G_4 + sC_5
 \end{bmatrix}
 \begin{bmatrix}
 v_1 \\
 v_2 \\
 v_3
 \end{bmatrix}
 =
 \begin{bmatrix}
 G_1 v_i \\
 0 \\
 0
 \end{bmatrix}$$

\therefore Gain of OA $= \infty$, v_2 is virtual short circuit. Also v_3 being the output of a voltage amplifier, we drop column $\textcircled{2}$ & row $\# 3$. So we get

Q1 (cont.)

$$\begin{bmatrix} G_1 + G_4 + G_3 + sC_2 & -G_4 \\ -G_3 & -sC_5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} G_1 V_i \\ 0 \end{bmatrix}$$

Given output is $V_0 = V_{\text{out}} = V_2$

Then by using Krammer's rule

$$V_2 = \frac{1}{\Delta} \begin{vmatrix} G_1 + G_4 + G_3 + sC_2 & G_1 V_i \\ -G_3 & 0 \end{vmatrix}$$

where $\Delta =$ determinant

$$\begin{vmatrix} G_1 + G_4 + G_3 + sC_2 & -G_4 \\ -G_3 & -sC_5 \end{vmatrix} \\ = - \left[s^2 C_2 C_5 + (G_1 + G_4 + G_3) s C_5 + G_3 G_4 \right]$$



Finally,

$$\frac{V_2}{V_i} = - \frac{1/(R_1 R_3 C_2 C_5)}{s^2 + \frac{s}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} \right) + \frac{1}{R_3 R_4 C_2 C_5}}$$

Q.2:

(a) Frequency is scaled by $\alpha = 2\pi \times 5000$ So $L \rightarrow L/\alpha$, $C \rightarrow C/\alpha$, R does not change.

The circuit becomes:

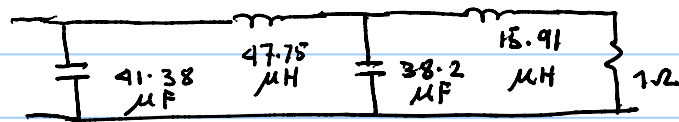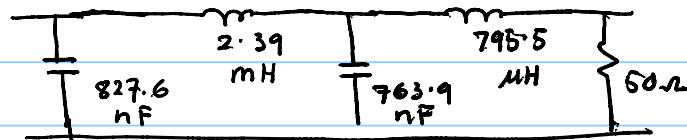(b) 1 Ω to 50 Ω, impedance scale factor $k_m = 50$ So $C \rightarrow C/50$, $L \rightarrow L \times 50$, $R \rightarrow R \times 50$. The new circuit will be

Q.3:

$$\text{Given } |H_N(j\omega)|^2 = \frac{1}{1 + \epsilon^2 \omega_n^{2m}} ; \text{ given } m=5$$

at $\omega_n = 1$ i.e. $\omega = 2\pi \times 1000$ rad/sec, loss = 1 dB

$$\text{i.e. } 10 \log_{10} \left[\frac{1}{1 + \epsilon^2} \right] = -1 \quad (\text{loss brings in - sign})$$

$$\epsilon^2 = 10^{-1} - 1 ; \epsilon = \sqrt{0.25892} = 0.5088$$

$$(a) \text{ At } 5 \text{ KHz}, \omega_n = 5 ; |H_N(j\omega)|^2 = \frac{1}{1 + \epsilon^2 (5)^{10}}$$

$$\text{In dB, } 10 \log_{10} [|H_N(j\omega)|^2] = -64.03 ; \text{ subst for } \epsilon^2$$

So loss is 64.03 dB

$$(b) \text{ loss of } 40 \text{ dB implies } 10 \log_{10} [|H_N(j\omega)|^2] = -40$$

$$\text{i.e. } \frac{1}{1 + \epsilon^2 (30)^{2m}} = 10^{-4} ; \omega_n = 30 @ 30 \text{ KHz}$$

$$1 + 0.25892 \times (30)^{2m} = 10^4 ; m = 1.55 \rightarrow \text{order } 2$$

i.e. a second order filter

Q.4: Equiripple passband implies a CHEB response.

From given specs. $A_p = 0.5 \text{ dB}$, $A_a = 35 \text{ dB}$

$$\omega_c = 2\pi \times 12 \times 10^3; \quad \omega_a = 2\pi \times 3.5 \times 10^3; \quad \omega_s = \frac{12}{3.5} = 3.428$$

$$\eta = \frac{10^{0.1 A_a} - 1}{10^{0.1 A_p} - 1} = \frac{10^{3.5} - 1}{10^{-0.5} - 1} = 25908.19$$

$$\sqrt{\eta} = 160.96$$

$$\text{The filter order } n \gg \frac{\cosh^{-1} \sqrt{\eta}}{\cosh^{-1}(\omega_s)} = 3.03$$

$$\text{Let } n = 4$$

Looking up from Tables (for $A_p = 0.5 \text{ dB}$, i.e. $\epsilon = 0.3493$)

$$H_N(s) \Big|_{LP} = \frac{1}{2 \epsilon} \cdot \frac{1}{s^4 + 1.197s^3 + 1.717s^2 + 1.025s + 0.379}$$

For the frequency denormalized HPF, we scale

$$s \rightarrow \frac{2\pi \times 12000}{s}. \text{ Thus,}$$

$$H(s) = \frac{35785.86 s^4}{37900 s^4 + 0.7728 \times 10^3 s^3 + 0.9761 \times 10^{15} s^2 + 0.5131 \times 10^{20} s + 0.3232 \times 10^{25}}$$