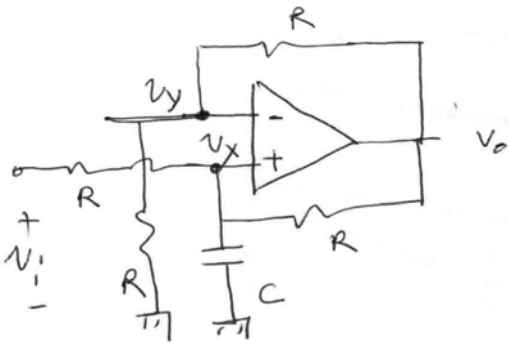


Non inverting integrator

OP-SIMUL
SIMPL

1/6



~~$$v_x = v_i \frac{1/sC}{R+1/sC} = v_i \frac{1}{1+sCR}$$~~

At v_x node:

$$-\frac{v_i - v_x}{R} + v_x \cdot sC + \frac{v_x - v_o}{R} = 0$$

$$\frac{v_i}{R} + \frac{v_o}{R} = v_x \left(\frac{1}{R} + sC + \frac{1}{R} \right) = v_x \left(\frac{2}{R} + sC \right)$$

But $v_y = v_x$ (ideal OP-AMP)



$$= \frac{v_o}{2}$$

$$\text{So } \frac{v_i}{R} + \frac{v_o}{R} = \frac{v_o}{2} \left(\frac{2}{R} + sC \right) = \frac{v_o}{R} + \frac{v_o}{2} sC$$

$$v_i = \frac{v_o}{2} sCR$$

$$\boxed{\frac{v_o}{v_i} = \frac{2}{sCR}}$$

Lossy Integrator:




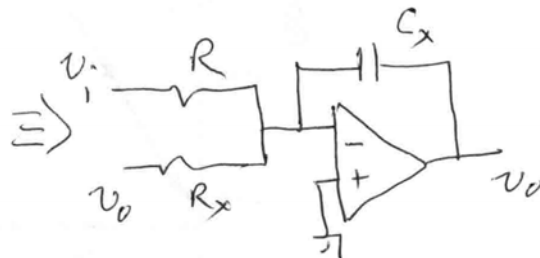
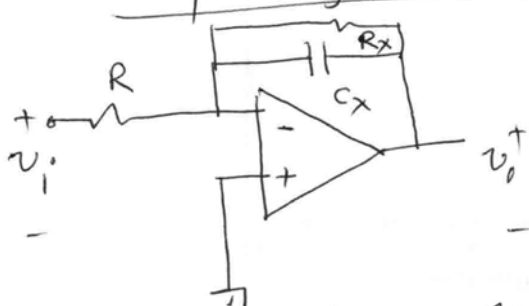


$$v_o = -v_i \frac{1}{sC_x R} - v_o \frac{1}{sC_x R_x}$$

$$v_o \left[1 + \frac{1}{sC_x R_x} \right] = -v_i \frac{1}{sC_x R}$$

$$\frac{v_o}{v_i} = -\frac{1}{sC_x R} \cdot \frac{sC_x R_x}{1 + sC_x R_x} = -\frac{R_x}{R} \cdot \frac{1}{1 + sC_x R_x}$$


$$= -\frac{1/RC_x}{s + 1/RC_x R_x}$$

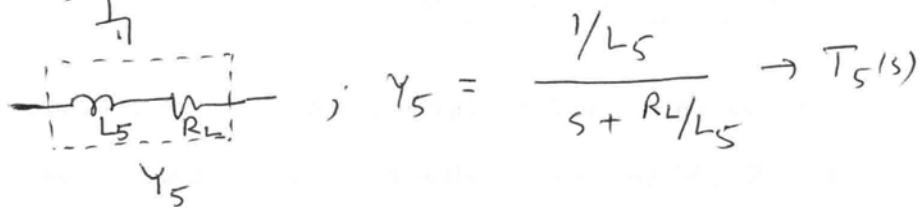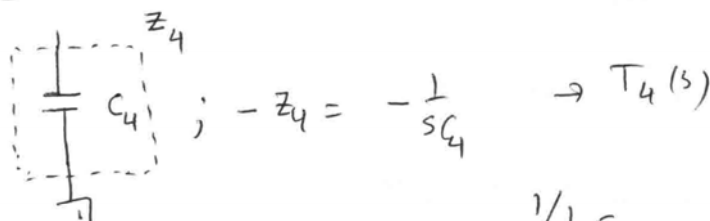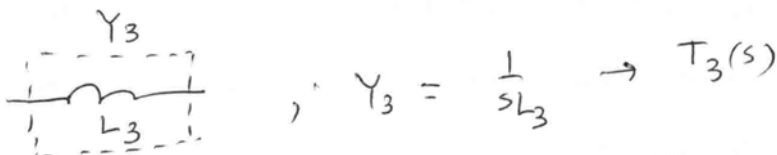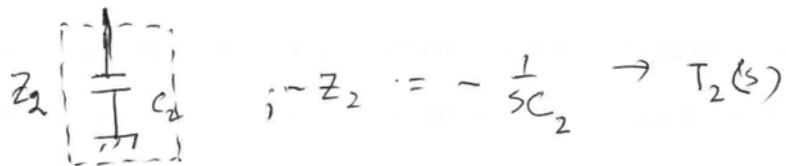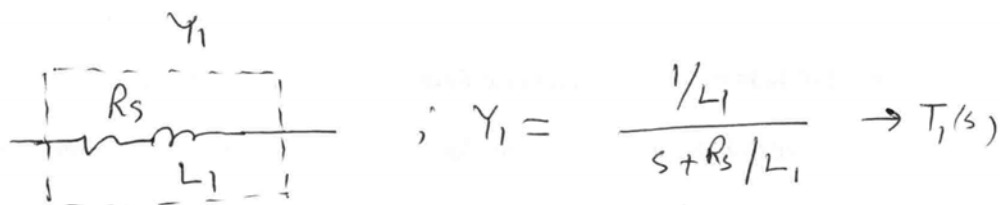

$T_1(s) \rightarrow$ a VTF, unitless. So convert Y_1 , an admittance to unitless by multiplying with R .

So $T_1(s) = RY_1 = \frac{R/L_1}{s + R_s/L_1} \rightarrow$ like a lossy integ, except for a -ve sign.

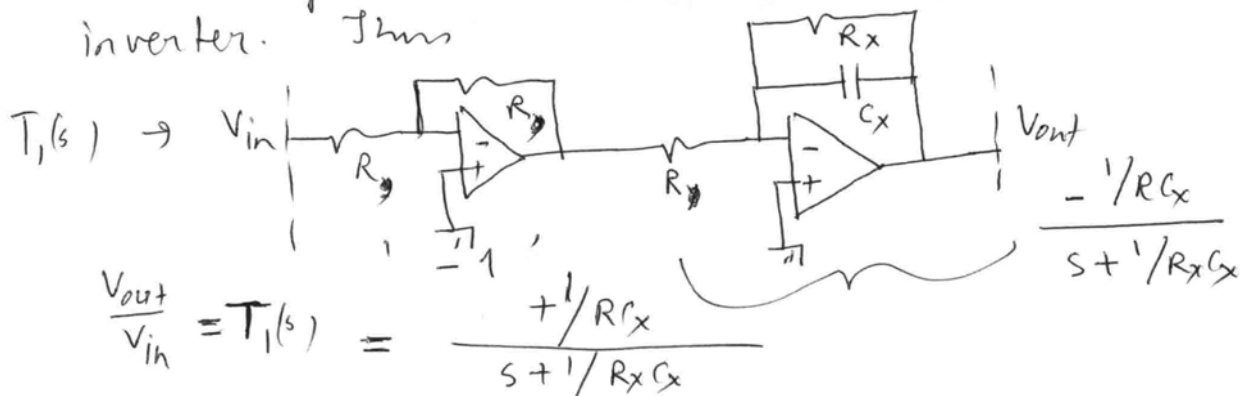But so to bring this -ve sign, we put a simple inverter. Thus



Now compare $Y_1 \rightarrow T_1 = \frac{R/L_1}{s + R_3/L_1}$

& try to obtain $\frac{1/C_x R}{s + 1/C_x R_x} = T_1$

Comparing $\frac{R}{L_1} = \frac{1}{C_x R}$


ie $R^2 = \frac{L_1}{C_x}$; But $\frac{R_3}{L_1} = \frac{1}{C_x R_x}$; $\frac{1}{C_x} = \frac{R_x R_3}{L_1}$

So $R^2 = \frac{L_1}{C_x} \cdot \frac{R_x R_3}{L_1} = R_x R_3$ OR $R = \sqrt{R_x R_3}$

choose, R_3 given
decides $R_x = \frac{R^2}{R_3}$

Again $\frac{R_3}{L_1} = \frac{1}{C_x R_x}$; $C_x = \frac{L_1}{R_x R_3}$

So keep R_x free to choose:

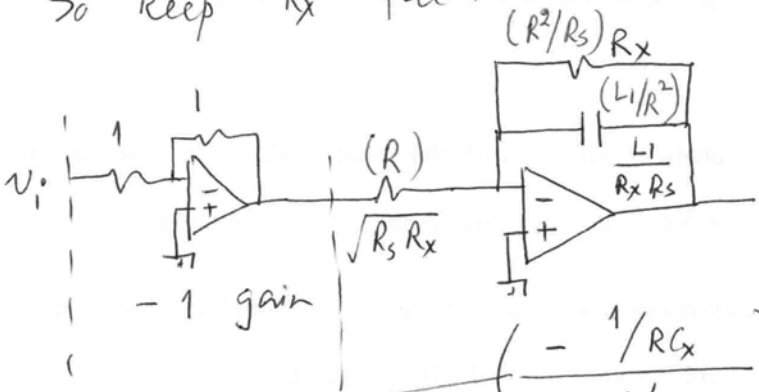


in terms of the components:

$$\frac{-\frac{1}{\sqrt{R_3 R_x}} \cdot \frac{L_1}{R_x R_3}}{s + \frac{1}{R_x} \cdot \frac{L_1}{R_x R_3}} = \frac{-\frac{\sqrt{R_3 R_x}}{L_1}}{s + \frac{R_3}{L_1}}$$


$$\therefore R = \sqrt{R_x R_3} = \frac{-R/L_1}{s + \frac{R_3}{L_1}}$$

Proof:

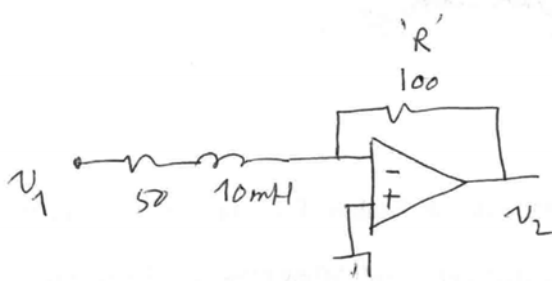

$$\frac{v_2}{v_1} = - \frac{100 / 10mH}{s + 50 / 10mH} \quad 4/6$$

Let $R_x = 100 \text{ } 50$

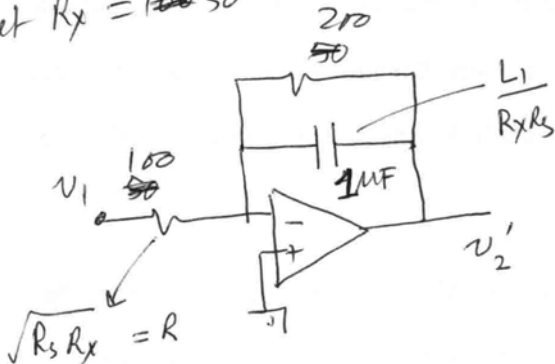

$$\frac{L_1}{R_x R_s} = \frac{10mH}{50 \times 50} = 200 \times 50$$

$$= \frac{10^{-2}}{2500} = 0.000004$$

$$= \frac{10^{-2}}{10^4} = 10^{-6} = 1 \mu F$$

we must get

$$= \frac{-10^4}{s + 5000}$$

$$\frac{v_2'}{v_1} = \frac{-10^4}{s + 5000}$$

$$\sqrt{R_s R_x} = R$$


$$= \sqrt{50 \times 100}$$

$$= 50$$

$$R_s R_x = R^2 = 10^4$$

$$R_x = \frac{10^4}{50} = 2 \times 10^2 = 200$$

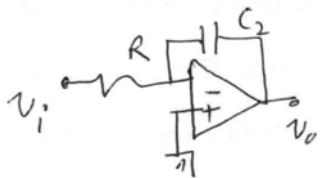Similarly, $T_2(s) = -\frac{Z_2}{R} = -\frac{1}{sC_2R}$



$$\frac{v_o}{v_i} = T_2(s) = -\frac{1}{sC_2R}$$

How we organize T_1 & T_2 here? :



Consider :

$$v_1' = (v_1 - v_2) Y_1 R = (v_1 - v_2) T_1$$

$$v_2 - v_3 = (v_1' - v_3') \left(-\frac{Z_2}{R}\right) = (v_1' - v_3') T_2$$

if $v_1 = v_s$ now

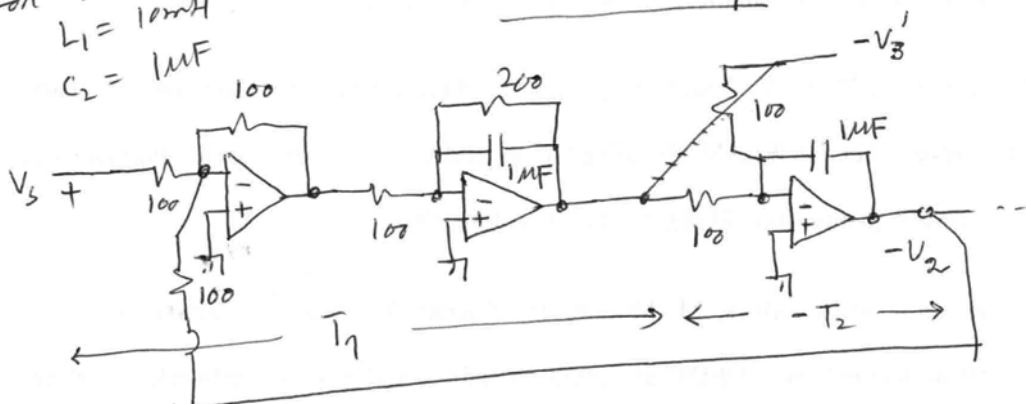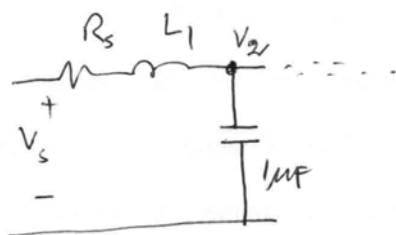
For $R = 100\Omega$ (assumed)
 $R_s = 50$
 $L_1 = 10mH$
 $C_2 = 1\mu F$



About $-v_3'$; Recall $-v_3' = (-v_2 + v_4) Y_3 R$


where $T_3 = Y_3 R = \frac{R}{sL_3} = \frac{1}{s(L_3/R)} = \frac{1}{sC_3'}$
 $C_3' = L_3/R$. A non inverting ~~amp~~ integrator

We could use :

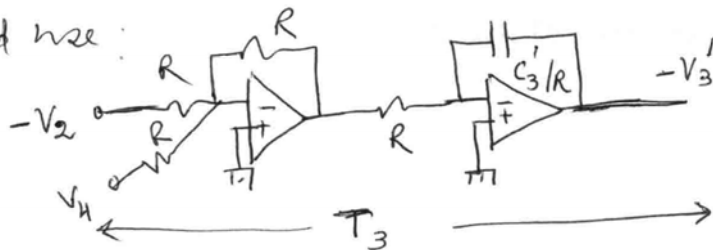


S_0 $T_1, -T_2, T_3$ together now:

6/6

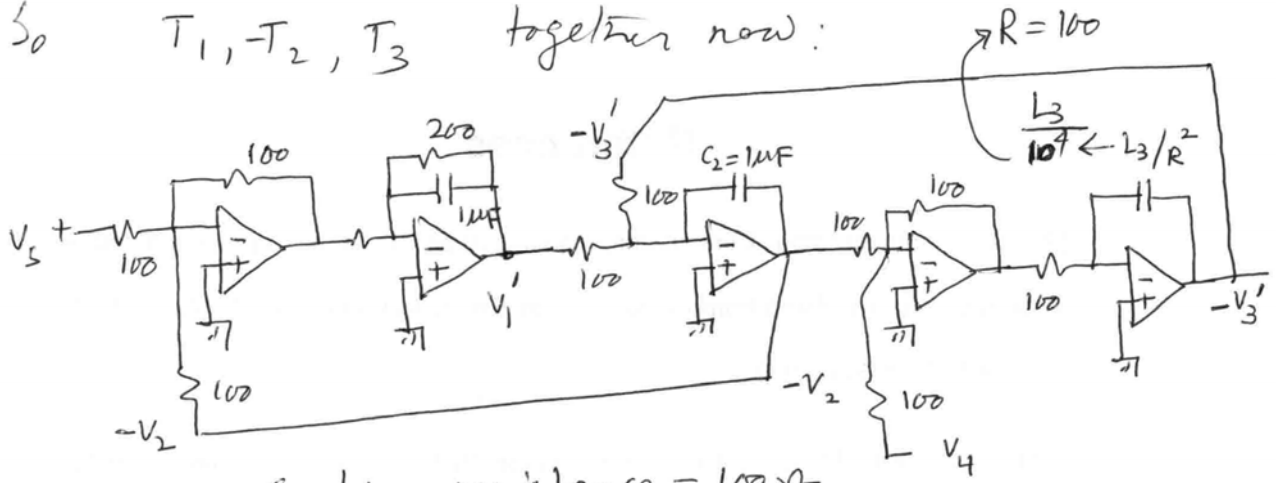

Scaling resistance = 100 Ω

We have simulated the operation of

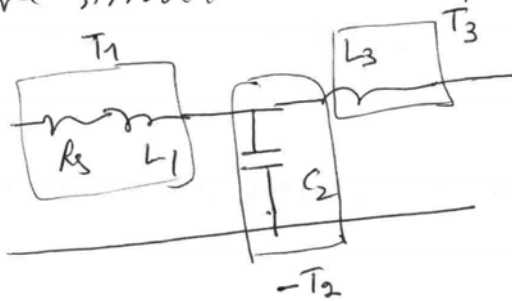

& continue this way