

# ANALOG FILTER DESIGN/ INTEGRATED CIRCUITS FILTER

(ELEC 6081)

(Winter 2009-'10 term)

## Project#1 (Grad)

An equi-ripple band-pass filter is required to satisfy the specifications:

- (a) The pass-band extends from  $\omega=1000$  rad/s to 4000 rad/s.
  - (b) The peak-peak ripple in the pass-band not to exceed 0.5 dB.
  - (c) The magnitude characteristic is to be at least 30 dB down at  $\omega=12000$  rad/s.
1. Synthesize the filter transfer function (it will be of order  $>2$ ). (5% marks)
  2. Provide a decomposition of the transfer function as cascade of second order and possibly first order transfer functions. (5% marks)
  3. Verify that the transfer function obtained satisfy the given specification (use numerical simulation, i.e., MATLAB). (5% marks)
  4. Provide a design for the above filter, using

Operational Simulation principle with OP-AMP based active filter. (30% marks)

*If you can produce your design using realistic model for the OP-AMP more credit will be given.*

5. From the work in step 2 above, use one of the second order transfer functions for the following tasks.
  - (a) Produce a design of the second order filter using OA. Use of nearest practical values of R,C elements (as obtained from the lab bins, i.e., for  $R= 1.231$  k $\Omega$ , use 1.2 k $\Omega$ , and for  $C=0.125$   $\mu$ F. use 0.1  $\mu$ F, or 0.1  $\mu$ F plus 20 nF in parallel) is encouraged. Provide SPICE simulation results and a comparison with the theoretical transfer function (second order). The theoretical transfer function can be obtained using numerical simulation (i.e., MATLAB). Use model of a practical OA such as  $\mu$ 741 from the SPICE data base. (15% marks)
  - (b) Produce a design of the second order filter using OTA and capacitors. Use of nearest practical values for the C elements (as obtained from the lab bins, i.e., for  $C=0.125$   $\mu$ F. use 0.1  $\mu$ F, or 0.1  $\mu$ F plus 20 nF in parallel) is encouraged. Provide SPICE simulation results and a comparison with the theoretical transfer function (second order). The theoretical transfer function can be obtained using numerical simulation (i.e., MATLAB). Use model of a practical OTA (as used in the lab work) from the SPICE data base. (15% marks)
  - (c) Produce a design of the second order filter using OA and switched capacitors. Use a clock frequency of 64 kHz. Use minimum capacitor value of 1 pF. Provide SPICE simulation results(exploit transmission line model for the  $z^{-1}$  variable) and a comparison

with the theoretical transfer function (second order). The theoretical transfer function can be obtained using numerical simulation (i.e., MATLAB). Use model of a practical OTA (as used in the lab work) from the SPICE data base. (15% marks)

6. Submit a report about your design work. The report must include the following. **If you omit any one part, you will lose the % mark for that part.** Do not commit *plagiarism* in producing your work. Such act will result in severe disciplinary actions against the student(s).

For each design:

- (a) Design equations (active device and filter system) used for each specific case (10% marks).
- (b) One set of sample calculations for circuit elements used in the design. (10% marks).
- (c) Schematic of the final network with practical component values shown in a **table** (15% marks).
- (d) Circuit Simulation results using SPICE or similar program (15% marks).
- (e) Comparison of the ideal response (numerical simulation) and the designed response, as obtained via circuit simulations (5% marks).
- (f) Discussion of your results and comments on your accomplishments (5% marks).

For the overall report:

- (g) Front cover and a table of contents (5% marks)
- (h) List of references (5% marks)

#### Interpretation of the marks distribution for the project and report

1. Items 1-3 amounts to **15%**
2. Items 6 (g)-(h) amounts to **10%**
3. Items 4 and 5(a)-(c) amounts to **75%** (=30%+15%+15%+15%). Each subdivision of this 75% is distributed as in items 6 (a)-(f). Thus if you score 70% (i.e 42 in 60) in the items of 6 (a)-(f), in relation to task 4, your score in that part will be (42/60) times 30, i.e 21 in 30. The same score in 6(a)-(f) in relation to task 5(a) will give you (42/60) times 15, i.e., 10.5 in 15.

**Note:** The above amounts to **50%** of the *course marks*. Thus a score of 80 in items (1)-(3) above will turn out to be 40 in the course. An additional **5%** is assigned to a student according to his/her rating given by his/her peers in the project group.

## ANALOG FILTER DESIGN/ INTEGRATED CIRCUITS FILTER

(ELEC 6081)

(Winter 2009-'10 term)

### Project#2 (Grad)

A band-reject filter is required to satisfy the specifications:

- (a) The stop-band extends from 1kHz to 10kHz.
- (b) The peak-peak ripple in the pass-band not to exceed 1.0 dB.
- (c) The magnitude characteristic at 2 kHz is to be at least 30 dB down from its peak value at DC.

1. Synthesize the filter transfer function (it will be of order  $>2$ ). (10% marks)
2. Provide a decomposition of the transfer function as cascade of second order and possibly first order transfer functions. (10% marks)
3. Verify that the transfer function obtained satisfy the given specification (use numerical simulation, i.e., MATLAB). (10% marks)

4. Provide a design for the above filter, using

Operational Simulation principle with OTA-C based active filter (30% marks)

5. From the work in step 2 above, use one of the second order transfer functions for the following tasks.

- (a) Produce a design of the second order filter using OA. Use of nearest practical values of R,C elements (as obtained from the lab bins, i.e., for  $R= 1.231 \text{ k}\Omega$ , use  $1.2 \text{ k}\Omega$ , and for  $C=0.125 \text{ }\mu\text{F}$ . use  $0.1 \text{ }\mu\text{F}$ , or  $0.1 \text{ }\mu\text{F}$  plus  $20 \text{ nF}$  in parallel) is encouraged. Provide SPICE simulation results and a comparison with the theoretical transfer function (second order). The theoretical transfer function can be obtained using numerical simulation (i.e., MATLAB). Use model of a practical OA such as  $\mu 741$  from the SPICE data base. (15% marks)

- (b) Produce a design of the second order filter using OTA and capacitors. Use of nearest practical values for the C elements (as obtained from the lab bins, i.e., for  $C=0.125 \text{ }\mu\text{F}$ . use  $0.1 \text{ }\mu\text{F}$ , or  $0.1 \text{ }\mu\text{F}$  plus  $20 \text{ nF}$  in parallel) is encouraged. Provide SPICE simulation results and a comparison with the theoretical transfer function (second order). The theoretical transfer function can be obtained using numerical simulation (i.e., MATLAB). Use model of a practical OTA (as used in the lab work) from the SPICE data base. (15% marks)

- (c) Produce a design of the second order filter using OA and switched capacitors. Use a clock frequency of 64 kHz. Use minimum capacitor value of 1 pF. Provide SPICE simulation results(exploit transmission line model for the  $z^{-1}$  variable) and a comparison with the theoretical transfer function (second order). The theoretical transfer function can

be obtained using numerical simulation (i.e., MATLAB). Use model of a practical OTA (as used in the lab work) from the SPICE data base. (15% marks)

6. Submit a report about your design work. The report must include the following. **If you omit any one part, you will loose the % mark for that part.** Do not commit *plagiarism* in producing your work. Such act will result in severe disciplinary actions against the student(s).

For each design:

- (a) Design equations (active device and filter system) used for each specific case (10% marks).
- (b) One set of sample calculations for circuit elements used in the design. (10% marks).
- (c) Schematic of the final network with practical component values shown in a **table** (15% marks).
- (d) Circuit Simulation results using SPICE or similar program (15% marks).
- (e) Comparison of the ideal response (numerical simulation) and the designed response, as obtained via circuit simulations (5% marks).
- (f) Discussion of your results and comments on your accomplishments (5% marks).

For the overall report:

- (g) Front cover and a table of contents (5% marks)
- (h) List of references (5% marks)

#### Interpretation of the marks distribution for the project and report

1. Items 1-3 amounts to **15%**
2. Items 6 (g)-(h) amounts to **10%**
3. Items 4 and 5(a)-(c) amounts to **75%** (=30%+15%+15%+15%). Each subdivision of this 75% is distributed as in items 6 (a)-(f). Thus if you score 70% (i.e 42 in 60) in the items of 6 (a)-(f), in relation to task 4, your score in that part will be (42/60) times 30, i.e 21 in 30. The same score in 6(a)-(f) in relation to task 5(a) will give you (42/60) times 15, i.e., 10.5 in 15.

**Note:** The above amounts to **50%** of the *course marks*. Thus a score of 80 in items (1)-(3) above will turn out to be 40 in the course. An additional **5%** is assigned to a student according to his/her rating given by his/her peers in the project group.

## ANALOG FILTER DESIGN/ INTEGRATED CIRCUITS FILTER

(ELEC 441)

(Winter 2009-'10 term)

Project#1 (UG)

An equi-ripple band-pass filter is required to satisfy the specifications:

- (a) The pass-band extends from  $\omega=1000$  rad/s to 4000 rad/s.
  - (b) The peak-peak ripple in the pass-band not to exceed 0.5 dB.
  - (c) The magnitude characteristic is to be at least 30 dB down at  $\omega=12000$  rad/s.
1. Synthesize the filter transfer function (it will be of order  $>2$ ). (5% marks)
  2. Provide a decomposition of the transfer function as cascade of second order and possibly first order transfer functions. (5% marks)
  3. Verify that the transfer function obtained satisfy the given specification (use numerical simulation, i.e., MATLAB). (5% marks)
  4. Provide a design for the above filter, using
    - (a) Cascade of OP-AMP based active filter. (30% marks)
    - (b) Cascade of OTA-C based active filter. (30% marks)

*You are encouraged to use realistic model for the OP-AMP in (a) above.*

5. From the work in step 2 above, use one of the second order transfer functions for the following task.
  - (a) Produce a design of the second order filter using OA and switched capacitors. Use a clock frequency of 64 kHz. Use minimum capacitor value of 1 pF. Provide SPICE simulation results(exploit transmission line model for the  $z^{-1}$  variable) and a comparison with the theoretical transfer function (second order). The theoretical transfer function can be obtained using numerical simulation (i.e., MATLAB). (15% marks)
6. Submit a report about your design work. The report must include the following. **If you omit any one part, you will loose the % mark for that part.** Do not commit *plagiarism* in producing your work. Such act will result in severe disciplinary actions against the student(s).

For each design:

- (a) Design equations (active device and filter system) used for each specific case (**10%** marks).
- (b) One set of sample calculations for circuit elements used in the design. (**10%** marks).
- (c) Schematic of the final network with *practical component* values (as obtained from the lab bins, i.e., for  $R= 1.231\text{ k}\Omega$ , use  $1.2\text{ k}\Omega$ , and for  $C=0.125\text{ }\mu\text{F}$ , use  $0.1\text{ }\mu\text{F}$ , or  $0.1\text{ }\mu\text{F}$  plus  $20\text{ nF}$  in parallel) shown in a **table** (**15%** marks).
- (d) Circuit Simulation results using SPICE or similar program (**15%** marks).
- (e) Comparison of the ideal response (numerical simulation) and the designed response, as obtained via circuit simulations (**5%** marks).
- (f) Discussion of your results and comments on your accomplishments (**5%** marks).

For the overall report:

- (g) Front cover and a table of contents (**5%** marks)
- (h) List of references (**5%** marks)

#### Interpretation of the marks distribution for the project and report

1. Items 1-3 amounts to **15%**
2. Items 6 (g)-(h) amounts to **10%**
3. Items 4(a)-(b) and 5(a) amounts to **75%** (=30%+30%+15%). Each subdivision of this 75% is distributed as in items 6 (a)-(f). Thus if you score 70% (i.e 42 in 60) in the items of 6 (a)-(f), in relation to task 4(a), your score in that part will be (42/60) times 30, i.e 21 in 30. The same score in 6(a)-(f) in relation to task 5(a) will give you (42/60) times 15, i.e., 10.5 in 15.

**Note:** The above amounts to **50%** of the *course marks*. Thus a score of 80 in items (1)-(3) above will turn out to be 40 in the course. An additional **5%** is assigned to a student according to his/her rating given by his/her peers in the project group.

## **ANALOG FILTER DESIGN/ INTEGRATED CIRCUITS FILTER**

**(ELEC 441, 6081)**

**(Winter 2009-'10 term)**

### **Project#2 (UG)**

A band-reject filter is required to satisfy the specifications:

- (a) The stop-band extends from 1kHz to 10kHz.
- (b) The peak-peak ripple in the pass-band not to exceed 1.0 dB.
- (c) The magnitude characteristic at 2 kHz is to be at least 30 dB down from its peak value at DC.

- 1. Synthesize the filter transfer function (it will be of order  $>2$ ). **(10% marks)**
- 2. Provide a decomposition of the transfer function as cascade of second order and possibly first order transfer functions. **(10% marks)**
- 3. Verify that the transfer function obtained satisfy the given specification (use numerical simulation, i.e., MATLAB). **(10% marks)**

4. Provide a design for the above filter, using

- (a) Cascade of OP-AMP based active filter. **(30% marks)**
- (b) Cascade of OTA-C based active filter. **(30% marks)**

*You are encouraged to use realistic model for the OP-AMP in (a) above.*

5. From the work in step 2 above, use one of the second order transfer functions for the following task.

- (a) Produce a design of the second order filter using OA and switched capacitors. Use a clock frequency of 64 kHz. Use minimum capacitor value of 1 pF. Provide SPICE simulation results (exploit transmission line model for the  $z^{-1}$  variable) and a comparison with the theoretical transfer function (second order). The theoretical transfer function can be obtained using numerical simulation (i.e., MATLAB). **(15% marks)**

6. Submit a report about your design work. The report must include the following. **If you omit any one part, you will loose the % mark for that part.** Do not commit *plagiarism* in producing your work. Such act will result in severe disciplinary actions against the student(s).

For each design:

- (a) Design equations (active device and filter system) used for each specific case (**10%** marks).
- (b) One set of sample calculations for circuit elements used in the design. (**10%** marks).
- (c) Schematic of the final network with practical component values (as obtained from the lab bins, i.e., for  $R= 1.231 \text{ k}\Omega$ , use  $1.2 \text{ k}\Omega$ , and for  $C=0.125 \text{ }\mu\text{F}$ . use  $0.1 \text{ }\mu\text{F}$ , or  $0.1 \text{ }\mu\text{F}$  plus  $20 \text{ nF}$  in parallel) shown in a **table** (**15%** marks).
- (d) Circuit Simulation results using SPICE or similar program (**15%** marks).
- (e) Comparison of the ideal response (numerical simulation) and the designed response, as obtained via circuit simulations (**5%** marks).
- (f) Discussion of your results and comments on your accomplishments (**5%** marks).

For the overall report:

- (g) Front cover and a table of contents (**5%** marks)
- (h) List of references (**5%** marks)

#### Interpretation of the marks distribution for the project and report

1. Items 1-3 amounts to **15%**
2. Items 6 (g)-(h) amounts to **10%**
3. Items 4(a)-(b) and 5(a) amounts to **75%** ( $=30\%+30\%+15\%$ ). Each subdivision of this 75% is distributed as in items 6 (a)-(f). Thus if you score 70% (i.e 42 in 60) in the items of 6 (a)-(f), in relation to task 4(a), your score in that part will be  $(42/60)$  times 30, i.e 21 in 30. The same score in 6(a)-(f) in relation to task 5(a) will give you  $(42/60)$  times 15, i.e., 10.5 in 15.

**Note:** The above amounts to **50%** of the *course marks*. Thus a score of 80 in items (1)-(3) above will turn out to be 40 in the course. An additional **5%** is assigned to a student according to his/her rating given by his/her peers in the project group.